

EE 209 Homework 2 Logic Function Synthesis

Name: _____

Due: See Blackboard


Score: _____

[BB] = Blackboard Submission. For non-BB problems, show work to get full credit.

HW 2 Blackboard Form

1. [BB] (12 pts.) When the circuit below was fabricated on a chip, a problem occurred. One of the first level OR gates continually outputs a '1' (a.k.a. a "stuck-at-1" fault) no matter what the inputs to the gate.

 - a. Propose and list a minimal number of input combinations that could be used to determine which gate had the fault (i.e. $a,b,c = 1,1,0$ and $a,b,c = 1,1,1$)? Describe how you could use these values to determine the gate with the error?
- b. If instead one of the OR gates was stuck at '0' would any set of input combinations be able to determine which gate had the error? Explain?





2. [BB] (14 pts) Write out the *algebraic* form of both the minterm and maxterm representation for each function (both for each one...meaning convert G to a canonical product as well.)

$$G = \sum_{A,B,C,D} (2,3,6,13,15)$$

3. [Practice-Only] (0 pts.) Given a 4-bit, unsigned input ($A[3:0]$) design a logic circuit using a sum of minterms approach with a single output, F, which outputs '1' if the input number is a multiple of 3 (i.e. $A[3:0]$ in $\{0_{10}, 3_{10}, 6_{10}, \dots\}$)

  4. [BB] (8 pts.) Complete the waveform for the circuit below.



5. [BB] (30 pts.) Using a Karnaugh map, find both the minimal POS and SOP expression for each of the following functions (both for each).
- $F = \sum_{ABC} (0,2,4,7)$
 - $G = \prod_{WXYZ} (2,3,7,8,11,12,14,15)$
 - $H(w,x,y,z)$ such that $H = 1$ for input combinations divisible by 2 or 3
($w,x,y,z=0000$ is divisible by 2 and 3).
6. [Practice Only] (0 pts.) Draw the specified implementation schematics.
- AND-OR implementation for 3a.
 - NOR-NOR implementation for 3b.
 - NAND-NAND implementation for 3c.
7. [BB] (36 pts.) Design a circuit that takes in a 3-bit signed-magnitude number, $A[2:0]$ ($A_2A_1A_0$), adds two to its decimal equivalent, and produces a 2's complement result, $Z[n:0]$. (i.e. $Z = A + 2$.) (Consider the signed magnitude combination representing -0 as an illegal input combination that should never occur.)
- Write out a truth table (consider how many outputs would be necessary for this problem)
 - Use Karnaugh Maps to produce minimal equations for each output bit
 - Now implement the same design again use a 3-to-8 decoder and at most 3 OR gates.

