

EE 209 Homework 3


Name: Solutions

Due: _____

Score: _____

1.

The waveform is below:

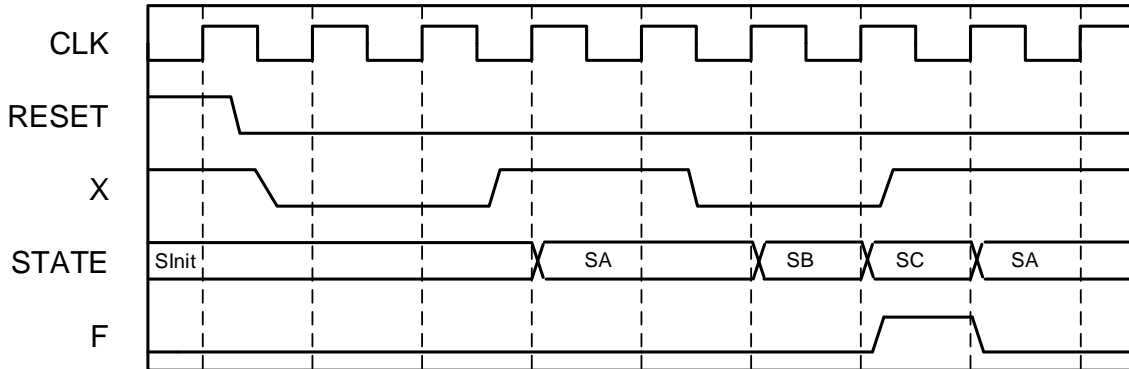

2.

- (a) There is only one D Flip flop, and Q_1 can be 0 or 1. Thus, there are 2 states for this circuit.
- (b) This is a Mealy Machine. Because the output F is the function of the current state and the external input A.
- (c) The maximum number of transition arrows originating from one state is 8. Because we have A, B and C three external inputs, and there are 8 possible combinations of one 3-bits binary number.
- (d) No. Because when A is equal to 1, the input of the D Flip flop is definitely 0. Thus, when the next clock tick comes, Q_1 is equal to 0 and F is 0 too.


3.

Because we have 4 states in the state diagram, we use two D flip-flops to implement state memory. We design the combinational logic for the next-state logic and the output function logic by building up the state/transition table (with E=ENTER, C=CORRECT).

Current State		Next State								Output
Sym.	Q1Q0	E C = 0 0		E C = 0 1		E C = 1 0		E C = 1 1		Alarm
		Sym.	Q1*Q0*	Sym.	Q1*Q0*	Sym.	Q1*Q0*	Sym.	Q1*Q0*	
OFF	00	OFF	00	OFF	00	OFF	00	MON	01	0
MON	01	MON	01	MON	01	1WR	10	OFF	00	0
AL	11	AL	11	AL	11	AL	11	AL	11	1
1WR	10	1WR	10	1WR	10	AL	11	OFF	00	0
		D1 D0		D1 D0		D1 D0		D1 D0		


After we get the state/transition table, we build the K-Maps to simplify expressions for D1, D0, and Alarm.

- D1 K-Map:

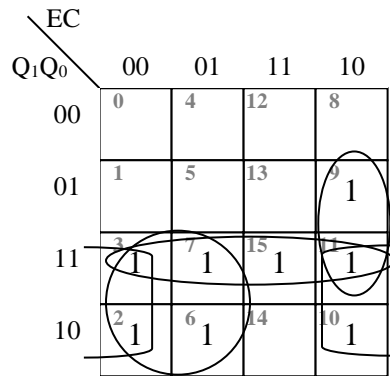

$$D_1 = Q_1Q_0 + \text{ENTER}'Q_1 + \text{CORRECT}'Q_1 + \text{CORRECT}'\cdot\text{ENTER}\cdot Q_0$$

- D0 K-Map:

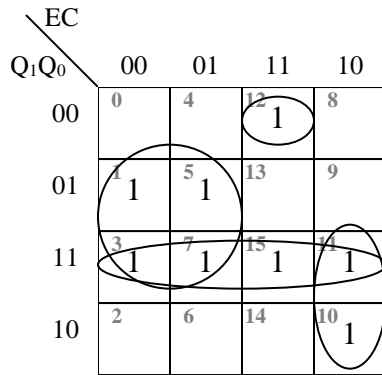

$$D_0 = Q_1Q_0 + \text{ENTER}'\cdot Q_0 + \text{ENTER}\cdot\text{CORRECT}'\cdot Q_1 + E C Q_1' Q_0'$$

- Alarm K-Map:


EC Q ₁ Q ₀		00	01	11	10
		00	01	11	10
00	0	4	12	8	
	1	5	13	9	
01	3	7	15	11	
	1	1	1	1	
10	2	6	14	10	

$$\text{Alarm} = Q_1Q_0$$

- The initial state is OFF which has the code $Q_1Q_0=00$. Thus we want both flip-flops to initialize to 0. To do this, connect RESET to the CLR inputs and tie the SET/PRE inputs to GND (never want to initialize to 1).

4. (a.)

(1) First, we build the state diagram.

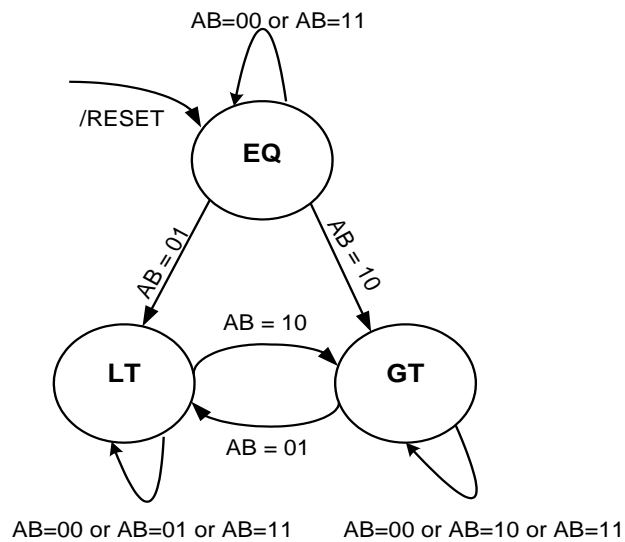

(2) Because we have 3 states in the state diagram, we use two D flip-flops to implement state memory. We design the combinational logic for the next-state logic and the output function logic by building up the state/transition table.

Curr. State		Next State						Output				
Sym.	Q_1Q_0	A B = 00		A B = 01		A B = 11		A B = 10		EQ	LT	GT
		Sym.	$Q_1^*Q_0^*$	Sym.	$Q_1^*Q_0^*$	Sym.	$Q_1^*Q_0^*$	Sym.	$Q_1^*Q_0^*$			
GT	00	GT	00	LT	11	GT	00	GT	00	0	0	1
EQ	01	EQ	01	LT	11	EQ	01	GT	00	1	0	0
LT	11	LT	11	LT	11	LT	11	GT	00	0	1	0
X	10	X	d d	X	d d	X	d d	X	d d	X	X	X
		$D_1 D_0$		$D_1 D_0$		$D_1 D_0$		$D_1 D_0$				

(3) Build the K-Maps to simplify expressions for D_1 , D_0 , EQ, LT and GT.

- D_1 K-Map:

		AB			
		00	01	11	10
Q ₁ Q ₀	00	0	1	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10
		d	d	d	d

$$D_1 = A'B + A'Q_1 + BQ_1$$

- D_0 K-Map:

		AB			
		00	01	11	10
Q ₁ Q ₀	00	0	1	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10
		d	d	d	d

$$D_0 = A'B + A'Q_0 + BQ_0$$

- EQ K-Map:

$$EQ = Q_1'Q_0 \quad \text{or} \quad EQ = Q_1 \text{ xor } Q_0$$

- LT K-Map:


$$LT = Q_1$$

- GT K-Map:

$$GT = Q_0'$$

- The initial state is EQ which has the code $Q_1Q_0=01$. Thus we want Q_1 to initialize to 0. To do this, connect RESET to the CLR input and tie the SET/PRE input to GND (never want to initialize to 1). However we want Q_0 to initialize to 1. To do this, connect RESET to the PRE/SET input and tie the CLR input to GND (never want to initialize to 0).


The waveform is below:

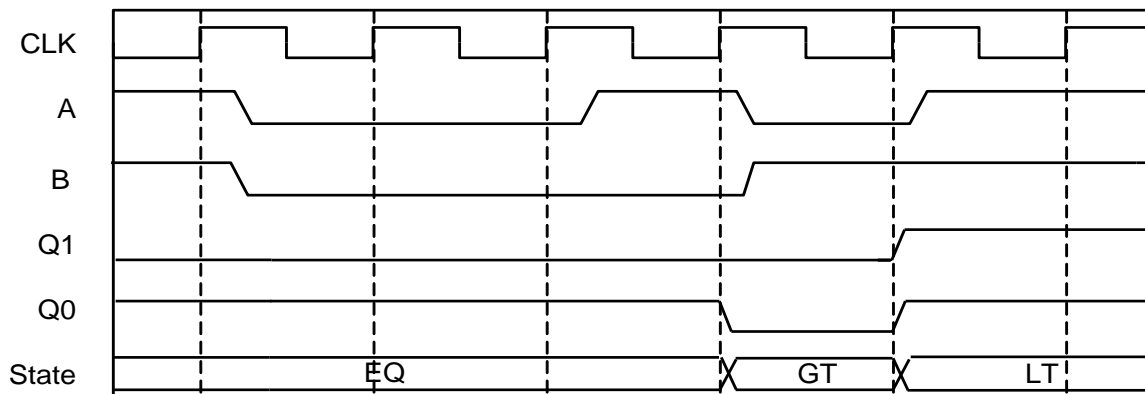

5. (a.) We need 8 states and each of them stores one 3-bit binary number ranging from 000 to 111.

State	S0	S1	S2	S3	S4	S5	S6	S7
Assignment (Q ₂ Q ₁ Q ₀)	000	001	010	011	100	101	110	111

The state diagram is below:

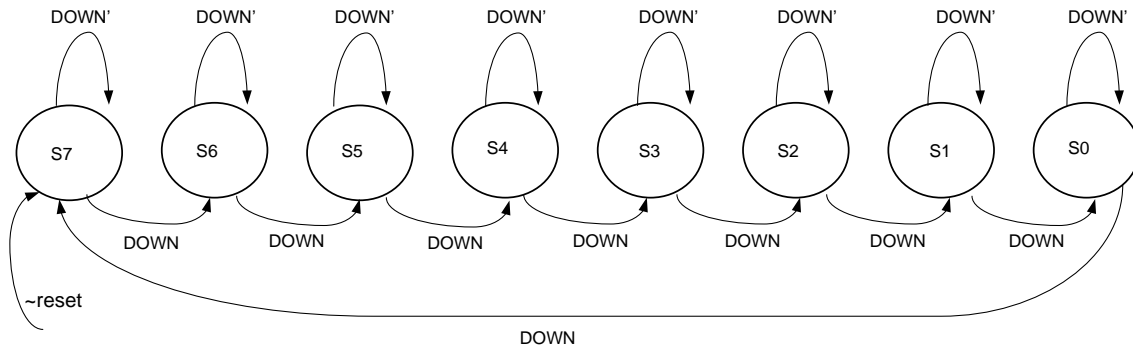

- (b) Because we have 8 states in the state diagram, we use three D flip-flops to implement state memory.

We design the combinational logic for the next-state logic and the output function logic by building up the state/transition table.

Current State		Next State / Output (Q _i is the output)			
		DOWN = 0		DOWN = 1	
Symbol	Q ₂ Q ₁ Q ₀	Symbol	Q ₂ * Q ₁ * Q ₀ *	Symbol	Q ₂ * Q ₁ * Q ₀ *
S0	0 0 0	S0	0 0 0	S7	1 1 1
S1	0 0 1	S1	0 0 1	S0	0 0 0
S2	0 1 0	S2	0 1 0	S1	0 0 1
S3	0 1 1	S3	0 1 1	S2	0 1 0
S4	1 0 0	S4	1 0 0	S3	0 1 1
S5	1 0 1	S5	1 0 1	S4	1 0 0
S6	1 1 0	S6	1 1 0	S5	1 0 1
S7	1 1 1	S7	1 1 1	S6	1 1 0
			D2 D1 D0		D2 D1 D0

After we get the state/transition table, we build the K-Maps to simplify expressions for D₂, D₁, D₀.

- D₂ K-Map:

DQ ₂ \ Q ₁ Q ₀	00	01	11	10
00	0	4 1	12	8 1
01	1	5 1	13 1	9
11	3	7 1	15 1	11
10	2	6 1	14 1	10

$$D_2 = D'Q_2 + Q_2Q_0 + Q_2Q_1 + DQ_2'Q_1'Q_0'$$

- D₁ K-Map:

DQ ₂ \ Q ₁ Q ₀	00	01	11	10
00	0	4	12 1	8 1
01	1	5	13	9
11	3 1	7 1	15 1	11 1
10	2 1	6 1	14	10

$$D_1 = Q_1Q_0 + D'Q_1 + DQ_1'Q_0'$$

- D₀ K-Map:

DQ ₂ \ Q ₁ Q ₀	00	01	11	10
00	0	4	12 1	8 1
01	1 1	5 1	13	9
11	3 1	7 1	15	11
10	2	6	14 1	10 1

$$D_0 = D'Q_0 + DQ_0'$$

- The initial state is 111 which has the code $Q_2Q_1Q_0=111$. Thus we want all flip-flops to initialize to 1. To do this, connect RESET to the PRE/SET inputs and tie the CLR inputs to GND (never want to initialize to 0).

(c) The waveform is below:

