

Spiral 1 / Unit 1

Combinational vs. Sequential Logic
Latency vs. Throughput (Pipelining)
Digital Design Goals
Logic Functions

Spiral Content Mapping

Spiral	Theory	Combinational Design	Sequential Design	System Level Design	Implementation and Tools	Project
1	<ul style="list-style-type: none"> Performance metrics (latency vs. throughput) Boolean Algebra Canonical Representations 	<ul style="list-style-type: none"> Decoders and muxes Synthesis with min/maxterms Synthesis with Karnaugh Maps 	<ul style="list-style-type: none"> Edge-triggered flip-flops Registers (with enables) 	<ul style="list-style-type: none"> Encoded State machine design 	<ul style="list-style-type: none"> Structural Verilog HDL CMOS gate implementation Fabrication process 	
2		<ul style="list-style-type: none"> Multi-bit adders Registers Counters Combinational design 	<ul style="list-style-type: none"> Bistables, latches, and flip-flops Counters Multiplexers 	<ul style="list-style-type: none"> Control state machine design Control path decomposition Decomposition 	<ul style="list-style-type: none"> ASIC theory Capacitors Delay and timing Memory Verilog 	
3				<ul style="list-style-type: none"> Memory Arithmetic Bus level testing Simple logic CPU 	<ul style="list-style-type: none"> Power and other topics EDA design process 	

Outcomes


- I know the difference between combinational and sequential logic and can name examples of each.
- I understand latency, throughput, and at least 1 technique to improve throughput
- I can identify when I need state vs. a purely combinational function
 - I can convert a simple word problem to a logic function (TT or canonical form) or state diagram
- I can use Karnaugh maps to synthesize combinational functions with several outputs
- I understand how a register with an enable functions & is built
- I can design a working state machine given a state diagram
- I can implement small logic functions with complex CMOS gates

COMBINATIONAL VS. SEQUENTIAL


Combinational vs. Sequential Logic

- All logic is categorized into 2 groups
 - Combinational logic:
 - Outputs = $f(\text{_____})$
 - Sequential Logic
 - Outputs = $f(\text{_____})$
 - Sequential logic has the notion of “_____” (remembering inputs or events that happened in the past)

Combinational vs. Sequential

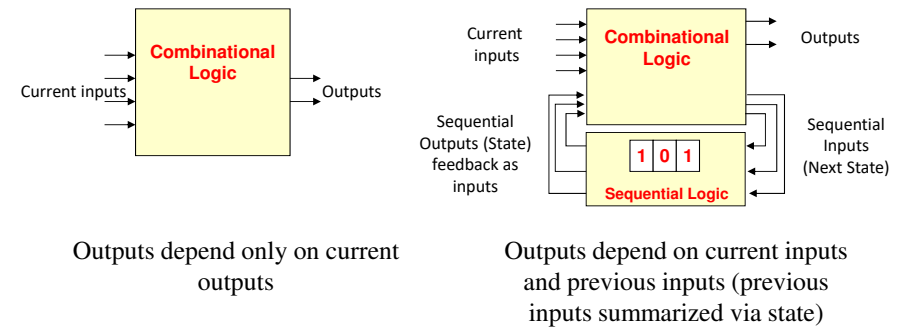


 Combinational Example: Staircase Light Switch




Water Tank Problem

 - Build a control system for a pump to keep the tank from going empty



Combinational Logic

 
- With *combinational logic* the outputs only depend on what the inputs are _____



It doesn't matter what the inputs were _____


Logic Functions

 - Map input combinations of n-bits to desired m-bit output
- Can describe function with a _____ and then find its circuit implementation




IN0	IN1	IN2	OUT0	OUT1
0	0	0	0	1
0	0	1	1	1
	...			
1	1	1	0	0


Logic Example

 

Sequential Example: Remote Control


 


 The channel is a state-dependent function of the first button pressed and the second (we must remember the 3 and then use it with the 2)




Registers

  - Registers are the most common sequential device
- Registers sample the data input (D) on the edge of a clock pulse (CP) and stores that value at the output (Q)
- Analogy: Taking a picture with your digital camera...when you press a button (clock pulse) the camera samples the scene (input) and _____ it as a snapshot (output) until the next trigger



Flip-Flops

 
- Flip-flops are the building blocks of registers
 - 1 Flip-flop PER bit of input/output
 - There are many kinds of flip-flops but the most common is the D- (Data) Flip-flop (a.k.a. D-FF)
- D Flip-flop triggers on the clock edge and captures the D-value at that instant and causes Q to remember it until the next edge
 - Positive Edge: instant the clock transition from low to high (0 to 1)



Registers and Flip-flops


- A register is simply a group of D flip-flops that all trigger on a single clock pulse

CLK	Q_{t+1}
Steady level of 0 or 1	Q_t
	Q_t
Positive Edge	D_t

 

Pulses and Clocks

- Registers need an edge to trigger
- We can generate pulses at specific times (creating an irregular pattern) when we know the data we want has arrived
- Other registers in our hardware should trigger at a regular interval
- For that we use a clock signal...
 - Alternating high/low voltage pulse train
 - Controls the ordering and timing of operations performed in the processor
 - 1 cycle is usually measured from rising/positive edge to rising/positive edge
- Clock frequency (F) = # of cycles per second
- Clock Period (T) = 1 / Freq.

 

Summary

- Combinational logic
 - Perform a specific function (mapping of 2^n input combinations to desired output combinations)
 - No internal state or feedback
 - Given a set of inputs, we will always get the same output after some time (propagation) delay
- Sequential logic (“Storage” devices)
 - Registers made up of flip-flops/latches are the fundamental building blocks
 - Controlled by a “clock” signal
 - Sample data on a “clock” edge and remember that value until the next edge

Combinational vs. Sequential

- Sequential logic (i.e. registers) is used to store values (“storage devices”)
 - A register in HW is analogous to a _____ in SW (a variable or register stores a value until needed at a later time)
- Combinational logic is used to process bits (i.e. perform operations on values)
 - Combinational logic in HW is analogous to _____ (_____) in SW

THROUGHPUT & LATENCY

Performance Depends on View Point?!


- What's faster:
 - A 747 Jumbo Airliner
 - An F-22 fighter jet
- If you are an individual interested in getting from point A to point B, then the _____
 - This is known as _____ [units of _____]
 - Time from the start of an operation until it completes
- If you are trying to _____ a large number of people, the _____ looks much better
 - This is known as _____ [units of _____]

Throughput vs. Latency

- If Latency is the **Time** it takes to perform **1 Job** to complete and Throughput = **Jobs / Time**...
- ...Is Throughput = **1 / Latency**?
- _____!
 – Latency is from the perspective of a _____
 – Throughput is from the perspective of _____
 – Parallelism is the great friend of throughput!
- We will see many times in this course some strategies for improving throughput and sometimes latency


Clocking Methodologies

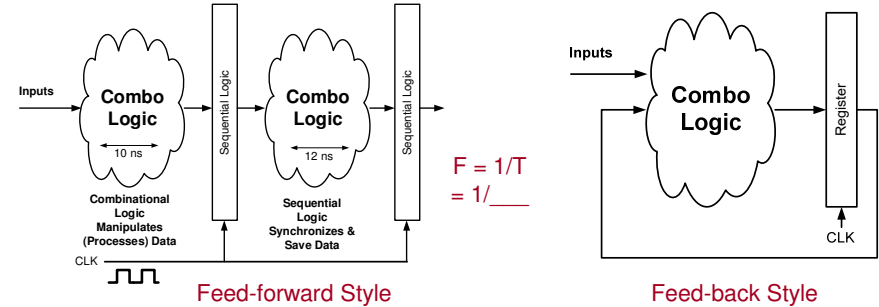- Typical designs use both combinational and sequential logic
 - Sequential logic: saves and synchronize data
 - Combinational logic: performs some operation on the data
- Can use feed-forward or feed-back methodology
- Clock cycle must be set for the _____ between registers



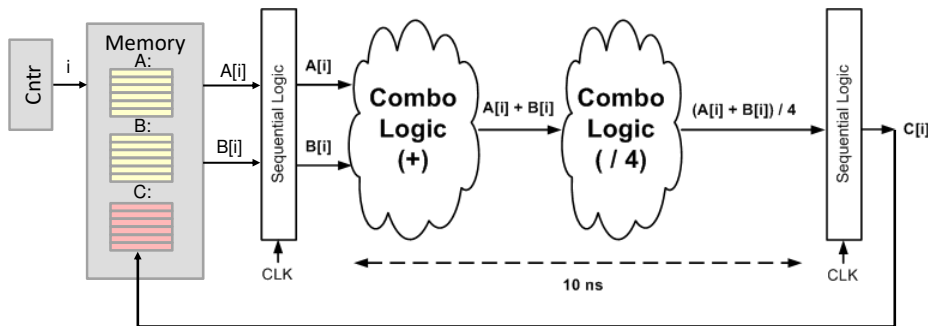Example


```
for(i=0; i < 100; i++)
    C[i] = (A[i] + B[i]) / 4;
```



10 ns per input set = _____ ns total

Pipelining Example
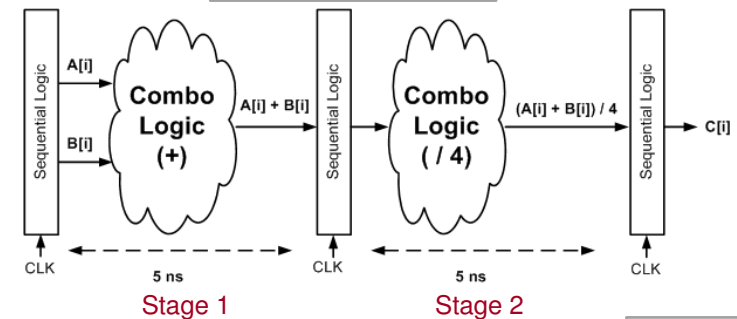
```
for(i=0; i < 100; i++)
    C[i] = (A[i] + B[i]) / 4;
```




	Stage 1	Stage 2
Clock 0	A[0] + B[0]	
Clock 1		
Clock 2		

Pipelining refers to insertion of registers to _____ combinational logic into smaller stages that can be _____ in time (i.e. create an assembly line)

Need for Registers

 - Provides separation between combinational functions
 - Without registers, fast signals could _____ to data values in the next operation stage




SW vs. HW Sorting (MergeSort)

REAL-WORLD EXAMPLE

Sorting: Software Implementation

 - Let's select a "good" sorting algorithm: mergesort
 - To sort n elements takes time $O(\text{_____})$
 - Big-O (e.g. $O(f(n))$) just means exec. time is roughly proportional to $f(n)$
- Let's then compare the performance of a SW implementation vs. a hardware-accelerated process




Merge Two Sorted Lists

- Consider the problem of merging two sorted lists into a new combined sorted list
- Keep a "read" pointer ($r1$ and $r2$) for each sorted array and a "write" (w) pointer to the destination
- Key concept: One comparison yields correct placement of 1 number in the output
 - Implies runtime of merge is $O(n)$


0 1 2 3
3 7 6 8 **Inputs Lists**

0 1 2 3
3 6 7 8 **Merged Result**

 


Recursive Sort (MergeSort)

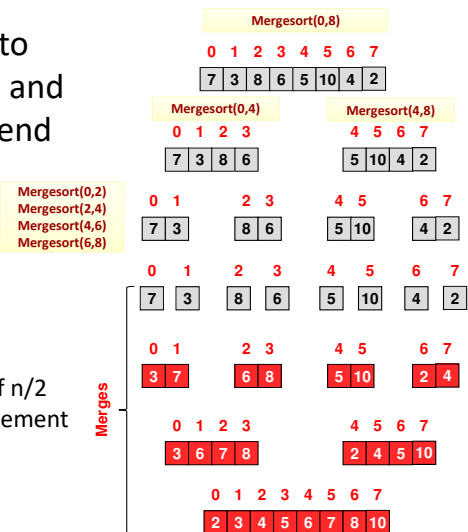- Break sorting problem into smaller sorting problems and merge the results at the end
- Mergesort(0..n)
 - If list is size 1, return
 - Else
 - Mergesort(0..n/2 - 1)
 - Mergesort(n/2 .. n)
 - Combine each sorted list of n/2 elements into a sorted n-element list




Recursive Sort (MergeSort)

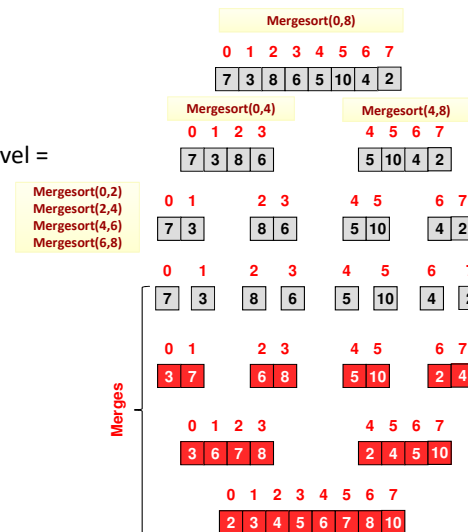- Run-time analysis
 - # of recursion levels = _____
 - Total operations to merge each level = _____
 - _____ operations total to merge two lists over all recursive calls at a particular level
- Mergesort = $O(n * \log_2(n))$




Sorting: Software Implementation

 - To perform the algorithm in software means the processor fetches instructions, executes them, which causes the processor to then read and write the data in memory into it's sorted positions
- **Sorting 64 element on a 2.8 GHz Xeon processor**
 - _____ microseconds
- **Can we do better w/ more HW?**



HW Sort Network

 - Start with a small building block in HW: **compare_and_swap (CAS)**
 - _____ input passed to Y0 and _____ to Y1




compare_and_swap
HW block diagram

```

if( X0 < X1 ) {
    Y0 = X0;  Y1 = X1;
} else {
    Y0 = X1;  Y1 = X0;
}
    
```


SW-Equiv.
Operation

 


HW Schematic

HW Sort Network

 - Now we can use multiple CAS blocks to sort multiple values




4-Input/Output Sorting Network

 

Simplified Diagram
(Each vertical line is a CAS between the attached elements)

<http://dbis.cs.tu-dortmund.de/cms/en/publications/2012/sorting-networks/sorting-networks.pdf>


HW Sort Network Example

 

<http://dbis.cs.tu-dortmund.de/cms/en/publications/2012/sorting-networks/sorting-networks.pdf>


HW Implementation

 - A full 64-input/output sorting network in HW may not be feasible due to number of input/output signals
- Let us use an 8-input/output sorting network
 - Use it _____ to produce 8 groups of 8 sorted numbers
 - Then _____ the 8 groups of 8 into a single group of 64




First Stage Sorting

 - We will read 8 numbers in 8 clocks from memory
- Sorting can be performed in a _____ and the outputs saved
- We will read in 8 new numbers while we place the previous group of 8 sorted numbers into a Queue/FIFO (_____)
- The next sorted group will go into a 2nd FIFO to be merged with the first




Select-Value Unit

 - Now that we have 2 sorted sequences of size N we need to merge them into a single sorted sequence of size _____
- We can design a "Select-Value" unit shown below




Merge Stages

 - If we have a total of 64 numbers to sort we can arrange our merging in stages
 - We can continue to merge until we get one sequence of 64 (the desired size)




Recall we merge two groups into 1

 


Merge Stages

 - We can overlap each stage
 - Merge 2 groups of 8 while we merge 2 groups of 16, etc.
 - Without care, data that is output from one stage may overwrite data in the next stage that has yet to be merged





Double (Ping-Pong) Buffers

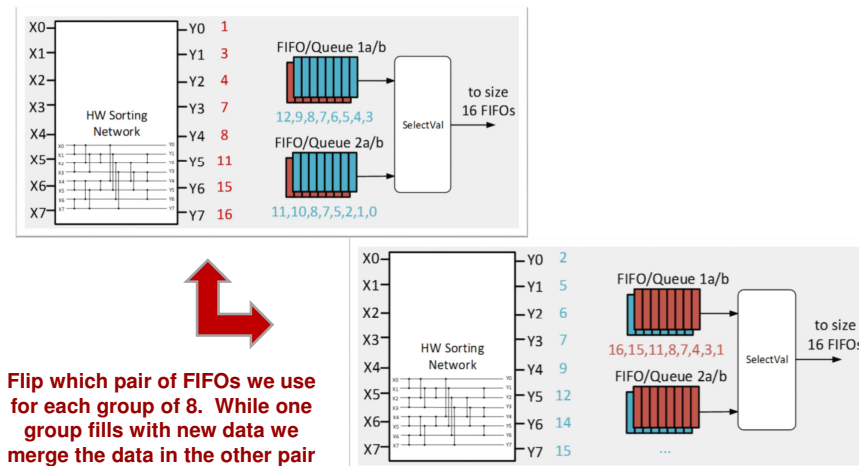- Need two sets of FIFOs at each stage (ping-pong buffers) where 1 set is used to fill while we process the other




Sorting: Hardware Implementation

  - Sorting 64 element on a 2.8 GHz Xeon processor [SW only]
 - 16 microseconds
- Sorting 64 numbers in [old] custom HW
 - CLK period = 30 ns => **30 microseconds total**
 - 30 ns is due to the 8 number HW sorter
 - Merging (Select-Val) stages are < 10 ns
 - Can we improve?




Pipelined Sorter

 - Cut sorting network into 3 stages
- In any stage a signal encounters ___ compare-and-swap elements



Sorting: Final Comparison

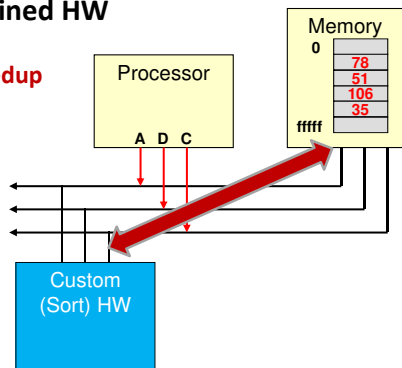- Sorting 64 element on a 2.8 GHz Xeon processor [SW only]
 - 16 microseconds total time
- Sorting 64 numbers in [old] custom HW
 - CLK period = 30 ns => 6 microseconds total = ~2.5x speedup
- Sorting 64 numbers in [old] pipelined HW
 - CLK period = 10 ns => **__ microseconds total = ~__ x speedup**
 - Processor is freed to do other work




Basic Gates

DIGITAL LOGIC

Digital Logic


- Digital Logic is built on...
 - Binary variables can be only one of two possible values (e.g. 0 or 1)
 - Three operations on binary variables
 - AND (all inputs true => output is true)
 - OR (any inputs true => output is true)
 - NOT (output is opposite of input)

AND, OR, NOT Gates

 


NOT (Inverter)
 
$$Z = X' \text{ or } \overline{X} \text{ or } \sim X$$



AND

$$Z = X \cdot Y$$

 

OR

$$Z = X + Y$$

X	Z
0	1
1	0

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

AND = 'ALL'
(true when ALL
inputs are true)

OR = 'ANY'
(true when ANY
input is true)

Gates

 - Gates can have more than 2 inputs but the functions stay the same
 - AND = output = 1 if _____ inputs are 1
 - Outputs 1 for only 1 input combination
 - OR = output = 1 if _____ input is 1
 - Outputs 0 for only 1 input combination



X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


3-input AND



X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


3-input OR

NAND and NOR Gates

 

NAND

$$Z = \overline{X \cdot Y}$$

 

NOR

$$Z = \overline{X + Y}$$

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND



X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

NAND

True if NOT ALL
inputs are true

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

OR




X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

NOR

True if NOT ANY
input is true

XOR and XNOR Gates

 


XOR

$$Z = X \oplus Y$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

 True if an **odd** # of inputs are true
2 input case: True if inputs are different



XNOR

$$Z = \overline{X \oplus Y}$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

True if an **even** # of inputs are true
2 input case: True if inputs are same

Speed, area, and power

DIGITAL DESIGN GOALS

Digital Design Goals

- When designing a circuit, we want to optimize for the following three things:
 - _____ (minimize)
 - Speed (maximize) / Delay (minimize)
 - _____ (minimize)
- Can usually only optimize 2 of the 3
 - There is a huge trade space! This is what engineering is all about!

Minimizing Circuit Area


- Approaches:
 - Reduce the _____ used to implement a circuit
 - Reduce the number of _____ to each gate
 - In general a gate with n inputs requires ____ transistors to implement
- Simplify logic expressions (usually by factoring and then canceling terms) to reduce the number of gates

Maximizing Speed

- Speed is affected by:
 - Levels of logic (path length)
 - _____
 - Number of _____ to the gate
 - Number of outputs a gate connects to (fan-out)
 - Feature size and implementation technology


Levels of Logic

 - Definition: _____ number of gates [not including inverters] on _____ path from an input to the output



Gate Delays

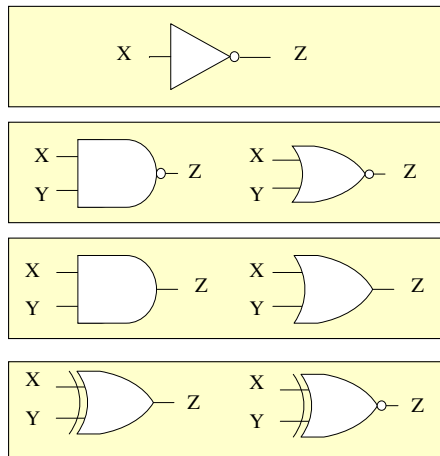- Order the gate types (1,2,3,4) in terms of fastest to slowest?
- Typical gate delay for a 2-input NAND or NOR is under a _____ ps.



Summary

- When designing a circuit, we want to optimize for the following three things:
 - Area (minimize)
 - Use fewer number of gates
 - Use gates w/ fewer inputs
 - Speed (maximize) / Delay (minimize)
 - Fewer levels of logic
 - Levels of logic = max. # of gates on a path from ANY input to output
 - Relative speed of gates: INV, NAND/NOR, AND/OR, XOR/XNOR
 - Power (minimize)
 - How much energy the circuit consumes when switching between 0 and 1
- Can usually only optimize 2 of the 3

LOGIC FUNCTIONS INTRO

Arithmetic vs. Logic Functions

Arithmetic $\Rightarrow f(x_1, x_2, \dots, x_n)$


- Domain $\Rightarrow \{\text{Real}\}^n$
- Range $\Rightarrow \text{Real}$

Logic $\Rightarrow f(x_1, x_2, \dots, x_n)$

- Domain $\Rightarrow \{0, 1\}^n$
 - Vector of n zeros or ones
 - 2^n such vectors are possible
- Range $\Rightarrow \{0, 1\}$

Logic Functions

 - Map input combinations of n-bits to desired m-bit output
 - When we design logic circuits we must describe the output for _____ possible input combination
 - Can describe function with a truth table and then find its circuit implementation



IN0	IN1	IN2	OUT0	OUT1
0	0	0	0	1
0	0	1	1	1
	...			
1	1	1	0	0

Logic Function Domain

- Should specify ALL input combinations
- Most common representation is a truth table
 - For those with SW experience, think of this as a large if..else if or switch structure to categorize the input

X	Y	Z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Truth Table

```

if(x,y,z == 000) then
...
else if (x,y,z == 001) then
...
else if (x,y,z == 010) then
...
    
```

If or Case statement

3-bit Prime Number Function

- Should specify **ALL** input combinations
- Most common representation is a **truth table**
 - For those with SW experience, think of this as a large if..else if or switch structure to categorize the input

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Primes between 0-7

Truth Table

OFF-set

ON-set

if(x,y,z == 000) then
P = 0
else if (x,y,z == 001) then
P = 0
else if (x,y,z == 010) then
P = 1
If or Case statement

ON-Set (terms) : Combinations where output=1
OFF-Set (terms) : Combinations where output=0

Multi-output Functions

- N-inputs, m-outputs
 - Rather than simply T/F output, may want to produce a set of signals (i.e. a multi-bit number, etc.)
- Write out all combos, interpret combos, then write in answer

I3	I2	I1	C1	C0
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

1's Count of Inputs

I3	I2	I1	M1	M0
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


Encode the highest input ID (ie. 3, 2, or 1) that is ON (=1)

Logic Function Examples

- Billy likes pizza but can only afford one-topping: **S**ausage, **P**epperoni, and **M**ushrooms. But today only there is a sale on a mushroom and sausage pizza.
- What pizza's can Billy afford? Describe this function with a truth table.

Logic Functions

 - 3 possible representations of a function
 - Equation
 - Schematic
 - Truth Table
- Can convert between representations
- Truth table is only _____ representation*
- We need a way to " _____ " (convert from TT to equation/schematic) a function




* Canonical Sums/Products (minterm/maxterm) representation provides a standard equation/schematic form that is unique per function

 Example: Automobile Buzzer

- Consider an automobile warning **Buzzer** that sounds if you leave the **Key** in the ignition and the **Door** is open **OR** the **Headlights** are on and the **Door** is open.
- We can easily derive an equation and implementation: $B = \underline{\hspace{2cm}}$

Key in Ignition $\underline{\hspace{1cm}}$ K
 Door Opened $\underline{\hspace{1cm}}$ D
 Headlights on $\underline{\hspace{1cm}}$ H
 Door Opened $\underline{\hspace{1cm}}$ D




B =

Example: Automobile Buzzer

- But we see that we can alter this equation...
 - From $B = KD + HD$
 - To $B = \underline{\hspace{2cm}}$
 - Buzzer sounds if the Door is open and *either* the Key is in the Ignition or the Headlights are on
- Which is better?
- Notice that equations/circuit are not unique
 - The truth table would be the same for both (i.e. unique)


D	K	H	B
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Truth Table is Unique

 

Non-unique circuit/equation

 Door Opened $\underline{\hspace{1cm}}$ D
 Key in Ignition $\underline{\hspace{1cm}}$ K
 Headlights on $\underline{\hspace{1cm}}$ H



Non-unique circuit/equation