

## Spiral 1 / Unit 3

Minterm and Maxterms

Canonical Sums and Products

2- and 3-Variable Boolean Algebra Theorems

DeMorgan's Theorem

Function Synthesis use Canonical  
Sums/Products

## Outcomes

- I know the difference between combinational and sequential logic and can name examples of each.
- I understand latency, throughput, and at least 1 technique to improve throughput
- I can identify when I need state vs. a purely combinational function
  - I can convert a simple word problem to a logic function (TT or canonical form) or state diagram
- I can use Karnaugh maps to synthesize combinational functions with several outputs
- I understand how a register with an enable functions & is built
- I can design a working state machine given a state diagram
- I can implement small logic functions with complex CMOS gates

## SYNTHESIZING LOGIC FUNCTIONS

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Primes between 0-7

I3	I2	I1	C1	c0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


1's Count of Inputs

- Given a logic function, how do we arrive at a circuit to implement this combinational function?

## The Problem

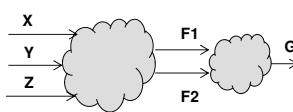
## Combining Functions

- Given intermediate functions F1 and F2, how could you use AND, OR, NOT to make G



X	Y	Z	F1	F2	G
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	1	1	0

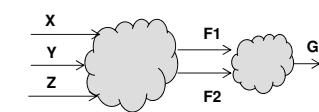- Given intermediate functions F1 and F2, how could you use AND, OR, NOT to make G




X	Y	Z	F1	F2	G
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	1	1	0

X	Y	Z	F1	F2	F1	F2'	___
0	0	0	0	0	0	1	0
0	0	1	1	0	1	1	1
0	1	0	1	0	1	1	1
0	1	1	1	0	1	1	1
1	0	0	1	0	1	1	1
1	0	1	1	0	1	1	1
1	1	0	1	0	1	1	1
1	1	1	1	1	1	0	0

$G = \underline{\hspace{2cm}}$

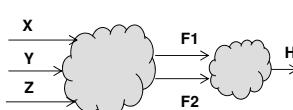
## Combining Functions

- Given intermediate functions F1 and F2, how could you use AND, OR, NOT to make H



X	Y	Z	F1	F2	H
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	1	1
0	1	1	1	1	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	0	1

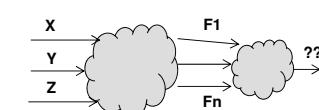- Is there a set of functions (F1, F2, etc.) that would allow you to build ANY 3-variable function
  - Think simple, think many



X	Y	Z	F1	F2	Fn	?
0	0	0				?
0	0	1				?
0	1	0				?
0	1	1				?
1	0	0				?
1	0	1				?
1	1	0				?
1	1	1				?



X	Y	Z	m0	m1	m2	m3	m4	m5	m6	m7	?
0	0	0									?
0	0	1									?
0	1	0									?
0	1	1									?
1	0	0									?
1	0	1									?
1	1	0									?
1	1	1									?

OR together any combination of m<sub>i</sub>'s

## Defining Minterms

- Remember these minterms are intermediate functions that we'll use to build larger functions
- Write the expression for each minterm of  $F(x,y,z)$

Row #		Minterm Expression	Minterms								
			x	y	z	$m_0$	$m_1$	$m_2$	$m_3$	$m_4$	$m_7$
0	$m_0$		0	0	0	1	0	0	0	0	0
1	$m_1$		0	0	1	0	1	0	0	0	0
2	$m_2$		0	1	0	0	0	1	0	0	0
3	$m_3$		0	1	1	0	0	0	1	0	0
4	$m_4$		1	0	0	0	0	0	0	1	0
5	$m_5$		1	0	1	0	0	0	0	0	1
6	$m_6$		1	1	0	0	0	0	0	0	1
7	$m_7$		1	1	1	0	0	0	0	0	1

## Applying Minterms to Synthesize a Function

- Each numbered minterm checks whether the inputs are equal to the corresponding combination. When the inputs are equal, the minterm will evaluate to 1 and thus the whole function will evaluate to 1.

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	$m_2$
0	1	1	$m_3$
1	0	0	$m_4$
1	0	1	$m_5$
1	1	0	$m_6$
1	1	1	$m_7$

use...

$$P = m_2 + m_3 + m_5 + m_7 \\ = x'yz' + x'yz + xy'z + xyz$$

when  $x,y,z = \{0,1,0\} = 2$  then

$$P = 0 \cdot 1 \cdot 0 + 0 \cdot 1 \cdot 0 + 0 \cdot 1 \cdot 0 + 0 \cdot 1 \cdot 0 \\ = 1 + 0 + 0 + 0 = 1$$

when  $x,y,z = \{1,0,1\} = 5$  then



$$P = 1 \cdot 0 \cdot 1 + 1 \cdot 0 \cdot 1 + 1 \cdot 0 \cdot 1 + 1 \cdot 0 \cdot 1 \\ = 0 + 0 + 1 + 0 = 1$$

when  $x,y,z = \{0,0,1\} = 5$  then

$$P = 0 \cdot 0 \cdot 1 + 0 \cdot 0 \cdot 1 + 0 \cdot 0 \cdot 1 + 0 \cdot 0 \cdot 1 \\ = 0 + 0 + 0 + 0 = 0$$
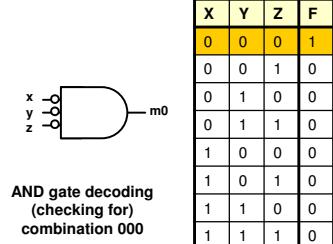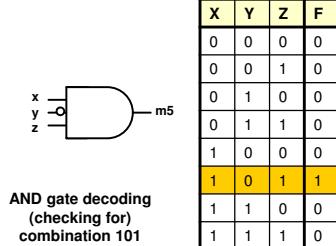
## Checkers / Decoders

- The  $m_i$  functions on the previous slide are just AND gate checkers
  - That combination can be changed by adding inverters to the inputs
  - We can think of the AND gate as "checking" or "decoding" a specific combination and outputting a '1' when it matches.



- A minterm can be generated for every combination of inputs
- Each minterm is the AND'ing of variables that will evaluate to 1 for only that combination
- A minterm "checks" or "decodes" a specific input combination and outputs 1 when found

Minterm 3	x	y	z	f
011 = $x' \cdot y \cdot z = m_3$	0	0	0	0
	0	0	1	0
	0	1	0	1
Minterm 5	0	1	1	1
101 = $x \cdot y' \cdot z = m_5$	1	0	0	0
	1	0	1	1
	1	1	0	0
	1	1	1	1

To make the minterm, complement the variables that equal 0 and leave the variables in their true form that equal 1.

## Using Decoders to Implement Functions


- Given an any logic function, it can be implemented with the superposition of decoders/checkers

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

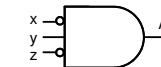


X	Y	Z	A
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

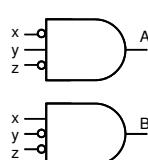


X	Y	Z	A	B
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

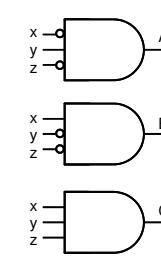


X	Y	Z	A	B	C
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	1

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

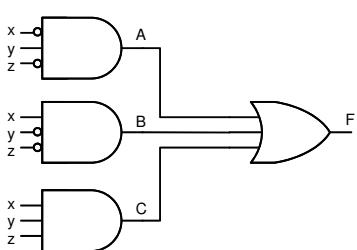


X	Y	Z	A	B	C	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	A	B	C	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

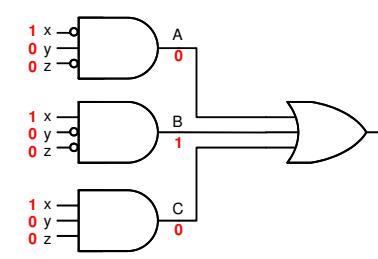


X	Y	Z	A	B	C	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

$$F(1,0,0) = 1$$

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

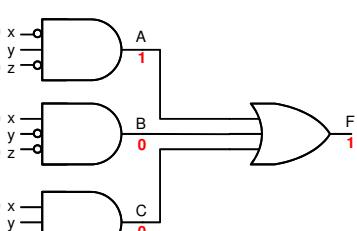


$$F(0,1,0) = 1$$

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

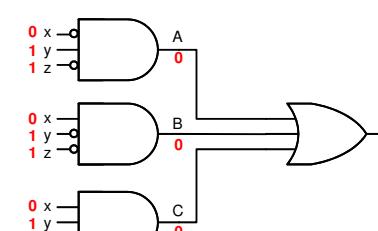

$$F(0,1,1) = 0$$

# Minterm Definition

- Minterm:** A product term where each input variable of a function appears as exactly one literal
  - Are the following minterms of  $f(x,y,z) \Rightarrow$
  - $x'y'z$
  - $xyz$
  - $x'y$
  - $x+y+z$


# Minterms

- Consider  $F(A,B)$
- One minterm per combination of the input variables
- Only one minterm can evaluate to 1 at any time

A	B	F	$m_0$	$m_1$	$m_2$	$m_3$
A	B	$A' \cdot B'$	$A' \cdot B$	$A \cdot B'$	$A \cdot B$	
0	0	0	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	1

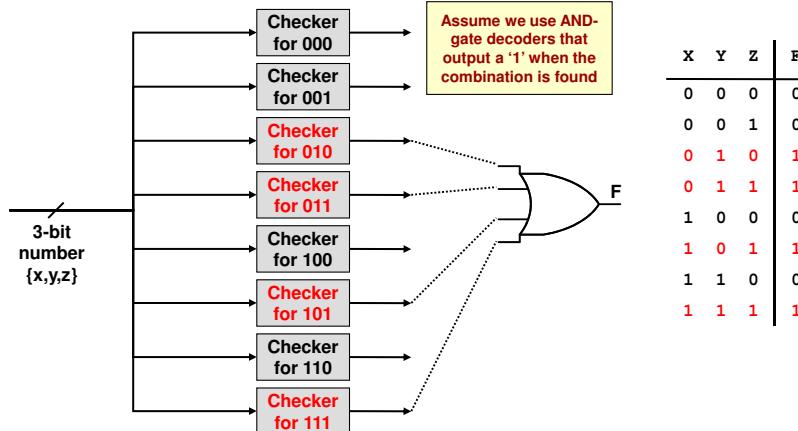
# Finding Equations/Circuits

- Given a function and checkers (called decoders) for each combination, we just need to OR together the checkers where  $F = 1$



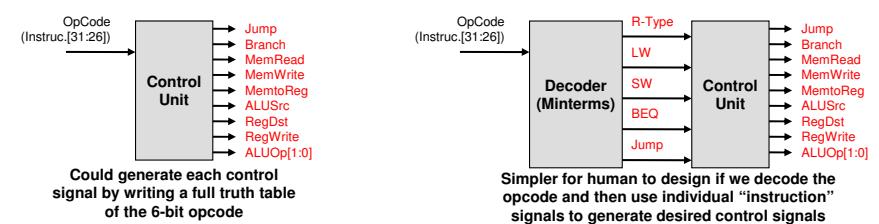
# Control Signal Generation

- Other control signals are a function of the opcode
- We could write a full truth table or (because we are only implementing a small subset of instructions) simply decode the opcodes of the specific instructions we are implementing and use those intermediate signals to generate the actual control signals




## Control Signal Truth Table

OpCode [5:0]	R-Type	LW	SW	BEQ	J	Jump	Branch	Reg Dst	ALU Src	MemtoReg	Reg Write	Mem Read	Mem Write	ALU Op[1]	ALU Op[0]
000000	1	0	0	0	0	0	0							1	0
100011	0	1	0	0	0	0	0							0	0
101011	0	0	1	0	0	0	0							0	0
000100	0	0	0	1	0	0	1							0	1
000010	0	0	0	0	1	1	0							X	X

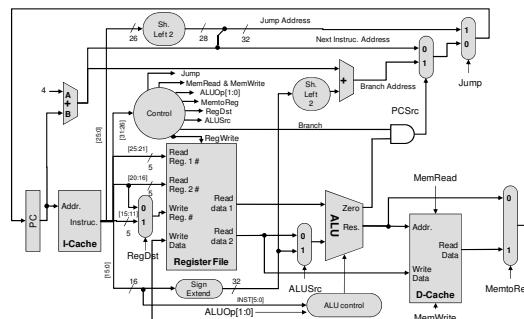


## Control Signal Logic

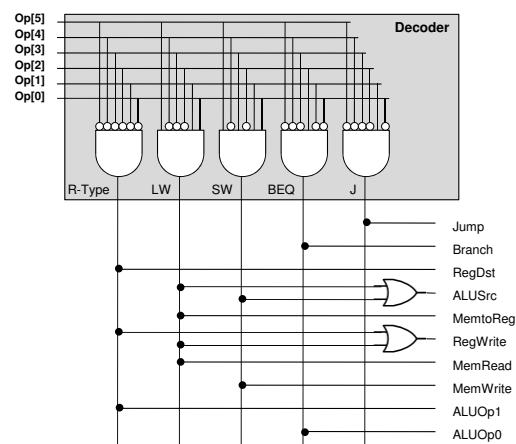

## Control Signal Truth Table

OpCode [5:0]	R-Type	LW	SW	BEQ	J	Jump	Branch	Reg Dst	ALU Src	MemtoReg	Reg Write	Mem Read	Mem Write	ALU Op[1]	ALU Op[0]	
000000	1	0	0	0	0	0	0	0	1	0	0	1	0	0	1	0
100011	0	1	0	0	0	0	0	0	0	1	1	1	1	0	0	0
101011	0	0	1	0	0	0	0	0	0	X	1	X	0	0	1	0
000100	0	0	0	1	0	0	1	0	1	X	0	X	0	0	0	1
000010	0	0	0	0	1	1	0				X	X	0	0	X	X

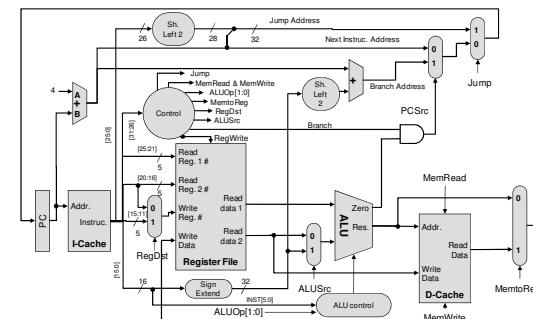

Using products of maxterms to implement a function

## MAXTERMS

## Question


- Is there a set of functions ( $F_1, F_2, \dots$ ) that would allow you to build ANY 3-variable function
  - Think simple, think many

X	Y	Z	F1	F2	Fn	?
0	0	0				?
0	0	1				?
0	1	0				?
0	1	1				?
1	0	0				?
1	0	1				?
1	1	0				?
1	1	1				?




X	Y	Z	m0	m1	m2	m3	m4	m5	m6	m7	?
0	0	0	1	0	0	0	0	0	0	0	?
0	0	1	0	1	0	0	0	0	0	0	?
0	1	0	0	0	1	0	0	0	0	0	?
0	1	1	0	0	0	1	0	0	0	0	?
1	0	0	0	0	0	0	1	0	0	0	?
1	0	1	0	0	0	0	0	1	0	0	?
1	1	0	0	0	0	0	0	0	1	0	?
1	1	1	0	0	0	0	0	0	0	1	?

OR together any combination of  $m_i$ 's

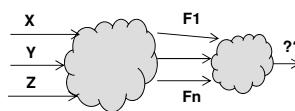
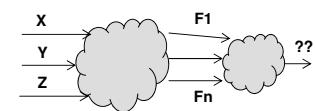
## Question

- OR...this set of functions would also work.



X	Y	Z	M0	M1	M2	M3	M4	M5	M6	M7	?	G
0	0	0									?	1
0	0	1									?	0
0	1	0									?	1
0	1	1									?	0
1	0	0									?	1
1	0	1									?	0
1	1	0									?	1
1	1	1									?	1

AND together any combination of  $M_i$ 's

$$G = M1 \bullet M3 \bullet M6$$

## Defining Maxterms

- Remember these maxterms are intermediate functions that we'll use to build larger functions
- Write the expression for each Maxterm of  $F(x,y,z)$

Row #		Maxterm	x	y	z	Maxterms							
						M <sub>0</sub>	M <sub>1</sub>	M <sub>2</sub>	M <sub>3</sub>	M <sub>4</sub>	M <sub>5</sub>	M <sub>6</sub>	M <sub>7</sub>
0	M <sub>0</sub>		0	0	0	0	1	1	1	1	1	1	1
1	M <sub>1</sub>		0	0	1	1	0	1	1	1	1	1	1
2	M <sub>2</sub>		0	1	0	1	1	0	1	1	1	1	1
3	M <sub>3</sub>		0	1	1	1	1	1	0	1	1	1	1
4	M <sub>4</sub>		1	0	0	1	1	1	1	0	1	1	1
5	M <sub>5</sub>		1	0	1	1	1	1	1	1	0	1	1
6	M <sub>6</sub>		1	1	0	1	1	1	1	1	1	0	1
7	M <sub>7</sub>		1	1	1	1	1	1	1	1	1	1	0

- Each numbered maxterm checks whether the inputs are equal to the corresponding combination. When the inputs are equal, the maxterm will evaluate to 0 and thus the whole function will evaluate to 0.

x	y	z	P	use...
0	0	0	0	M <sub>0</sub>
0	0	1	0	M <sub>1</sub>
0	1	0	1	
0	1	1	1	
1	0	0	0	M <sub>4</sub>
1	0	1	1	
1	1	0	0	M <sub>6</sub>
1	1	1	1	

$$\begin{aligned}
 P &= M_0 \bullet M_1 \bullet M_4 \bullet M_6 \\
 &= (x+y+z) \bullet (x+y+z') \bullet (x'+y+z) \bullet (x'+y+z')
 \end{aligned}$$

when  $x,y,z = \{0,0,1\} = 1$  then

$$\begin{aligned}
 P &= (0+0+1) \bullet (0+0+1') \bullet (0'+0+1) \bullet (0'+0'+1) \\
 &= 1 \bullet 0 \bullet 1 \bullet 1 = 0
 \end{aligned}$$

when  $x,y,z = \{1,1,0\} = 6$  then

$$\begin{aligned}
 P &= (1+1+0) \bullet (1+1+0') \bullet (1'+1+0) \bullet (1'+1'+0) \\
 &= 1 \bullet 1 \bullet 1 \bullet 0 = 0
 \end{aligned}$$


when  $x,y,z = \{1,1,1\} = 7$  then

$$\begin{aligned}
 P &= (1+1+1) \bullet (1+1+1') \bullet (1'+1+1) \bullet (1'+1'+1) \\
 &= 1 \bullet 1 \bullet 1 \bullet 1 = 1
 \end{aligned}$$
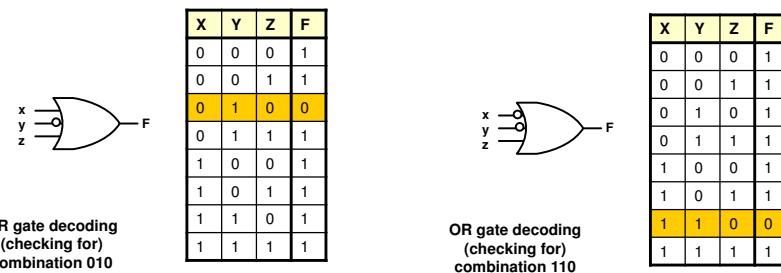
## Maxterm Definition


- Maxterm:** A sum term where each input variable of a function appears exactly once in that term (either in its true or complemented form)
  - $f(x,y,z) \Rightarrow$ 
    - $x' + y' + z$
    - $x + y + z$
    - $y + z'$
    - $x'y'z'$

- An OR gate only outputs '0' for 1 combination
  - That combination can be changed by adding inverters to the inputs
  - We can think of the OR gate as "checking" or "decoding" a specific combination and outputting a '0' when it matches.


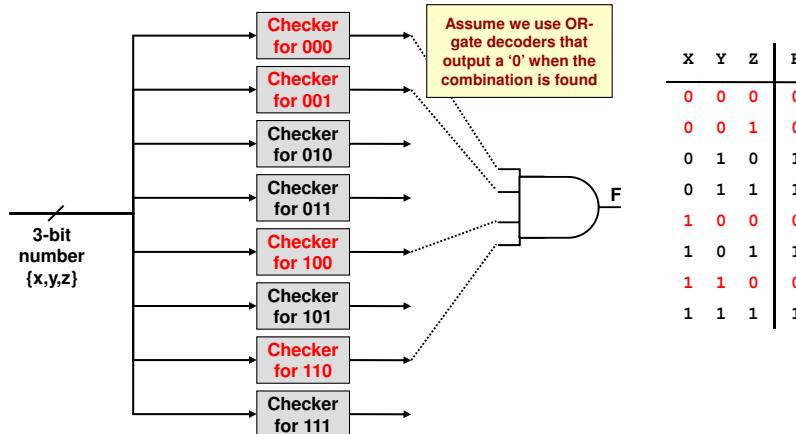
## Finding Equations/Circuits

- Given a function and checkers (called decoders) for each combination, we just need to AND together the checkers where F = 0



## LOGIC FUNCTION NOTATION

## Canonical Sums

- We \_\_\_\_\_ together all the minterms where  $F = 1$ 
  - $(\Sigma = \text{SUM or OR of all the minterms})$

$$F = m_2 + m_3 + m_5 + m_7$$

Canonical Sum:

$$F = \sum_{xyz} (2, 3, 5, 7)$$

List the minterms where  $F$  is 1.

	X	Y	Z	F
$m_0$	0	0	0	0
$m_1$	0	0	1	0
$m_2$	0	1	0	1
$m_3$	0	1	1	1
$m_4$	1	0	0	0
$m_5$	1	0	1	1
$m_6$	1	1	0	0
$m_7$	1	1	1	1

## Canonical Form Practice

- $G = \sum_{XYZ} ( ) = \prod_{XYZ} ( )$
  - $x \ y \ z \ g$
  - $0 \ 0 \ 0 \ 1$
  - $0 \ 0 \ 1 \ 0$
  - $0 \ 1 \ 0 \ 1$
  - $0 \ 1 \ 1 \ 0$
  - $1 \ 0 \ 0 \ 0$
  - $1 \ 0 \ 1 \ 1$
  - $1 \ 1 \ 0 \ 1$
  - $1 \ 1 \ 1 \ 0$
- 
- $B = \sum_{X,Y,Z} (5,6,7)$
  - $x \ y \ z \ f$
  - $0 \ 0 \ 0 \ 1$
  - $0 \ 0 \ 1 \ 1$
  - $0 \ 1 \ 0 \ 0$
  - $0 \ 1 \ 1 \ 0$
  - $1 \ 0 \ 0 \ 1$
  - $1 \ 0 \ 1 \ 1$
  - $1 \ 1 \ 0 \ 0$
  - $1 \ 1 \ 1 \ 1$

P. 60 and 61 in the Lecture Notes

## Canonical Products

- We \_\_\_\_\_ together all the maxterms where  $F = 0$

$$F = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

Canonical Product:

$$F = \prod_{xyz} (0, 1, 4, 6)$$


List the maxterms where  $F$  is 0.

	X	Y	Z	F
$M_0$	0	0	0	0
$M_1$	0	0	1	0
$M_2$	0	1	0	1
$M_3$	0	1	1	1
$M_4$	1	0	0	0
$M_5$	1	0	1	1
$M_6$	1	1	0	0
$M_7$	1	1	1	1
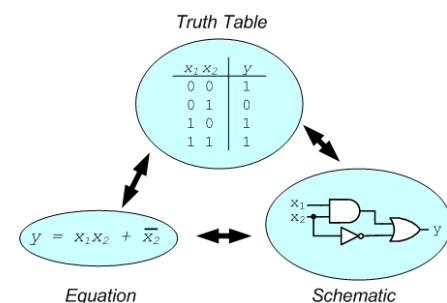
## Logic Functions

- A logic function maps input combinations to an output value ('1' or '0')
- 3 possible representations of a function
  - Equation
  - Schematic
  - Truth Table
- Can convert between representations
- Truth table is only unique representation\*

\* Canonical Sums/Products (minterm/maxterm) representation provides a standard equation/schematic form that is unique per function



## Unique Representations

- Canonical => Same functions will have same representations
- Truth Tables along with Canonical Sums and Products specify a function *uniquely*
- Equations/circuit schematics are NOT inherently canonical


Truth Table	Canonical Sum	Canonical Product
x y z   P		
0 0 0   0		
0 0 1   0		
0 1 0   1		
0 1 1   1		
1 0 0   0		
1 0 1   1		
1 1 0   0		
1 1 1   1		

$P = \sum_{x,y,z} (2,3,5,7)$       ON-Set of P (minterms)  
 $P = \prod_{x,y,z} (0,1,4,6)$       OFF-Set of P (maxterms)

Yields AND-OR circuit      Yields OR-AND circuit

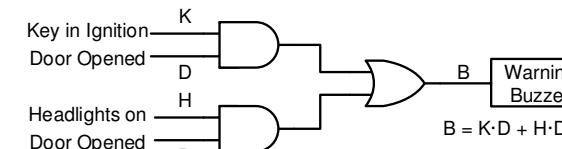
## Example: Automobile Buzzer

- Consider an automobile warning Buzzer that sounds if you leave the Key in the ignition and the Door is open OR the Headlights are on and the Door is open.
- We can easily derive an equation and implementation:  $B = KD + HD$


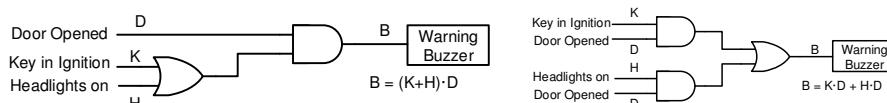
## Example: Automobile Buzzer

- But we see that we can alter this equation...
  - From  $B = KD + HD$
  - To  $B = D(K+H)$ 
    - Buzzer sounds if the Door is open and *either* the Key is in the Ignition or the Headlights are on
- Which is better?
- What is the canonical minterm/maxterm representation?



## Example Form

- Given a function,  $B(D,K,H)$  we can define the minterm functions (which serve as intermediate functions) and then generate the overall function from the minterms
  - $B = \Sigma$
  - $B = \Pi$

Row	D	K	H	Minterm	Designation	Maxterm	Designation	B
0	0	0	0	$D' \cdot K' \cdot H'$	$m_0$	$D+K+H$	$M_0$	0
1	0	0	1	$D' \cdot K' \cdot H$	$m_1$	$D+K+H'$	$M_1$	0
2	0	1	0	$D' \cdot K \cdot H'$	$m_2$	$D+K'+H$	$M_2$	0
3	0	1	1	$D' \cdot K \cdot H$	$m_3$	$D+K'+H'$	$M_3$	0
4	1	0	0	$D \cdot K' \cdot H'$	$m_4$	$D'+K+H$	$M_4$	0
5	1	0	1	$D \cdot K' \cdot H$	$m_5$	$D'+K+H'$	$M_5$	1
6	1	1	0	$D \cdot K \cdot H'$	$m_6$	$D'+K'+H$	$M_6$	1
7	1	1	1	$D \cdot K \cdot H$	$m_7$	$D'+K'+H'$	$M_7$	1

## 2 & 3 Variable Theorems

<b>T6</b>	$X+Y = Y+X$	<b>T6'</b>	$X \cdot Y = Y \cdot X$	Commutativity
<b>T7</b>	$(X+Y)+Z = X+(Y+Z)$	<b>T7'</b>	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	Associativity
<b>T8</b>	$XY+XZ = X(Y+Z)$	<b>T8'</b>	$(X+Y)(X+Z) = X+YZ$	Distribution & Factoring
<b>T9</b>	$X + XY = X$	<b>T9'</b>	$X(X+Y) = X$	Covering
<b>T10</b>	$XY + XY' = X$	<b>T10'</b>	$(X+Y)(X+Y') = X$	Combining
<b>T11</b>	$XY + X'Z + YZ = XY + X'Z$	<b>T11'</b>	$(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$	Consensus
<b>DM</b>	$(X+Y)' = X' \cdot Y'$	<b>DM'</b>	$(X \cdot Y)' = X' + Y'$	DeMorgan's

## DeMorgan's Theorem


- Inverting output of an AND gate = inverting the inputs of an OR gate
- Inverting output of an OR gate = inverting the inputs of an AND gate

A function's inverse is equivalent to inverting all the inputs and changing AND to OR and vice versa

$A \cdot B$		↔		$\overline{A \cdot B}$																															
<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Out</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Out	0	0	1	0	1	1	1	0	1	1	1	0					<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Out</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Out	0	0	1	0	1	1	1	0	1	1	1	0
A	B	Out																																	
0	0	1																																	
0	1	1																																	
1	0	1																																	
1	1	0																																	
A	B	Out																																	
0	0	1																																	
0	1	1																																	
1	0	1																																	
1	1	0																																	
$A+B$		↔		$\overline{A+B}$																															
<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Out</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Out	0	0	1	0	1	0	1	0	0	1	1	0					<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Out</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Out	0	0	1	0	1	0	1	0	0	1	1	0
A	B	Out																																	
0	0	1																																	
0	1	0																																	
1	0	0																																	
1	1	0																																	
A	B	Out																																	
0	0	1																																	
0	1	0																																	
1	0	0																																	
1	1	0																																	

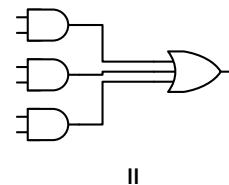
## AND-OR / NAND-NAND

- Canonical Sums yield
  - AND-OR Implementation
  - NAND-NAND Implementation




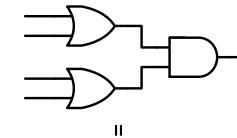
## OR-AND / NOR-NOR

- Canonical Products yield
  - OR-AND Implementation
  - NOR-NOR Implementation



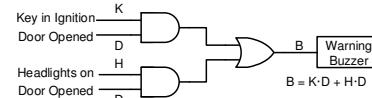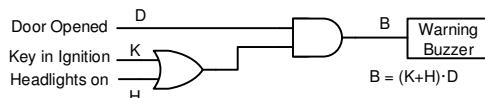
## Example: Automobile Buzzer

- Convert each implementation to use either just NOR or just NAND gates + inverters


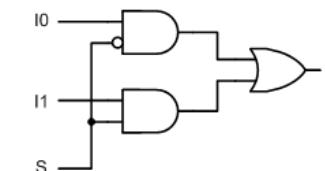
## Convert to NAND-NAND

- Convert the 2-to-1 mux below to use just NAND or NOR gates?



## Logic Synthesis

- Describe the function
  - Usually with a truth table
- Find the sum of products or product of sums expression
  - Fewer 1's in the output => use canonical sum
  - Fewer 0's in the output => use canonical product
- Use Boolean Algebra (T8-T11) to find a simplified expression

## Exercise 1

- Synthesize this function in two ways
  - First use the canonical sum
  - Then use the canonical product

T8	$XY + XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$
T9	$X + XY = X$	T9'	$X(X+Y) = X$
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$
T11	$XY + XZ + YZ = XY + XZ$	T11'	$(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Primes between 0-7

## Exercise 2

- Synthesize this function in two ways
  - First use the canonical sum
  - Then use the canonical product

T8	$XY+XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$
T9	$X + XY = X$	T9'	$X(X+Y) = X$
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$
T11	$XY + XZ + YZ = XY + XZ$	T11'	$(X+Y)(X+Z)(Y+Z) = (X+Y)(X+Z)$

I3	I2	I1	M1	M0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Encode the highest input ID  
(ie. 3, 2, or 1) that is ON (=1)

## Exercise 3

- Synthesize this function in two ways
  - First use the canonical sum
  - Then use the canonical product

T8	$XY+XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$
T9	$X + XY = X$	T9'	$X(X+Y) = X$
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$
T11	$XY + XZ + YZ = XY + XZ$	T11'	$(X+Y)(X+Z)(Y+Z) = (X+Y)(X+Z)$

I3	I2	I1	C1	C0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

1's Count of Inputs