

Spiral 2-1

Datapath Components:

Counters

Adders

Design Example: Crosswalk Controller

Spiral Content Mapping

Spiral	Theory	Combinational Design	Sequential Design	System Level Design	Implementation and Tools	Project
1	<ul style="list-style-type: none"> Performance metrics (latency vs. throughput) Boolean Algebra Canonical Representations 	<ul style="list-style-type: none"> Decoders and muxes Synthesis with min/maxterms Synthesis with Karnaugh Maps 	<ul style="list-style-type: none"> Edge-triggered flip-flops Registers (with enables) 	<ul style="list-style-type: none"> Encoded State machine design 	<ul style="list-style-type: none"> Structural Verilog HDL CMOS gate implementation Fabrication process 	
2	<ul style="list-style-type: none"> Shannon's Theorem 	<ul style="list-style-type: none"> Synthesis with muxes & memory Adder and comparator design 	<ul style="list-style-type: none"> Bistables, latches, and Flip-flops Counters Memories 	<ul style="list-style-type: none"> One-hot state machine design Control and datapath decomposition 	<ul style="list-style-type: none"> MOS Theory Capacitance, delay and sizing Memory constructs 	
3				<ul style="list-style-type: none"> HW/SW partitioning Bus interfacing Single-cycle CPU 	<ul style="list-style-type: none"> Power and other logic families EDA design process 	


Learning Outcomes

- I understand the control inputs to counters
- I can design logic to control the inputs of counters to create a desired count sequence
- I understand how smaller adder blocks can be combined to form larger ones
- I can build larger arithmetic circuits from smaller building blocks
- I understand the timing and control input differences between asynchronous and synchronous memories

DATAPATH COMPONENTS

Digital System Design

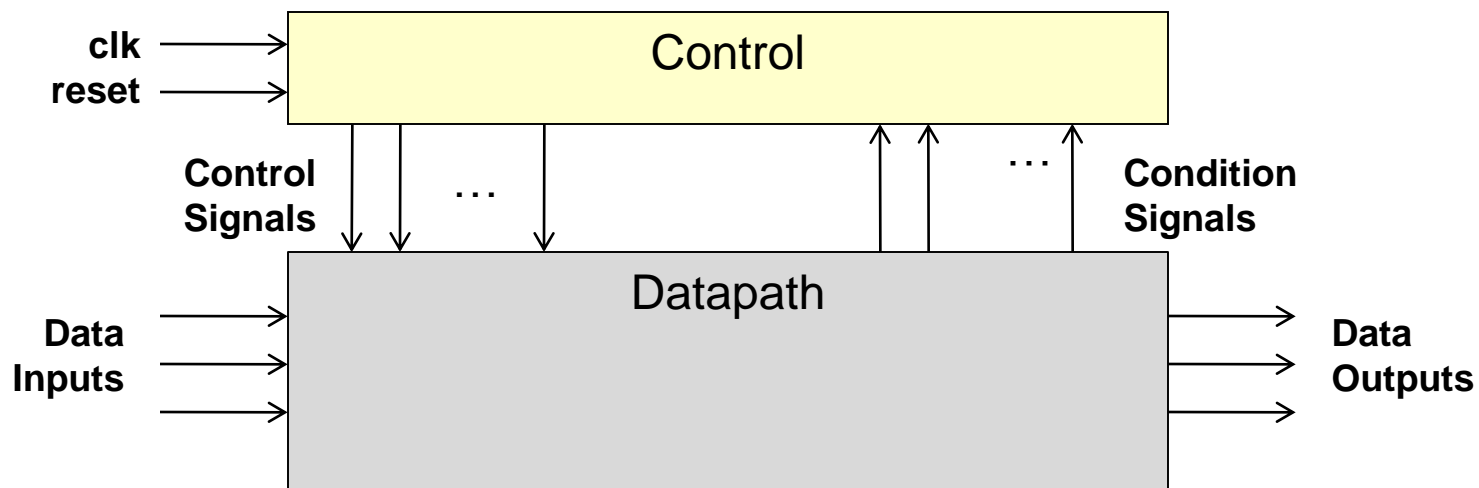
- Control (**CU**) and Datapath Unit (**DPU**) paradigm
 - Separate logic into datapath elements that operate on data and control elements that generate control signals for datapath elements
 - Datapath: Adders, muxes, comparators, counters, registers (shift, with enables, etc.), memories, FIFO's
 - Control Unit: State machines/sequencers



COUNTERS

Counters

 
- Count (Add 1 to Q) at each clock edge
 - Up Counter: $Q^* = Q + 1$
 - Can also build a down counter as well ($Q^* = Q - 1$)
- Standard counter components include other features
 - Resets: Reset count to 0
 - Enables: Will not count at edge if $EN=0$
 - Parallel Load Inputs: Can initialize count to a value P (i.e. $Q^* = P$ rather than $Q+1$)



How would you design the adder block above for a 4-bit counter?
Only 4-inputs, use T.T. and K-Maps!


Sample 4-bit Counter

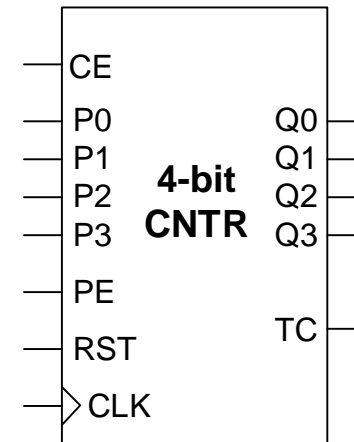- 4-bit Up Counter
 - RST: a synchronous reset input
 - PE and P_i inputs: loads Q with P when PE is active
 - CE: Count Enable
 - Must be active for the counter to count up
 - TC (Terminal Count) output
 - Active when $Q=1111$ AND counter is enabled
 - $TC = EN \cdot Q_3 \cdot Q_2 \cdot Q_1 \cdot Q_0$
 - Mealy output
 - Indicates that on the next edge it will roll over to 0000



CLK	RST	PE	CE	Q*
0,1	X	X	X	Q
↑↑	1	X	X	0
↑↑	0	1	X	P
↑↑	0	0	0	Q
↑↑	0	0	1	Q+1

Counters

 

SR=active
at clock
edge, thus
Q=0

$Q^*=Q+1$

Enable
= off,
thus Q
holds

$Q^*=Q+1$

$Q^*=Q+1$


PE =
active,
thus
Q=P

$Q^*=Q+1$

$Q^*=Q+1$


Mealy TC output:
 $EN \cdot Q_3 \cdot Q_2 \cdot Q_1 \cdot Q_0$

Counter Exercise

 


Counter Design

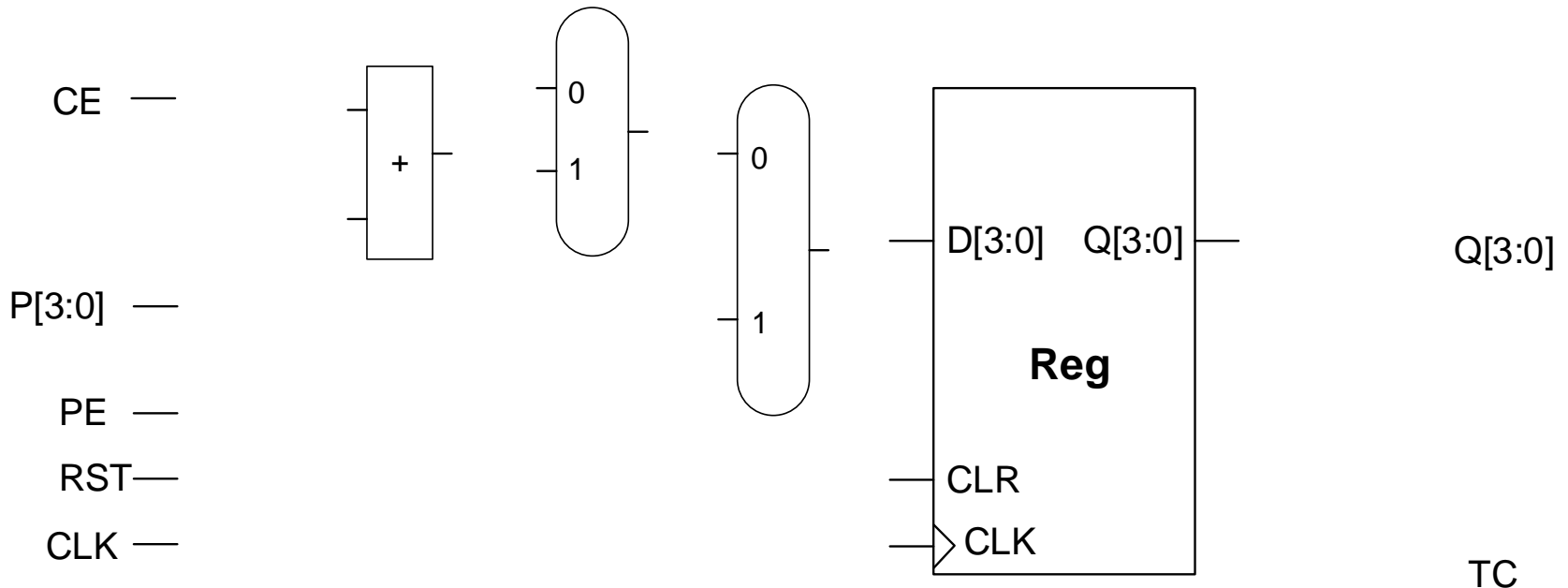- Sketch the design of the 4-bit counter presented on the previous slides



Counter Example

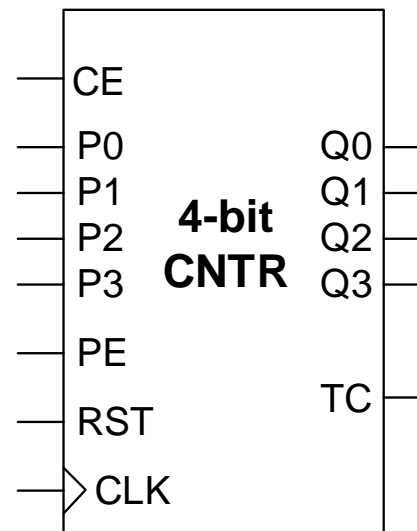- Design a circuit that counts each clock cycle to produce the pattern 5, 6, 7, 8, 9, 5, 6, 7, 8, 9, 5...9, 5...9,...




ADDERS

Adder Intro

- So how would we build a circuit to add two numbers?
- Let's try to design a circuit that can add **ANY** two 4-bit numbers, $X[3:0]$ and $Y[3:0]$
 - How many inputs?
 - Can we use K-Maps or sum of minterms, etc?
 
$$\begin{array}{r}
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$



Adder Intro



- **Idea:** Build a circuit that performs one column of addition and then use 4 instances of those circuits to perform the overall 4-bit addition
- Let's start by designing a circuit that adds 2-bits: X and Y that are in the same column of addition

$$\begin{array}{r} 0110 = X \\ + 0111 = Y \\ \hline 1101 \end{array}$$

Addition – Half Adders

- Addition is done in columns
 - Inputs are the bit of X, Y
 - Outputs are the Sum Bit and Carry-Out (C_{out})
- Design a Half-Adder (HA) circuit that takes in X and Y and outputs S and C_{out}


X	Y	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 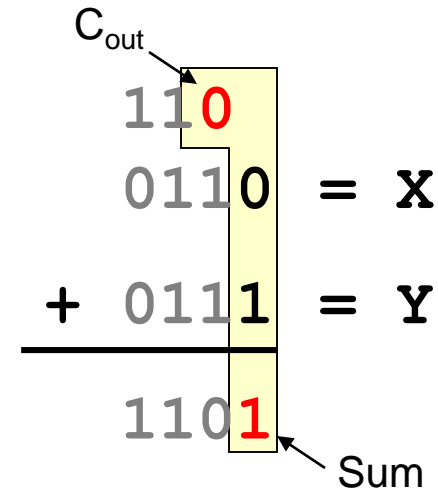

Addition – Half Adders

- We'd like to use one adder circuit for each column of addition
- Problem:
 - No place for Carry-out of last adder circuit
- Solution
 - Redesign adder circuit to include an input for the carry


 
$$\begin{array}{r}
 110 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$



Addition – Full Adders

- Add a Carry-In input(C_{in})
- New circuit is called a Full Adder (FA)

X	Y	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  



Addition – Full Adders

- Find the minimal 2-level implementations for C_{out} and S ...

X	Y	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder Logic

  
- $S = X \text{ xor } Y \text{ xor } C_{in}$
 - Recall: XOR is defined as true when ODD number of inputs are true...exactly when the sum bit should be 1
- $C_{out} = XY + XC_{in} + YC_{in}$
 - Carry when sum is 2 or more (i.e. when at least 2 inputs are 1)
 - Circuit is just checking all combinations of 2 inputs



Addition – Full Adders

- Use 1 Full Adder for each column of addition

 
$$\begin{array}{r} 0110 \\ + 0111 \\ \hline \end{array}$$



Addition – Full Adders

- Connect bits of top number to X inputs

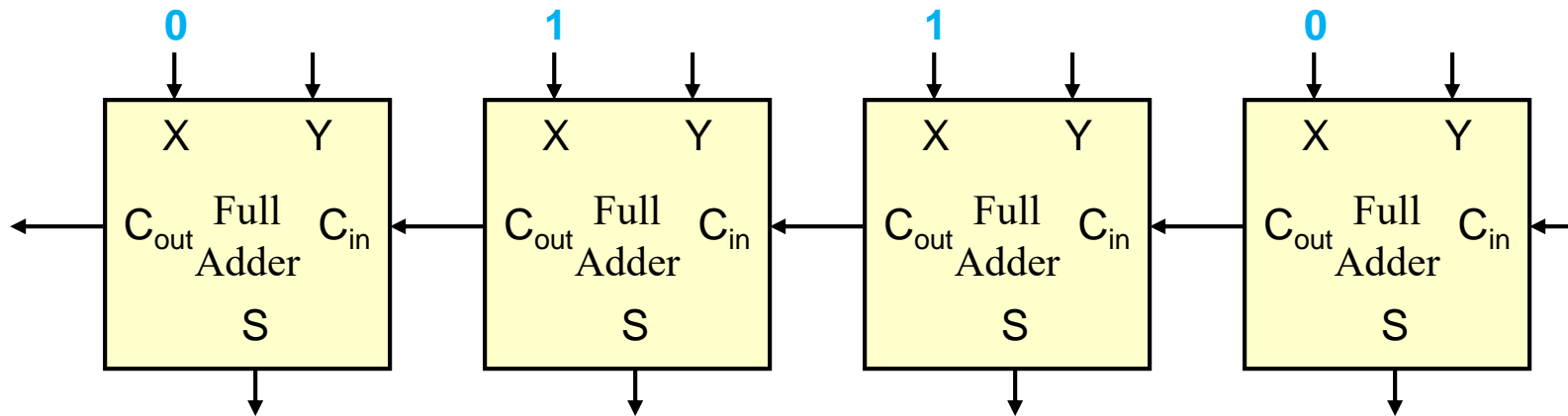
$$\begin{array}{r}
 0110 \\
 + 0111 \\
 \hline
 \end{array}$$



Addition – Full Adders

- Connect bits of bottom number to Y inputs
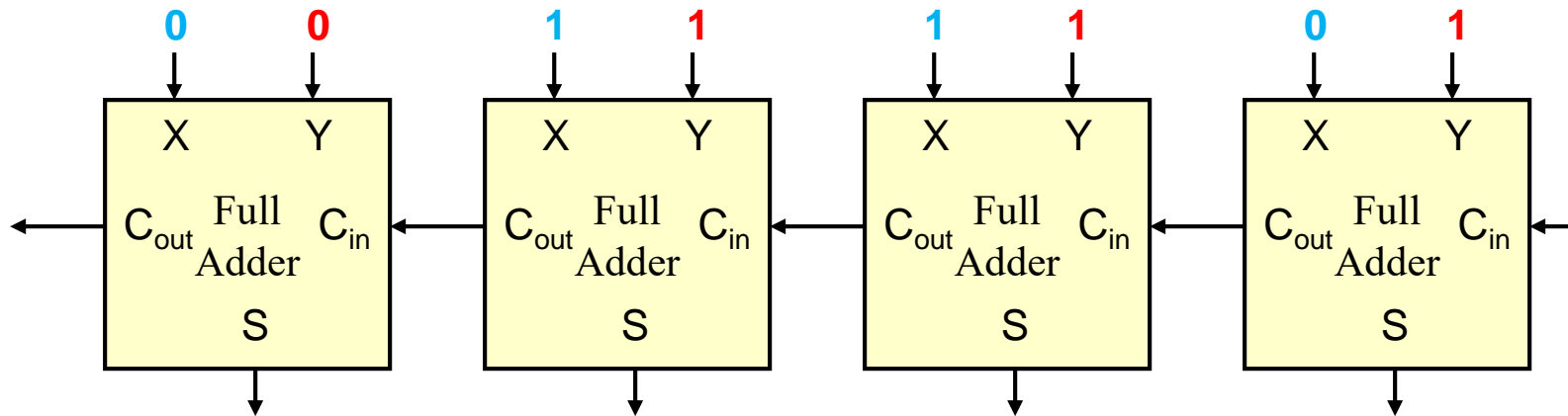
$$\begin{array}{r}
 0110 = X \\
 + 0111 = Y \\
 \hline
 \end{array}$$




Addition – Full Adders

- Be sure to connect first C_{in} to 0

$$0110 = X$$


$$+ 0111 = Y$$

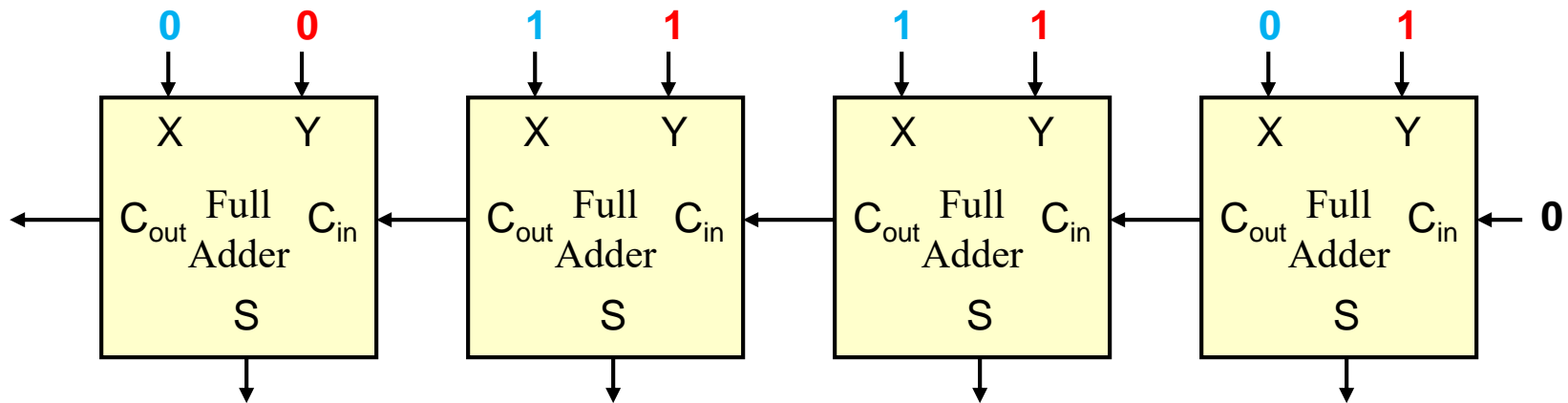

Addition – Full Adders

- Use 1 Full Adder for each column of addition

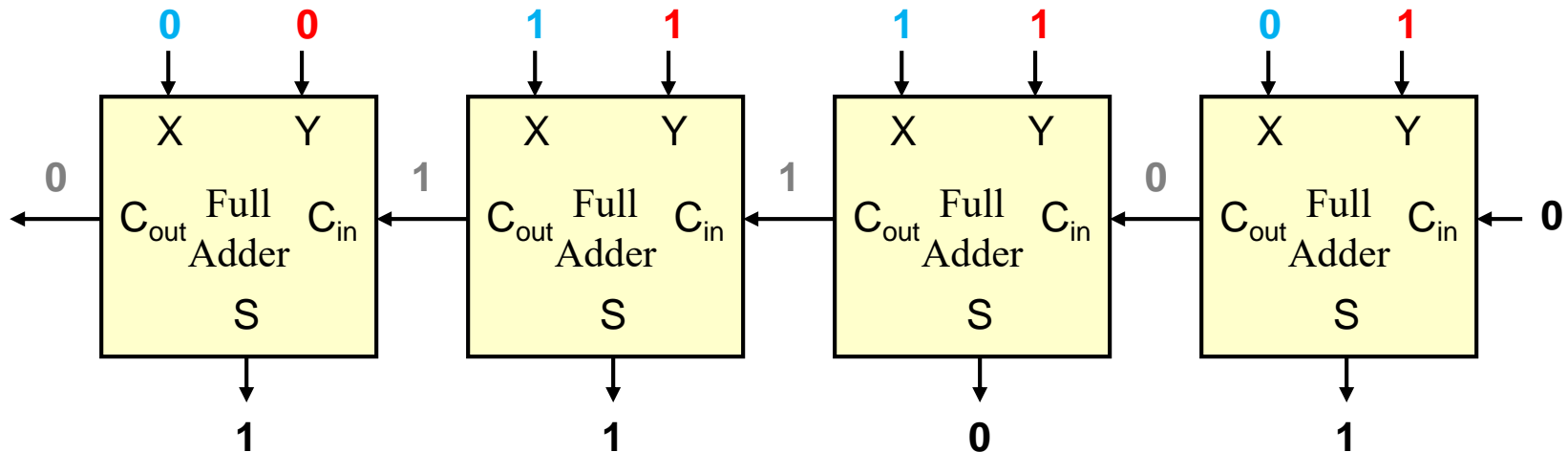
$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$



Addition – Full Adders

- Use 1 Full Adder for each column of addition

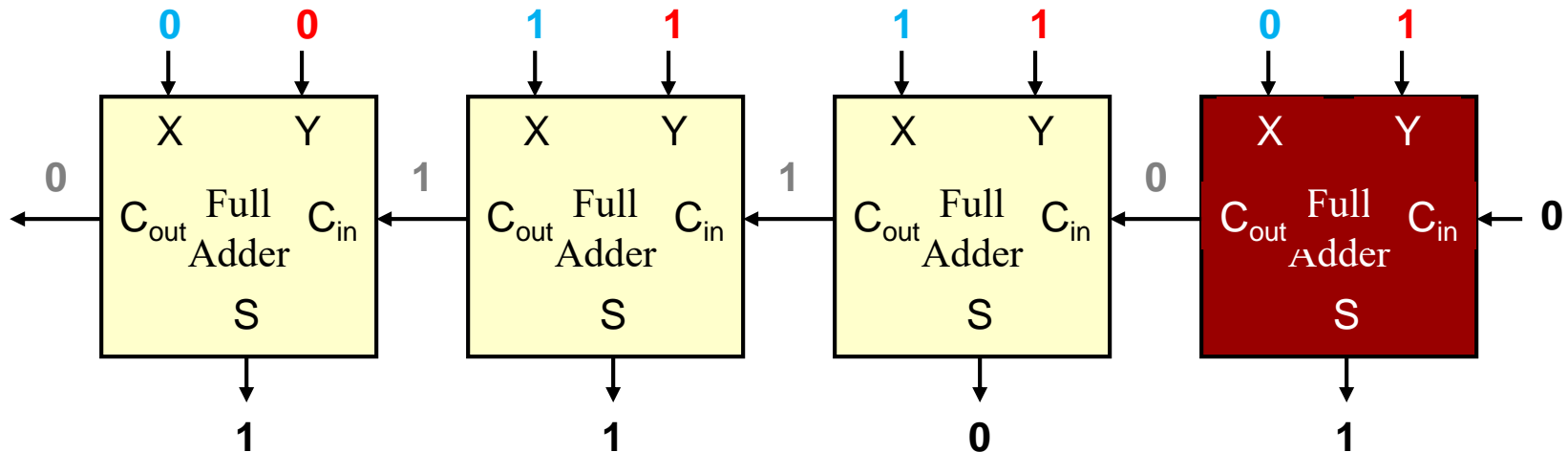
$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$



Addition – Full Adders

- Use 1 Full Adder for each column of addition

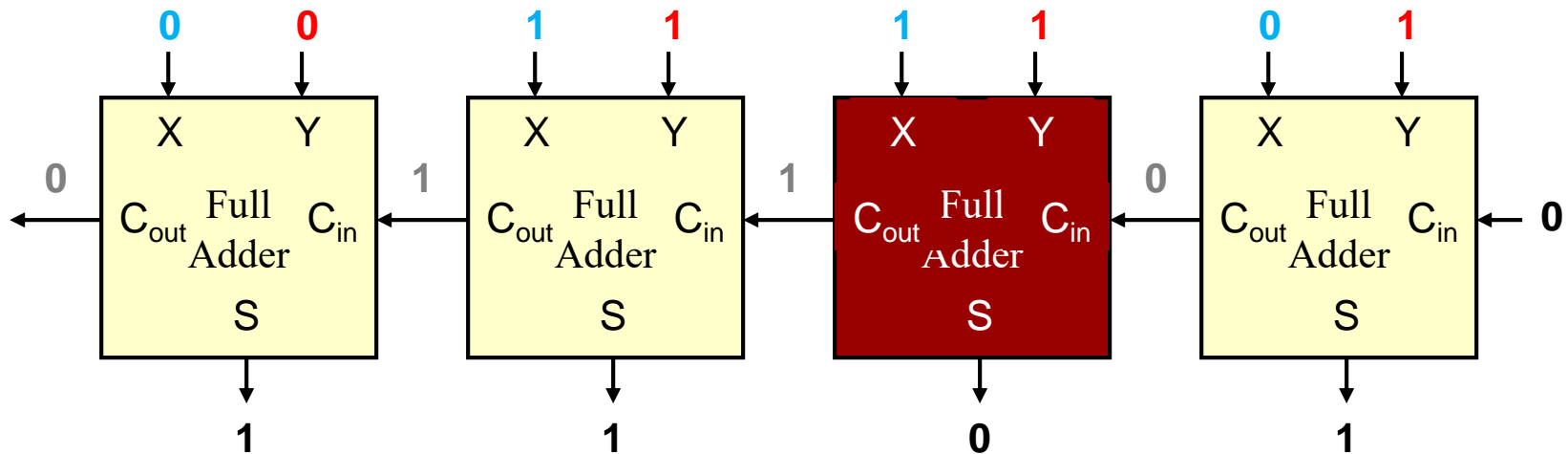
$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$



Addition – Full Adders

- Use 1 Full Adder for each column of addition

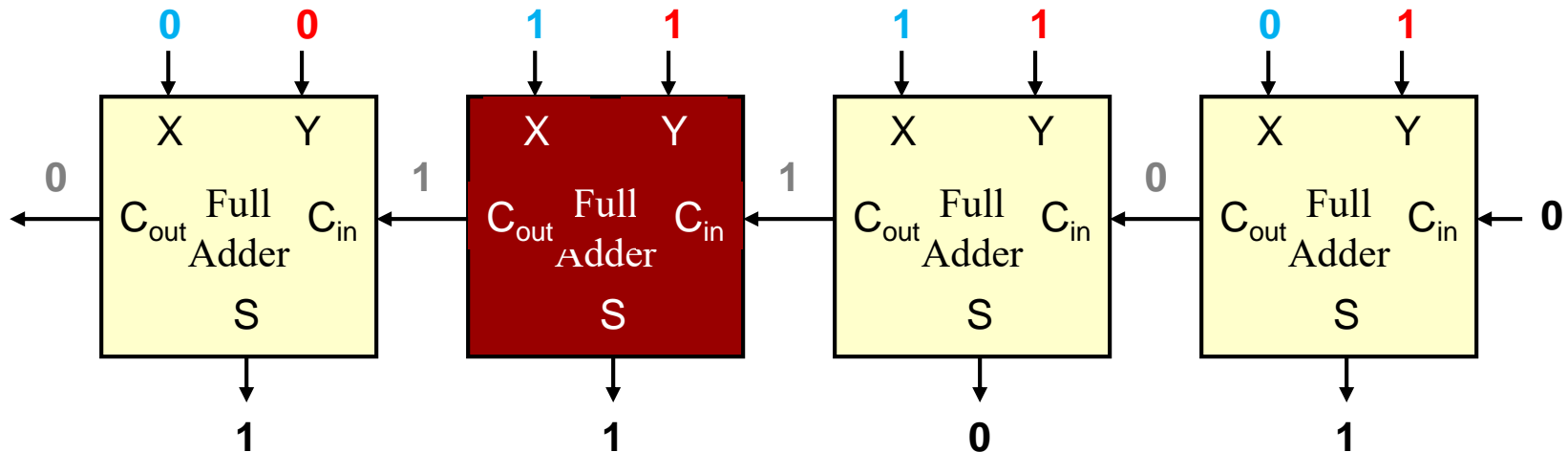
$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$



Addition – Full Adders

- Use 1 Full Adder for each column of addition

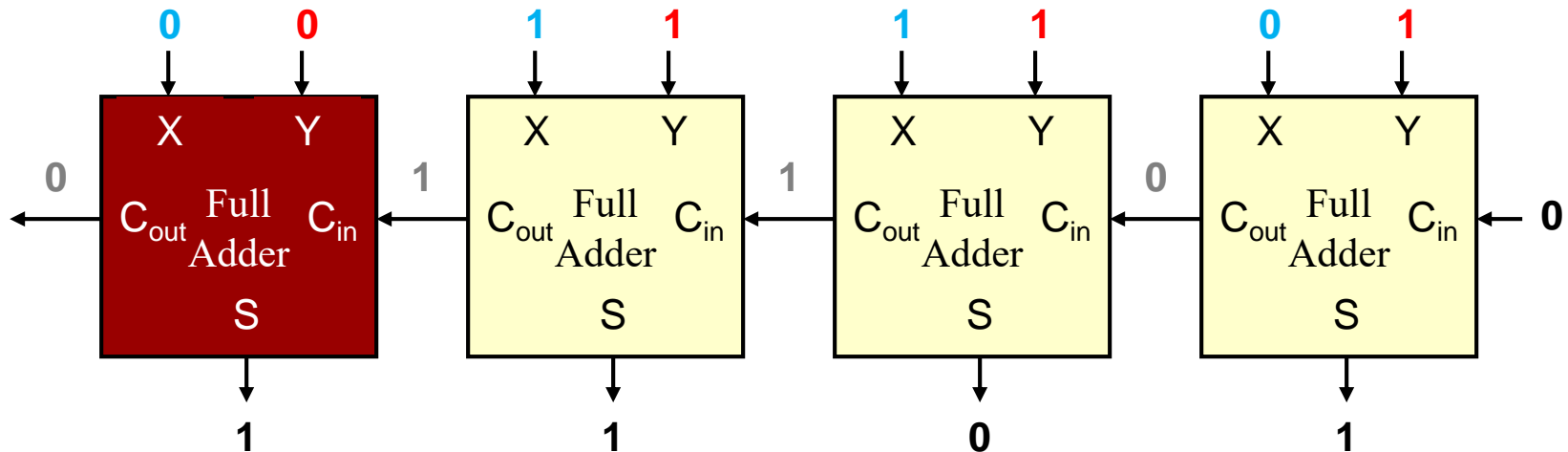
$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$



Performing Subtraction w/ Adders

- To subtract
 - Flip bits of Y
 - Add 1

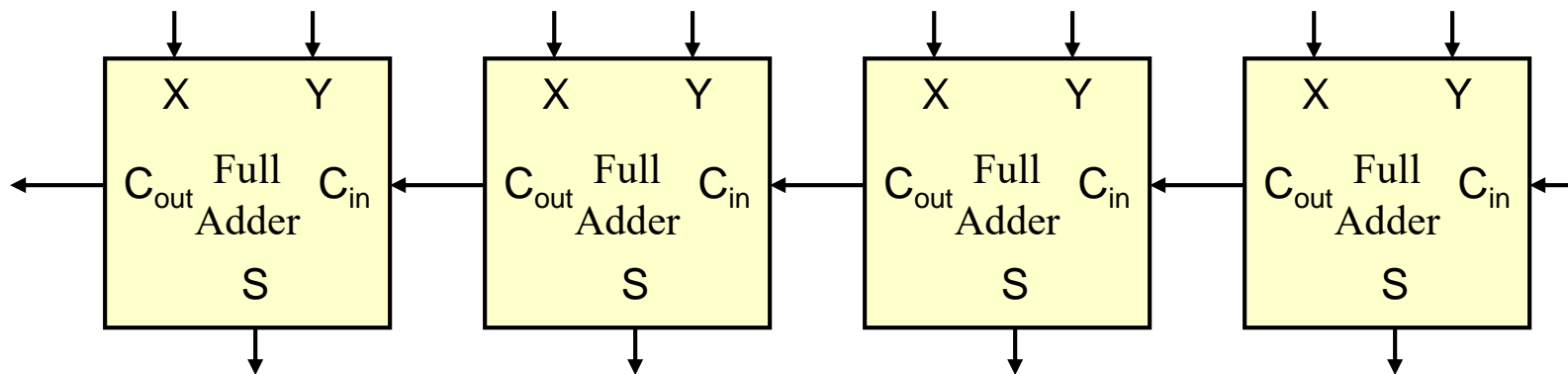
$$\begin{array}{r}
 0101 = X \\
 - 0011 = Y \\
 \hline
 0010
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1100 \\
 1 \\
 \hline
 0010
 \end{array}$$



Performing Subtraction w/ Adders

- To subtract
 - Flip bits of Y
 - Add 1

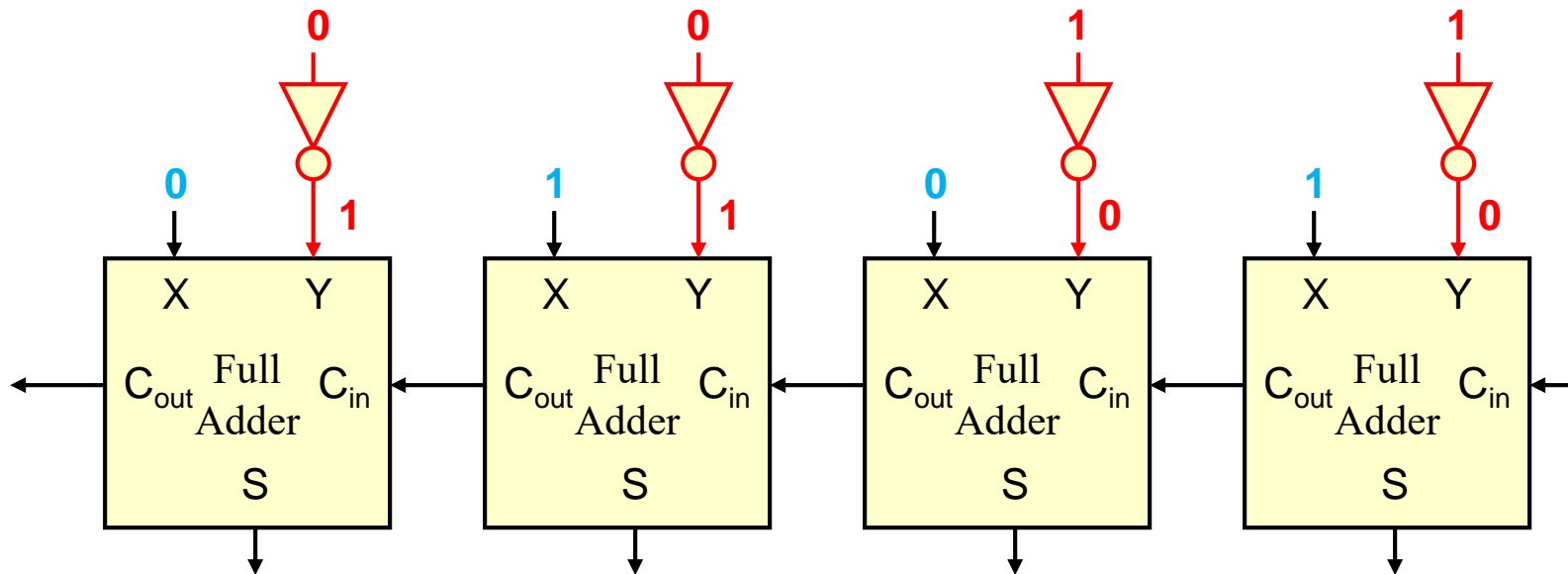
$$\begin{array}{r}
 0101 = X \\
 - 0011 = Y \\
 \hline
 0010
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1100 \\
 \quad 1 \\
 \hline
 0010
 \end{array}$$



Performing Subtraction w/ Adders

- To subtract
 - Flip bits of Y
 - Add 1

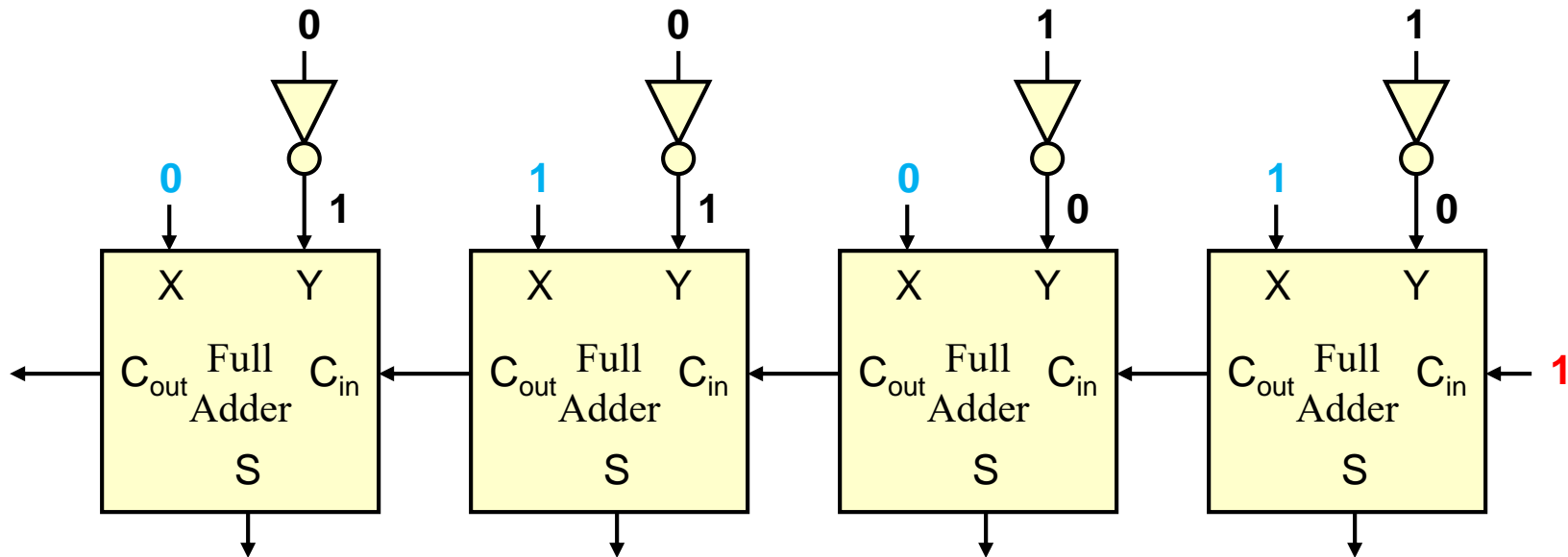
$$\begin{array}{r}
 0101 = X \\
 - 0011 = Y \\
 \hline
 0010
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1100 \\
 1 \\
 \hline
 0010
 \end{array}$$



Performing Subtraction w/ Adders

- To subtract
 - Flip bits of Y
 - Add 1

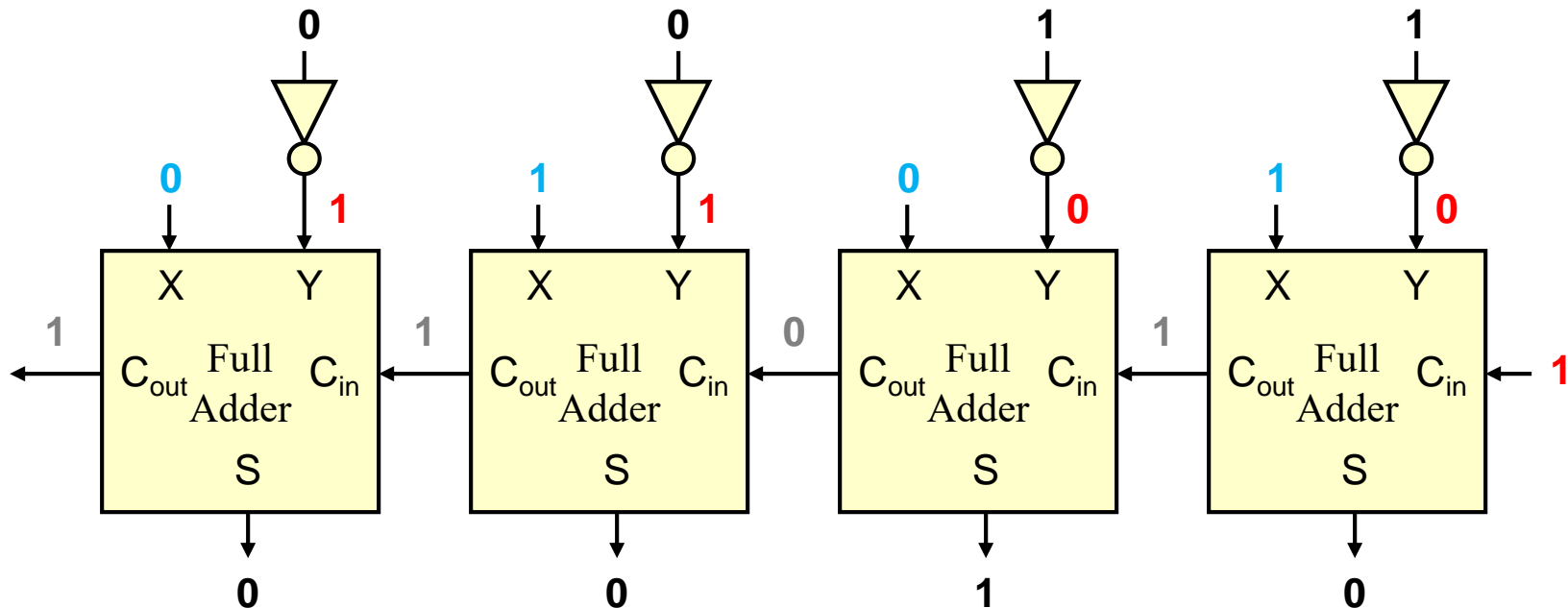
$$\begin{array}{r}
 0101 = X \\
 - 0011 = Y \\
 \hline
 0010
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1100 \\
 1 \\
 \hline
 0010
 \end{array}$$



4-bit Adders



- 74LS283 chip implements a 4-bit adder
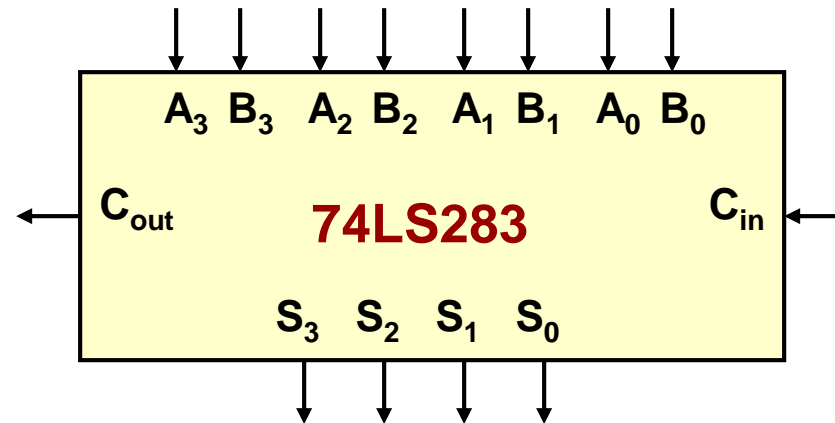
$$\begin{array}{r} A_3 A_2 A_1 A_0 = A \\ + B_3 B_2 B_1 B_0 = B \\ \hline S_4 S_3 S_2 S_1 S_0 = S \end{array}$$



Building an 8-bit Adder

  
- Use (2) 4-bit adders to build an 8-bit adder to add $X=X[7:0]$ and $Y=Y[7:0]$ and produce a sum, $S=S[7:0]$ and a carry-out, $C8$.
 - Make sure you understand the difference between system labels (actual signal names from the top level design) and device labels (placeholder names for the signals inside each block).



 EXERCISES



Adding Many Bits

- You know that an FA adds $X + Y + C_i$
- Use FA and/or HA components to add 4 individual bits:
 $A + B + C + D$




Adding 3 Numbers

  - Add $X[3:0] + Y[3:0] + Z[3:0]$ to produce $F[?:0]$ using the adders shown plus any FA and HA components you need




Mapping Algorithms to HW

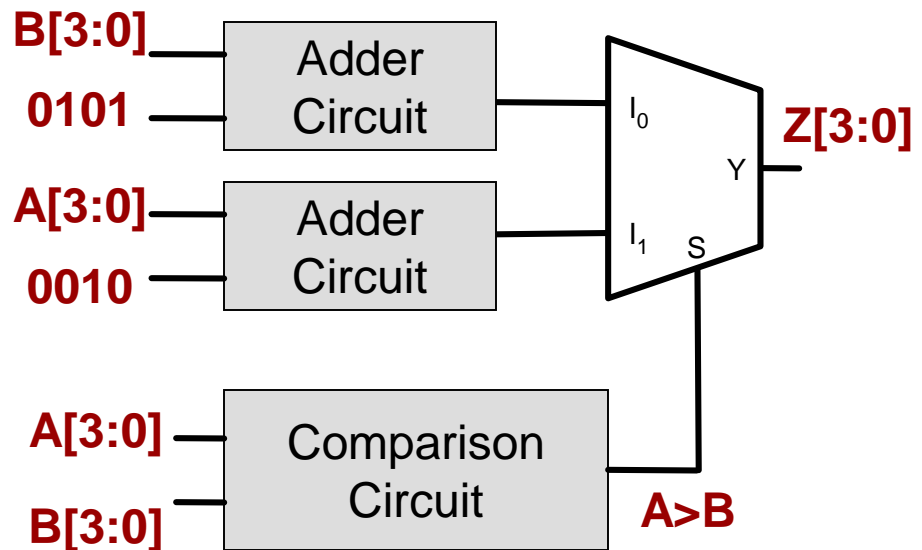- Wherever an if..then..else statement is used usually requires a mux
 - if($A[3:0] > B[3:0]$)
 - $Z = A+2$
 - else
 - $Z = B+5$





Mapping Algorithms to HW

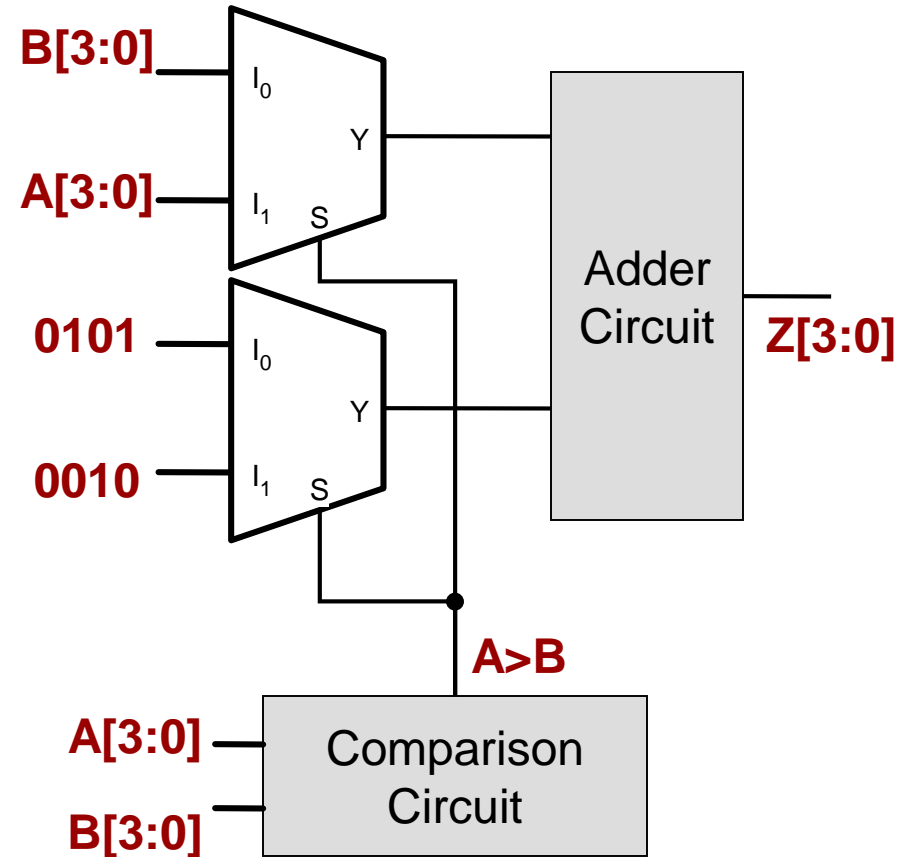- Wherever an if..then..else statement is used usually requires a mux
 - if($A[3:0] > B[3:0]$)
 - $Z = A+2$
 - else
 - $Z = B+5$



Adder / Subtractor

  
- If $\text{sub}/\sim\text{add} = 1$
 - $Z = X[3:0] - Y[3:0]$
- Else
 - $Z = X[3:0] + Y[3:0]$



Adder / Subtractor

- If $\text{sub}/\sim\text{add} = 1$
 - $Z = X[3:0] - Y[3:0]$
- Else
 - $Z = X[3:0] + Y[3:0]$

SUB/ ~ADD	Y _i	B _i
0	0	
0	1	
1	0	
1	1	

 


Another Example

- Design a circuit that takes a 4-bit binary number, X , and two control signals, $A5$ and $M1$ and produces a 4-bit result, Z , such that:
- $Z = X + 5$, when $A5, M1 = 1, 0$
- $Z = X - 1$, when $A5, M1 = 0, 1$
- $Z = X$, when $A5, M1 = 0, 0$

4-bit Adder Input

A5	M1	B3	B2	B1	B0
0	0				
0	1				
1	0				
1	1	d	d	d	d

 


ROMS AND MEMORIES

Memories

- Memories store (write) and retrieve (read) data
 - Read-Only Memories (ROM's): Can only retrieve data (contents are initialized and then cannot be changed)
 - Read-Write Memories (RWM's): Can retrieve data and change the contents to store new data

ROM's

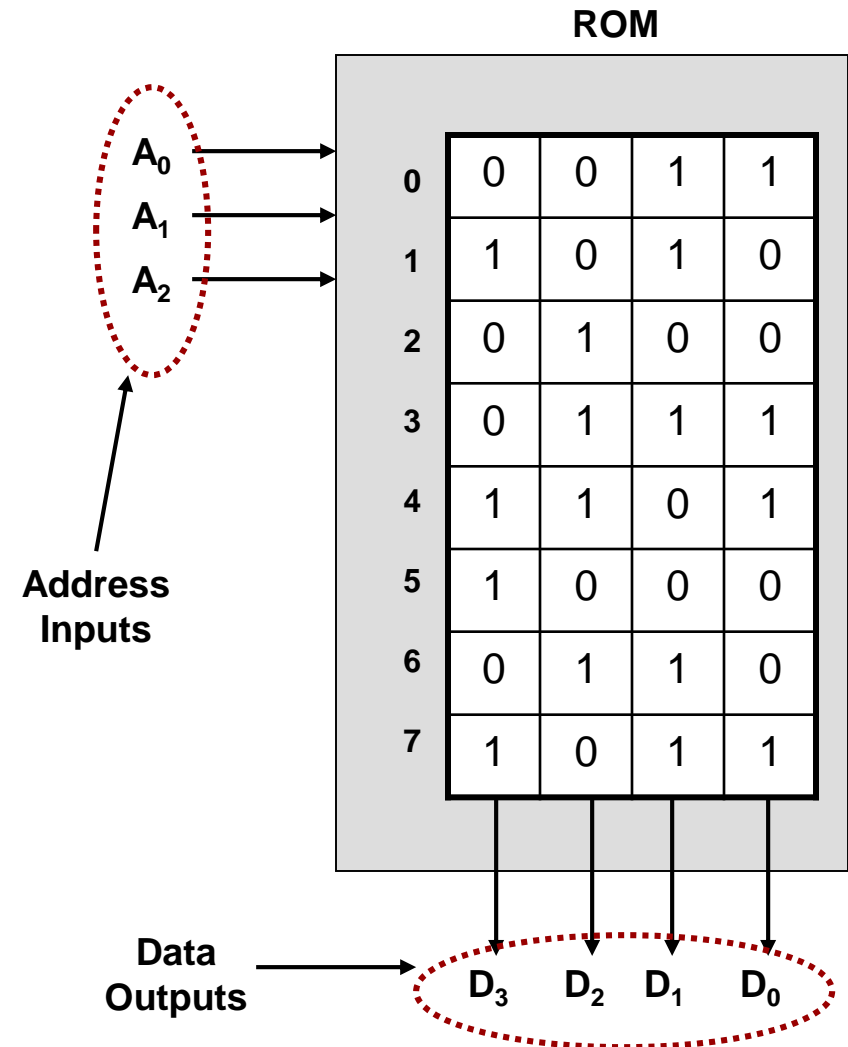
- Memories are just tables of data with rows and columns
- When data is read, one entire row of data is read out
- The row to be read is selected by putting a binary number on the address inputs



ROM's

 
- Example

- Address = 4 dec. = 100 bin. is provided as input
- ROM outputs data in that row (1101 bin.)




Memory Dimensions

 - Memories are named by their dimensions:
 - Rows x Columns
- n rows and m columns $\Rightarrow n \times m$ ROM
- 2^n rows $\Rightarrow n$ address bits (or k rows $\Rightarrow \log_2 k$ address bits)
- m cols. $\Rightarrow m$ data outputs




RWM's

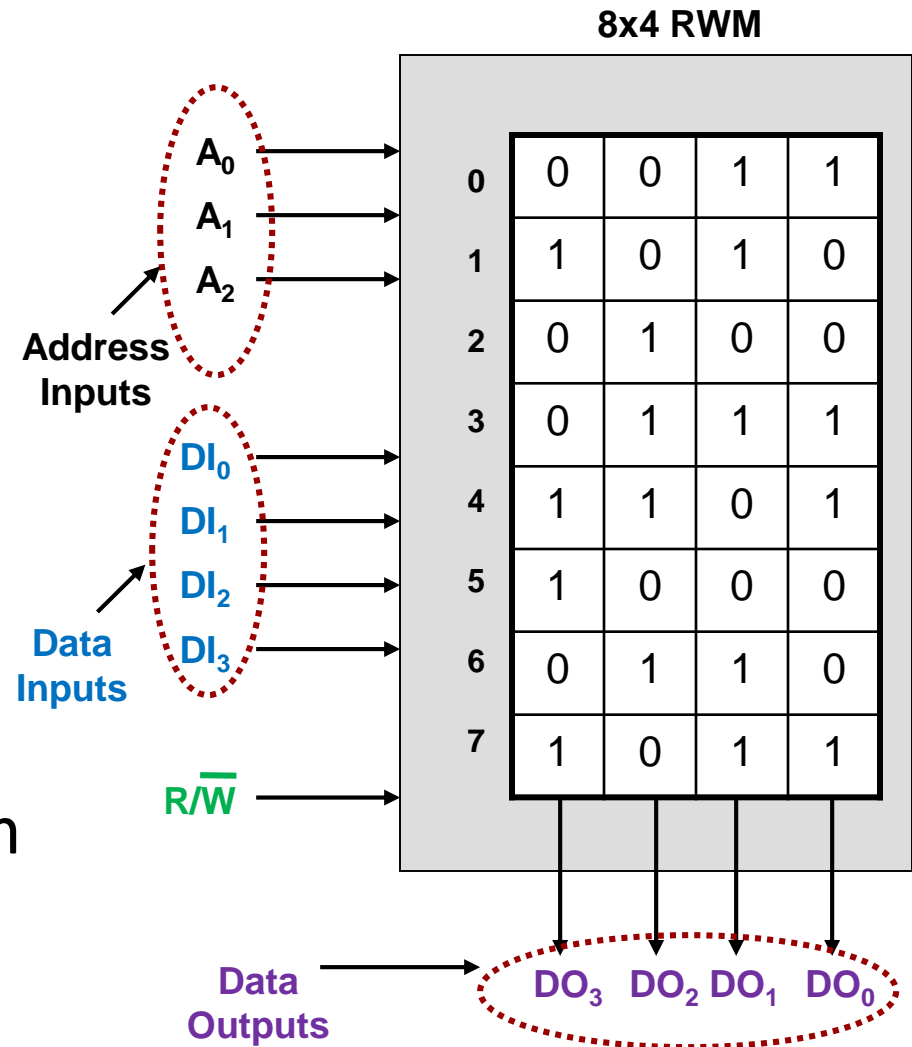- Writable memories provide a set of **data inputs** for **write data** (as opposed to the **data outputs** for **read data**)
- A control signal R/\bar{W} ($1=READ / 0 = WRITE$) is provided to tell the memory what operation the user wants to perform





RWM's

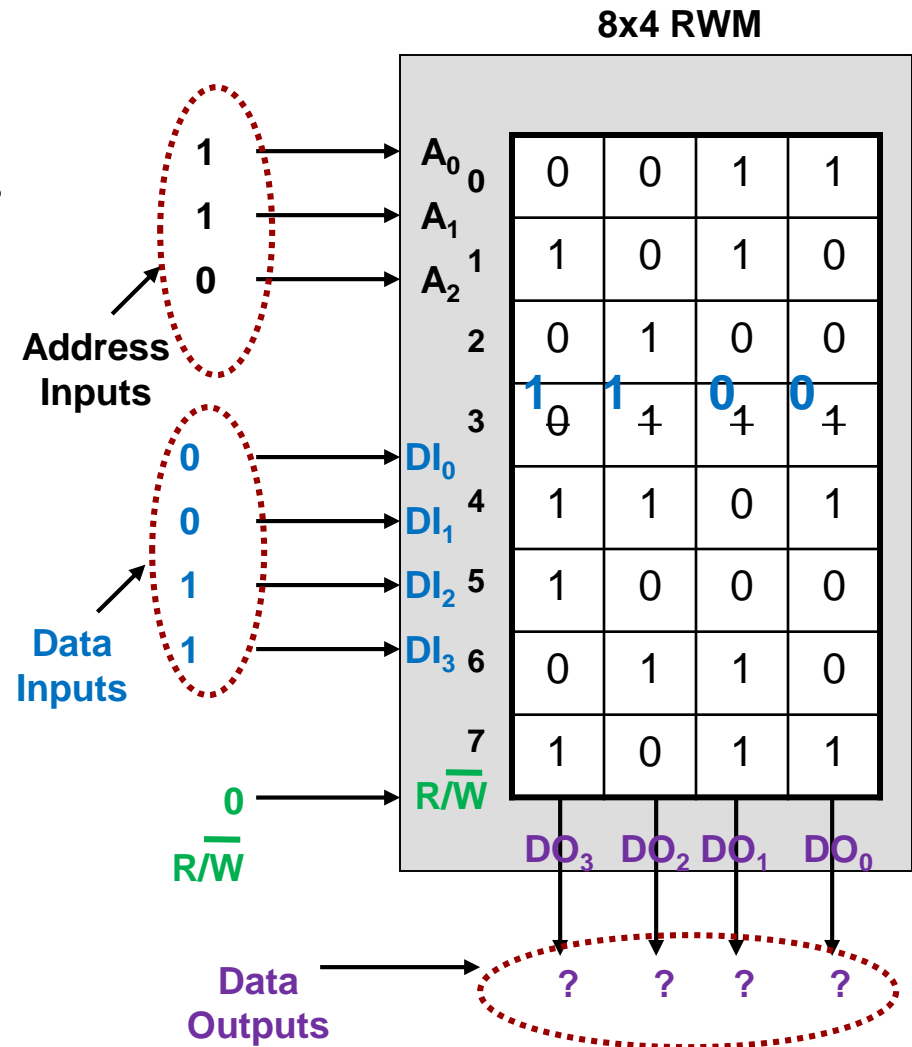- Write example
 - Address = 3 dec. = 011 bin.
 - DI = 12 dec. = 1100 bin.
 - $R/\overline{W} = 0 \Rightarrow$ Write op.
- Data in row 3 is overwritten with the new value of 1100 bin.




Asynchronous Memories

 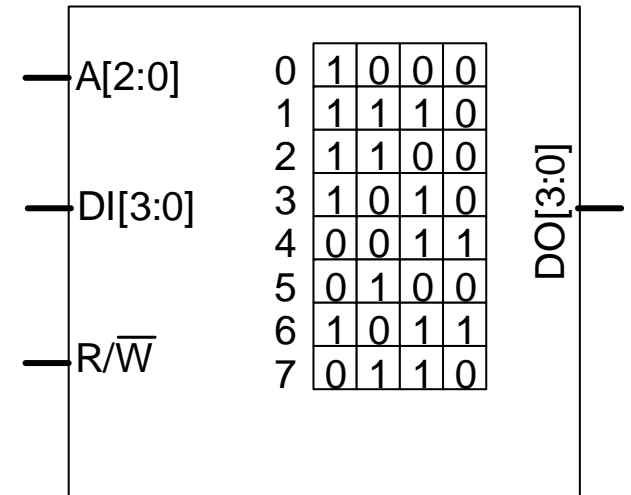- Notice that there is no clock signal with this memory
- Devices that do not use a clock signal are called "asynchronous" devices
- For these memories, the address must be kept valid and stable for at least t_{acc} amount of time



Asynchronous vs. Synchronous Memories



- Asynchronous memories use no CLK signal
 - For read: Address and R/W signal must be **held steady for a certain period of time** before DO outputs become valid
 - For write: Address, DI, and R/W signal must be **held steady for a certain period of time** before internal memory is updated
- Synchronous memories use a CLK signal
 - For read: Address and R/W signal will be **registered on the CLK edge** and then DO will become valid during that subsequent clock cycle
 - For write: Address, DI and R/W signals will be **registered on the CLK edge** and then the internal memory updated during the subsequent clock cycle

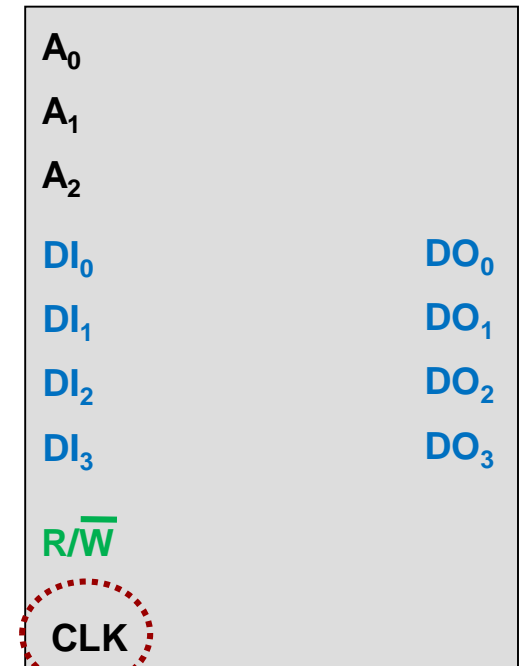

Synchronous memories add a clock signal and the input values at a clock edge will only be processed during the subsequent clock cycle


Synchronous Timing

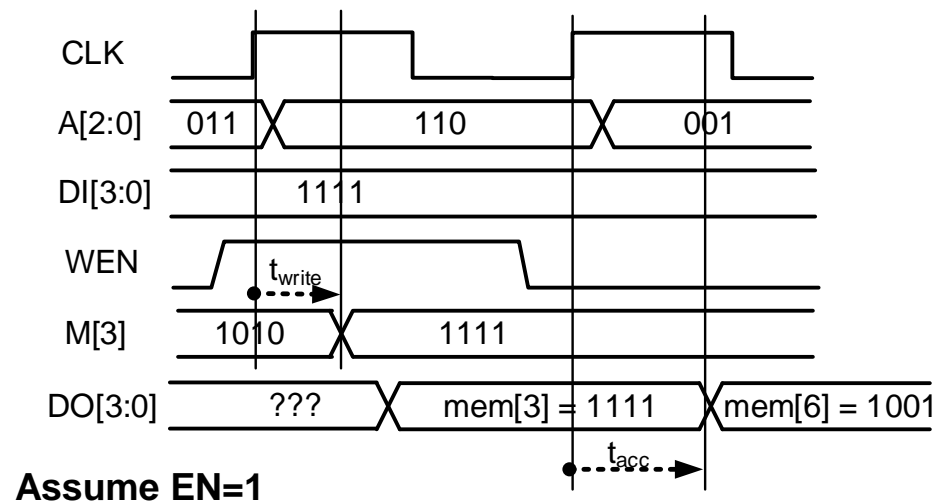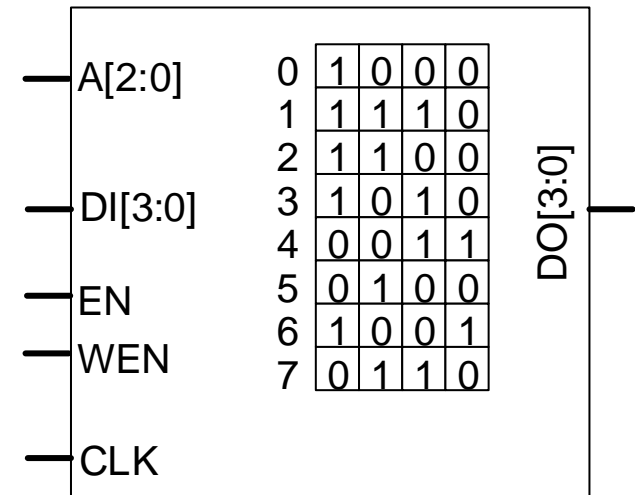- For **synchronous** memories the address must be valid and stable at the clock edge but then may be changed
- EN = Overall enable (unless it is 1) the memory won't read or write (we assume EN=1)
- WEN = Write enable
 - 1 = Write / 0 = read



Using Memories

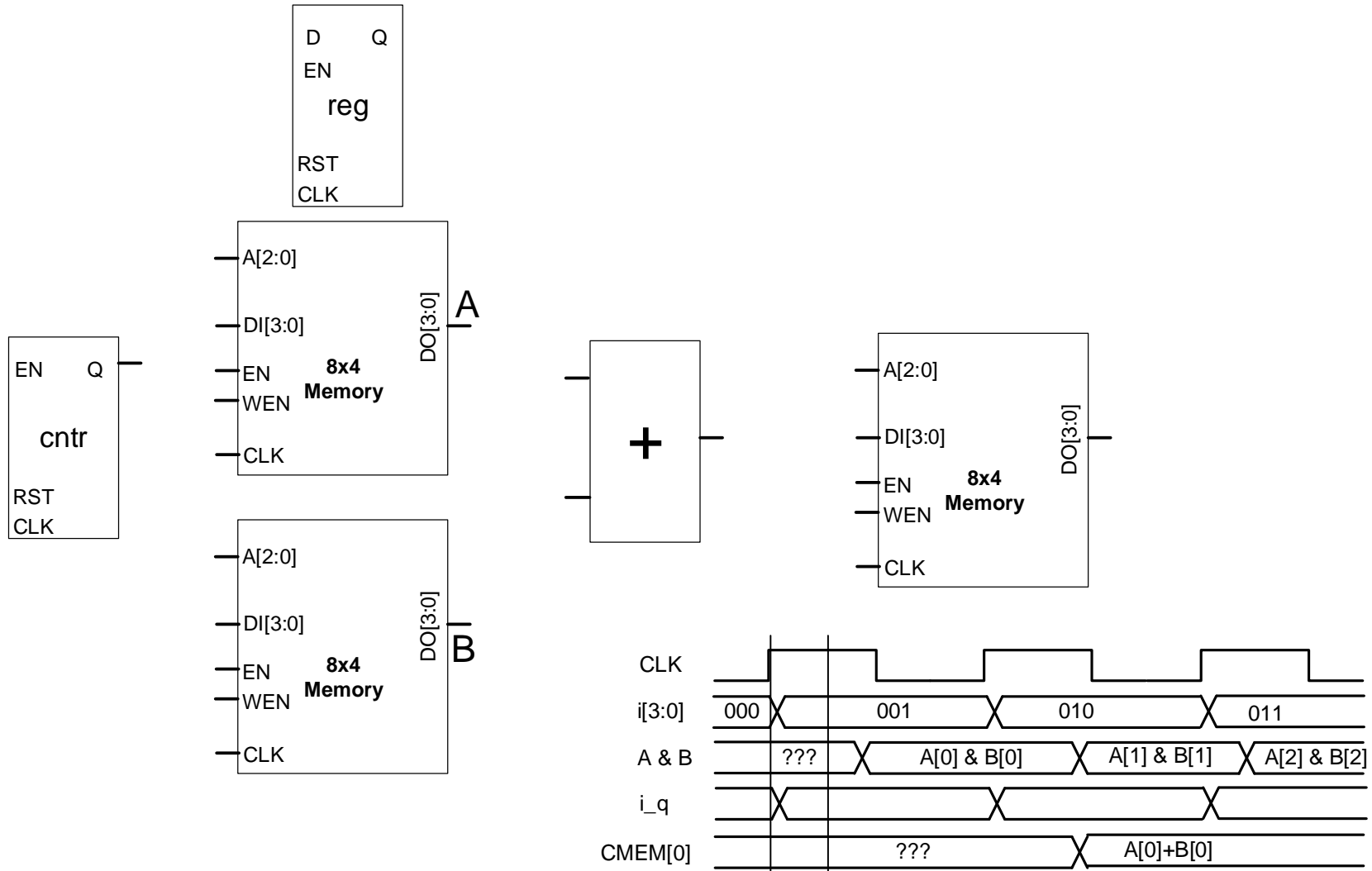- Add two 8 number arrays ($C[i] = A[i] + B[i]$)




Crosswalk Controller

SYSTEM DESIGN EXAMPLE


Digital System Design

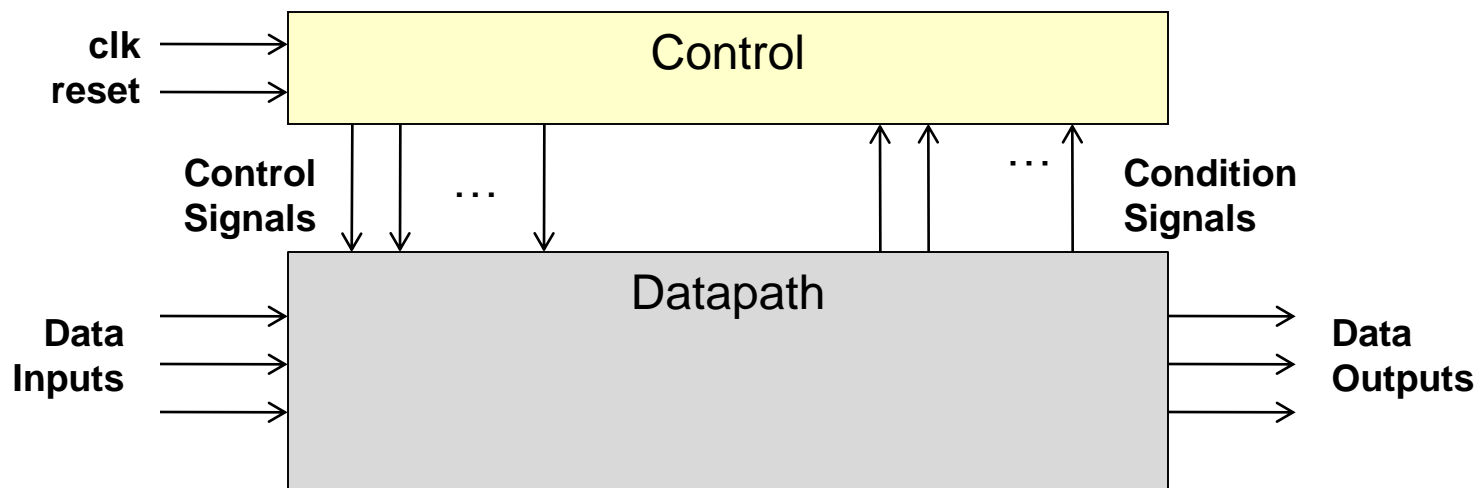- Control and Datapath Unit paradigm
 - Separate logic into datapath elements that operate on data and control elements that generate control signals for datapath elements
 - Datapath: Adders, muxes, comparators, counters, registers (w/ enables)
 - Control Unit: State machines/sequencers





Crosswalk Controller

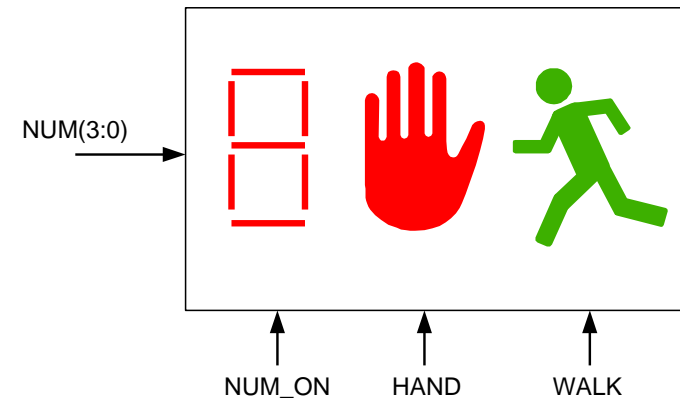- Design a crosswalk controller to adhere to the following description
- 8 ticks of the clock in the WALK phase
- 8 ON/OFF BLINKING hand cycles (16 total ticks)
- Count 8 down to 1 on the NUM display while hand is blinking
- 16 cycles in the SOLID hand




Crosswalk State Machine

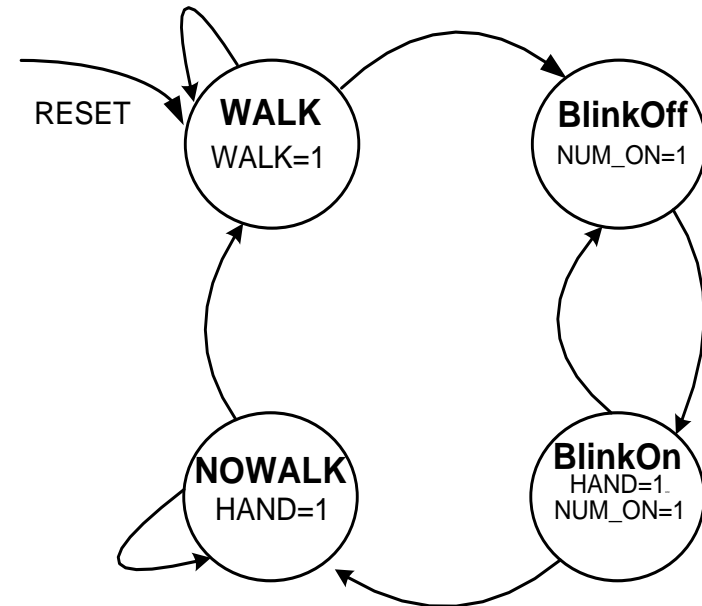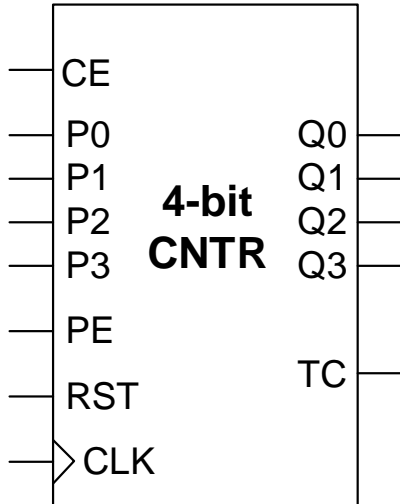- Use a 4-bit counter to count cycles along with an additional gate or two...



Crosswalk Controller Operation

 

Summary

- You should now be able to build:
 - Registers (w/ Enables)
 - Counters
 - Adders