

Spiral 2-2

Arithmetic Components and Their Efficient Implementations


Learning Outcomes

- I understand the control inputs to counters
- I can design logic to control the inputs of counters to create a desired count sequence
- I understand how smaller adder blocks can be combined to form larger ones
- I can build larger arithmetic circuits from smaller building blocks
- I understand the timing and control input differences between asynchronous and synchronous memories

DATAPATH COMPONENTS

Digital System Design

 - Control (**CU**) and Datapath Unit (**DPU**) paradigm
 - Separate logic into datapath elements that operate on data and control elements that generate control signals for datapath elements
 - Datapath: Adders, muxes, comparators, counters, registers (shift, with enables, etc.), memories, FIFO's
 - Control Unit: State machines/sequencers



Overflow

- Overflow occurs when the result of an arithmetic operation is _____ to be represented with the given number of bits
 - Unsigned overflow occurs when adding or subtracting unsigned numbers
 - Signed (2's complement overflow) overflow occurs when adding or subtracting 2's complement numbers

Detecting Overflow Helps Us Perform Comparison


OVERFLOW & COMPARISON

Unsigned Overflow

Overflow occurs when you cross this discontinuity

$$10 + 7 = 17$$

 With 4-bit *unsigned* numbers we can only represent 0 – 15. Thus, we say overflow has occurred.




2's Complement Overflow

$$5 + 7 = +12$$

$$-6 + -4 = -10$$

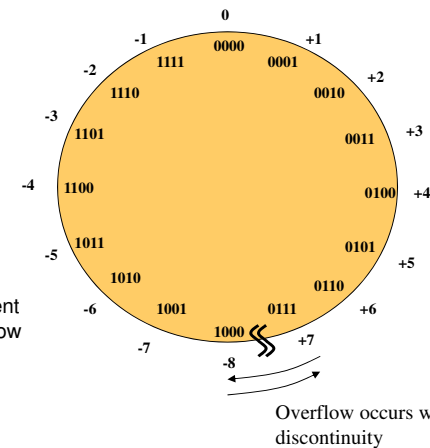With 4-bit *2's complement* numbers we can only represent -8 to +7. Thus, we say overflow has occurred.



Testing for Overflow

- Most fundamental test
 - Check if answer is _____ (i.e. Positive + Positive yields a negative)
- Unsigned overflow test [**Different** for add or sub]
 - Addition: If carry-out of final position equals _____
 - Subtraction: If carry-out of final addition equals _____
- Signed (2's complement) overflow test [**Same** for add or sub]
 - Only occurs if _____
 - Alternate test: if _____ of final column are different

Testing for Unsigned Overflow

- Unsigned Overflow has occurred if...
 - Unsigned Addition: If final carry-out = ____
 - Unsigned Subtraction: If final carry-out = ____

$$\begin{array}{r} 1011 \\ + 0110 \\ \hline \end{array}$$

$$\begin{array}{r} 1011 \\ + 0011 \\ \hline \end{array}$$

$$\begin{array}{r} 1011 \\ - 0110 \\ \hline \end{array}$$

$$\begin{array}{r} 0110 \\ - 1011 \\ \hline \end{array}$$

Testing for 2's Comp. Overflow

- 2's Complement Overflow Occurs If...
 - Test 1: If pos. + pos. = neg. or neg. + neg. = pos.
 - Test 2: If carry-in to MSB position and carry-out of MSB position are different

$$\begin{array}{r} 0101 \quad (5) \\ + 0110 \quad (6) \\ \hline \end{array}$$


$$\begin{array}{r} 1100 \quad (-4) \\ + 1001 \quad (-7) \\ \hline \end{array}$$

$$\begin{array}{r} 0011 \quad (3) \\ + 0010 \quad (2) \\ \hline \end{array}$$

$$\begin{array}{r} 1110 \quad (-2) \\ + 1010 \quad (-6) \\ \hline \end{array}$$

Checking for Overflow

 - Produce additional outputs to indicate if unsigned (UOV) or signed (SOV) overflow has occurred



COMPARISON

Comparison Via Subtraction

- Suppose we want to compare two numbers: A & B
- Suppose we let $DIFF = A - B$...what could the result tell us
 - If $DIFF < 0$, then _____
 - If $DIFF = 0$, then _____
 - If $DIFF > 0$, then _____
- How would we know $DIFF == 0$?
 - If all bits of our answer _____.
- How would we know $DIFF < 0$ (i.e. negative)?
 - Signed: _____! (but what about overflow)
 - Unsigned: Huh? In unsigned there are no negative results

Computing $A < B$ from "Negative" Result

Unsigned


- Perform A-B
- If A-B would yield a negative result, this will appear as _____ in an unsigned subtraction
- And we know unsigned subtraction overflow occurs if _____
- So just check if _____

Signed

- Perform A-B
- If **there is no overflow ($V=0$)**, simply check if _____
- But if there is overflow??
 - Recall overflow has the effect of flipping the sign of the result to the opposite of what it should be.
- So if **there is overflow ($V=1$)** check is _____ (i.e. positive)
- Summary: A-B is "truly" negative if:


Unsigned Comparator

 - A comparator can be built by using a subtractor



Signed Comparator

 - A comparator can be built by using a subtractor



Summary


- You should now be able to build:
 - Fast Adders
 - Comparators

ADDER TIMING

Addition – Full Adders


- Be sure to connect first C_{in} to 0
 
$$\begin{array}{r} 0110 = X \\ + 0111 = Y \\ \hline \end{array}$$




Timing

 - A chain of full adders presents an interesting timing analysis problem
- To correctly compute its own Sum and Carry-out, each full adder requires the carry-in from the _____ full adder
- Because hardware works in parallel, the full adders further down the chain may _____ produce the _____ outputs because the carry has not had time to _____ to them




Timing Example

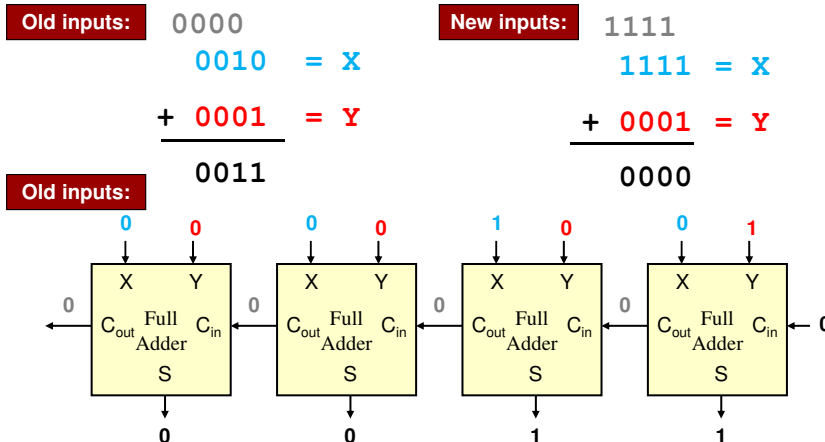- Assume that we were adding one set of inputs and then change to a new set of inputs:




Timing

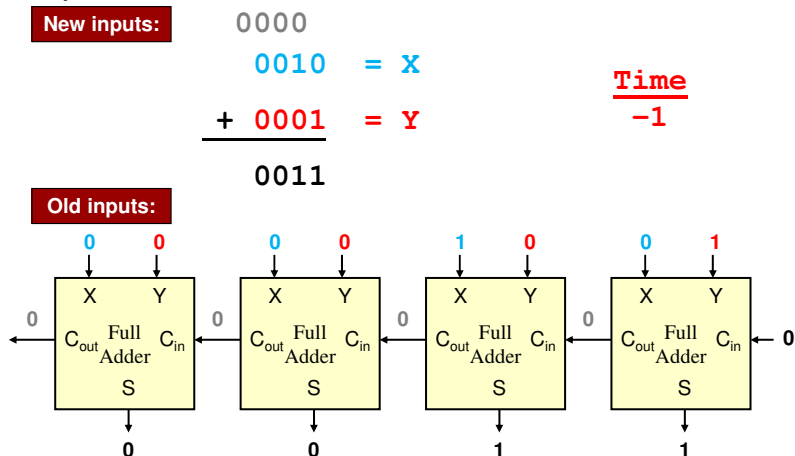- At the time just before we enter the new input values, all carries are 0's




Timing

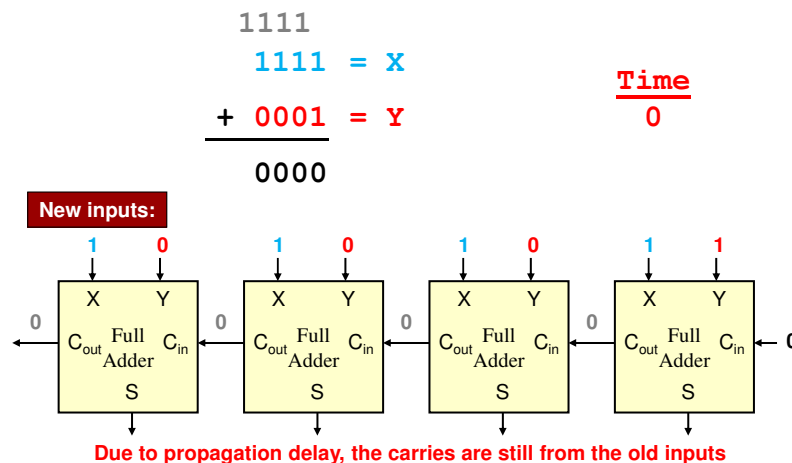- Now we enter the new inputs and all the FA's starting adding their respective inputs



Timing

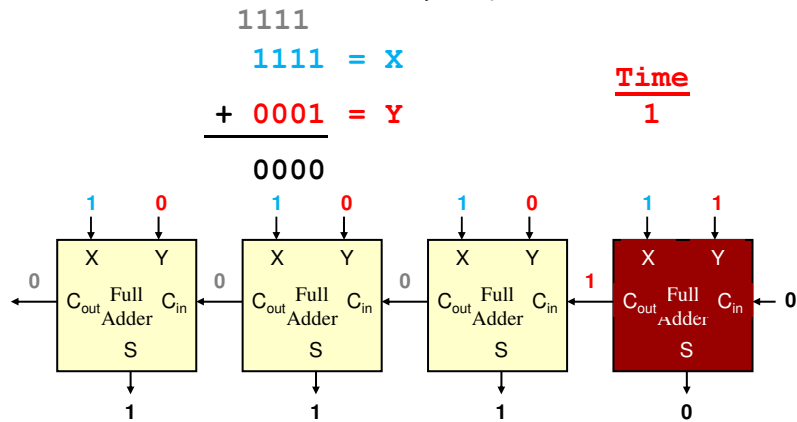
- Each adder computes from the current inputs (notice the sum of 1110 is incorrect at this point)



Now the carries are all based off the new inputs


Timing

 - The carry is "rippling" through each adder




Timing

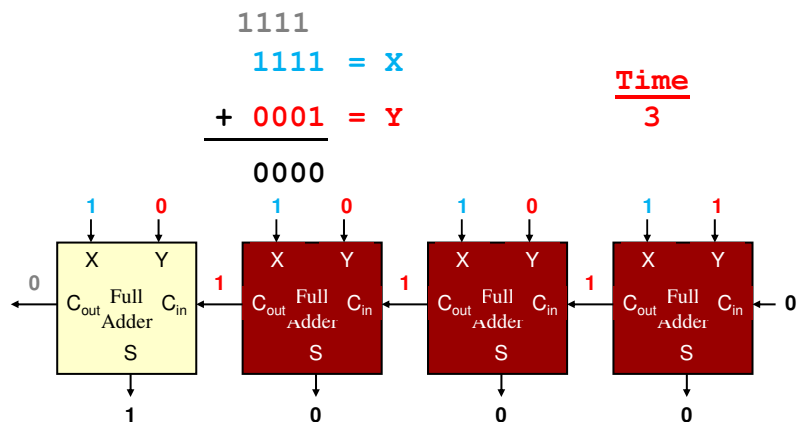- The carry is "rippling" through each adder





Timing

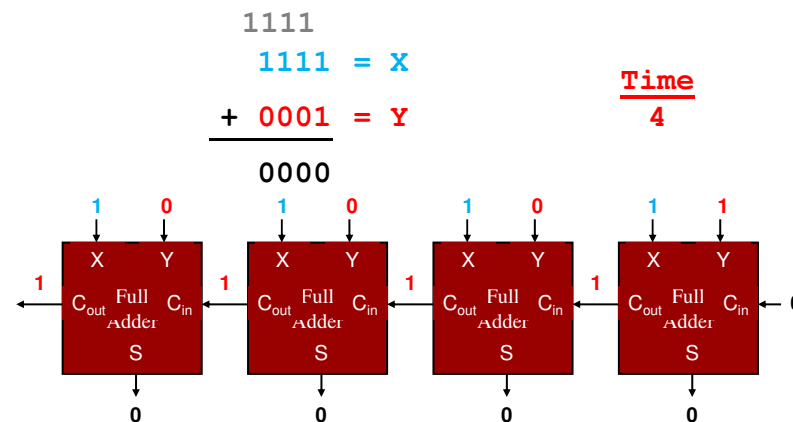- Only after the carry propagates through all the adders is the sum valid and correct




"Ripple-Carry" Adder

  - The longest path through a chain of full adders is the carry path
- We say that the carry "ripples" through the adder



Ripple Carry Adder Delay

 - An n-bit ripple carry adder has a worst case delay proportional to _____





Glitches

- _____ output values due to _____ arrival times of gate inputs

Output Glitches

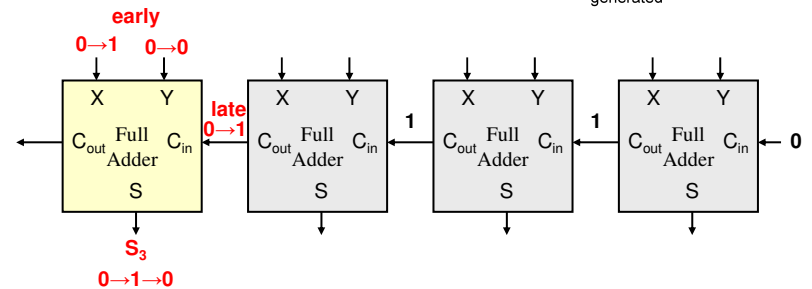 
- Delay of the carry causes glitches on the sum bits
- Glitch = momentarily, incorrect output value



Critical Path

- Critical Path = _____ possible delay path

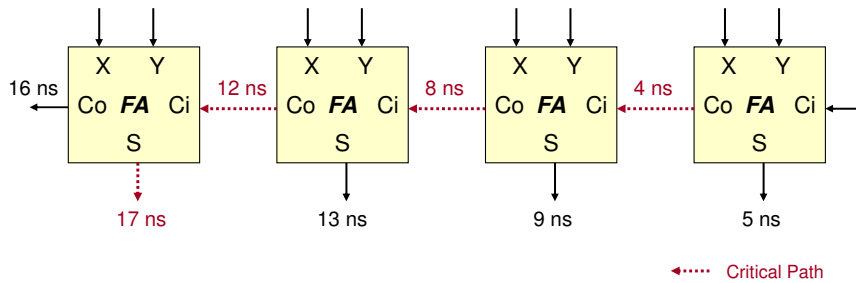Assume $t_{sum} = 5 \text{ ns}$,
 $t_{carry} = 4 \text{ ns}$



MULTIPLIERS


Unsigned Multiplication Review

- Same rules as decimal multiplication
- Multiply each bit of Q by M shifting as you go
- An m-bit * n-bit mult. produces an _____ bit result (i.e. n-bit * n-bit produces _____ bit result)
- Notice each partial product is a shifted copy of M or 0 (zero)


$$\begin{array}{r} 1010 \text{ M (Multiplicand)} \\ * 1011 \text{ Q (Multiplier)} \\ \hline \end{array}$$

Signed Multiplication Techniques

 - When adding signed (2's comp.) numbers, some new issues arise
- Must _____



 
$$\begin{array}{r} 1001 = -7 \\ * 0110 = +6 \\ \hline \end{array}$$




$$\begin{array}{r} 1001 = -7 \\ * 0110 = +6 \\ \hline \end{array}$$

Signed Multiplication Techniques

 - Also, must worry about negative multiplier
 - MSB of multiplier has negative weight
 - If MSB=1, _____


 
$$\begin{array}{r} 1100 = -4 \\ * 1010 = -6 \\ \hline \end{array}$$




$$\begin{array}{r} 1100 = -4 \\ * 1010 = -6 \\ \hline \end{array}$$

Combinational Multiplier

- Partial Product (PP_i) Generation
 - Multiply Q[i] * M
 - if Q[i]=0 => PP_i = ____
 - if Q[i]=1 => PP_i = ____


Combinational Multiplier

 - Partial Product (PP_i) Generation
 - Multiply Q[i] * M
 - if Q[i]=0 => PP_i = ____
 - if Q[i]=1 => PP_i = ____
 - _____ gates can be used to generate each partial product




Multiplication Overview

 - Multiplication approaches:
 - Sequential: Shift-and-Add produces one product bit per clock cycle time (usually slow)
 - Combinational: Array multiplier uses an array of adders
 - Can be as simple as N-1 ripple-carry adders for an NxN multiplication



 
AND Gate Array produces partial product terms



Combinational Multiplier

- Partial Products must be added together
- Combinational multipliers require long propagation delay through the adders
 - propagation delay is proportional to the number of partial products (i.e. number of bits of input) and the width of each adder


Array Multiplier

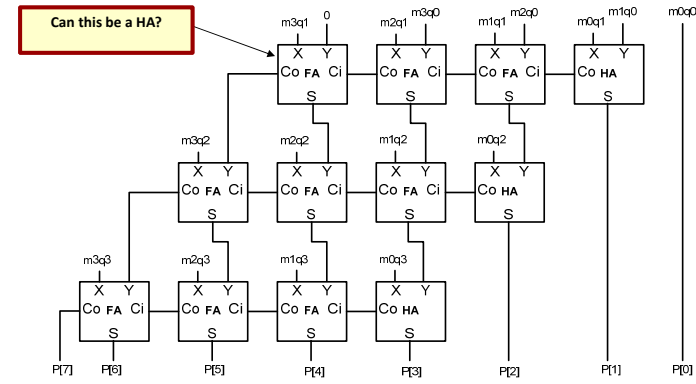

- Maximum delay = _____
 - Do you look for the longest path or the shortest path between any input and output?
 - Compare with the delay of a shift-and-add method

Adder Propagation Delay

 
$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$



Critical Path


- Critical Path = Longest possible delay path

 Assume $t_{sum} = 5 \text{ ns}$,
 $t_{carry} = 4 \text{ ns}$




..... Critical Path

Combinational Multiplier

 

Critical Paths

 


Combinational Multiplier Analysis

- Large Area due to _____-bit adders
 - n-1 because the first adder adds the first two partial products and then each adder afterwards adds one more partial product
- Propagation delay is in two dimensions
 - proportional to _____

Pipelined Multiplier

 
- Now try to pipeline the previous design



Determine the maximum stage delay to decide the pipeline clock rate. Assume zero-delay for stage latches. How does the latency of the pipeline compare with the simple combinational array of the previous stage?



Carry-Save Multiplier

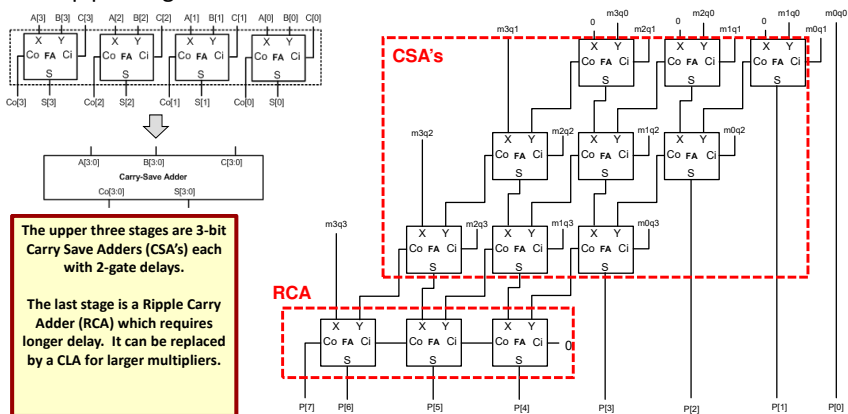- Instead of propagating the carries to the left in the same row, carries are now sent down to the next stage to reduce stage delay and facilitate pipelining





Carry Save Adders

  - Consider the decimal addition of $47 + 96 + 58 = 201$
- One way is to add _____ to get _____ and _____
- Here the _____ column cannot be added _____ is produced
- In the carry-save style, we add the _____ column and _____ column simultaneous



Carry-Save (3,2) Adders

- A carry save adder is also called a (3,2) adder or a (3,2) counter (refer to Computer Arithmetic Algorithms by Israel Koren) as it takes three vectors, adds them up, and reduces them to two vectors, namely a **sum vector** and a **carry vector**
- CSA's are based on the principle that carries do not have to be added _____, but can be combined _____
- An n-bit CSA consist of n disjoint full adders

  


Carry-Lookahead Adders

FAST ADDERS

Ripple Carry Adders

 - Ripple-carry adders (RCA) are slow due to carry propagation
 - At least 2 levels of logic per full adder



Fast Adders

- Rather than calculating one carry at a time and passing it down the chain, can we compute a group of carries at the same time
- To do this, let us define some new signals for each column of addition:
 - $p_i = \text{_____}$: This column will propagate a carry-in (if there is one) to the carry-out.
 p_i is true when A_i or B_i is 1 $\Rightarrow p_i = \text{_____}$
 - $g_i = \text{_____}$: This column will generate a carry-out whether or not the carry-in is '1'
 g_i is true when A_i and B_i is 1 $\Rightarrow g_i = \text{_____}$
- Using these signals, we can define the carry-out (c_{i+1}) as:


$$c_{i+1} = \text{_____}$$


Carry Lookahead Logic

- Define each carry in terms of p_i , g_i and the initial carry-in (c_0) and not in terms of carry chain (intermediate carries: c_1, c_2, c_3, \dots)
- $c_1 = \text{_____}$
- $c_2 = \text{_____}$
- $c_3 = \text{_____}$
- $c_4 = \text{_____}$

Carry Lookahead Analogy

 
- Consider the carry-chain like a long tube broken into segments. Each segment is controlled by a valve (propagate signal) and can insert a fluid into that segment (generate signal)
- The carry-out of the diagram below will be true if g_1 is true or p_1 is true and g_0 is true, or p_1 , p_0 and c_1 is true



 


Carry Lookahead Adder

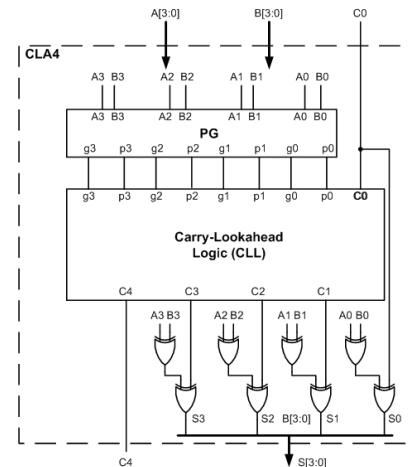- Use carry-lookahead logic to generate all the carries in one shot and then create the sum
- Example 4-bit CLA shown below
- How many levels of logic is the adder?




4-bit Adders

 - 74LS283 chip implements a 4-bit adder using CLA methodology



16-Bit CLA

 - But how would we make a 16-bit adder?
- Should we really just chain these fast 4-bit adders together?
 - Or can we do better?



16-bit RCA Delay = _____ = _____ gate delays
 Delay of the above adder design = _____ = _____ gates
 Let us improve by looking ahead at a higher level to produce C16, C12, C8, C4 in parallel

What's the difference between the equation for G here and C4 on the previous slides

Define P and G as the overall Propagate and Generate signals for a set of 4 bits

$$\begin{aligned}
 P &= p_3 \cdot p_2 \cdot p_1 \cdot p_0 \\
 G &= g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0
 \end{aligned}$$


REVIEW ON YOUR OWN FOR CLA LAB

16-bit CLA Closer Look

- Each 4-bit CLA only propagates its overall carry-in if each of the 4 columns propagates:
 - $P0 = p3 \bullet p2 \bullet p1 \bullet p0$
 - $P1 = p7 \bullet p6 \bullet p5 \bullet p4$
 - $P2 = p11 \bullet p10 \bullet p9 \bullet p8$
 - $P3 = p15 \bullet p14 \bullet p13 \bullet p12$
- Each 4-bit CLA generates a carry if any column generates and the more significant columns propagate
 - $G0 = g3 + (p3 \bullet g2) + (p3 \bullet p2 \bullet g1) + (p3 \bullet p2 \bullet p1 \bullet g0)$
 - ...
 - $G3 = g15 + (p15 \bullet g14) + (p15 \bullet p14 \bullet g13) + (p15 \bullet p14 \bullet p13 \bullet g12)$
- The higher order CLL logic (producing C4,C8,C12,C16) then is realized as:
 - $(C4) \Rightarrow C1 = G0 + (P0 \bullet c0)$
 - ...
 - $(C16) \Rightarrow C4 = G3 + (P3 \bullet G2) + (P3 \bullet P2 \bullet G1) + (P3 \bullet P2 \bullet P1 \bullet G0) + (P3 \bullet P2 \bullet P1 \bullet P0 \bullet c0)$
- These equations are exactly the same CLL logic we derived earlier

16-Bit CLA


- Understanding 16-bit CLA hierarchy...

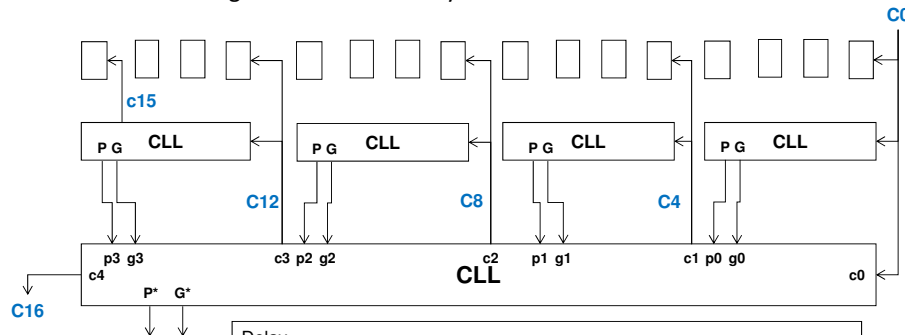

Delay =
 = ___ = Delay in producing pi,gi
 = ___ = Delay in producing Pi*,Gi*
 = ___ = Delay in producing C4,C8,C12,C16
 = ___ = Delay in producing c15
 = ___ = Delay in producing S15

64-Bit CLA

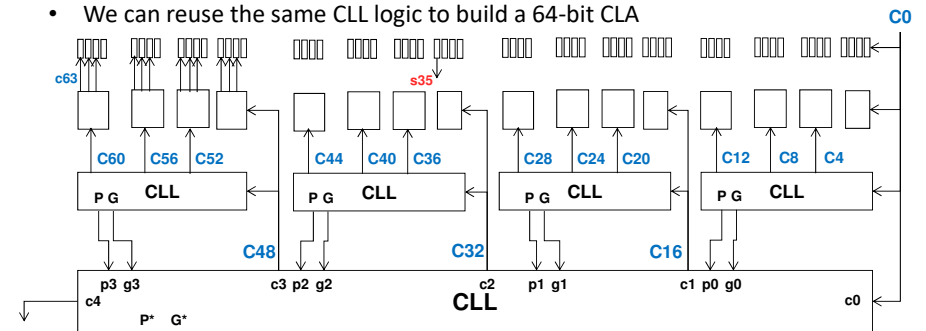- We can reuse the same CLL logic to build a 64-bit CLA



= ___ = Delay in producing S63
 Is the delay in producing s63 the same as in s35?
 = ___ = Delay in producing S2
 = ___ = Delay in producing S0

= ___ = Delay in producing pi*,gi*
 = ___ = Delay in producing Pj**,Gj**
 = ___ = Delay in producing C48
 = ___ = Delay in producing C60
 = ___ = Delay in producing C63
 = ___ = Delay in producing S63
 = ___ = Total Delay