

Spiral 2-3





Negative Logic
One-hot State Assignment
System Design Examples

Learning Outcomes

- I understand the active-low signal convention and how to interface circuits that use both active-high and active-low signals
- I can take any state diagram and create a corresponding state machine using one-hot implementation by using one FF per state and creating the D-input circuit by converting each incoming transition arrow to a state into a logic gate and OR-ing them together
- I understand how to decompose an algorithm into states for each step and appropriate datapath units for each operator



NEGATIVE (ACTIVE-LO) LOGIC

DeMorgan Equivalents

    



Negative Logic

  - Recall it is up to us humans to _____ to the two voltage levels
 - Thus, far we've used (unknowingly) the _____ logic convention where 1 means true and 0 means false
 - In _____ logic 0 means true and 1 means false




Why Active-low

  - Some digital circuits are better at _____ (draining/sucking) electric current than _____ (producing) current



Negative Logic 'AND' Function


Traditional P.L. AND

 

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

Traditional AND gate functionality assumes positive logic convention


N.L. AND function

 

X	Y	Z
1	1	1
1	0	1
0	1	1
0	0	0

Given negative logic signals, we can invert to positive logic, perform the AND operation, then convert back to negative logic

N.L. AND = P.L. OR

 


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

However, we then see that an OR gate implements the negative logic 'AND' function

Negative Logic 'OR' Function


Traditional P.L. OR

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

Traditional OR gate functionality assumes positive logic convention


N.L. OR function

 

X	Y	Z
1	1	1
1	0	0
0	1	0
0	0	0

Given negative logic signals, we can invert to positive logic, perform the OR operation, then convert back to negative logic

N.L. OR = P.L. AND

 


X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1


However, we then see that an AND gate implements the negative logic 'OR' function

Negative Logic

 A negative logic OR function is equivalent to an AND gate



 A negative logic AND function is equivalent to an OR gate





These are the preferred way of showing the N.L. functions because the inversion bubbles explicitly show where N.L. is being converted to P.L. and the basic gate schematics retain their meaning (when we see an AND gate we know we're doing some king of AND function with the bubbles indicating N.L.)


Active-hi vs. Active-low

- Active-hi convention
 - 1 = on/true/active
 - 0 = off/false/inactive
- Active-low convention
 - 0 = on/true/active
 - 1 = off/false/inactive
- To convert between conventions

Enables

  


Decoder w/ Active Low Enable and Outputs

 


Bubbles and signals starting with a slash '/' indicate an active-low input or output...not an inverter...the inverters are actually in the logic diagram on the next pages...

Active-Lo Outputs

 


When E=inactive (inactive means 0), Outputs turn off (off means 1)
When E=active (active means 1), Selected outputs turn on (on means 0)

Active-Lo Enable

 

When E=inactive (inactive means 1), Outputs turn off (off means 0)
When E=active (active means 0), Selected outputs turn on (on means 1)


Active-Lo Enable

 

When E=inactive (inactive means 1), Outputs turn off (off means 1)
When E=active (active means 0), Selected outputs turn on (on means 0)


Decoder w/ Multiple Enables

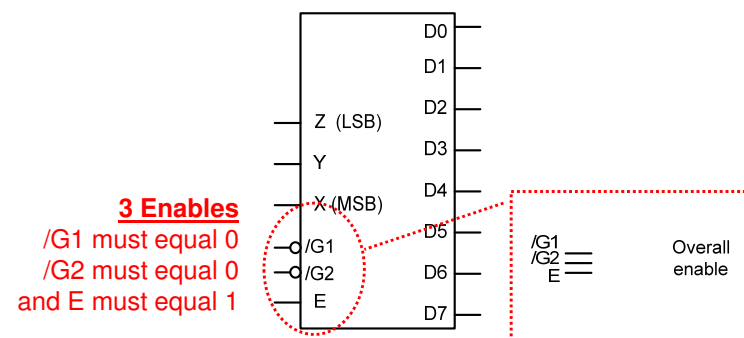- When a decoder has multiple enables, all enables _____ for the decoder to be enabled




Active Low CLR and PRESET

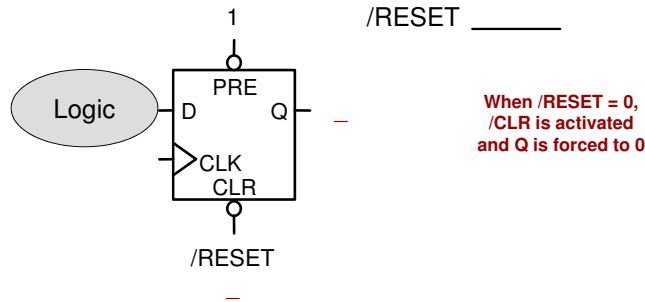- The reset signal might also be active low (0 = Reset, 1 = Normal operations)
- FFs can be made with active low /CLR & /PRE




Active Low CLR and PRESET

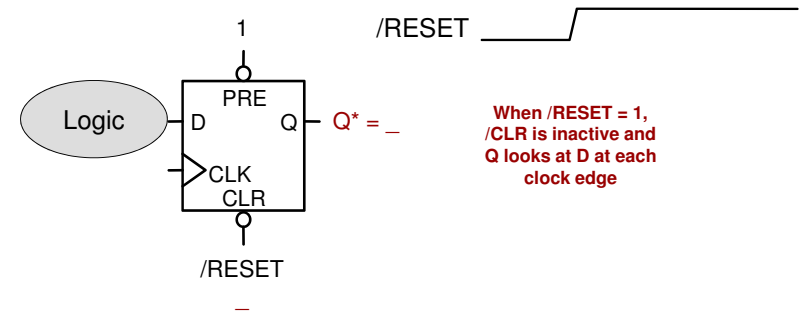- Need to be able to initialize Q to a known value (0 or 1)



ONE-HOT STATE ASSIGNMENT

Digital System Representation

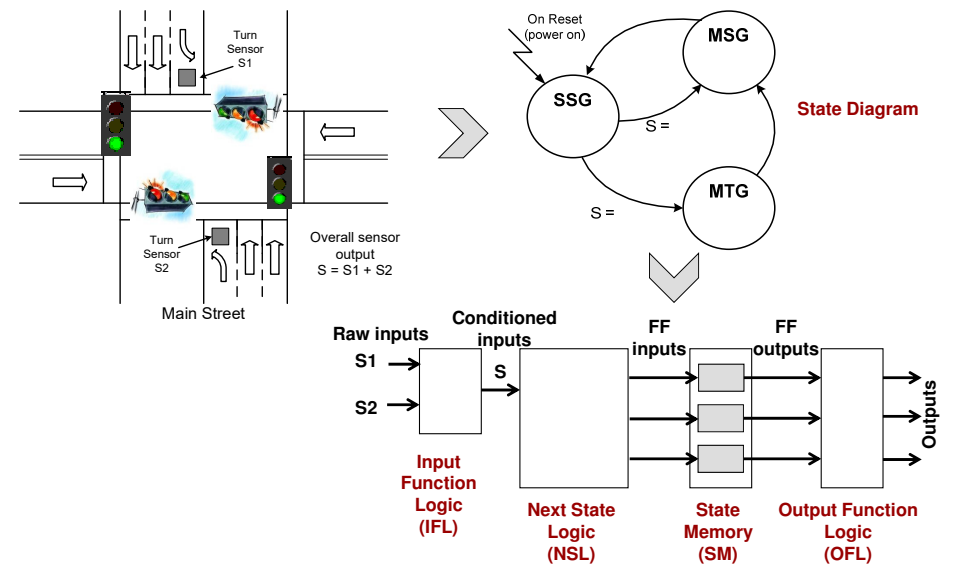

Encoded State Assignment Review



State Diagrams

- States
- Transition Conditions
- Outputs

State Machine



- State Memory => FF's
 - n-FF's => 2ⁿ states
- Next State Logic (NSL) + Input Function Logic (IFL)
 - combinational logic for FF inputs
- Output Function Logic (OFL)
 - MOORE: f(state)
 - MEALY: f(state + inputs)

  State Machines require sequential logic to remember the current state (w/ just combo logic we could only look at the current value of X, but now we can take 4 separate actions when X=0)




State Assignment

  - Design of the traffic light controller with main turn arrow
- Represent states with some binary code, but what kind?
 - Encoded: 3 States => _____ : ___=SSG, ___=MSG, ___=MTG
 - One-hot: Separate FF per state: ___=SSG, ___=MSG, ___=MTG




NSL Implementation in 1-Hot Method

- In one-hot assignment, NSL is designed by simple observation
- For each state, examine each _____ transition
 - Each incoming arrow will be one case in our logic
 - We can just _____ each condition together
- Describe each transition as a combination of what state it originates from & any associated conditions
- Ex. Two arrows converge on MS: "Q_{MS} should be '1' on the next clock when..."
 - Current state is _____OR...
 - Current state is _____AND_____

 


	Q _{SS}	Q _{MT}	Q _{MS}
SS	1	0	0
MT	0	1	0
MS	0	0	1

One-hot State Assignment

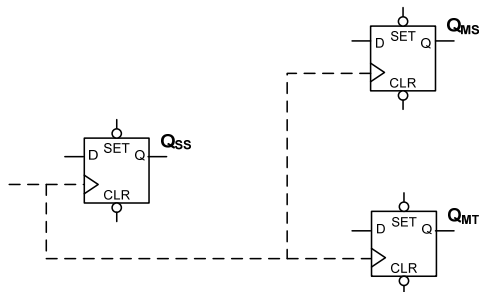


NSL Implementation in 1-Hot Method

 - Two arrows converge on MS: "Q_{MS} should be '1' on the next clock when..."
 - Current state is MT ...OR...
 - Current state is SS AND S=0
- Q*_{MS} = D_{MS} = Q_{MT} + Q_{SS}•S'
- Q*_{MT} = D_{MT} =
- Q*_{SS} = D_{SS} =
- What about initial state? Preset the appropriate flop.



	Q _{SS}	Q _{MT}	Q _{MS}
SS	1	0	0
MT	0	1	0
MS	0	0	1

One-hot State Assignment

 

Array Multiplier (Combinational)
Add and Shift Method (Sequential)

MULTIPLICATION TECHNIQUES

Multiplication Techniques

- A multiplier unit can be
 - Purely Combinational: Each partial product is produced in _____ and fed into an _____ of adders to generate the product
 - Sequential and Combinational: Produce and add 1 partial product at a time (_____)

Combinational Multiplier Analysis


- Large Area due to _____-bit adders
 - $n-1$ because the first adder adds the first two partial products and then each adder afterwards adds one more partial product
- Propagation delay is in two dimensions
 - proportional to _____

Add and Shift Method

- Sequential algorithm
- $n\text{-bit} * n\text{-bit}$ multiply
- Adds 1 partial product per clock
- Shift running sum 1-bit right each clock
- Three $n\text{-bit}$ Registers, 1 Adder
- At start:
 - $M = \text{Multiplicand}$
 - $Q = \text{Multiplier}$
 - $A = \text{Answer} \Rightarrow$ initialized to 0
- After completion
 - A and Q concatenate to form $2n\text{-bit}$ answer

Add and Shift Hardware
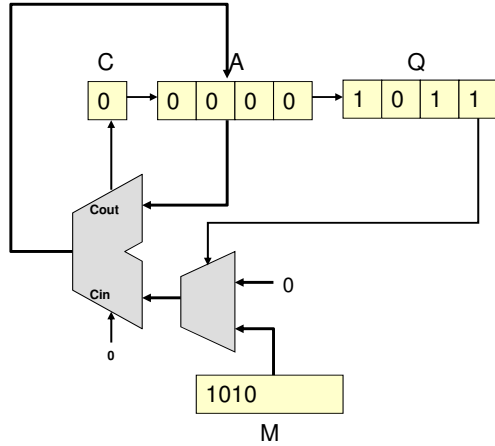
$$\begin{array}{r} 1010 = M \\ * 1011 = Q \\ \hline \end{array}$$




Add and Shift Algorithm

- C= __, A= __
- Repeat the following _____
 - If Q[0] = 0, A = _____
 - Else if Q[0] = 1, A= _____
 - Shift _____ 1-bit (0 → _____)

$$\begin{array}{r} 1010 \\ * 1011 \\ \hline \end{array}$$



Add and Shift Multiplication
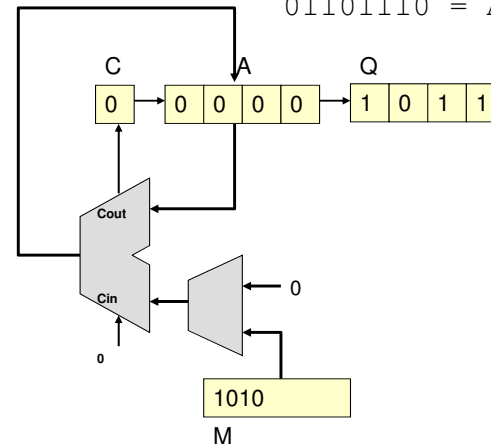
$$\begin{array}{r} 1010 = M \\ * 1011 = Q \\ \hline 01101110 = \text{Ans} \end{array}$$




M	A	Q
1010	0000	1011

Add and Shift Multiplication

 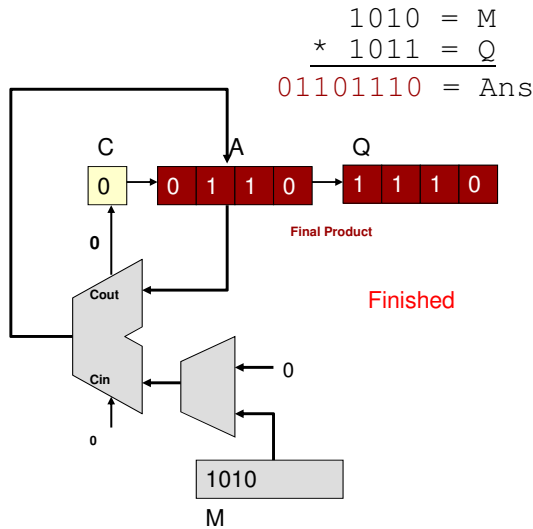

1101 * 0101 Example

 


C=0	M=1101 A=0000	Q=0101	Description
0	1101	0101	A=A+M
			Shift Right C,A,Q
			A=A+0
			Shift Right C,A,Q
			A=A+M
			Shift Right C,A,Q
			A=A+0
			Shift Right C,A,Q

Sequential Multiplier Analysis

- Pros:
 - _____
- Cons:
 - _____

Digital System Design

 
- Control and Datapath Unit paradigm
 - Separate logic into datapath elements that operate on data and control elements that generate control signals for datapath elements
 - Datapath: Adders, muxes, comparators, counters, registers (w/ enables)
 - Control Unit: State machines/sequencers



Let's Practice our Design Skills


- Break design into control and datapath

 - This is the datapath
- 1 Adder
- 2-to-1 mux
- 2 shift registers (A/Q)
- 1 normal reg (M)
- 1 FF w/ Enable (C)



State Machine Control

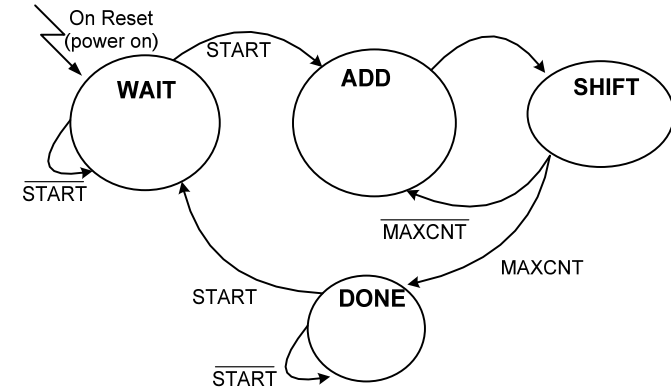- From our high level datapath we can arrive at a high-level state diagram




Refining our Design

- But now we need to refine our design to actual components, specific control bits, etc.


Sample Shift Register

 - Shift registers come in many flavors, we'll just look at one example
- 4-bit Bi-directional Shift Register
 - RST: synchronous reset
 - S[1:0]: Hold, Right Shift, Left Shift, or Load
 - DSL and DSR
 - Data to shift in from left or right



CLK	ACL R	S ₁	S ₀	Q*[3:0]	(case)
0,1	X	X	X	Q[3:0]	
↑	1	X	X	0000	Reset
↑	0	0	0	Q[3:0]	Hold
↑	0	0	1	D _{SR} , Q[3:1]	Right
↑	0	1	0	Q[2:0], D _{SL}	Left
↑	0	1	1	D[0:3]	Load


Shift Registers

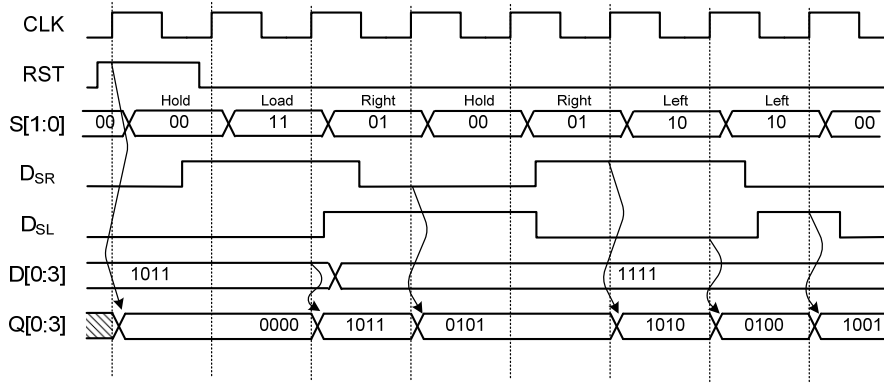

Complete the DataPath

Assume you build the state machine below and produce 4-signals that tell us which state we are in:


- Qwait
- Qadd
- Qsh
- Qdone

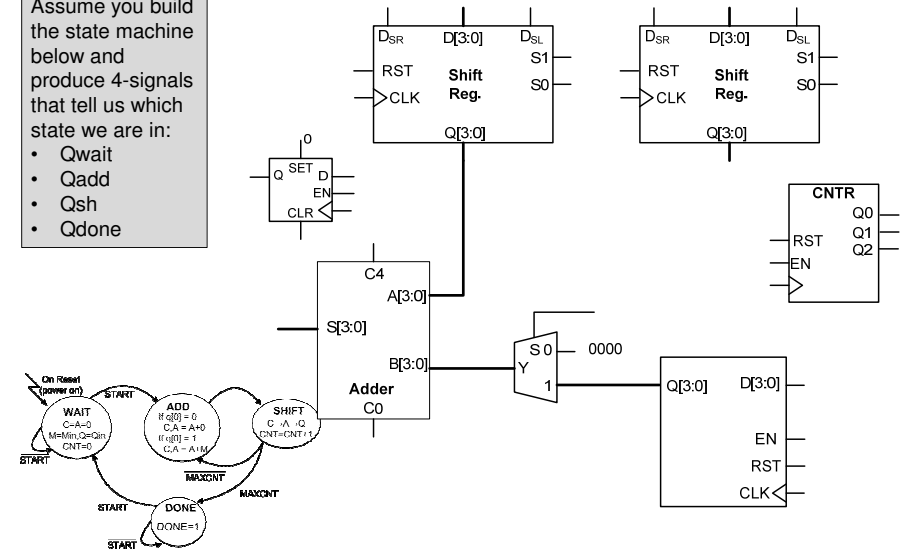

SIMPLE & PRIORITY ENCODERS

Encoders

 
- Another common datapath component
- Opposite function of decoders
- Takes in 2^n inputs and produces an n-bit number



Encoders

- What's inside an encoder?

I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	Y_2	Y_1	Y_0
1	0	0	0	0	0	0	0			
0	1	0	0	0	0	0	0			
0	0	1	0	0	0	0	0			
0	0	0	1	0	0	0	0			
0	0	0	0	1	0	0	0			
0	0	0	0	0	1	0	0			
0	0	0	0	0	0	1	0			
0	0	0	0	0	0	0	1			

 


Deriving equations for Y_0 , Y_1 , Y_2 is made simpler because of the assumption that only 1 input can be active at a time.

Encoders

- What's inside an encoder?

I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	Y_2	Y_1	Y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

$$Y_2 = \underline{\hspace{2cm}}$$

$$Y_1 = \underline{\hspace{2cm}}$$

$$Y_0 = \underline{\hspace{2cm}}$$

Encoders


- A simple binary encoder can be made with just _____ gates

Problems

- There is a problem...
 - Our assumption is that only 1 input can be active at a time
 - What happens if 2 or more inputs are active or if 0 inputs are active

2 or More Active Inputs

 - What if I5 and I2 are active at the same time?
 - Substitute values into equation
- Output will be '111' = 7
- Output is neither 2 nor 5, it's something different, 7




$$Y_2 = I_4 + I_5 + I_6 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$

$$Y_0 = I_1 + I_3 + I_5 + I_7$$


0 Active Inputs

 - What if no inputs are active?
 - Substitute values into equation
- Output will be _____
- Problem: '000' means that input 0 was active
 - Can't _____ between when '000' means input 0 was active or no inputs was active




Priority Encoders

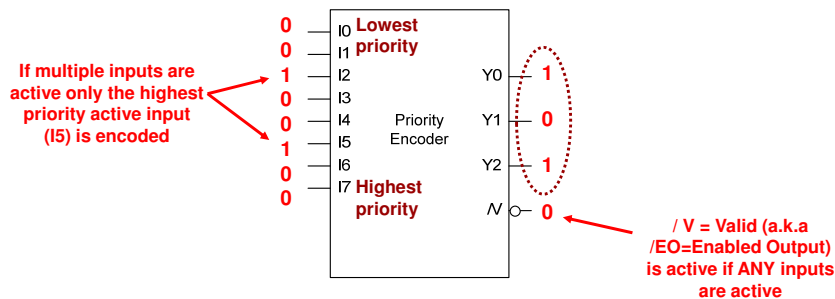- Fix the 2 problems seen above
- Problem of more than 2 active inputs
 - Assign priority to inputs and only encode the highest priority active input
- Problem of zero active inputs
 - Create an extra output to indicate if any inputs are active
 - We will call this output the "Valid" output (/V)




Priority Encoders

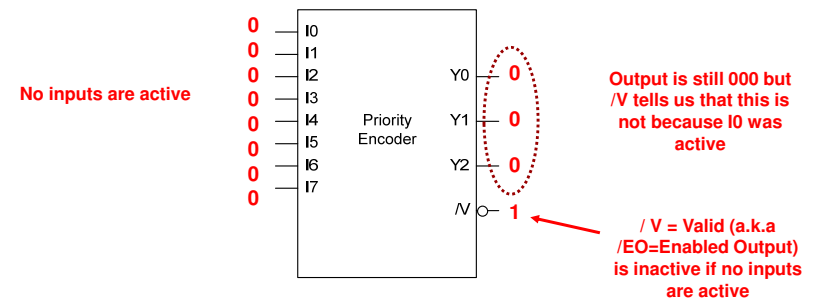- Fix the 2 problems seen above
- Problem of more than 2 active inputs
 - Assign priority to inputs and only encode the highest priority active input
- Problem of zero active inputs
 - Create an extra output to indicate if any inputs are active




Encoder Application: Interrupts

 - I/O Devices in a computer need to request attention from the CPU...they need to "interrupt" the processor
- CPU cannot have a dedicated line to each I/O device (too many inputs and outputs) plus it can only service one device at a time




Encoder Application: Interrupts

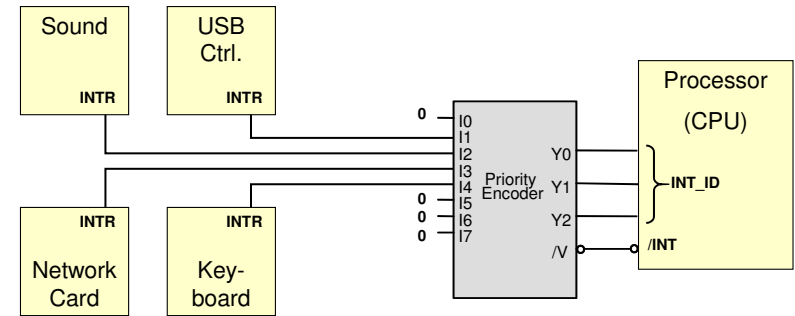- Solution: Priority Encoder
- /INT input of CPU indicates SOME device is requesting attention
- INT_ID inputs identify who is requesting attention



Encoder Application: Interrupts

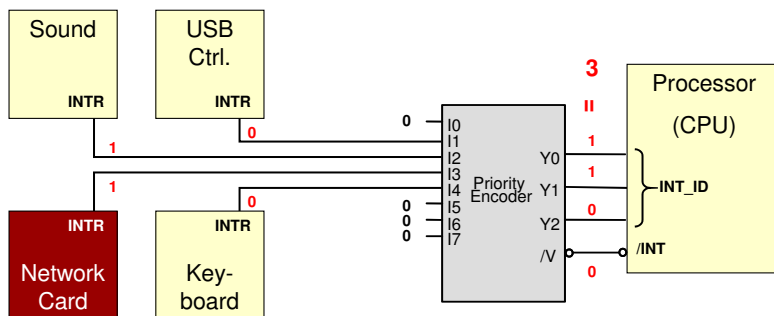
- Example: Sound and Network request interrupt at the same time
- Network is highest priority and is encoded
- After network is handled, sound will cause interrupt



VENDING MACHINE


Vending Machine Controller

- Consider a vending machine that sells Coke, Diet Coke, Sprite and Dr. Pepper
 - Drinks cost _____
 - Sensors indicate (for 1 clock cycle) when a user has entered a nickel, dime, quarter, or dollar bill
 - Max. input amount is _____ (beyond that the machine is not responsible for counting)
 - Individual buttons for each drink allow the user to select their drink and if at least \$1 has been entered, a release signal for each drink should be asserted
 - Making change will be considered in a future lab

 


Digital System Design

 - Control and Datapath Unit paradigm
 - Separate logic into datapath elements that operate on data and control elements that generate control signals for datapath elements
 - Datapath: Adders, muxes, comparators, counters, registers (w/ enables)
 - Control Unit: State machines/sequencers




Money Collection & Release FSM

 - Consider the state machine and datapath only for money collection and release signal generation



Pseudocode for collection algorithm:

Money Collection Datapath

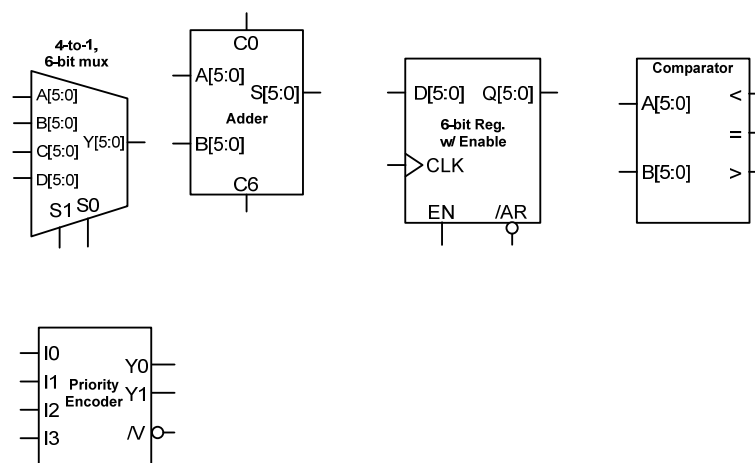

Sample Operation Waveform

