

Spiral 2-5

Sequential Logic Constructs

Learning Outcomes


- I understand how a bistable works
 - I understand how a bistable holds, sets, and resets
- I understand the issues that glitches pose to bistables and the need for latches
- I understand the difference between level-sensitive and edge-sensitive
- I understand how to create an edge-triggered FF from 2 latches

How sequential building blocks work

BISTABLES, LATCHES, AND FLIP-FLOPS

Sequential Logic

 - Suppose we have a sequence of input numbers on X[3:0] that are entered over time that we want to sum up
- Possible solution: Route the outputs back to the inputs so we can add the current sum to the input X




Sequential Logic

- Suppose we have a sequence of input numbers on X[3:0] that are entered over time that we want to sum up
- Possible solution: Route the outputs back to the inputs so we can add the current sum to the input X
- Problem 1: No way to initialize sum
- Problem 2: Outputs can race around to inputs and be added more than once per input number

→
9, 3, 2


Possible Solution

 

Outputs can feedback to inputs and update them sum more than once per input

Sequential Logic

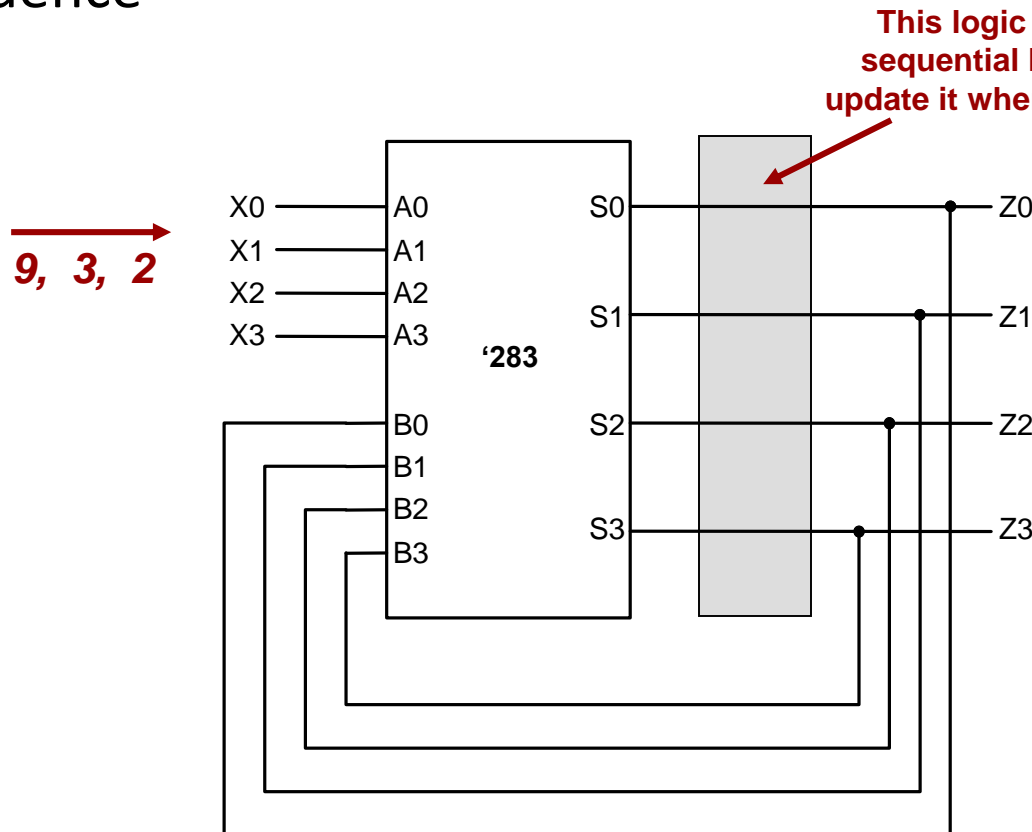- Add logic at outputs to just capture and remember the new sum until we're ready to input the next number in the sequence




The data can still loop around and add up again (2+2=4) but if we just hold our output = 2 then the feedback loop will be broken

We remember initial sum of 2 until input 3 arrives at which point we'd capture & remember the sum 5.



Sequence Adder

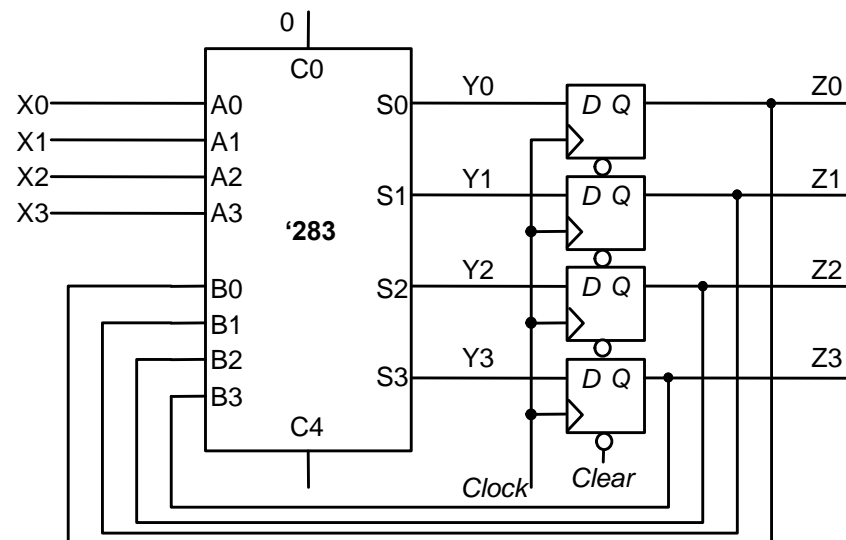- If X changes once per cycle then Z should also change once per cycle
- That is why we will use a register (flip-flops) to ensure the outputs can only update once per cycle





Sequence Adder

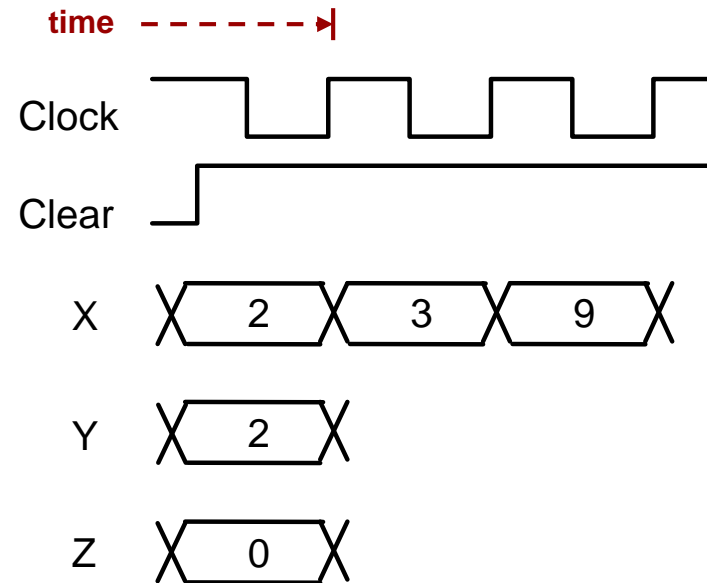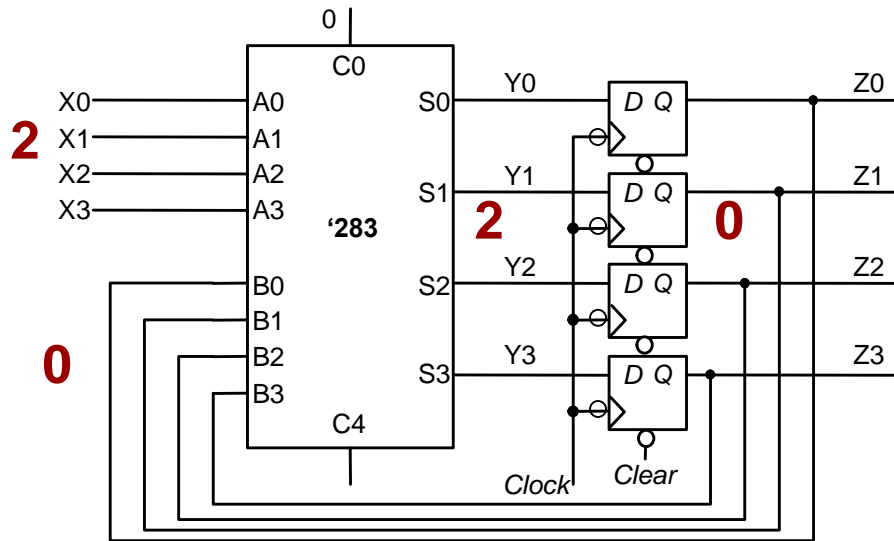- The 0 on Clear will cause Z to be initialized to 0, but then Z can't change until the next positive edge
- That means we will just keep adding $0 + 2 = 2$





Sequence Adder

 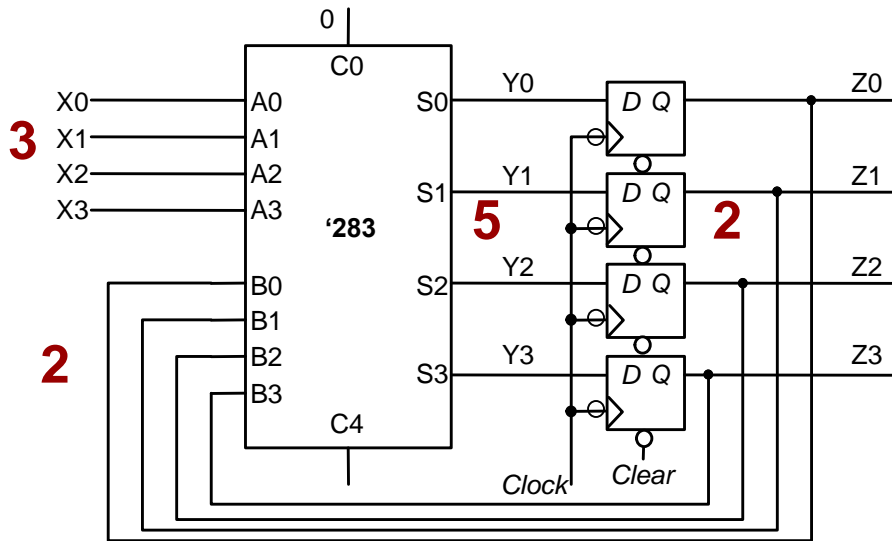- At the edge the flip-flops will sample the D inputs and then remember 2 until the next positive edge
- That means we will just keep adding $3 + 2 = 5$



Sequence Adder

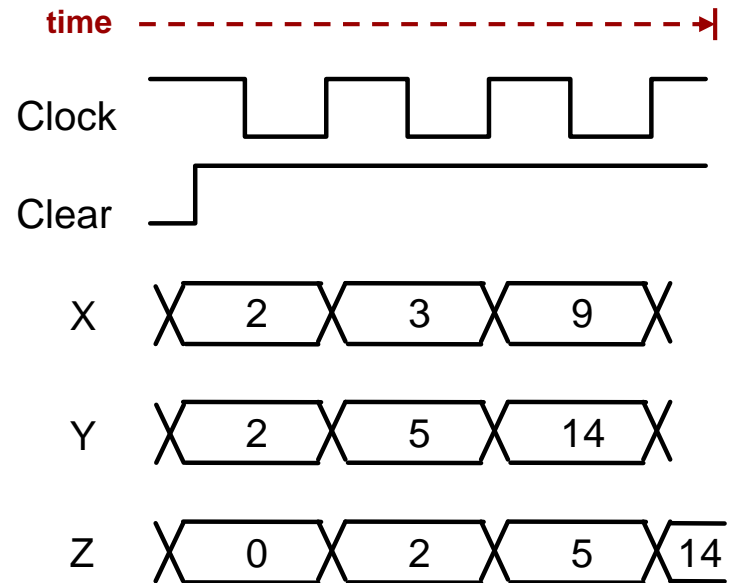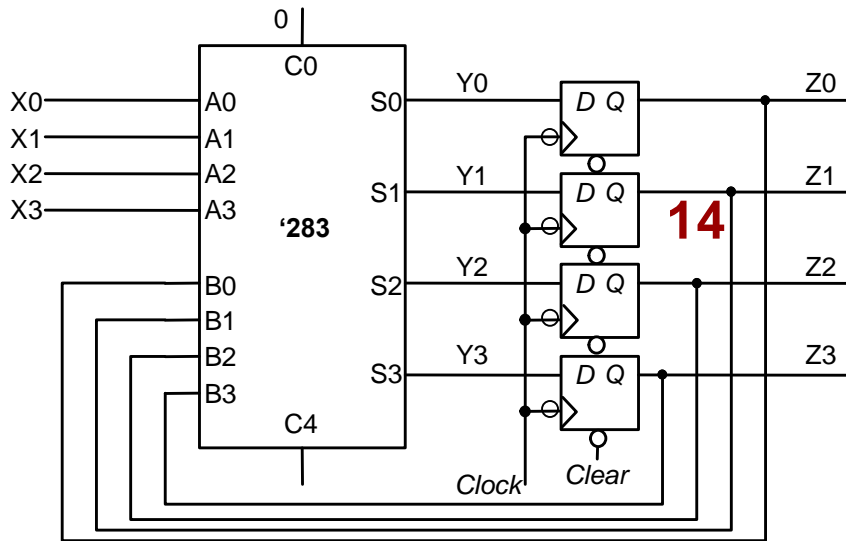- Finally, at the positive edge the flip-flops will sample the D inputs and then remember 14




Sequential Logic

- But how do flip-flops work?
 - Our first goal will be to design a circuit that can remember one bit of information
 - Easiest approach...
-
- But how do you change the input?
 - A signal should only have one driver

SET/RESET BISTABLES


RS (or SR) Bistable

 - Terminology
 - Set = Force output to 1
 - Reset = Force output to 0
- Set/Reset Bistable Circuit
 - A circuit that can set or reset its output...
 - ...but then can remember its current output value once the inputs are removed



RS (SR) Bistable

 - Cross-Connected NOR gates (outputs feed back to inputs)
- When Set = 1, Q should be forced to 1
- When Reset = 1, Q should be forced to 0
- When neither are 1, Q should remain at its present value




RS (SR) Bistable

Always start your analysis from the output Q and cycle it around the loop

S	R	Q	Q'
0	0		
1	0		
0	1		
1	1		


2 0 NOR Q' = Q

 

3 Process continues, outputs are remembered


RS (SR) Bistable

S	R	Q	Q'
0	0	Q_0	Q_0'
1	0		
0	1		
1	1		

 

RS (SR) Bistable


S	R	Q	Q'
0	0	Q_0	Q_0'
1	0	1	0
0	1	0	1
1	1		

 

RS (SR) Bistable


S	R	Q	Q'
0	0	Q_0	Q_0'
1	0	1	0
0	1	0	1
1	1		

 • 1,1 combination violates the Q, Q' relationship



RS (SR) Bistable


S	R	Q	Q'
0	0	Q_0	Q_0'
1	0	1	0
0	1	0	1
1	1	0 (illegal)	0 (illegal)

 

- 1,1 combination violates the Q, Q' relationship
- It cannot be “remembered”...meaning as soon as R or S goes to 0 then it will set and reset; if R and S goto 0 at the same instant, then we will have unpredictable behavior

Another Waveform

 - Waveform for an SR bistable with active-hi inputs (cross-connected NOR gates)





Criteria for a Bistable

1. Able to independently set (preset) \Rightarrow Force $Q=1$
2. Able to independently reset (clear) \Rightarrow Force $Q=0$
3. Able to remember (hold) $\Rightarrow Q = Q_0$

  Exercises

- Complete the waveforms below for an RS bistable with active hi inputs




A problem with bistables

MOTIVATION FOR LATCHES

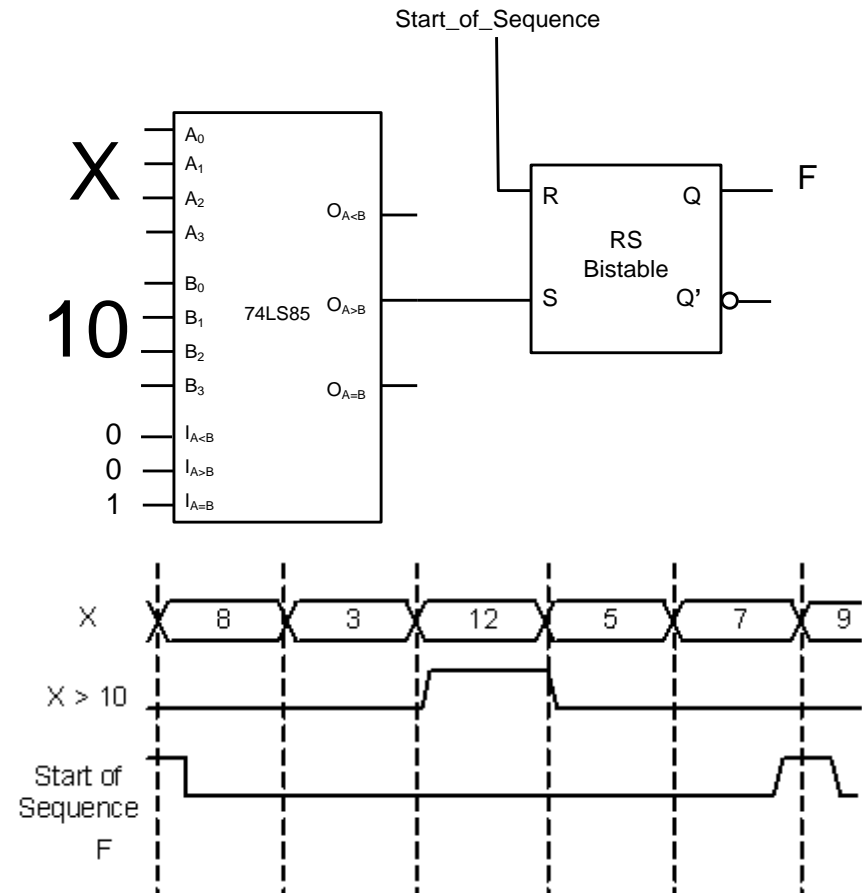
Problem w/ Bistables

- Bistables will remember input values whether we want them to or not
- Imagine we connect the Set input to the output of a comparator to check if any number in a sequence is > 10 and then remember that



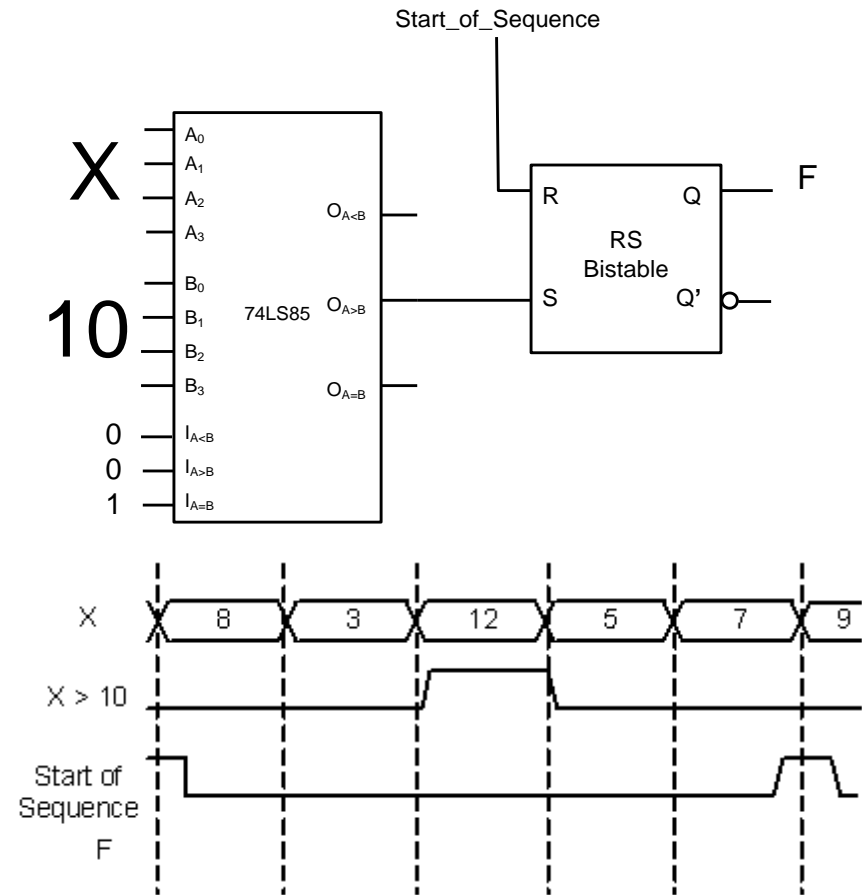
Problem w/ Bistables

- When inputs change in a combinational circuit, the outputs may transition back and forth between 1 and 0
- This is called a “glitch” and is caused due to the propagation delay of the combinational logic



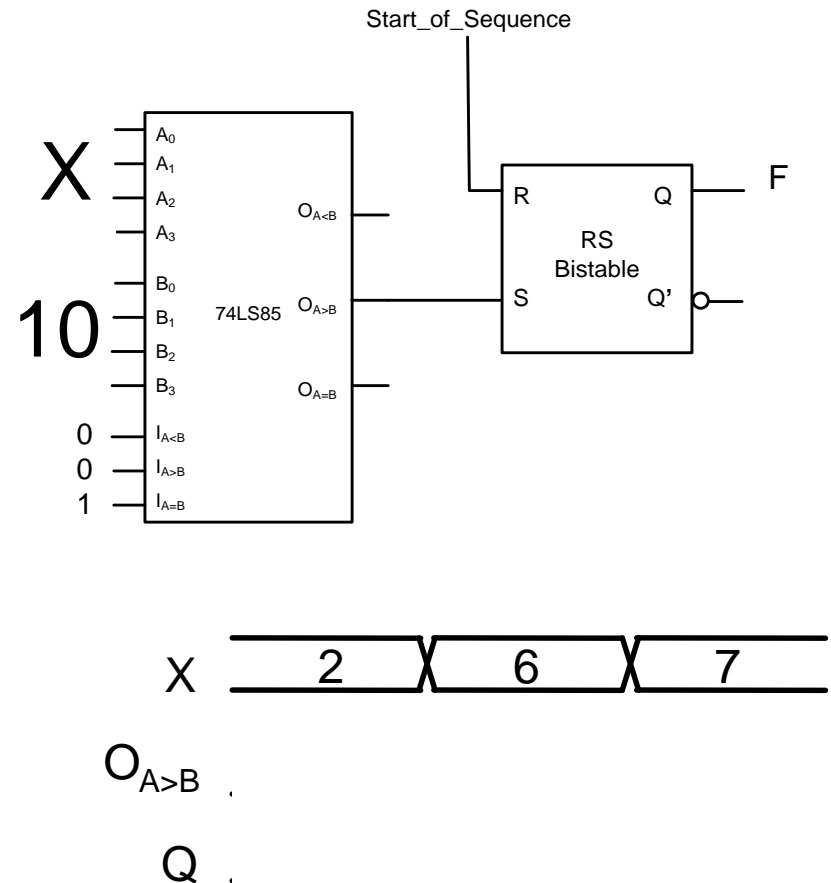
Problem w/ Bistables

- Suppose we get a sequence: 2,6,7
- At the end Q should still = 0 since no numbers > 10
- However, if when the inputs change a small glitch occurs on $A > B$, the bistable will remember that and set $Q = 1$



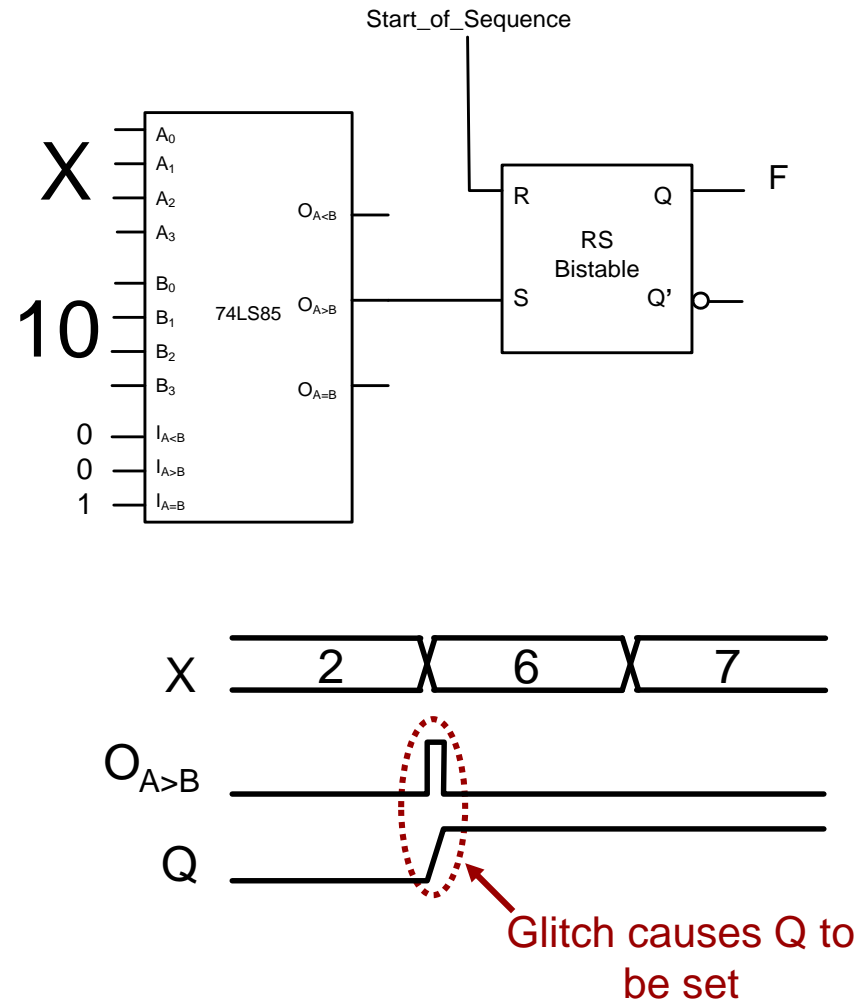
Problem w/ Bistables

- Output should have been 0 at end of sequence
- Problem: Glitch was remembered
- Need some way to ignore inputs until they are stable and valid




Clock Signals

 - A clock signal is an alternating sequence of 1's and 0's
- It can be used to help ignore the inputs of a bistable when there might be glitches or other invalid values
- Idea:
 - When clock is 0, ignore inputs
 - When clock is 1, respond to inputs



Latches

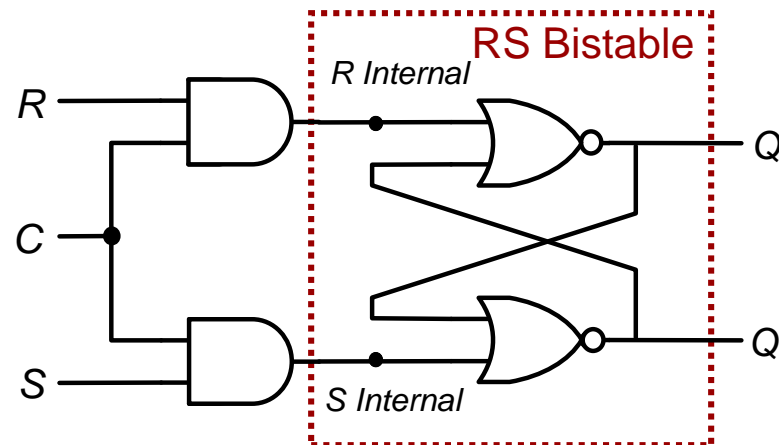
- Latches are bistables that include a new **clock input**
- The clock input will tell the latch when to ignore the inputs (when $C=0$) and when to respond to them (when $C=1$)



RS Latch


Latches

RS Latch
(C=0)

 

C=0 causes S=R=0 and thus Q and Q' remain unchanged

RS Latch
(C=1)

 


C=1 allows S,R to pass and thus Q and Q' are set, reset or remain unchanged based on those inputs

Latches

- Rule
 - When clock = 0, inputs don't matter, outputs remain the same
 - When clock = 1, inputs pass to the inner bistable and the outputs change based on those inputs


SR-Latch

 - When $C = 0$, Q holds (remembers) its value
- When $C = 1$, Q responds as a normal SR-bistable




CLK	S	R	Q	Q'
0	x	x	Q_0	Q_0'
1	0	0	Q_0	Q_0'
1	1	0	1	0
1	0	1	0	1
1	1	1	illegal	


SR-Latch

 

CLK	S	R	Q	Q'
0	x	x	Q_0	Q_0'
1	0	0	Q_0	Q_0'
1	1	0	1	0
1	0	1	0	1
1	1	1	illegal	

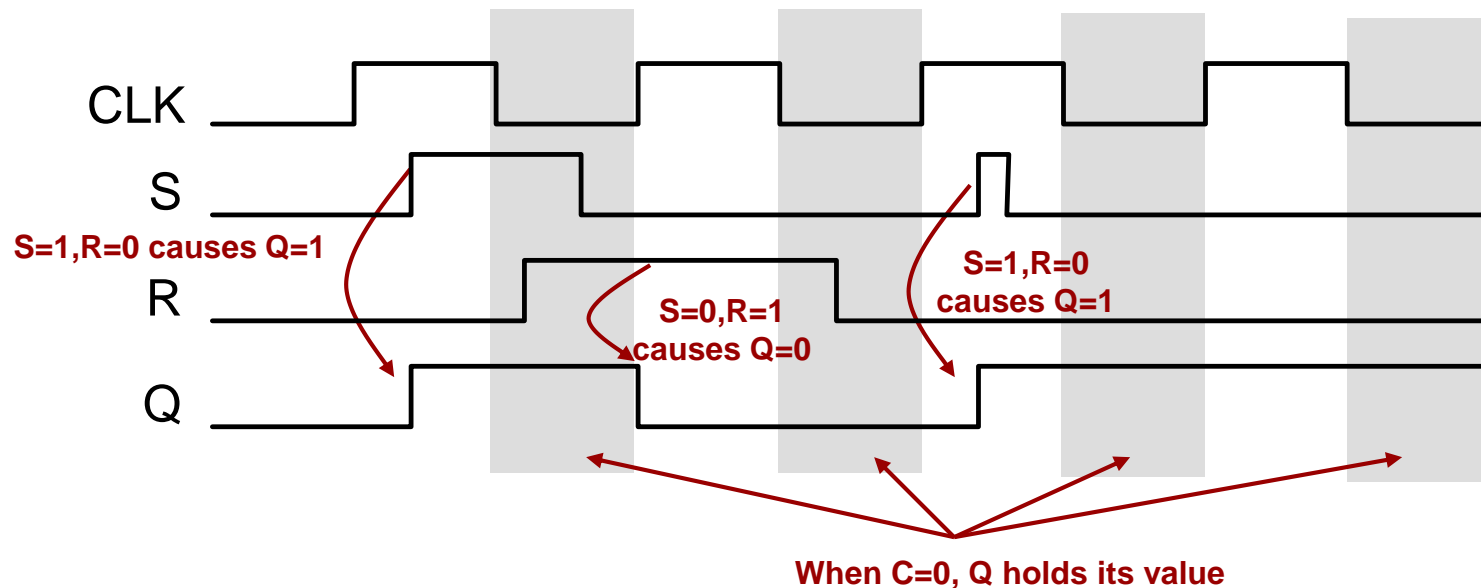


RS (SR) Latches

 

C	S	R	Q	Q'
0	x	x	Q_0	Q_0'
1	0	0	Q_0	Q_0'
1	1	0	1	0
1	0	1	0	1
1	1	1	illegal	illegal



When C=0, ignore inputs

When C=1, outputs change based on inputs

 

Solution with Latches

 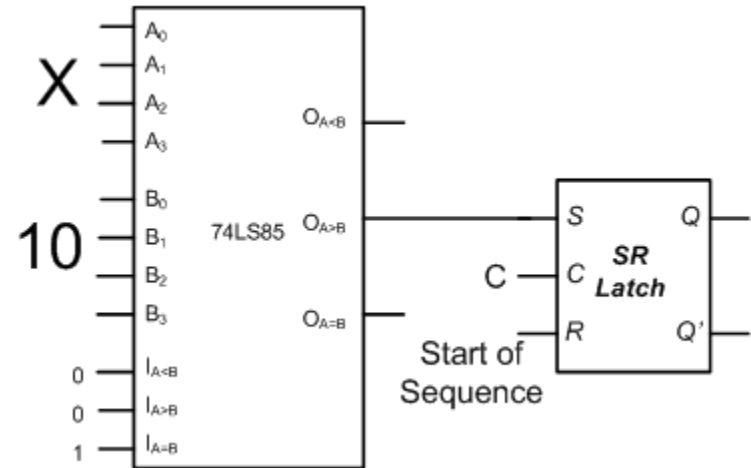
- $C = 0$ when inputs change
 - In fact, in a real digital system, it is C 's transition to 0 that triggers the inputs to change
 - Glitches occur during this time and are filtered
- When $C = 1$, inputs are stable and no glitches will occur



MOTIVATION FOR D-LATCHES

Adding a Sequence of Numbers

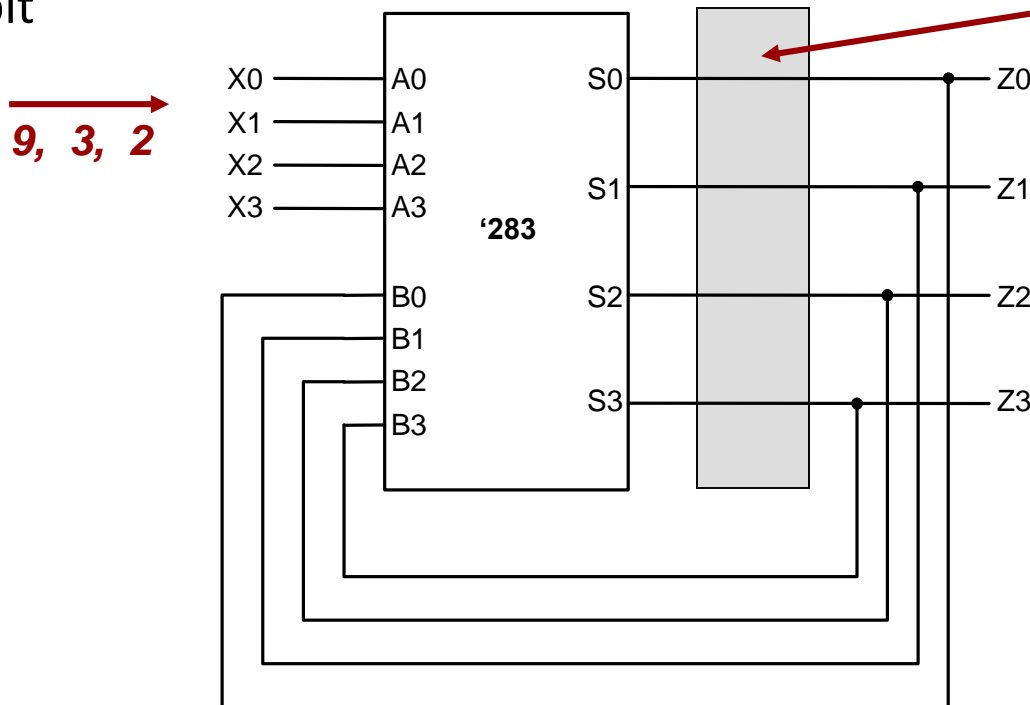- Back to our example of adding a sequence of numbers
 - RS latches require 2 inputs (S,R) per output bit Q
 - In this scenario, we only have 1-bit of input per output
 - We'll modify an SR latch to become a latch that can remember 1 input bit




This logic should *remember* (i.e. sequential logic) the sum and only update it when the next number arrives

Just remember initial sum of 2 until 3 arrives.

The data can still loop around and add up again (2+2=4) but if we just remember our output = 2 then the feedback loop will be broken


D-Latches

 - D-Latches (Data latches) store data when the clock is low and pass data when the clock is high
- D-Latch is just an SR Latch with the D-input run into the S-input and inverted into the R-input



D-Latches

Hold Mode

 


C	D	Q	Q'
0	x	Q_0	Q_0'
1	0	0	1
1	1	1	0

Hold Mode

Transparent Mode

 
When $C=0$, outputs don't change no matter what the inputs do



When $C=1$, outputs change based on inputs

D-Latches

Hold Mode

 

C	D	Q	Q'
0	x	Q ₀	Q ₀ '
1	0	0	1
1	1	1	0


Hold Mode

Transparent Mode

D-LATCH 7475

As clock is LOW, don't look at the D input

 Triggering Rule: The Q output follow the D input (i.e. Q=D) when the clock or gate input is high (i.e. the latch is enabled). When the latch is disabled (Clock = LOW) the output remains put.



D-Latches

- When $C = 0$, $Q = Q_0$
 - Hold mode \Rightarrow Q stays the same
- When $C = 1$, $Q = D$
 - Transparent mode \Rightarrow Q follows D

Bistables vs. Latches

Bistables

- No clock input
 - outputs can change anytime the inputs change (including glitches)

Latches

- Clock/Gate/Enable input
 - outputs can only change during clock high/low time

Notation

- To show that Q remembers its value we can put it in the past tense:
 - $Q = Q_0$ (Current Value of Q = Old Value of Q)
- OR put it in the future tense
 - $Q^* = Q$ (Next Value of Q = Current Value of Q)

Indicates "next-value" of Q

C	D	Q	Q'
0	x	Q_0	Q_0'
1	0	0	1
1	1	1	0

Current Value = Old Value


C	D	Q*	Q''*
0	x	Q	Q'
1	0	0	1
1	1	1	0

Next Value = Current Value

Adding a Sequence of Numbers

- Suppose we have a sequence of numbers that comes in over time that we want to sum up
- Possible solution: Route the outputs back to the inputs so we can add the current sum to the input X
- Problem 1: No way to initialize sum
- Problem 2: Outputs can race around to inputs and be added more than once per input number


9,3,2 →

 

Outputs feedback to inputs and update them sum more than once per input

Adding a Sequence of Numbers

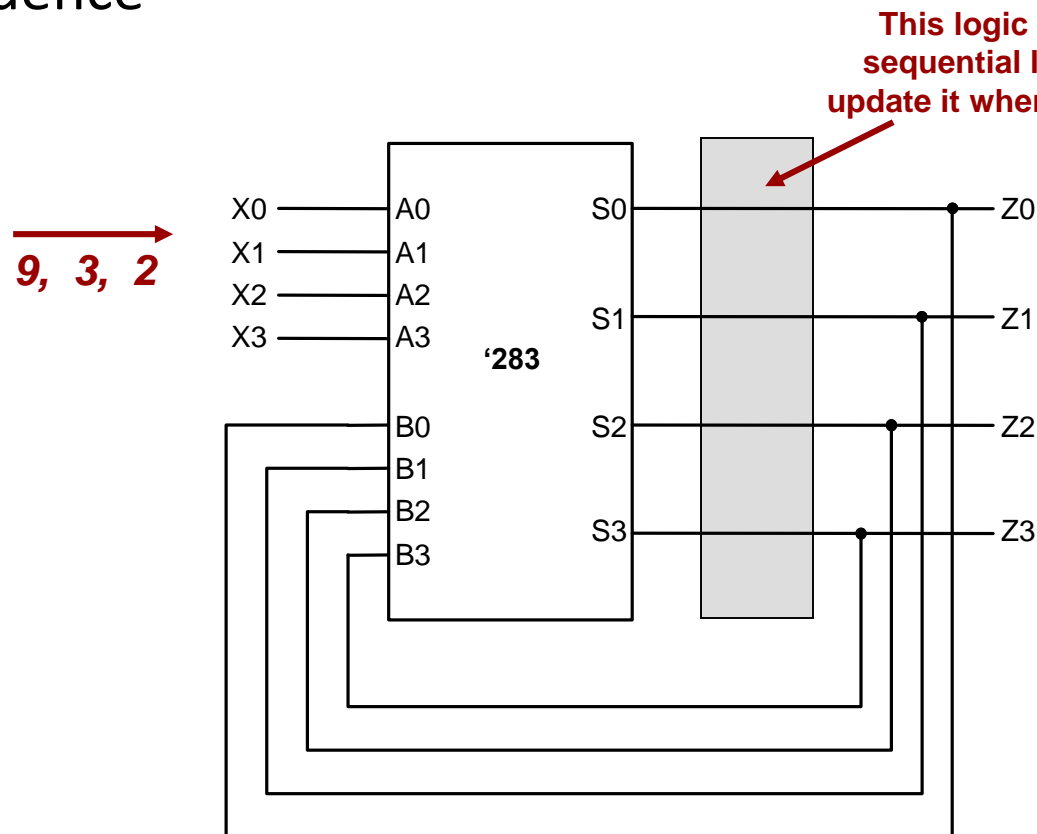- Add logic at outputs to just capture and remember the new sum until we're ready to input the next number in the sequence




This logic should *remember* (i.e. sequential logic) the sum and only update it when the next number arrives

Just remember initial sum of 2 until 3 arrives.

The data can still loop around and add up again ($2+2=4$) but if we just remember our output = 2 then the feedback loop will be broken


Adding a Sequence of Numbers

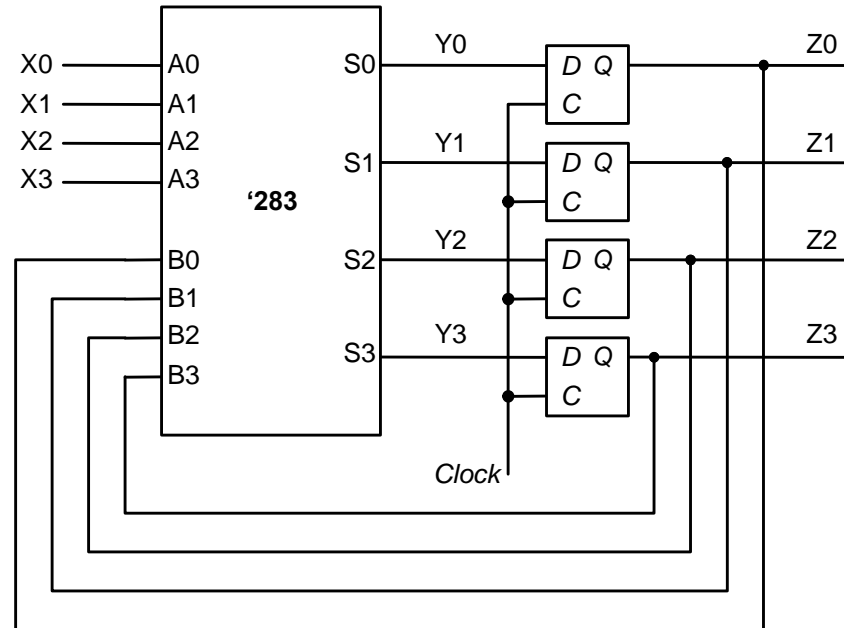- What if we put D-Latches at the outputs




Adding a Sequence of Numbers

- We'll change X on every clock period

 


When C=0 => Q* = Q
When C=1 => Q* = D

 


Adding a Sequence of Numbers

- Since the clock starts off low, the outputs of the latches can't change and just hold at 0

2


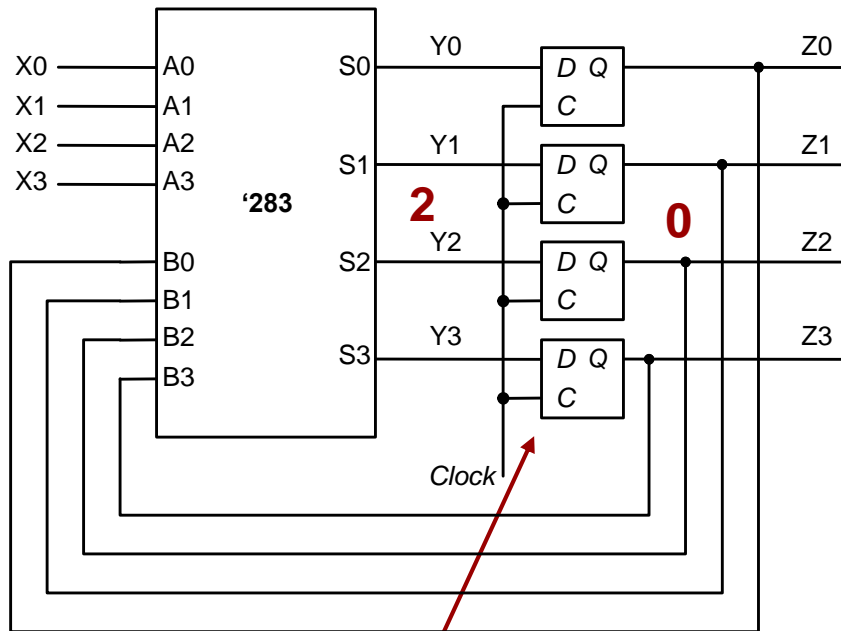


When C=0 => Q* = Q
When C=1 => Q* = D

 

Adding a Sequence of Numbers

 
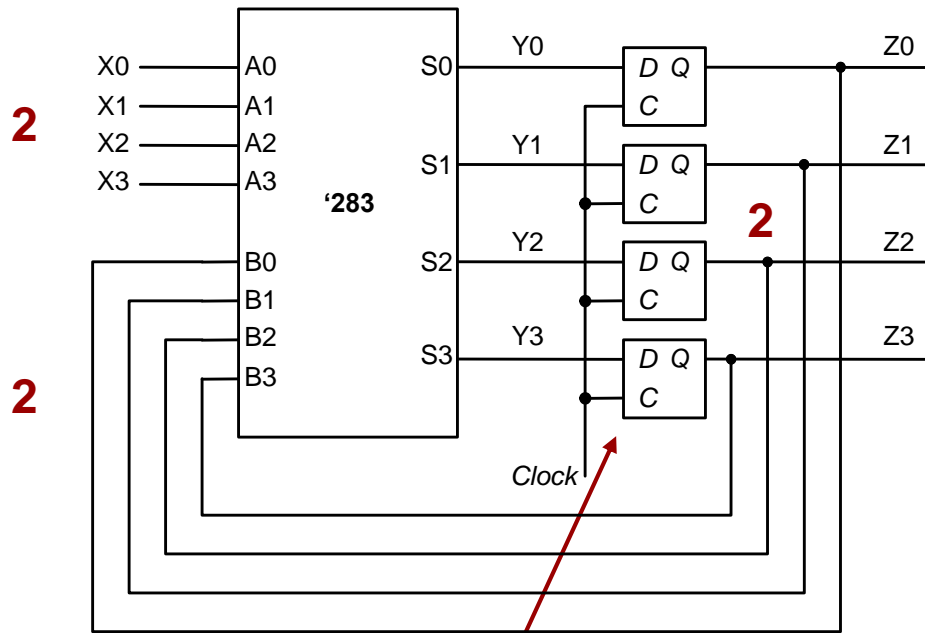
- When the clock goes high the D goes through to Q and is free to loop back around



When C=0 => Q* = Q
When C=1 => Q* = D

Adding a Sequence of Numbers

 
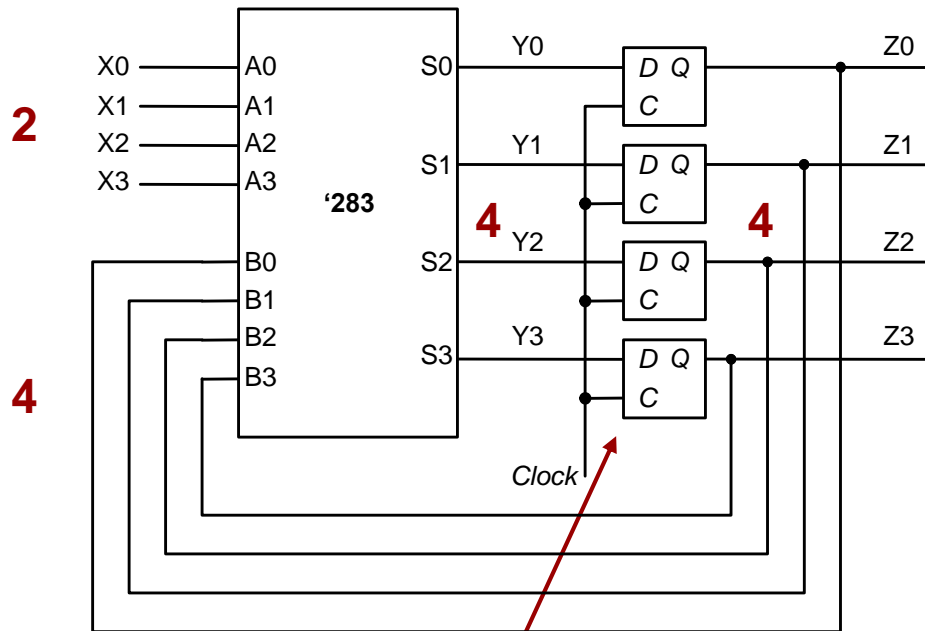
- Once it loops back around it will be added again, change the Y value and go through to Z and loop back around again



When C=0 => Q* = Q
When C=1 => Q* = D

Adding a Sequence of Numbers

 
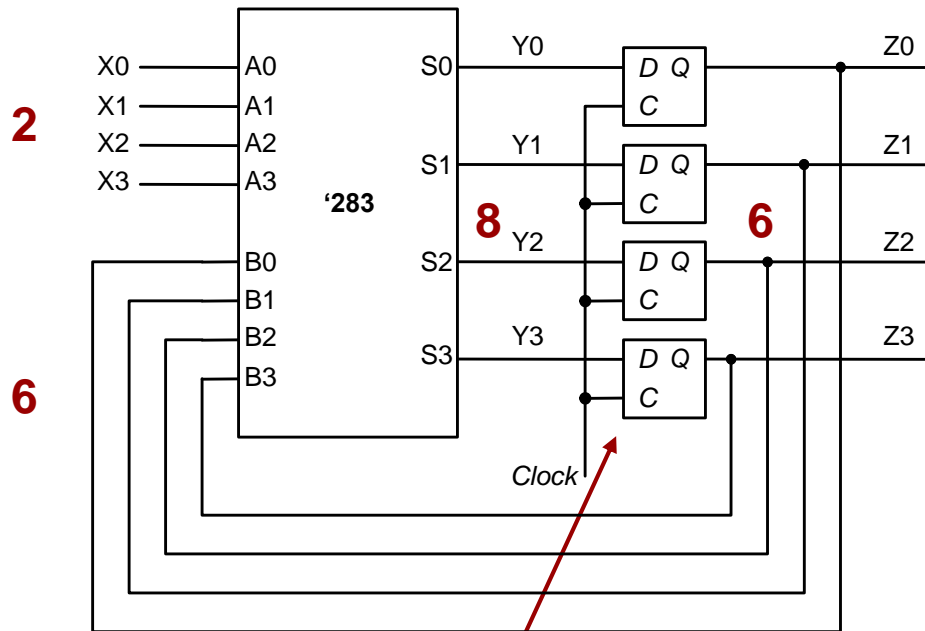
- This feedback loop continues until the clock goes low again



When C=0 => Q* = Q
When C=1 => Q* = D

Adding a Sequence of Numbers

 
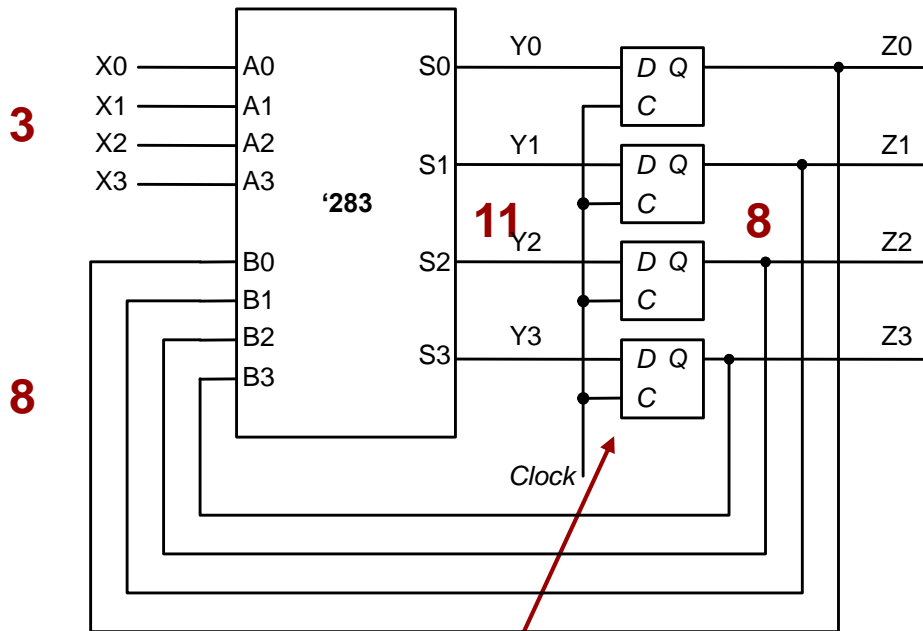
- When the clock goes low again, the outputs will hold at their current value 8 until the clock goes high



When C=0 => Q* = Q
When C=1 => Q* = D

Adding a Sequence of Numbers

 
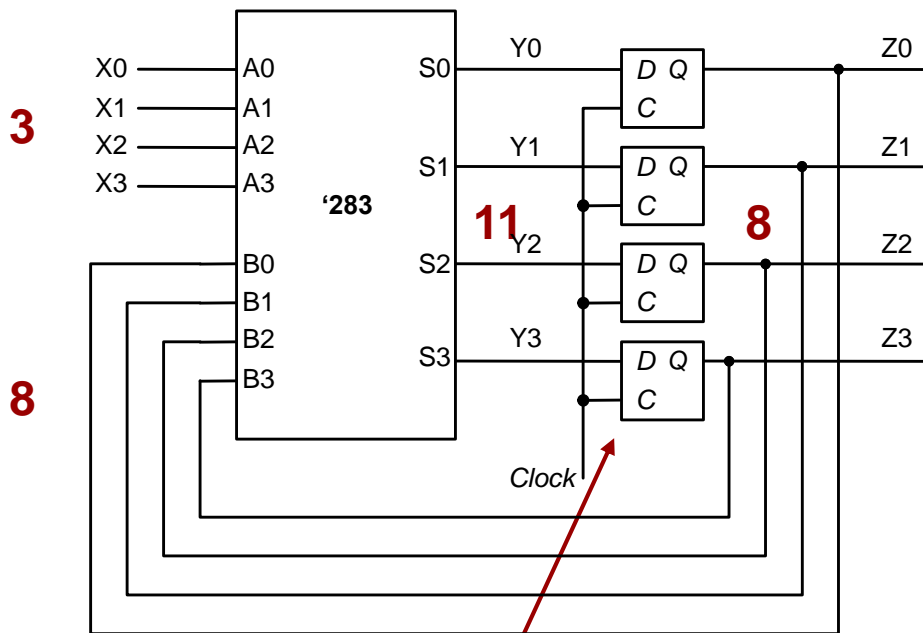
- When the clock goes high, the outputs will be free to change and we will get the feedback problem



When C=0 => Q* = Q
When C=1 => Q* = D

Adding a Sequence of Numbers

 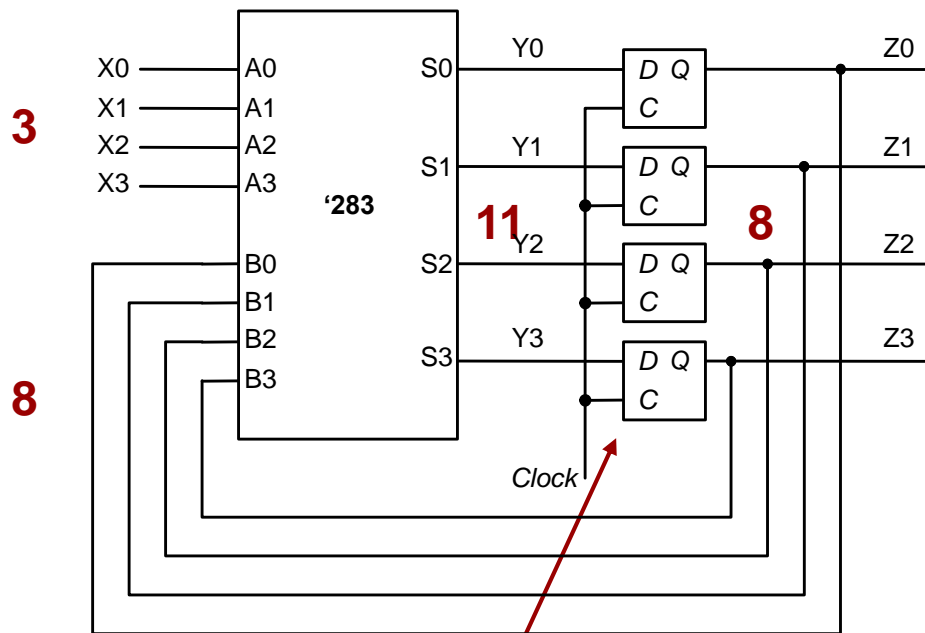- Latches clearly don't work
- The goal should be to get **one change of the outputs per clock period**




When C=0 => Q* = Q
When C=1 => Q* = D

FLIP-FLOPS

Flip-Flops vs. Latches



Bistables

- Asynchronous
- No clock input

 



Latches

  - Asynchronous
- Clock/Enable input
- Level Sensitive
 - Outputs can change anytime Clock = 1




Flip-Flops

  - Synchronous
- Clock Input
- Edge-Sensitive
 - Outputs change only on the positive (negative) edges



Flip-Flops

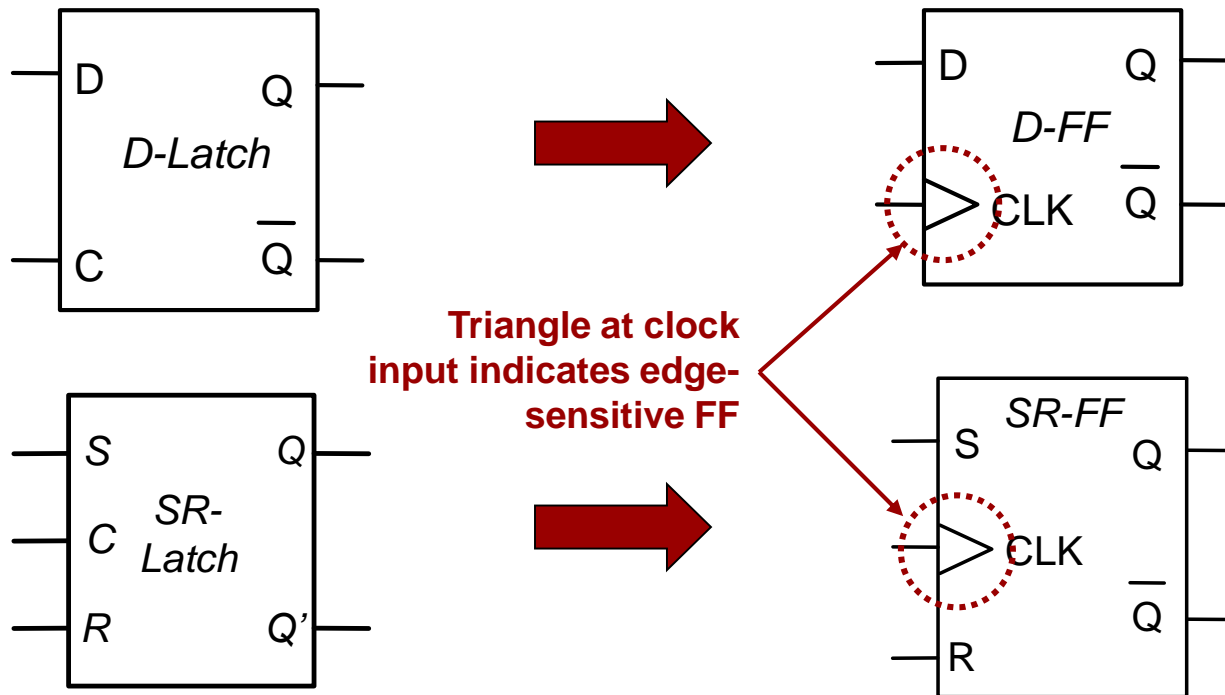
- Change D Latches to D Flip-Flops
- Change SR Latches to SR Flip-Flops



Flip-Flops


- To indicate negative-edge triggered use a bubble in front of the clock input

Positive-Edge Triggered
D-FF

 

No bubble indicates
positive-edge
triggered

Negative-Edge Triggered
D-FF

 


Bubble indicates
negative-edge
triggered

Positive-Edge Triggered D-FF

- Q looks at D only at the positive-edge


CLK	D	Q*	Q'*
0	x	Q	Q'
1	x	Q	Q'
↑	0	0	1
↑	1	1	0

 



Q only samples D at the positive edges and then holds that value until the next edge

Shift Register

 - A shift register is a device that acts as a 'queue' or 'FIFO' (First-in, First-Out).
- It can store n bits and each bit moves one step forward each clock cycle
 - One bit comes in the overall input per clock
 - One bit 'falls out' the output per clock




Shift Register

  

BUILDING A FLIP FLOP



Master-Slave D-FF

 - To build an **edge-triggered** D-FF we can use two D-Latches




These 2 latches form a flip-flop

Complete the Waveform

  


Master-Slave D-FF

 - To implement a positive edge-triggered D-FF change the clock inversion



Negative-Edge Triggered

 


Positive-Edge Triggered

ASYNCHRONOUS VS. SYNCHRONOUS PRESET & CLEAR

Synchronous vs. Asynchronous


- The new preset and clear inputs can be built to be **synchronous** or **asynchronous**
- These terms refer to when the initialization takes place
 - Asynchronous...initialize when signal is activated
 - Synchronous...initialize at clock edge

Synchronous

 

Synchronous /PRE or /CLR means the signal must be active at a clock edge before Q will initialize


Asynchronous

 

Asynchronous /PRE or /CLR means Q will initialize as soon as the /PRE or /CLR signal is activated

Preset / Clear Example

 - Assume an **asynchronous** Preset and Clear



Preset / Clear Example

- Assume an **synchronous** Preset and Clear

