

Spiral 2-7

Capacitance, Delay and Sizing

Learning Outcomes

- I understand the sources of capacitance in CMOS circuits
- I understand how delay scales with resistance, capacitance and voltage
- I can determine appropriate width of PMOS and NMOS transistors based on the configuration of the transistors and given current conduction parameters
- I understand how fan-in and fan-out affect the delay of a circuit
 - I understand how to use sizing to drive larger fan-out loads
- I understand the sources of static and dynamic power consumption and how they are affected by changes in various parameters


WHAT IS CAPACITANCE?




Capacitor Schematic Symbol

Capacitance

 - Capacitors are formed by separating two _____ substances with an _____
- Capacitors “_____” charge
- Capacitance measures how much charge is needed to achieve a certain voltage (electric potential)
 - $C = \frac{Q}{V}$
- Capacitance measured in Farads (F)



 
Connected to a source, charge will be stored on the conductive plates creating a positive voltage between the conductive plates



To change the voltage at the capacitor we must change the voltage (if we turn off the voltage source charge will drain off the capacitor)

Charging/Discharging Capacitors

- Charging a capacitor gets more “_____” as more charge is added
- Eventually, no more charge can be added and the capacitor acts like an open circuit

 

Capacitor I-V Relationship

- Fact $C = \frac{Q}{V}$, or $Q = CV$
- Also recall $i = \frac{Q}{t} = \frac{dQ}{dt}$
- Thus, substituting $i = \frac{dQ}{dt} = \underline{\hspace{2cm}}$
- Current is linearly related (slope = C) to the _____ in voltage (not the absolute voltage)
 - No voltage _____ (constant voltage) means no _____

Measures of Capacitance

- $C = \frac{A\varepsilon}{d}$



- ε is the permittivity of the insulator substance (intrinsic material property)
 - ε defined as 1 for a vacuum
 - Silicon dioxide (separates gate from silicon) = 3.9
 - Pure silicon = 11.68
- A is the _____ of the conductive materials
- d is the _____ (or thickness of the capacitor)

First-order RC circuit step response

RC CIRCUIT ANALYSIS

Resistance / Capacitance Analogy

Charge = Water

Resistance = Limit of water flow

Voltage Source = Water Pressure


Capacitance = Total Water Needed

Current Flows When voltage changes

Switching Time = Time to fill or drain the capacitor ("bucket") of charge
Thus, increase the voltage or decrease the resistance/capacitance.


Voltage, Resistance & Capacitance

- Let's analyze a simple circuit
 - Known as an RC circuit (resistor & capacitor in series)
 - Assume $t < 0$, _____
 - For $t > 0$, $V_s = \underline{\hspace{2cm}}$ (voltage source turns on)
 - Current through R must be same as current "through" C
 - $i = \frac{V_R}{R} = C \frac{dV_C}{dt} \Rightarrow i = \underline{\hspace{2cm}}$
 - Now let's solve for dV_C/dt
 - $\frac{dV_C}{dt} = \underline{\hspace{2cm}}$
 - We can solve this differential equation
 - $V_C(t) = V_{dd} + [V_C(0) - V_{dd}]e^{-\frac{t}{RC}}$
 - For $V_C(0)=0$ we have $V_C(t) = \underline{\hspace{2cm}}$

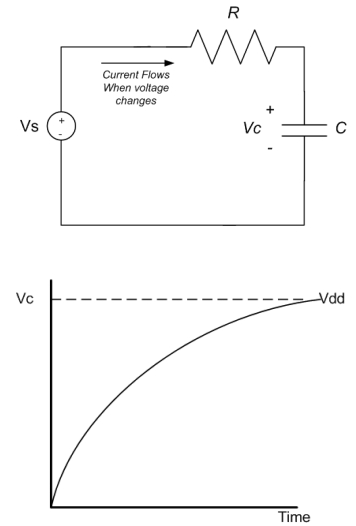

Voltage, Resistance & Capacitance


- Let's analyze a simple circuit
 - Known as an RC circuit (resistor & capacitor in series)
 - Assume $t < 0$, $V_s = V_{dd}$ then $V_C = V_{dd}$
 - For $t > 0$, $V_s = 0$ (voltage source = GND)
 - Current through R must be same as current "through" C
 - $\frac{V_C}{R} = -C \frac{dV_C}{dt} \Rightarrow i = \frac{V_{dd} - V_C}{R} = C \frac{dV_C}{dt}$
 - Now let's solve for dV_C/dt
 - $\frac{dV_C}{dt} = -\frac{V_C}{RC} \Rightarrow \frac{dV_C}{dt} + \frac{V_C}{RC} = 0$
 - We can solve this differential equation
 - $V_C(t) = V_C(0)e^{-\frac{t}{RC}}$
 - For $V_C(0)=V_{dd}$ we have $V_C(t) = \underline{\hspace{2cm}}$

 

Time Constant

- Notice the charging (discharging) time is determined by product of $R \cdot C$
- We refer to this as the _____, τ
 - $\tau = RC$
- As the product of RC increases we get _____ switching times
- We can show that the time it takes to charge/discharge a capacitor to a fraction of V_{dd} is given in the table below


Voltage Range	Time
0 to 50% ($t_p = \text{prop. delay}$)	_____ *RC
0 to 63% (τ)	RC
10% to 90% ($t_r = \text{rise time/delay}$)	_____ *RC

 

DELAY

MOSFET Parasitic Capacitance


- In order to examine the delay of a MOSFET, we have to determine nature and amount of _____ capacitance associated with MOS transistor
 - Parasitic: Unintentional, _____ capacitors
 - It's not that we want caps, we're _____ due to the structure of the MOSFET.
- The oxide layer separating gate and substrate is a more obvious capacitor
- However the _____ around the source and drain also form capacitors

 

14


Transistor R and C values

 - Observation: Output of one transistor usually drives input of another
 - Sources of resistance
 - _____
 - _____ connecting _____
 - Sources of capacitance
 - _____ of the next transistor
 - Other small capacitances



Resistor and Capacitor Delay


- Outputs connect to other inputs
- To change the output voltage (really the input of the next gate), we must conduct enough charge to raise or lower its present voltage
- Resistance limits the amount of charge that can be transferred per unit time
- Capacitance determines how much charge must be present to attain a certain voltage
- Time it takes to attain a certain voltage is proportional to $R \cdot C$

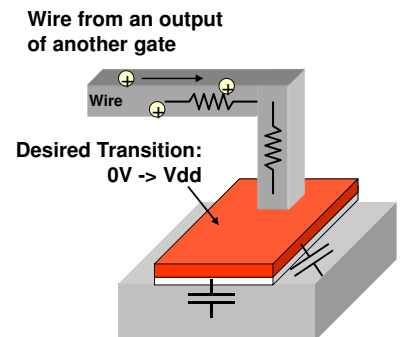

Switching Time ~
Resistance * Capacitance


Where RC Circuits Occur

 - Consider a CMOS gate driving others (_____)
 - The output connects to the gate inputs of the loads (fan-out) and thus can be modeled as a capacitive load (C_L)





Where RC Circuits Occur

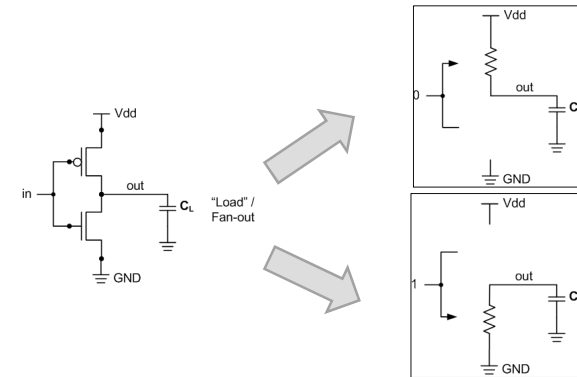- Depending on the inverter input the PMOS or NMOS will be in _____ mode and can be modeled as resistors
 - Thus we have an RC circuit either charging or discharging the output (C_L)



Defining Delays


- We model
 - The next gate(s) and other parasitic capacitances as a lumped capacitance
 - The PDN or PUN transistors as resistors (since they are operating in linear mode when the input is near VDD or GND)
- t_{PLH} and t_{PHL} refer to the _____ delay of a circuit when the output changes from low to high (_____) [t_{PLH}] or high to low (_____) [t_{PHL}]
 - $t_{PLH} \approx 0.69R_P C_L = \frac{C_L V_{DD}}{k_p [V_{DD} - V_{Tp}]^2}$
 - $t_{PHL} \approx 0.69R_N C_L = \frac{C_L V_{DD}}{k_n [V_{DD} - V_{Tn}]^2}$
- We say the delay of the gate is then:
 - $t_{PD} \approx (t_{PLH} + t_{PHL}) / 2$
- Important: What reduces delay?
 - _____

  

CMOS SIZING


Sizing – PMOS is Slower than NMOS!

- Recall the equations for current through a transistor in linear mode
 - $|I_{ds}| = \frac{1}{2} K' \left(\frac{W}{L}\right) [2(|v_{gs}| - |V_T|)|V_{ds}| - |V_{ds}|^2]$
 - Ohm's law says $I = V/R$ so in the equation above $\frac{1}{R} \propto K' \frac{W}{L}$
- Problem _____ ($K_N \approx$ _____ K_P)
 - PMOS are _____ at conducting than NMOS
 - This will leave to imbalances in _____ (i.e. _____)
 - To balance the delay when pulling up vs. pulling down we can play with _____
- Solution: Make _____ by about a factor of 2 or 2.5

 

Sizing – Inverter

 - Assume $K_p \approx \frac{K_n}{2}$
- Find the ratio and W_p and W_n that balances the delay of output during falling and rising transitions



Sizing – Simple CMOS Gates


- Goal: Make any gate have the same worst case resistance as an inverter
- The ratio of the $\{W/L\}_{PUN} / \{W/L\}_{PDN}$ should be about two (or higher) to make up for slow PMOS

Important Notes:

For parallel transistors consider only the case if 1 is on (Remember if $R||R$ then $R_{eff}=R/2$ which is a better case so we assume only one is on)

Series transistors in series add lengths/resistance

 
All paths in a PxN should have same resistance



Sizing – Complex CMOS Gates

PUN: make each path $W/L = 2$

PDN: make each path $W/L = 1$

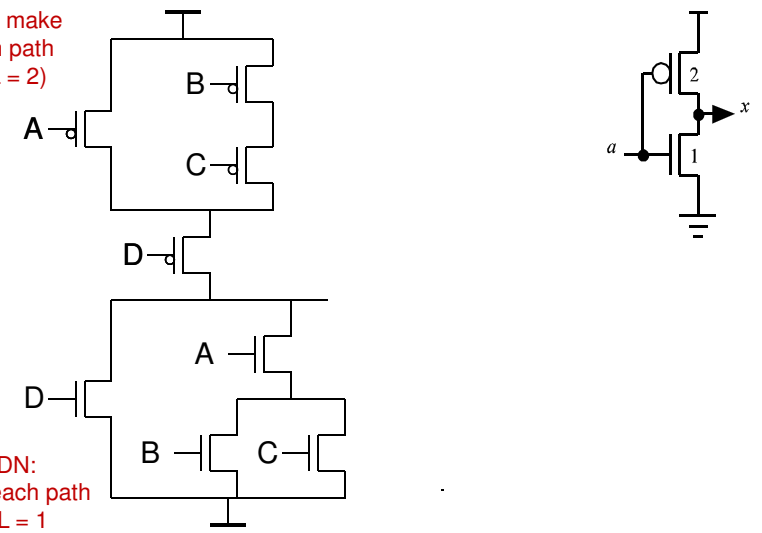


Compound Gate Example

$$Y = \overline{D \cdot (A + B + C)}$$

PUN: make each path W/L = 2)

PDN: make each path W/L = 1

 


Compound Gate Example

$$Y = \overline{AB + CD}$$

PUN: make each path W/L = 2)



PDN: make each path W/L = 1

 

FANIN & FANOUT


Fanout

  - Fanout refers the number of gates an output connects to
- As the fanout increases C_L _____ and _____ means the delay _____



Increasing Drive Strength

 - So far we've always modeled an idea inverter for our transistor sizes
 - Ideal inverter => NMOS: 1/1 and PMOS 2/1 or 3/1
- We can counteract the increase in CL by _____ through increasing transistor _____
 - NMOS and PMOS widths increase by:





Fan-in

- Fan-in refers to the number of inputs to a gate
- Each input adds intrinsic, parasitic _____
 - $t_{phl} = 0.69 \cdot R_n(\text{_____})$
 - To discharge C2 requires going 2L (i.e. $2R_N$)
 - To discharge C3 requires 3L (i.e. $3R_N$)
- This means delay grows quadratically with fan-in but linearly with fanout
 - $t_{pd} \sim \text{_____}$
- Important: Rarely want FI > _____

Fanin = 2




Fanin = 5

  

Mitigating Delay

 
- May increase widths _____
 - Bottom transistor has _____ width
- Order transistors to allow the **latest** arriving input control the transistor _____ to the output
 - If Z is the latest arriving input we want to put it _____ to the output



INTERCONNECT DELAY

Ideal vs. Realistic Wire

 
- Ideal wire should have $R=0$ and little capacitance
- In real life it has some small R and C
- $R = \rho L/A$
 - ρ = resistivity of material (some intrinsic property)
 - L = length of wire
 - A = cross-section area of the material
- As technology scales (we build smaller devices) _____ and _____ means resistance goes _____



Modeling Interconnect Delay


- Interconnect delay is starting to (already is) _____ switching delay
- Important design considerations
 - Long wire traces slow a signal down, thus global signals on a chip require special attention

A real wire can be modeled as...

 

Dealing With Interconnect

 - Clock, reset, and other signals must be routed carefully and a whole tree of buffers inserted to decrease the delay



DYNAMIC POWER

Power

- Power consumption decomposed into:
 - Static: Power constantly being dissipated (grows with # of transistors)
 - Dynamic: Power consumed for switching a bit (1 to 0)
- $P_{DYN} = I_{DYN} * V_{DD} \approx \frac{1}{2} C_{TOT} V_{DD}^2 f$
 - Recall, $I = C dV/dt$
 - V_{DD} is the logic '1' voltage, f = clock frequency
- Dynamic power favors parallel processing vs. higher clock rates
 - V_{DD} value is tied to f , so a reduction/increase in f leads to similar change in V_{DD}
 - Implies power is proportional to f^3 (a cubic savings in power if we can reduce f)
 - Take a core and replicate it 4x => 4x performance and 4x power
 - Take a core and increase clock rate 4x => 4x performance and 64x power
- Static power
 - Leakage occurs no matter what the frequency is

Temperature

- Temperature is related to power consumption
 - Locations on the chip that burn more power will usually run hotter
 - Locations where bits toggle (register file, etc.) often will become quite hot especially if toggling continues for a long period of time
 - Too much heat can destroy a chip
 - Can use sensors to dynamically sense temperature
- Techniques for controlling temperature
 - External measures: Remove and spread the heat
 - Heat sinks, fans, even liquid cooled machines
 - Architectural measures
 - Throttle performance (run at slower frequencies / lower voltages)
 - Global clock gating (pause..turn off the clock)
 - None...results can be catastrophic
- Fun video to be played now!