

# EE 457 Unit 1

## Overview of Digital System Design

# Credits

- These slides were derived from Gandhi Puvvada's EE 457 Class Notes


Clocking Strategies

# REGISTERS & DATA ENABLES

# Registers

- A Register is a group of D-FF's tied to a common clock and clear (reset) input
  - Clear can be asynchronous or synchronous
- Used to store multiple bit values on each clock cycle


CLK	RST	$D_i$	$Q_i^*$
1,0	X	X	$Q_i$
↑↑	1	X	0
↑↑	0	0	0
↑↑	0	1	1

 

4-bit Register
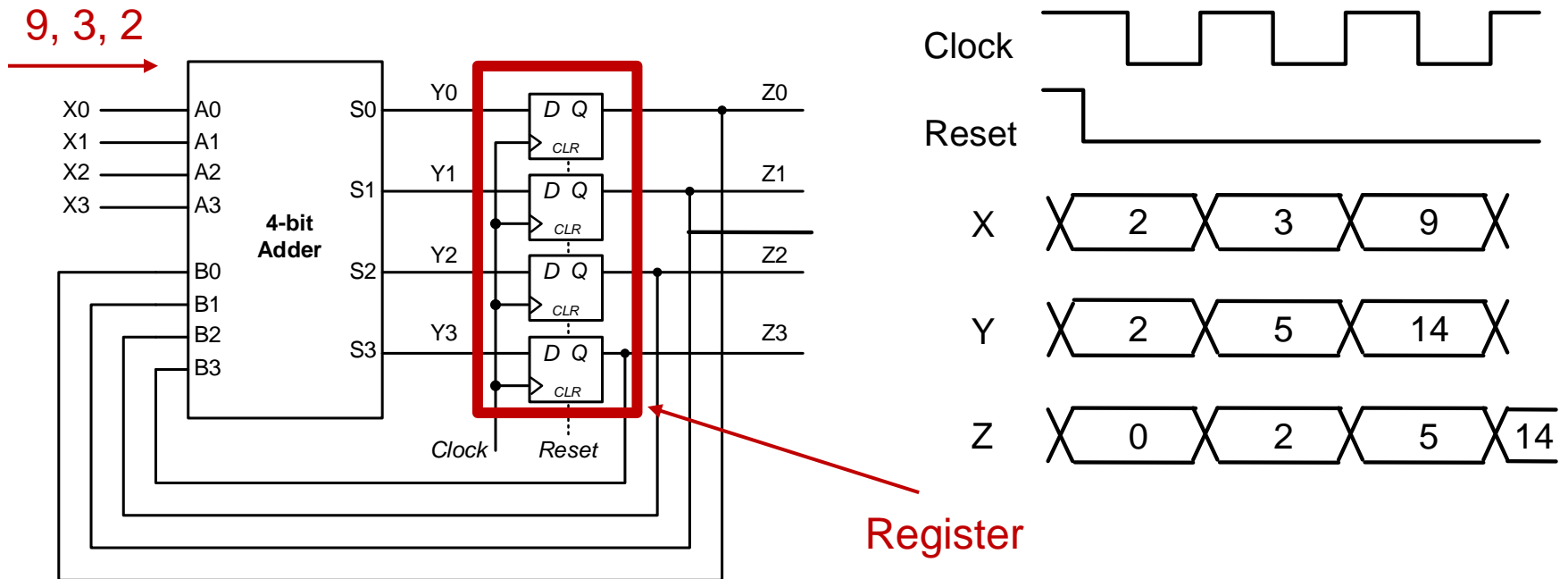
# Example: Accumulator


- Sum a time-based sequence of numbers
- A register usually stores a single logic value (i.e. a number)




# Synchronous vs. Asynchronous

- The set/preset and clear inputs can be built to be **synchronous** or **asynchronous**
- These terms refer to when the initialization takes place
  - Asynchronous Reset (AR): Initialization of Q takes effect immediately regardless of the CLK
  - Synchronous Reset (SR): Initialization of Q takes effect only at an edge (clear must be active at the edge)

## Synchronous

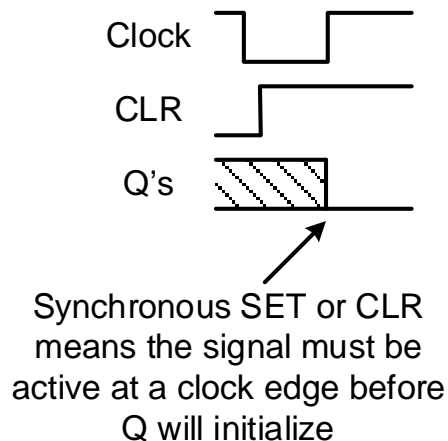


## Asynchronous

 
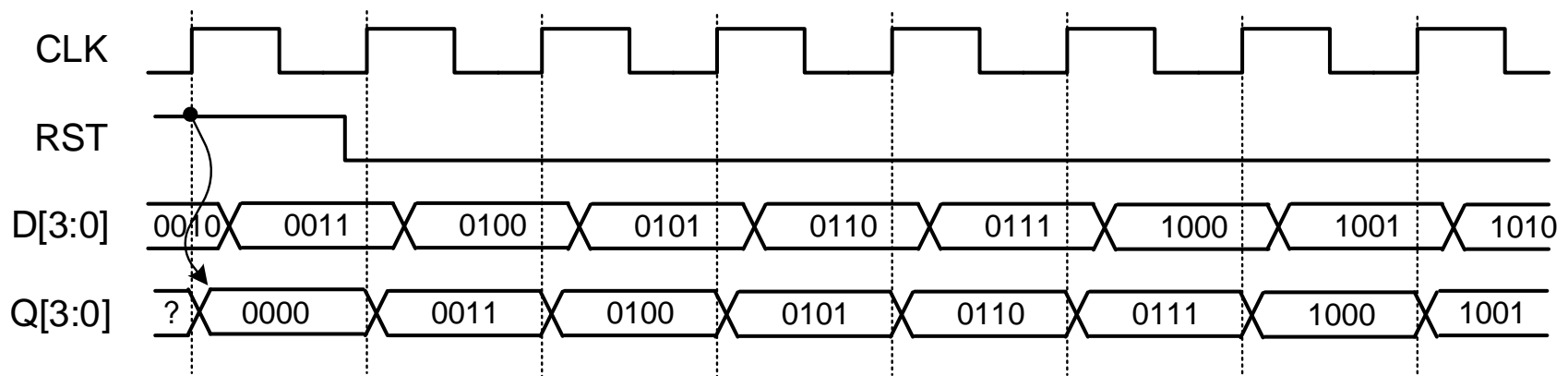
# Registers


- Whatever the D value is at the clock edge is sampled and passed to the Q output until the next clock edge




4-bit Register – On clock edge, D is passed to Q
 
# Selective Loading/Registering of Data

- What if we only want a register to capture data on *selective* clocks (and not on *EVERY* clock)
  - Clocks are indicated with a “LOAD” signal



 Want to load the register on the indicated clock cycles and have it retain its value in the other cycles





4-bit Register



 
 
# Clocking Option 1

- Use Load as the clock signal
- Doesn't Work. Clocks too early



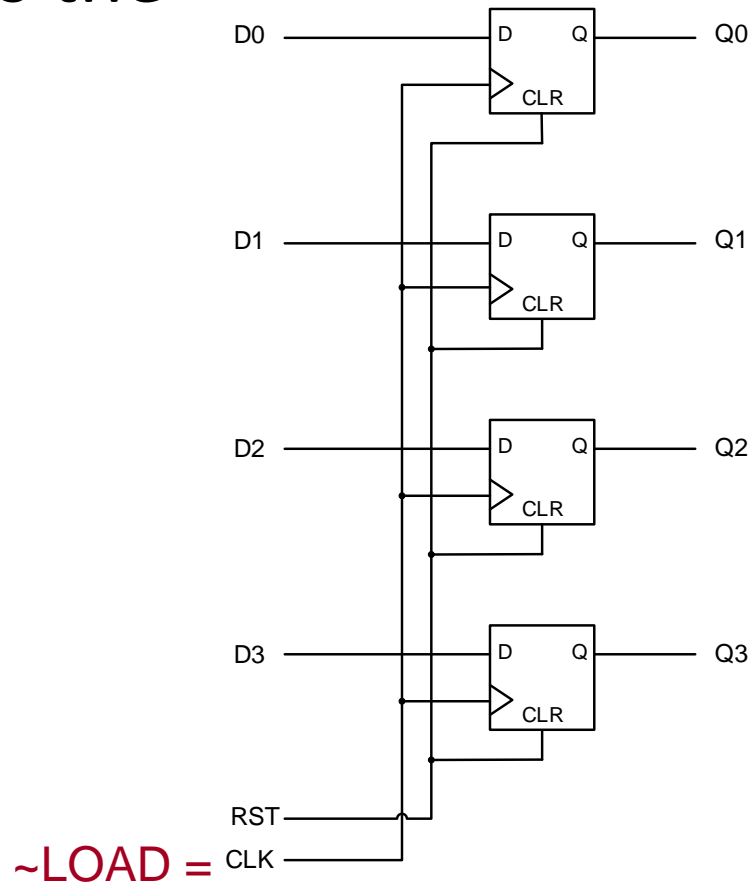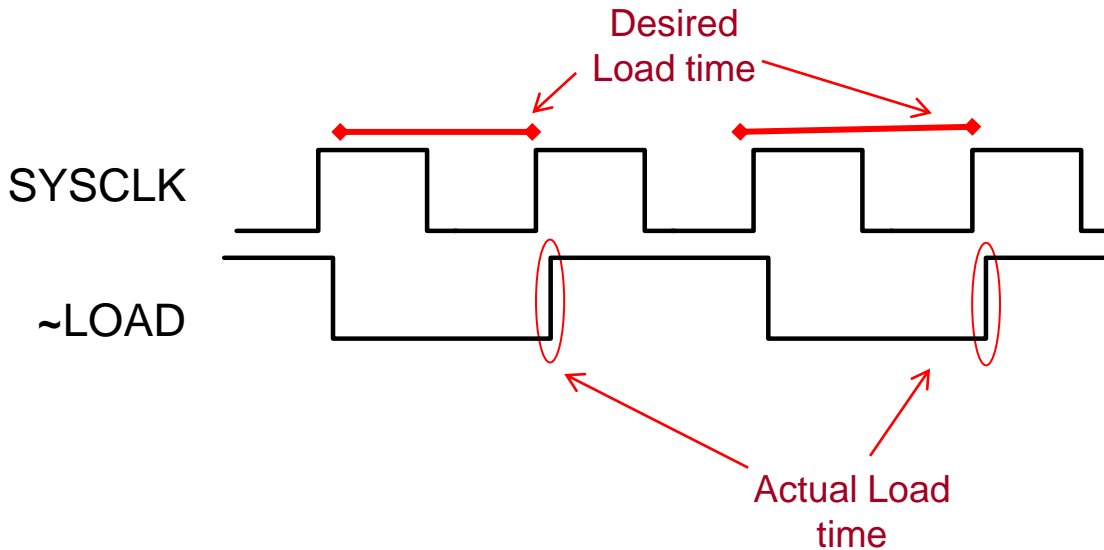
# Clocking Option 2

- Use  $\sim$ Load (inverted Load) as the clock signal
- Doesn't Work...Glitches or successive loading cycles



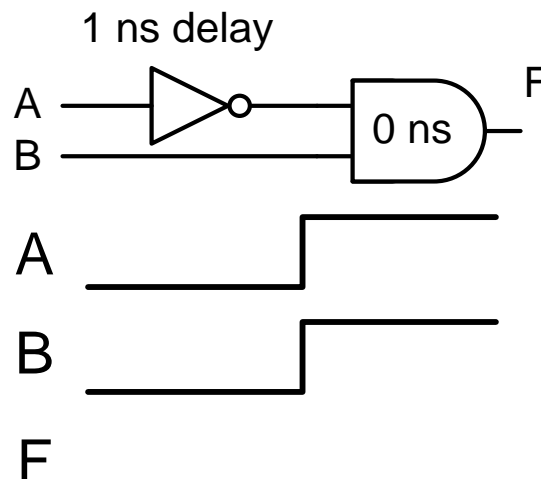
# Glitches

- Temporary (transient) incorrect / toggling output values due to differing delay paths of the inputs
  - Eventually output settles to correct value
  - Unless a circuit is specially designed, glitches are possible on all circuits




 
# Successive Loading Clocks

- If load is held high on two successive clock cycles you may only see one edge



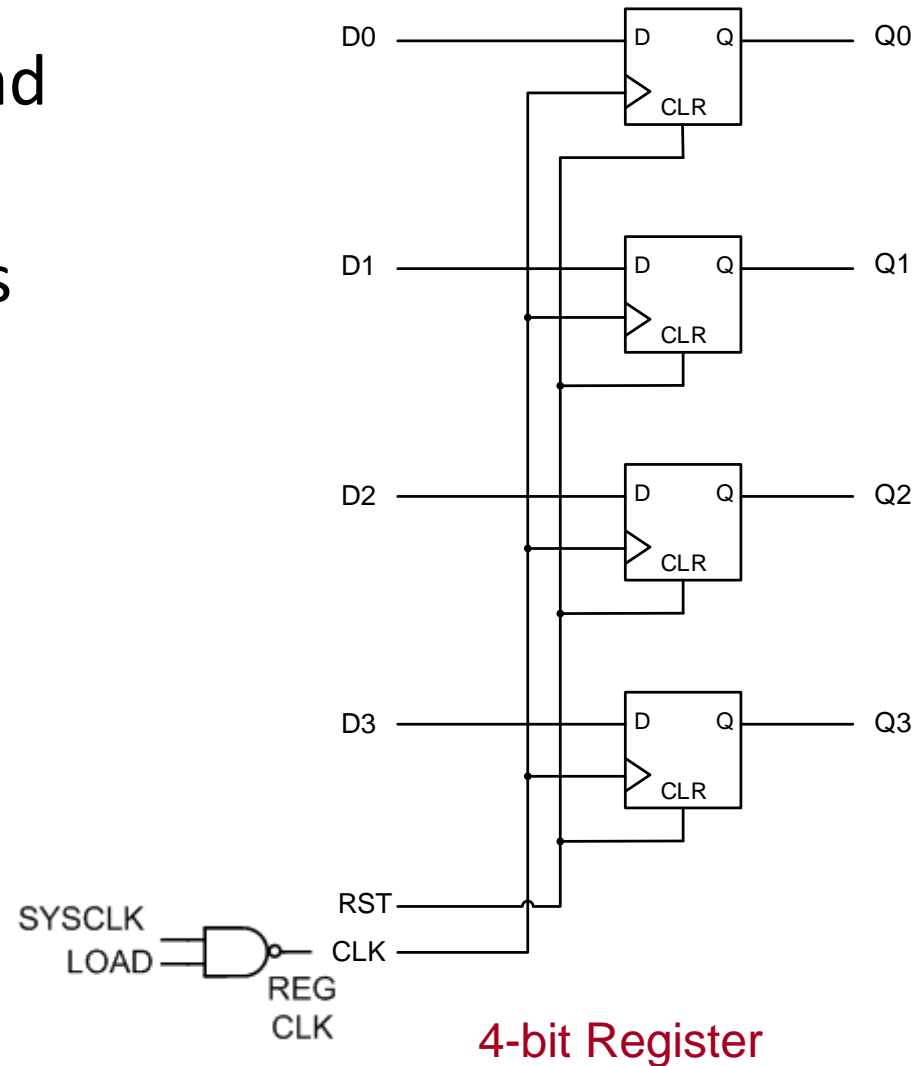 
# Option 3

- Gate the clock with the load signal
- Also susceptible to glitches


 
# Option 4: Feedback mux

- Registers (D-FF's) will sample the D bit every clock edge and pass it to Q
- Sometimes we may want to hold the value of Q and ignore D even at a clock edge
- We can add an enable input and some logic in front of the D-FF to accomplish this




**FF with Data Enable**  
 (Always clocks, but selectively chooses old value, Q, or new value D)


CLK	AR	EN	D <sub>i</sub>	Q <sub>i</sub> *
X	1	X	X	0
0,1	0	X	X	Q <sub>i</sub>
↑↑	0	0	X	Q <sub>i</sub>
↑↑	0	1	0	0
↑↑	0	1	1	1
 
# Registers w/ Enables

- When  $EN=0$ , Q value is passed back to the input and thus Q will maintain its value at the next clock edge
- When  $EN=1$ , D value is passed to the input and thus Q will change at the edge based on D



 
When  $EN=0$ , Q is recycled back to the input



When  $EN=1$ , D input is passed to FF input
 
# Registers w/ Enables


- The D value is sampled at the clock edge only if the enable is active
- Otherwise the current Q value is maintained






# Register With or Without An Enable

Free-Running Register

 

Register with Load (Data) Enable

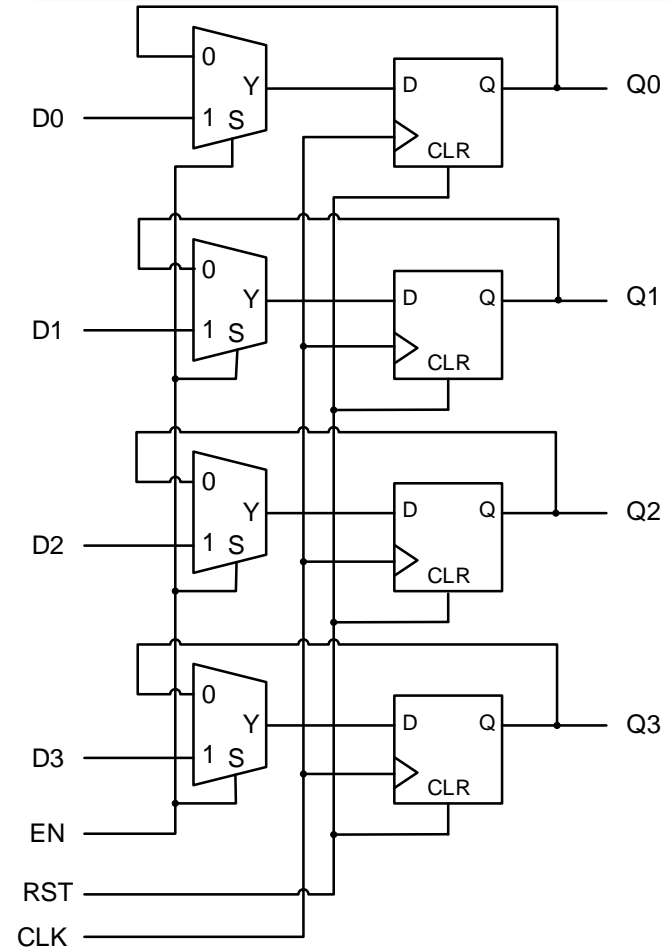


When to use one vs. the other?

- Free-running register: Do you want to update the stored value EVERY edge
- Register w/ Enable: In all other cases...

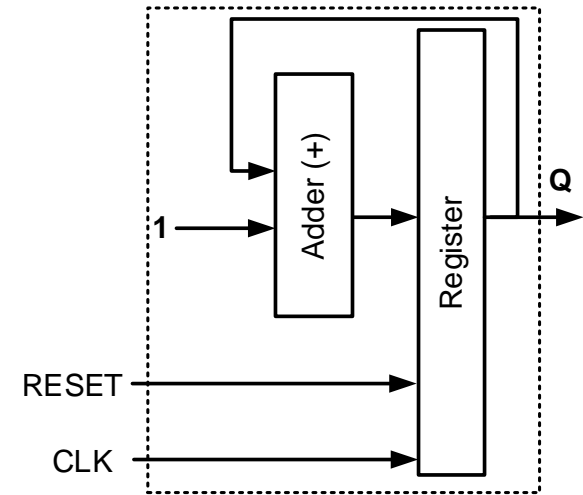
# Counters

- Increment (Add 1 to Q) at each clock edge
  - Up Counter:  $Q^* = Q + 1$
- Standard counter components include other features
  - Enables: Will not count at edge if  $EN=0$
  - Resets: Reset count to 0
  - Parallel Load Inputs: Can initialize count to a value P (i.e.  $Q^* = P$  rather than  $Q+1$ )


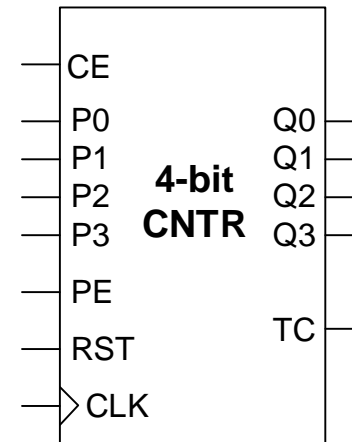
# Sample 4-bit Counter


- 4-bit Up Counter
  - RST: synchronous reset input
  - PE and  $P_i$  inputs: loads Q with P when PE is active
  - CE: Count Enable
    - Must be active for the counter to count up
  - TC (Terminal Count) output
    - Active when  $Q=1111$  AND counter is enabled
    - $TC = EN \cdot Q_3 \cdot Q_2 \cdot Q_1 \cdot Q_0$
    - Indicates that on the next edge it will roll over to 0000
    - Used to create 8-, 12-, 16-bit, etc. counters from these 4-bit building blocks




CLK	RST	PE	CE	$Q^*$
0,1	X	X	X	Q
↑↑	1	X	X	0
↑↑	0	1	X	P[3:0]
↑↑	0	0	1	Q+1
↑↑	0	0	0	Q
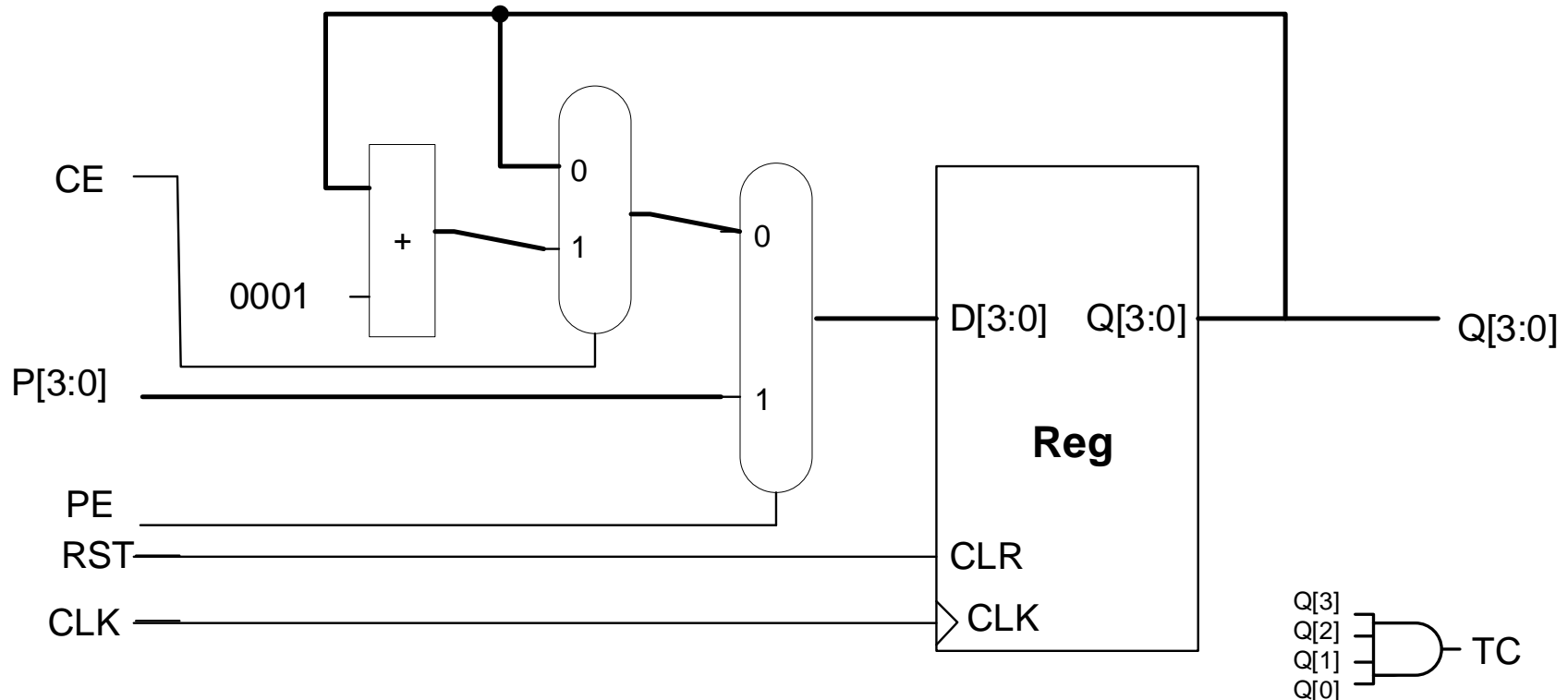
# Counter Design

- Sketch the design of the 4-bit counter presented on the previous slides



# Counters

 

SR=active at clock edge, thus  $Q=0$

$Q^*=Q+1$

Enable = off, thus Q holds

$Q^*=Q+1$

$Q^*=Q+1$

PE = active, thus  $Q=P$

$Q^*=Q+1$

$Q^*=Q+1$

Mealy TC output:  
 $EN \cdot Q_3 \cdot Q_2 \cdot Q_1 \cdot Q_0$

# Reference Verilog

- Verilog description of a register with enable and counter with load and count enable

```
module reg16e(  
    input clk,  
    input reset,  
    input en,  
    input [15:0] d,  
    output reg [15:0] q  
);  
  
always @(posedge clk)  
begin  
    if(reset)  
        q <= 16'd0;  
    else if(en)  
        q <= d;  
end  
endmodule
```

**16-bit Register w/ Enable**

```
module cntr16ce(  
    input clk,  
    input reset,  
    input load,  
    input ce,  
    input [15:0] d,  
    output reg [15:0] q  
);  
  
always @(posedge clk)  
begin  
    if(reset == 1)  
        q <= 16'd0;  
    else if(load == 1)  
        q <= d;  
    else if(ce == 1)  
        q <= q+1;  
end  
endmodule
```

**16-bit Counter w/ Load  
and Count Enable**

# Data Register Summary

- Understand the operation of a free-running register, register w/ data/load enable, and a counter with count enables, etc.


Datapath and Control Unit Decomposition

# **SYNCHRONOUS SYSTEM DESIGN TECHNIQUES**




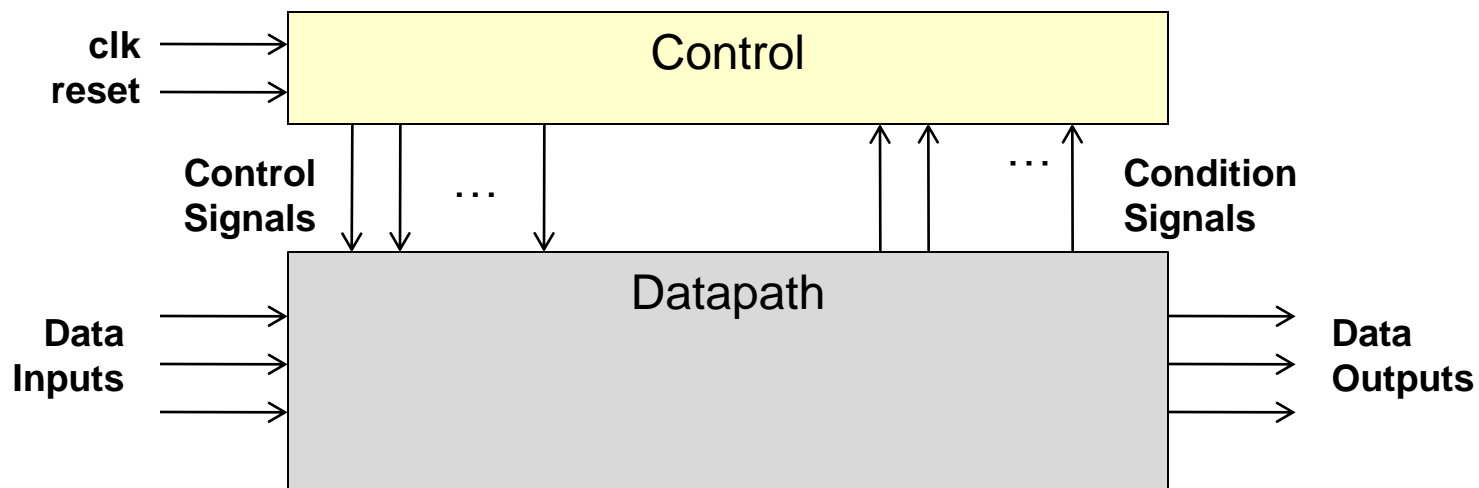
# Digital System Design

- Control (**CU**) and Datapath Unit (**DPU**) paradigm
  - Separate logic into datapath elements that operate on data and control elements that generate control signals for datapath elements
  - Datapath: Adders, muxes, comparators, counters, registers (w/ enables), memories, FIFO's
  - Control Unit: State machines/sequencers



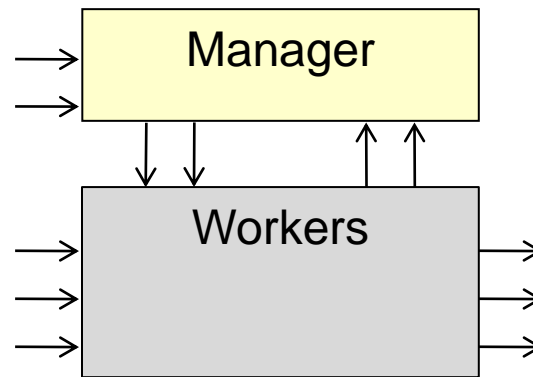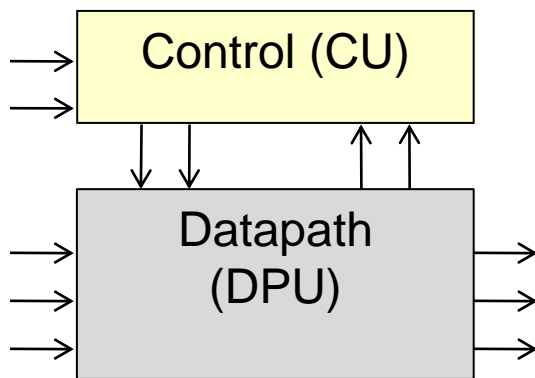
# Datapath + Control

- The control unit acts as scheduler and manager while the datapath “does” the work
  - Similar division of labor in many other areas
  - Control signals include: mux selects, load enables, count enables, output enables, etc.



Construction Company

 


# Datapath Design Example

- Design a datapath to support the following RTL (Register Transfer Level) operations
  - Identify the control signals & other datapath components

**Desired Operations:**




$C \leftarrow A+B,$	if $F,G=0,0$
$C \leftarrow A-B,$	if $F,G=0,1$
$R \leftarrow P+Q,$	if $F,G=1,0$
$R \leftarrow P-Q,$	if $F,G=1,1$

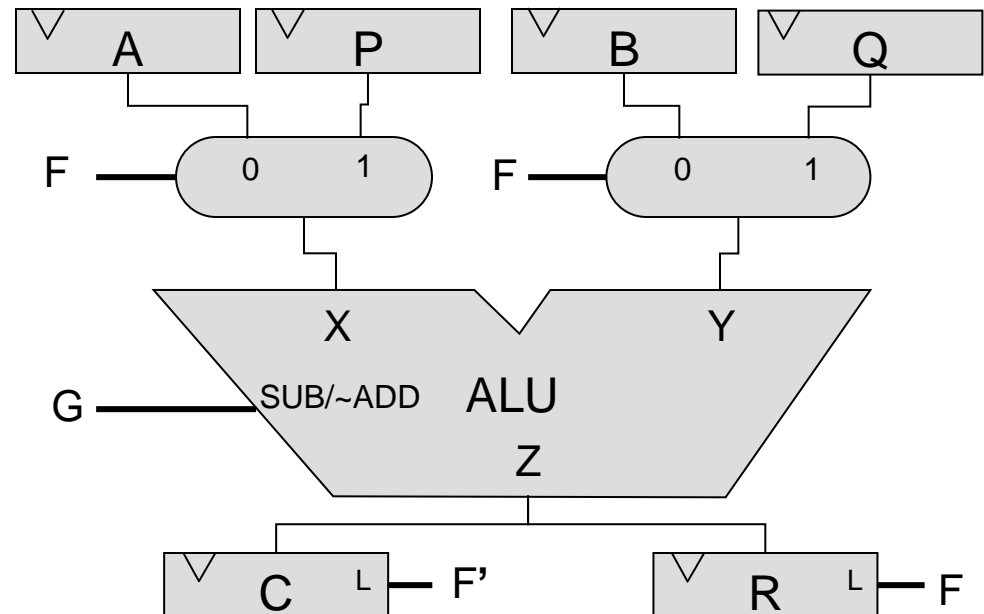

One-hot State Machine Design

# STATE MACHINE (CONTROL UNIT) DESIGN

# Digital System Representation

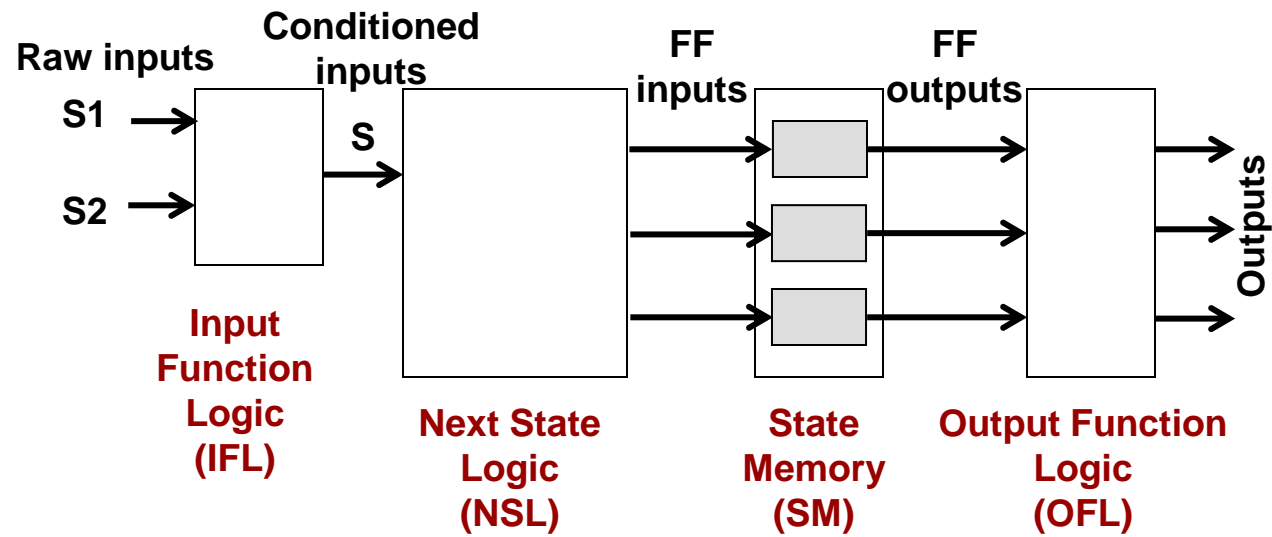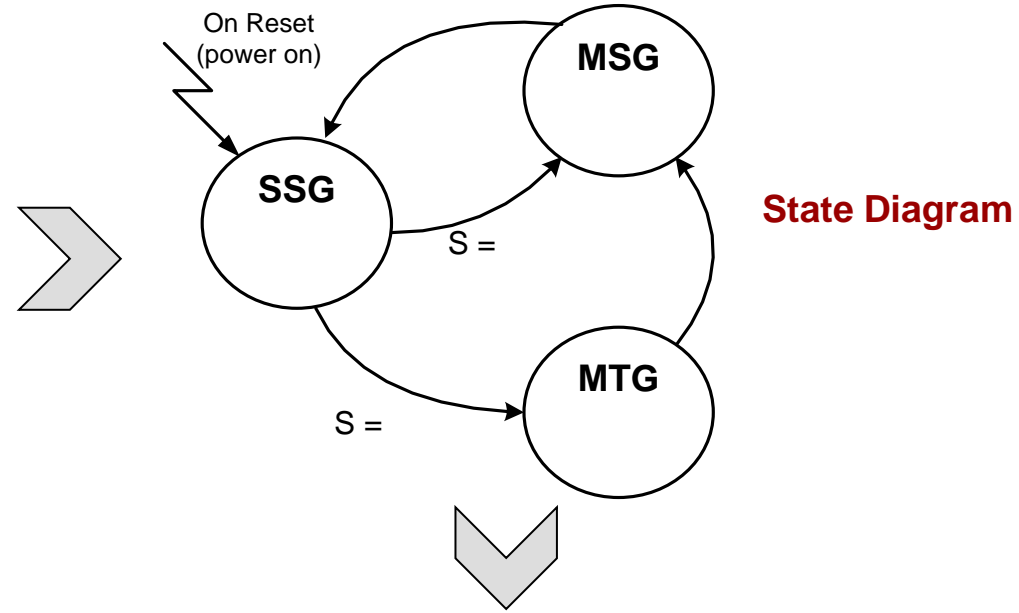 


# State Machine Review

## State Diagrams

 1. States
2. Transition Conditions
3. Outputs


State Machines require sequential logic to remember the current state (w/ just combo logic we could only look at the current value of X, but now we can take 4 separate actions when X=0)



State Diagram for "101" Sequence Detector



## State Machine

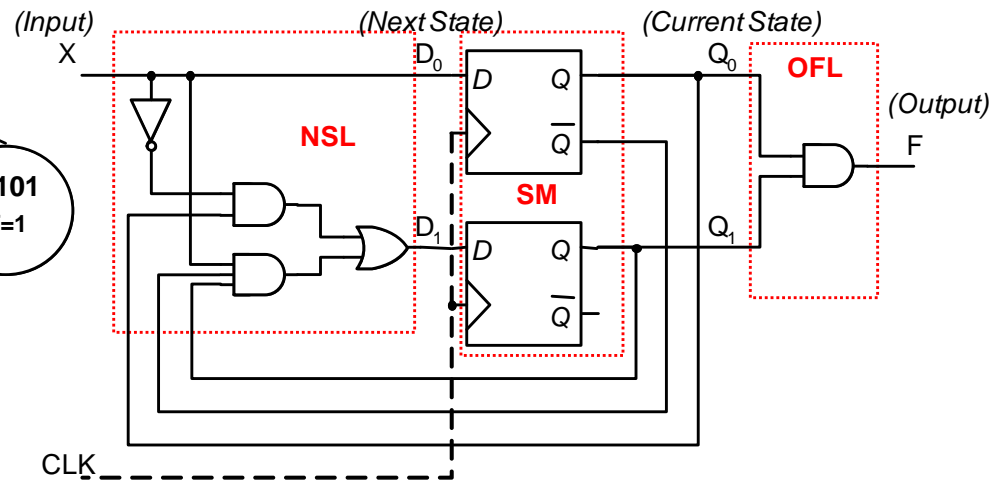1. State Memory => FF's
  - n-FF's =>  $2^n$  states
2. Next State Logic (NSL) + Input Function Logic (IFL)
  - combinational logic for FF inputs
3. Output Function Logic (OFL)
  - MOORE:  $f(\text{state})$
  - MEALY:  $f(\text{state} + \text{inputs})$


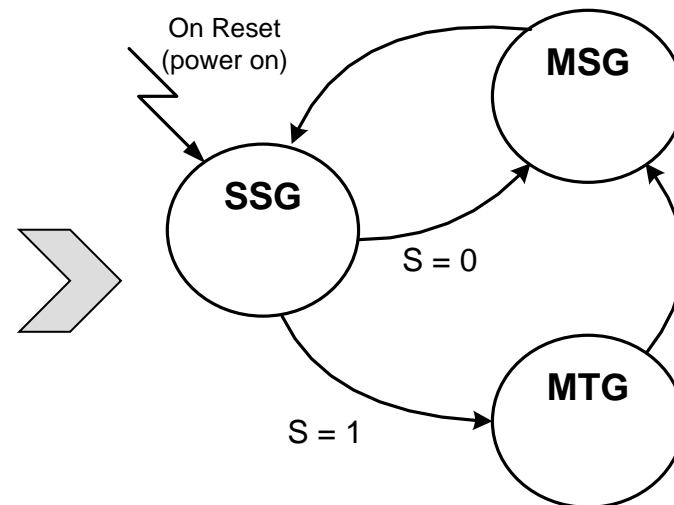 
# State Assignment


- Design of the traffic light controller with main turn arrow
- Represent states with some binary code, but what kind?
  - Encoded: 3 States => 2 bit code: 00=SSG, 01=MSG, 10=MTG
  - One-hot: Separate FF per state: 100=SSG, 010=MSG, 001=MTG



**State Diagram**

 
# NSL Implementation in 1-Hot Method

- In one-hot assignment, NSL is designed by simple observation
- For each state, examine each incoming transition
  - Each incoming arrow will be one case in our logic
  - We can just OR each condition together
- Describe each transition as a combination of what state it originates from & any associated conditions
- Ex. Two arrows converge on MS:
  - “ $Q_{MS}$  should be ‘1’ on the next clock when...”
  - Current state is MT **...OR...**
  - Current stat is SS **AND**  $S=0$



	$Q_{SS}$	$Q_{MT}$	$Q_{MS}$
SS	1	0	0
MT	0	1	0
MS	0	0	1


**One-hot State Assignment**

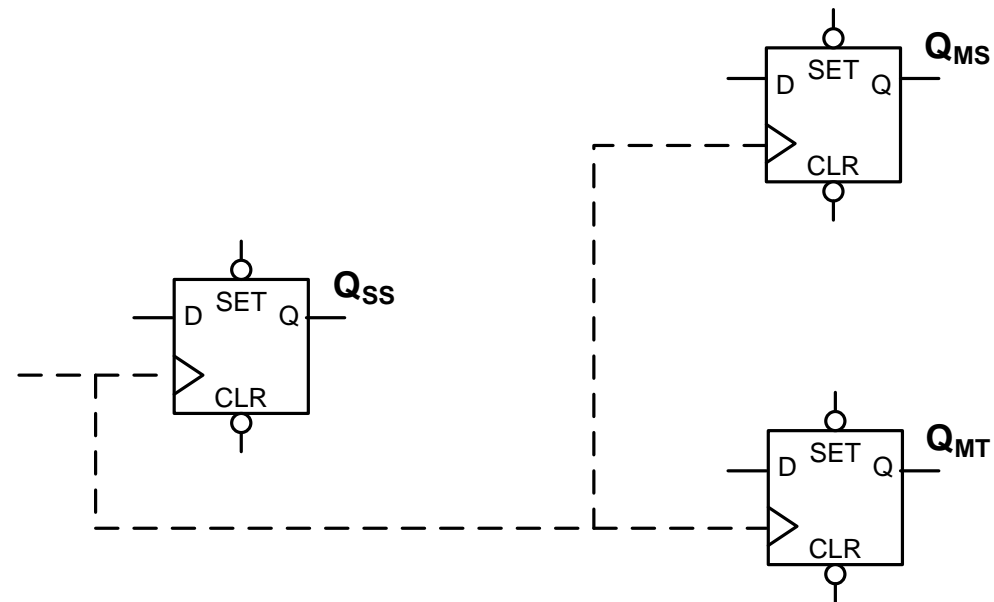



 
# NSL Implementation in 1-Hot Method

- Two arrows converge on MS:
  - “ $Q_{MS}$  should be ‘1’ on the next clock when...”
    - Current state is MT ...**OR**...
    - Current stat is SS **AND**  $S=0$
- $Q^*_{MS} = D_{MS} = Q_{MT} + Q_{SS} \bullet S'$
- $Q^*_{MT} = D_{MT} =$
- $Q^*_{SS} = D_{SS} =$
- What about initial state? Preset the appropriate flop.**



	$Q_{SS}$	$Q_{MT}$	$Q_{MS}$
SS	1	0	0
MT	0	1	0
MS	0	0	1



**One-hot State Assignment**

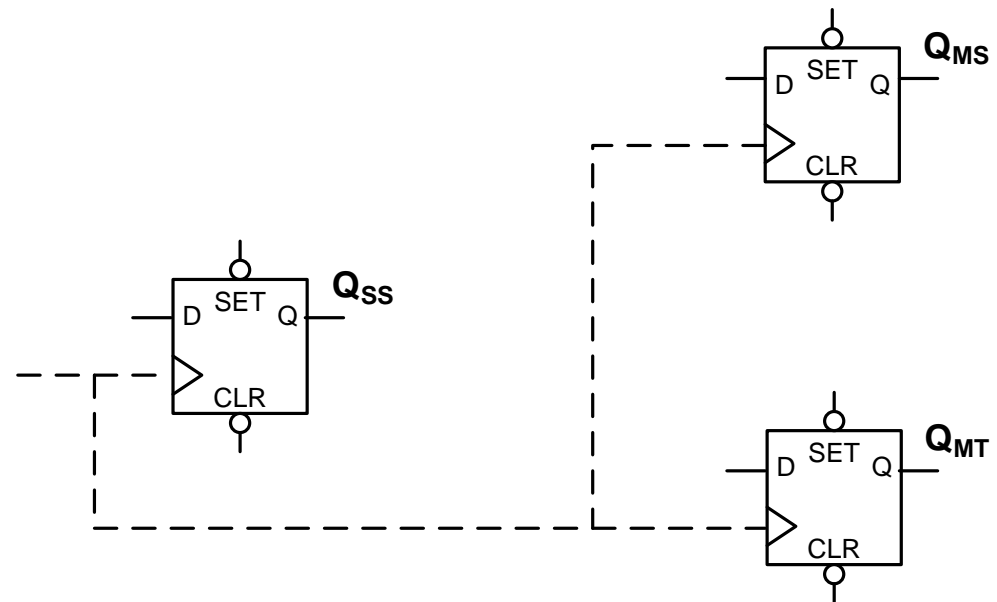

# Illustrative Example


- Consider the following state diagram

s

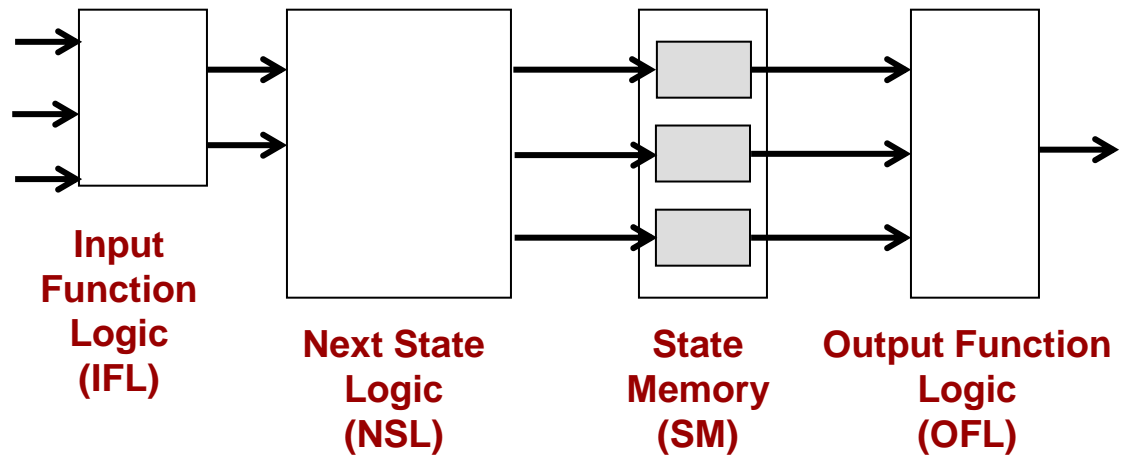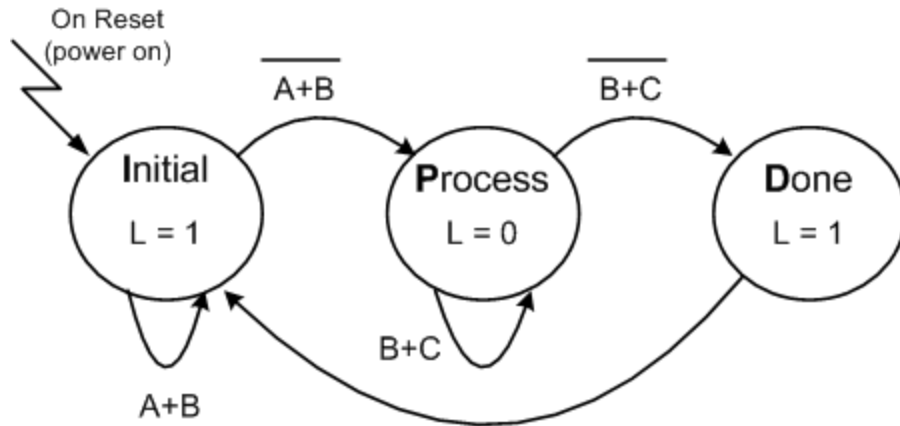
 
# State Assignment & NSL

- Let us choose a one-hot state assignment (one FF per state)



- Next State Equations:

$$- D_I = Q_I^* =$$


$$- D_P = Q_P^* =$$

$$- D_D = Q_D^* =$$


# IFL, NSL, & OFL

- Now we can draw the logic for each section



IFL

 

NSL


 


OFL

  

 
 
# Waveform

- Recall,  $X = A+B$  and  $Y = B + C$
- L is a combinational function of the current state


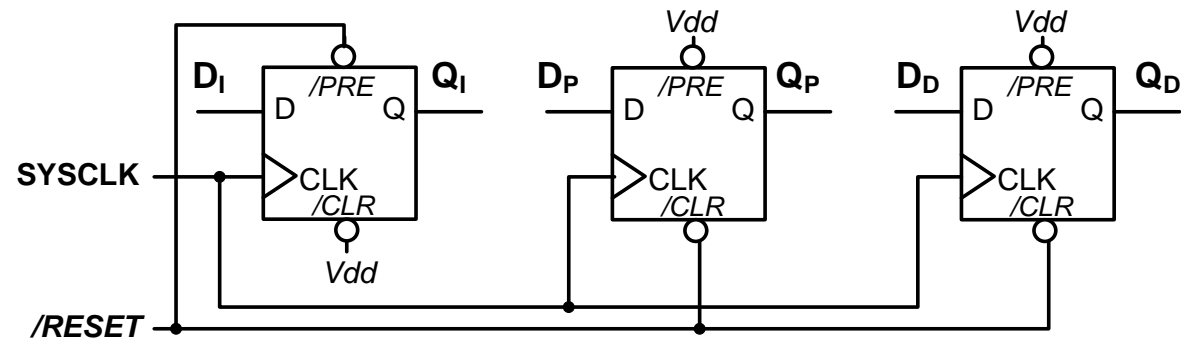 
# State Assignment & NSL

- Let us choose a one-hot state assignment (one FF per state)



- Next State Equations:



$$- D_I = Q_I^* = Q_I \bullet (A+B) + Q_D$$

$$- D_P = Q_P^* = Q_P \bullet (B+C) + Q_I \bullet (A+B)'$$

$$- D_D = Q_D^* = Q_P \bullet (B+C)'$$

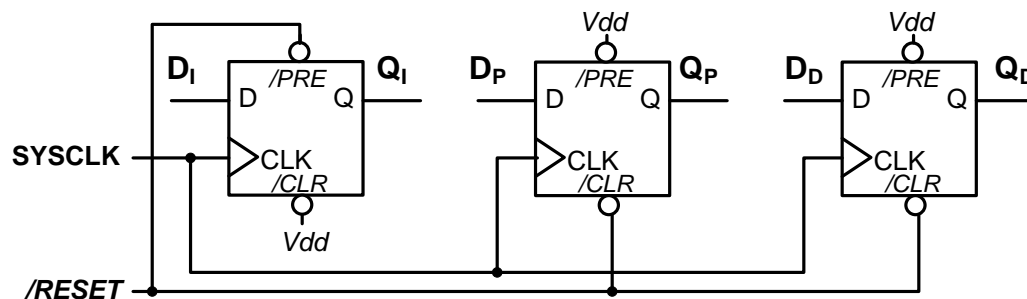
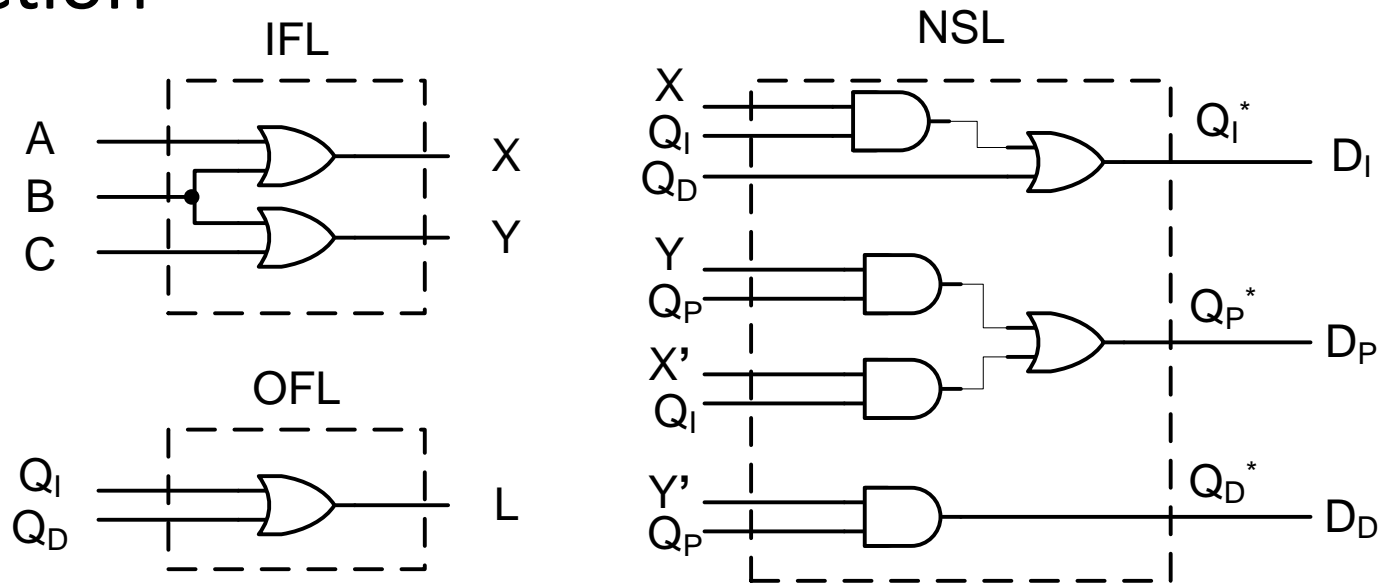
# IFL, NSL, & OFL

- Now we can easily draw the logic for each section


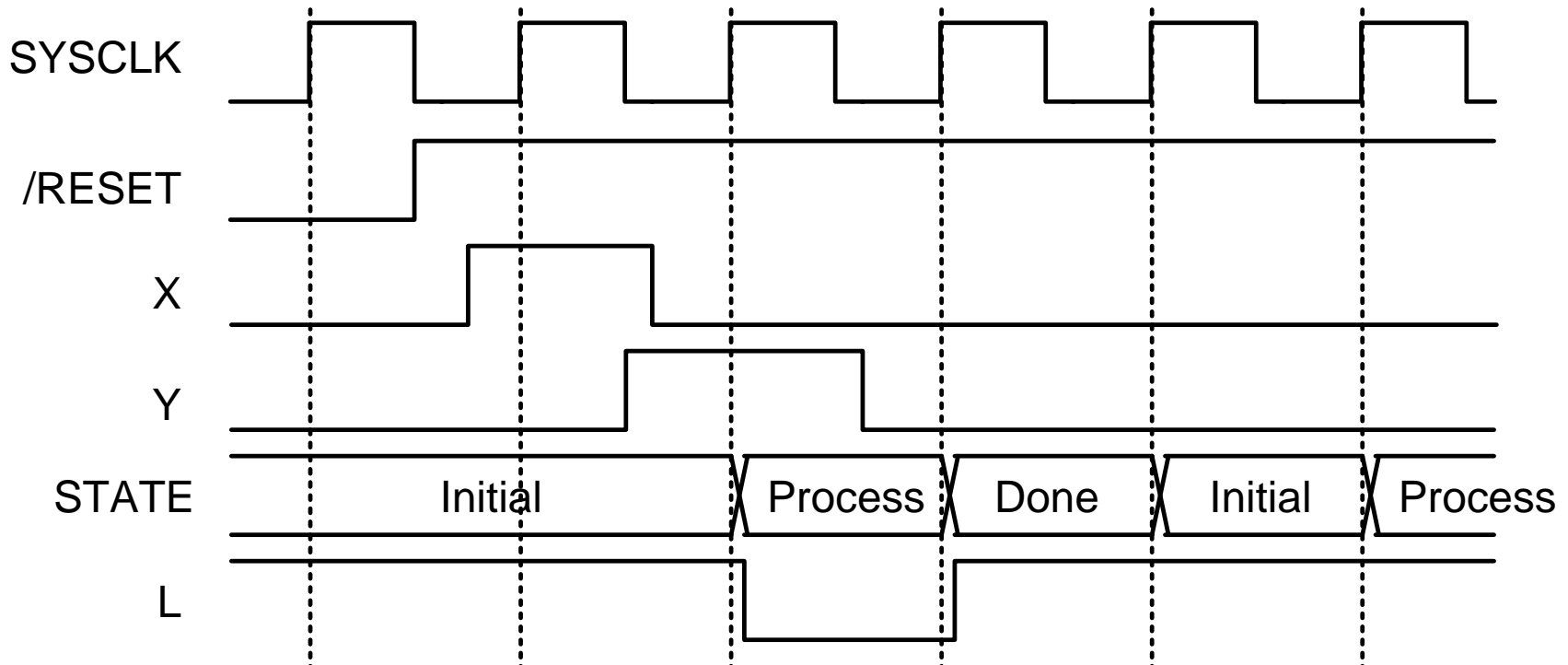 
# Waveform

- Recall,  $X = A+B$  and  $Y = B + C$
- L is a combinational function of the current state





# State Machine Summary

- 4 sections of state machine circuitry: IFL, NSL, SM, OFL
- In one-hot state encoding, a system with 5 states requires 5 flip-flops (one flip-flop per state)
- In an encoded state encoding, a system with 5 states requires 3 flip-flops ( $\log_2 n$  FF's for  $n$  states)
- When designing the NSL for a state, enumerate the conditions associated with the incoming transitions to that state
- To implement the power-on reset condition in a one-hot state encoding, connect the RESET signal to the PRESET input for the one FF associated with the initial state, and to the CLEAR signals of the other FF(s).

Mealy- vs. Moore-style outputs

# STATE MACHINE OUTPUTS


# State Machine Outputs

- State Machine outputs can be classified according to how the outputs are produced
  - If  $Outputs = f(current\ state, other\ inputs)...$   
**MEALY-Style**
  - If  $Outputs = f(current\ state)...$   
**MOORE-Style**
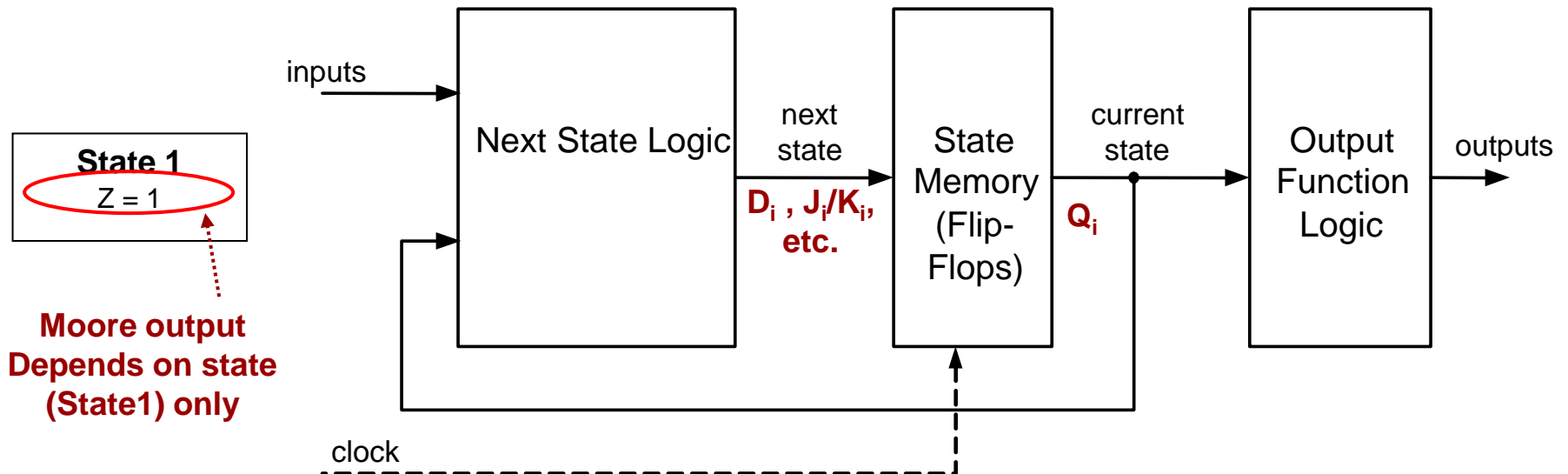
# Moore-Style Outputs

- Moore-style outputs only depend on the current state
- Thus, they are valid **early** in the clock cycle and **stay steady/valid** nearly the entire
- Often requires extra states compared to Mealy-style implementations


The inputs do not feed into the OFL, thus Moore-Style


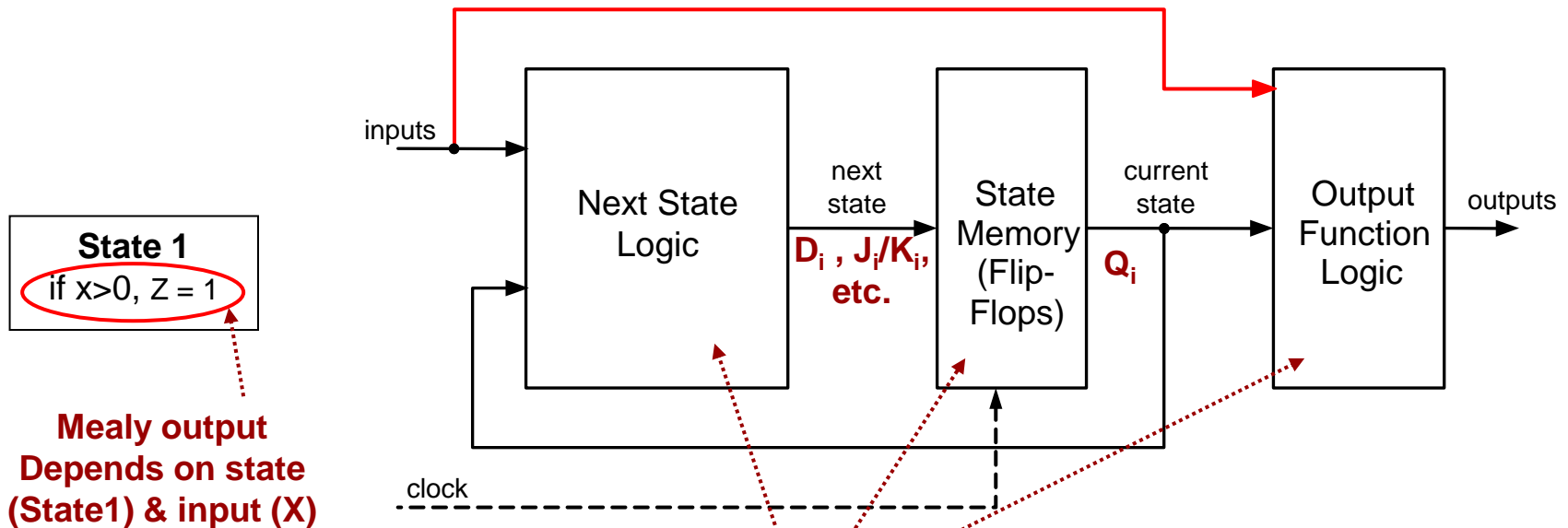
# Mealy-Style Outputs

- Mealy-style outputs depend not only on the current state but the external inputs
- Thus, they may not be valid until *late* in the clock cycle and *may change* during the cycle if the inputs change



The inputs feed into the output function logic, thus Mealy



Notice the 3 sections of a state machine drawn out here
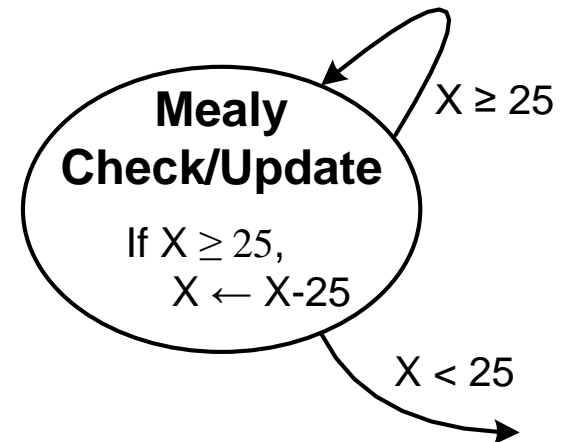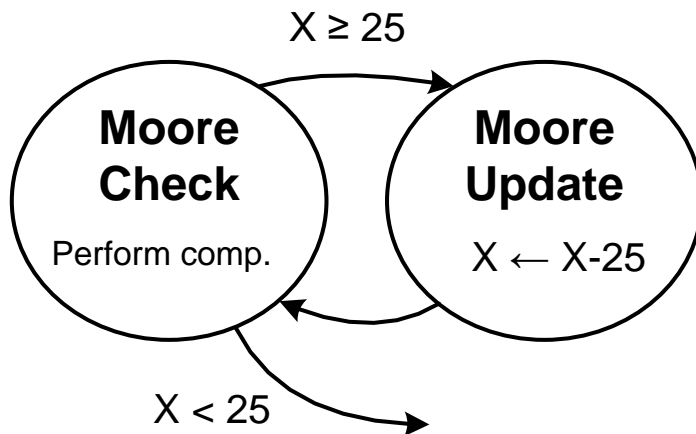
# Mealy vs. Moore Update

- Consider the update/loading of a register,  $X$ , with  $X-25$
- Need to generate an  $X\_LOAD$  signal
  - Can be Moore or Mealy-style




# Divider

- Consider design of a sequential divider,  $(X / Y)$
- Algorithm:
  - Repeatedly subtract  $Y$  from  $X$  while  $X - Y \geq 0$  (or really  $X \geq Y$ ).
  - Quotient,  $Q$ , is simply how many subtractions were performed (i.e. count how many times we performed  $X = X - Y$ )
  - Use a subtractor to compute  $X - Y$  (if subtractor needs to borrow, then we know  $X - Y < 0$  (or really  $X < Y$ ))
- Sample Operation:  $X = 13, Y = 5$ 
  - $Q = 0$
  - $X = X - Y = 13 - 5 = 8, Q = 1$
  - $X = X - Y = 8 - 5 = 3, Q = 2$
  - Remainder =  $X = 3$

# Divider Datapath



- Datapath for Divider

 


 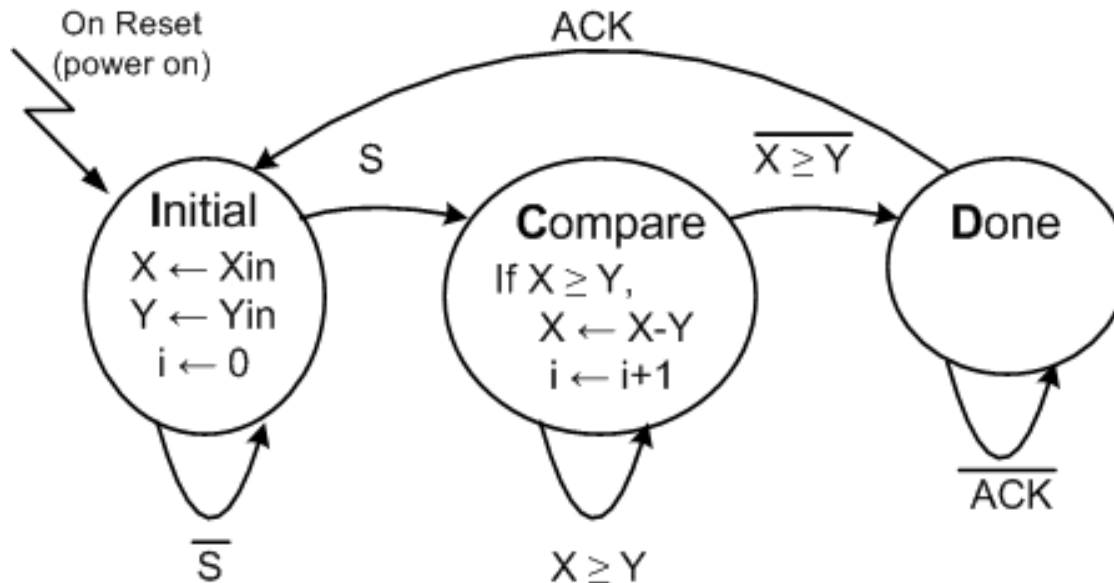
# Divider Control Unit


- Complete the state diagram
  - What is the logic for X\_Load



# Mealy vs. Moore Comparison

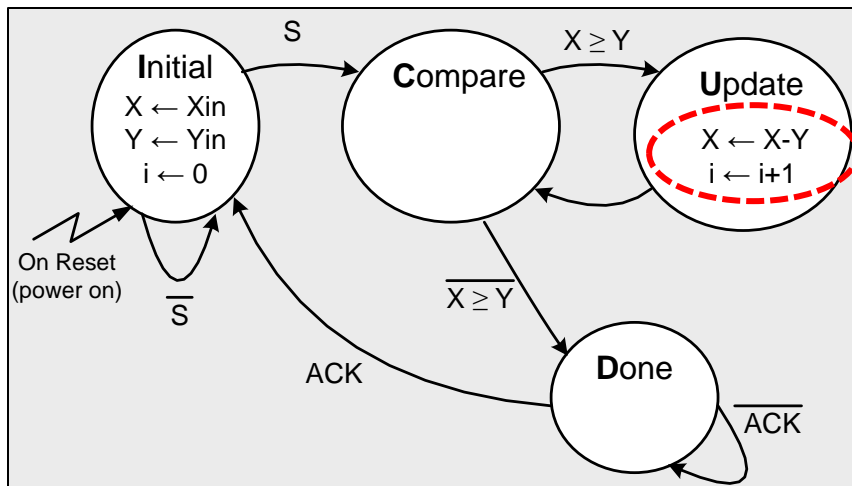
## Moore Implementation

- We need to compare X with Y to determine if we should increment our quotient and update X
- If we want Moore-style enable and increment signals, we need a separate compare & update state




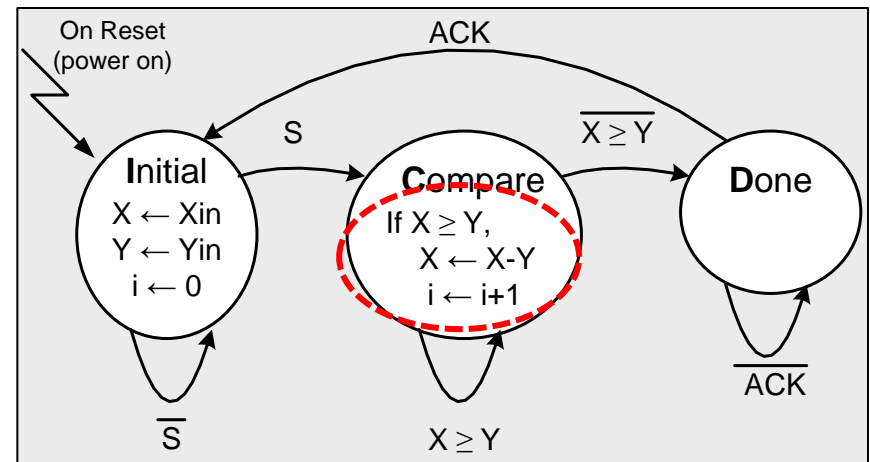
## Mealy Implementation

- In a Mealy-style implementation we can compare and use the result to produce the enable and increment signals in the same clock


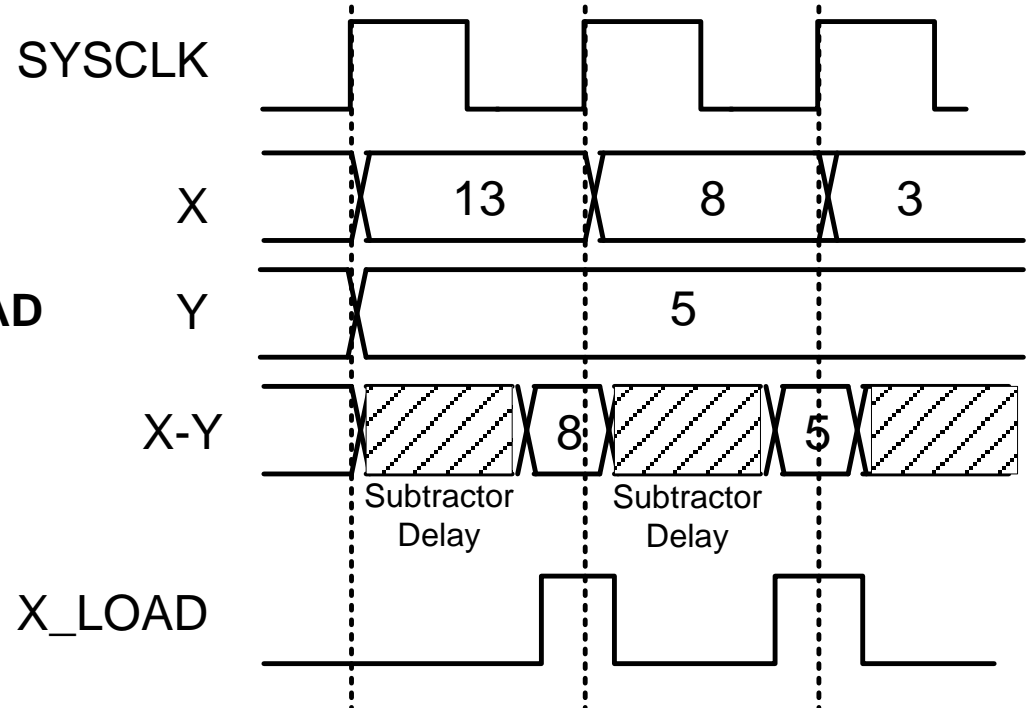 
# Mealy Timing

- In Mealy-style implementation, we must ensure the clock is long enough for control signals to be produced



# Control Signal Timing

- When identifying control signals in the datapath, be sure to consider if the signal should be valid

## —“During the clock”


- Must be valid shortly after the beginning of the clock (e.g. mux selects, etc.)
- Usually must be produced as Moore-style output or fast, Mealy output

## —“At the end of the clock”

- Must be valid by the end of the clock (e.g. register load enables)
- Can be produced by combo logic in datapath

 
# Datapath Design Example

- Design a datapath to support the following RTL (Register Transfer Level) operations
  - Identify the control signals & other datapath components



# Divider Datapath

- Datapath for Divider

 

# MIN/MAX FINDER

# Min/Max Finder Description

- Sixteen 4-bit unsigned numbers are stored in a 16x4 (16 rows/addresses of 4-bits each)
- Iterate over all numbers and determine the maximum (largest) and minimum (smallest) number
- First implement assuming (2) 4-bit comparators are available
- Repeat the implementation assuming (1) 4-bit comparator is available
- Remember in HW we try to perform as many operations in parallel as possible to achieve speed (e.g. perform iteration counter increment in same clock as iteration)
- How many clocks do you think we need?


	0	1	2	3	4	5	6
data	30	51	52	53	54	10	21

```
int min = data[0];
int max = data[0];
for(int i=1; i < N; i++)
{
    if(data[i] < min)
        min = data[i];
    if(data[i] > max)
        max = data[i];
}
```


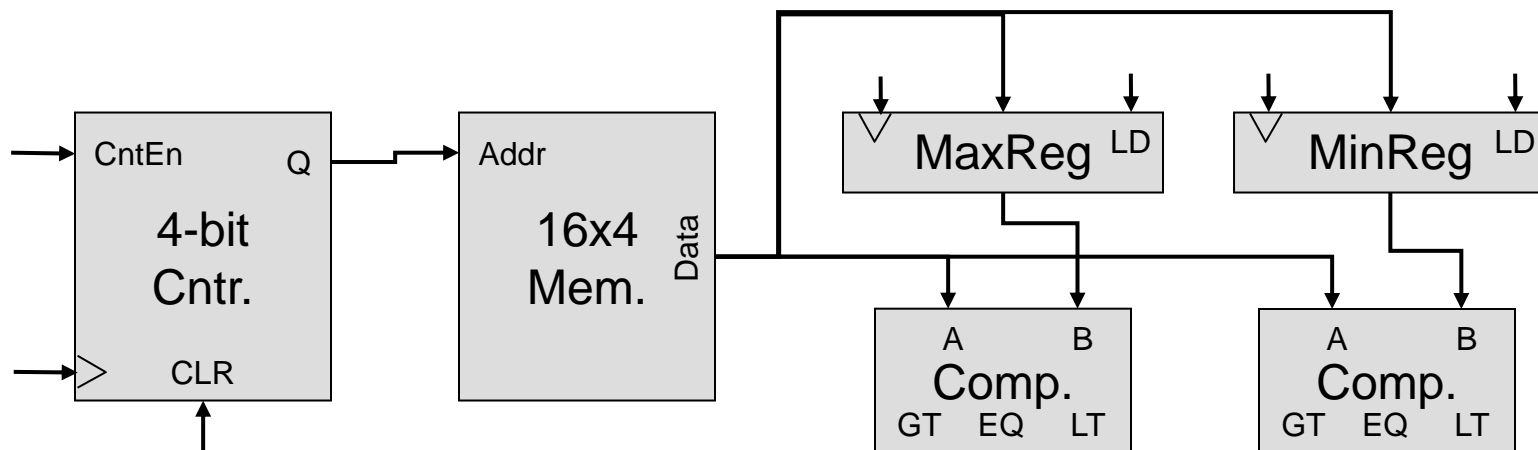
# Datapath Components


- The datapath requires...
  - Two comparators (as per our first implementation description)
  - A 16x4 memory
  - (2) registers to store current min / max
  - (1) 4-bit counter to counter iterations & address memory




# Datapath Components

- Algorithm
  - After a START signal is applied, load the zero-th (0-th) number in the memory in both MAX and MIN registers.
  - Enter an iterative loop for the first thru fifteenth numbers with both the current known MAX and MIN values, updating the registers appropriately
  - When all iterations are done (or about to be done?) go to a DONE state
- Draw a flow chart or state diagram

# Flow Chart

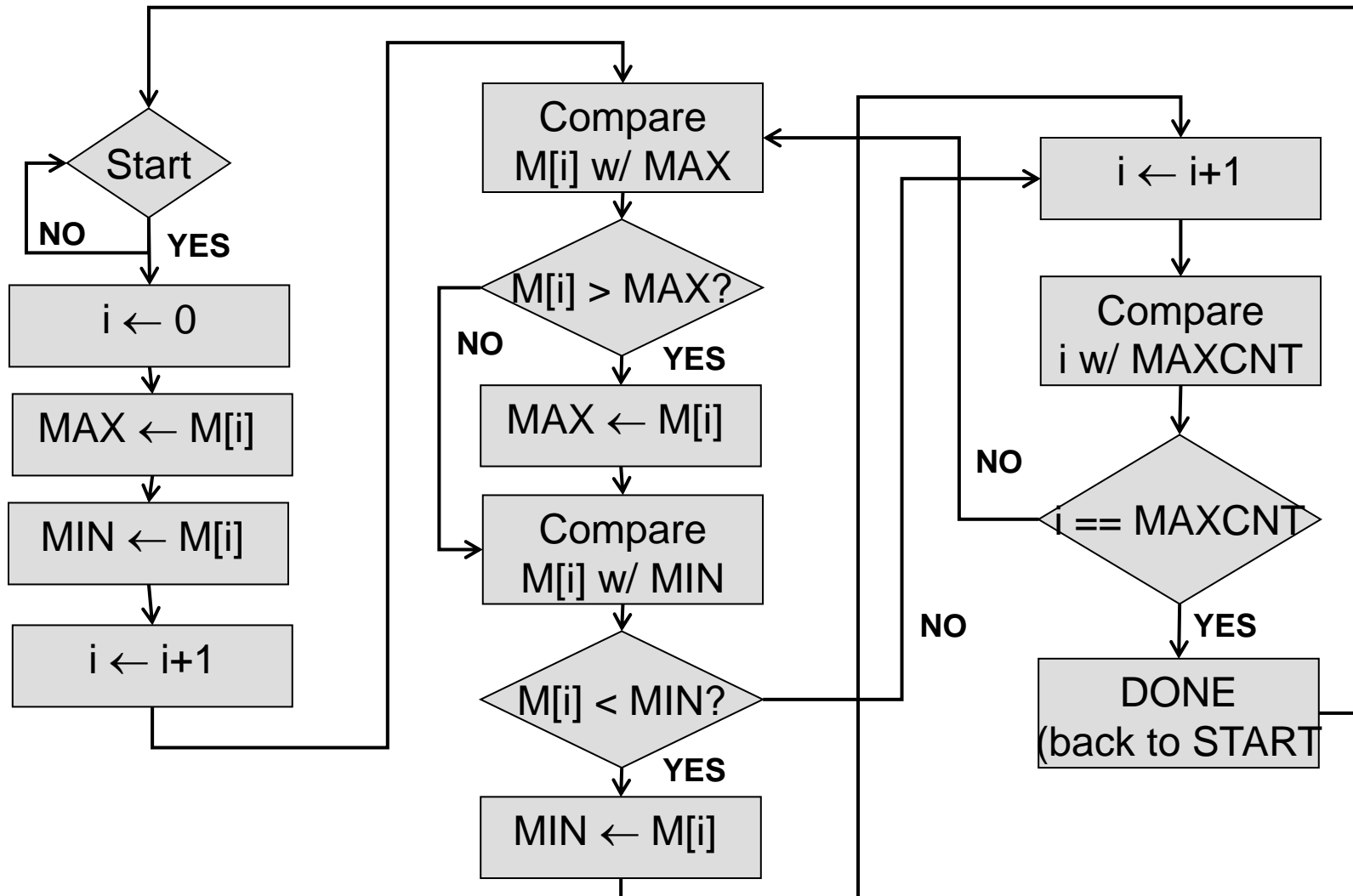

# MinMax Control Unit


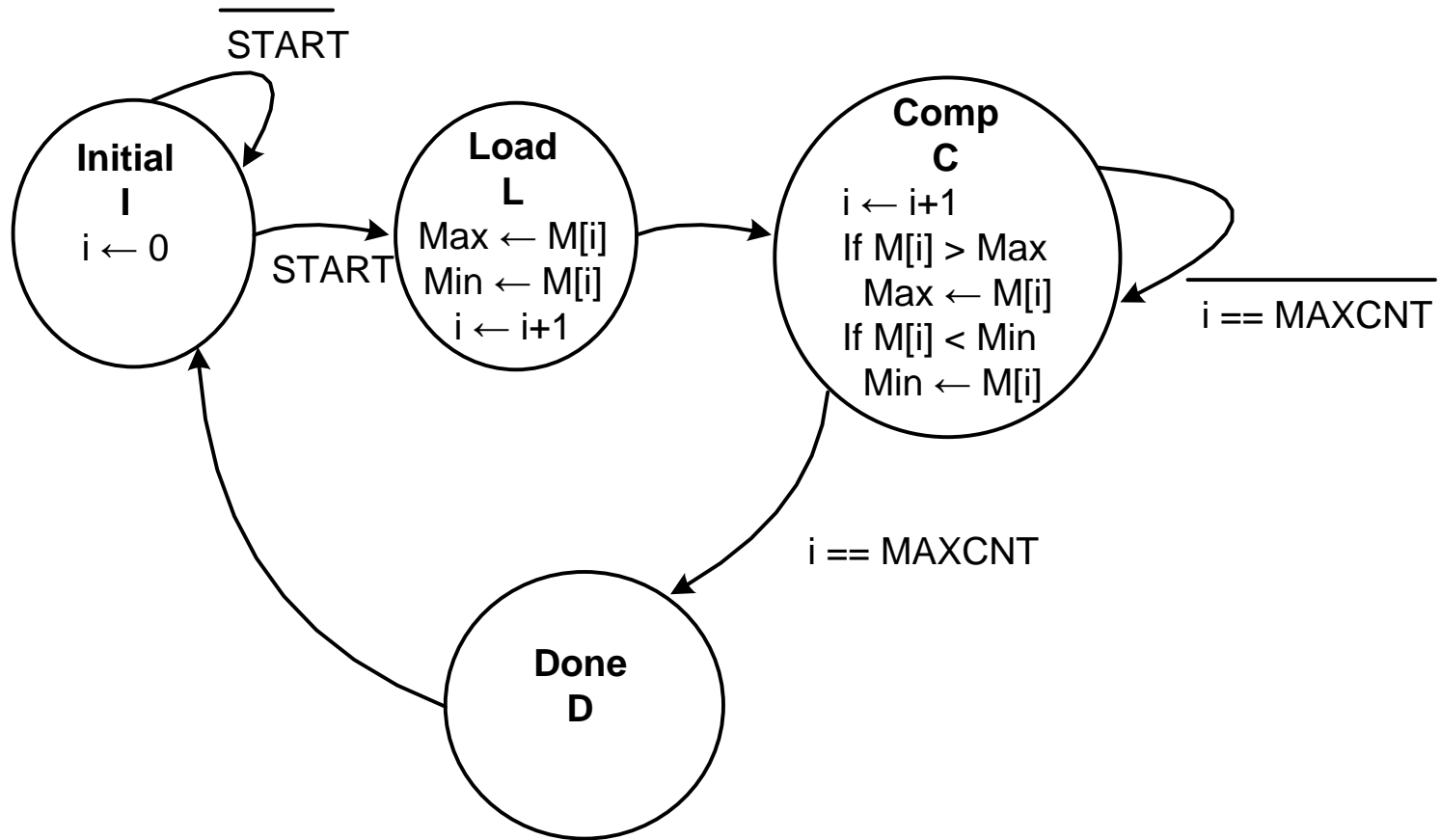


# Control Signal Timing Example

- Consider the following statement of building a counter such that  $i$  increments ( $i \leftarrow i+1$ ) on each clock
  - (During the clock / At the end of the clock) you enable the counter so that (during the clock / at the end of the clock) it actually increments
- Consider designing a minutes & seconds counter circuit with separate counters for each
  - **Option 1:** After 60 seconds (during 61<sup>st</sup> second) enable the minutes counter
  - **Option 2:** During the 60<sup>th</sup> second (after 59 seconds) enable the minutes counter

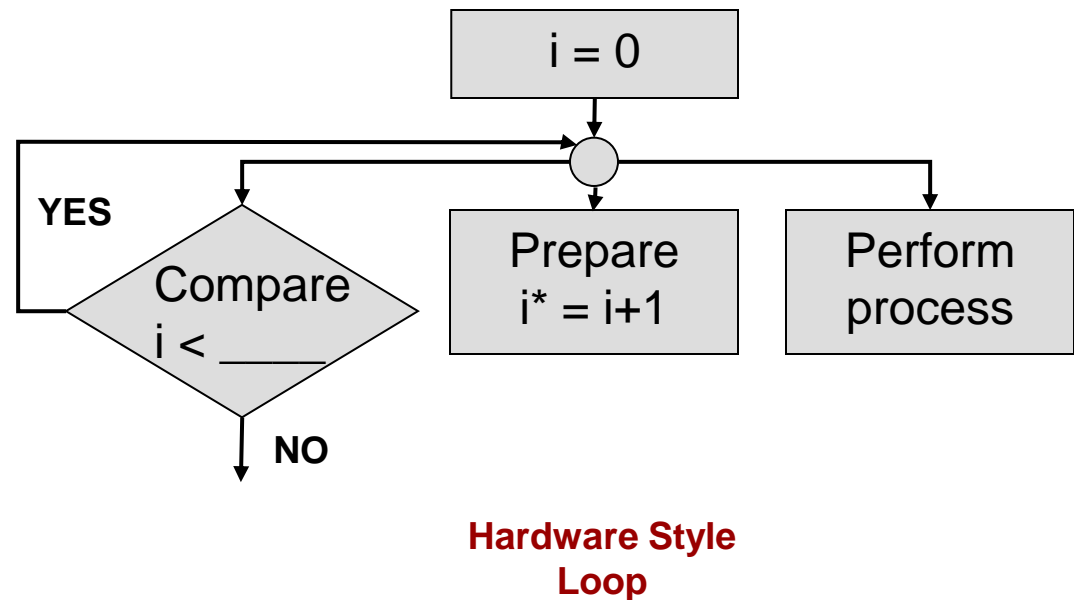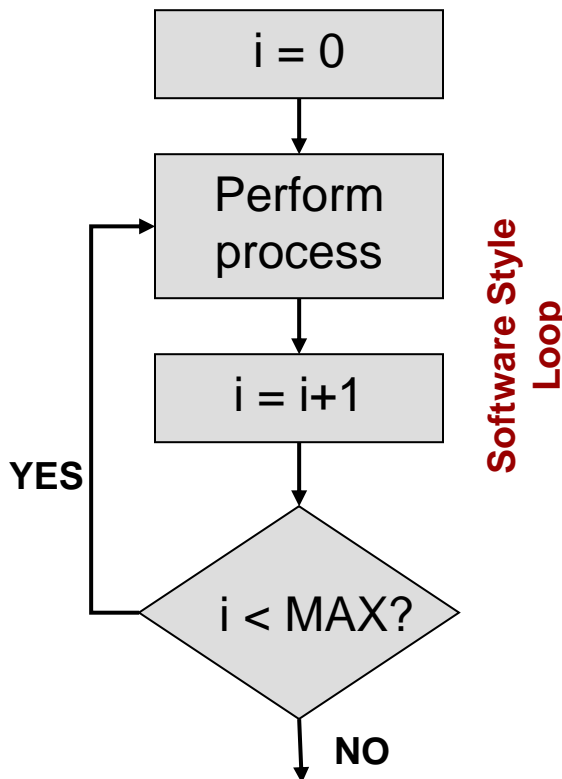
# Early or Late?

- Consider a counting loop to iterate MAX times
- In hardware we try to perform as many operations in parallel as possible
- To iterate MAX times, what should we compare with  $i$ ?



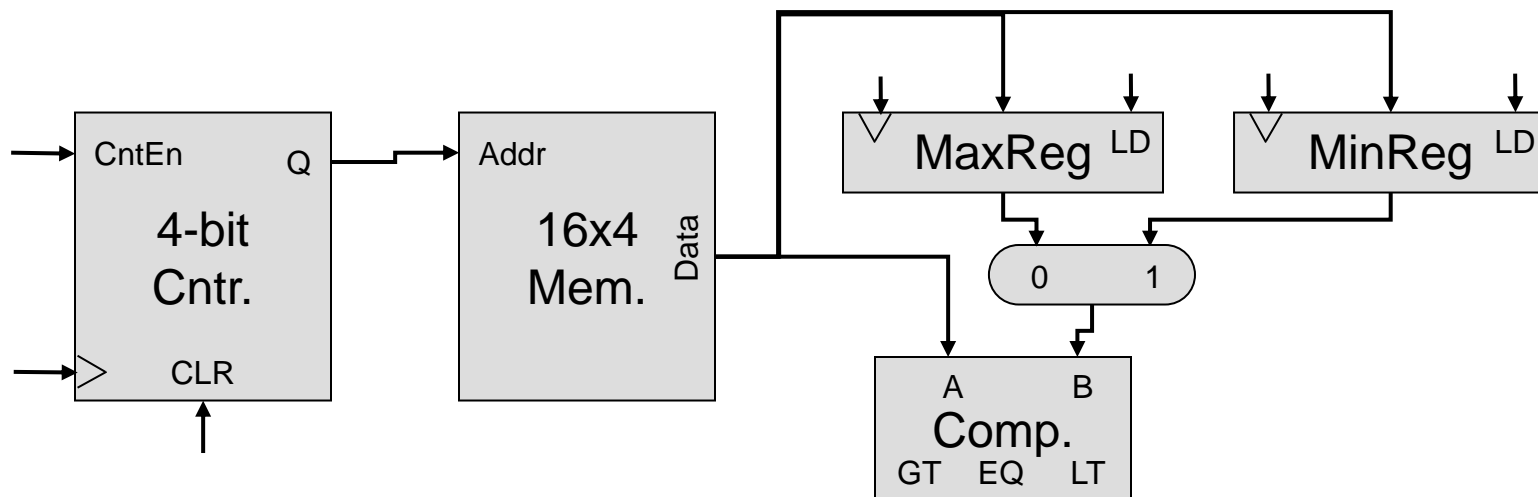
# 1 Comparator Datapath

- The datapath requires...
  - Two comparators (as per our first implementation description)
  - A 16x4 memory
  - (2) registers to store current min / max
  - (1) 4-bit counter to counter iterations & address memory





# 1-Comparator Implementation

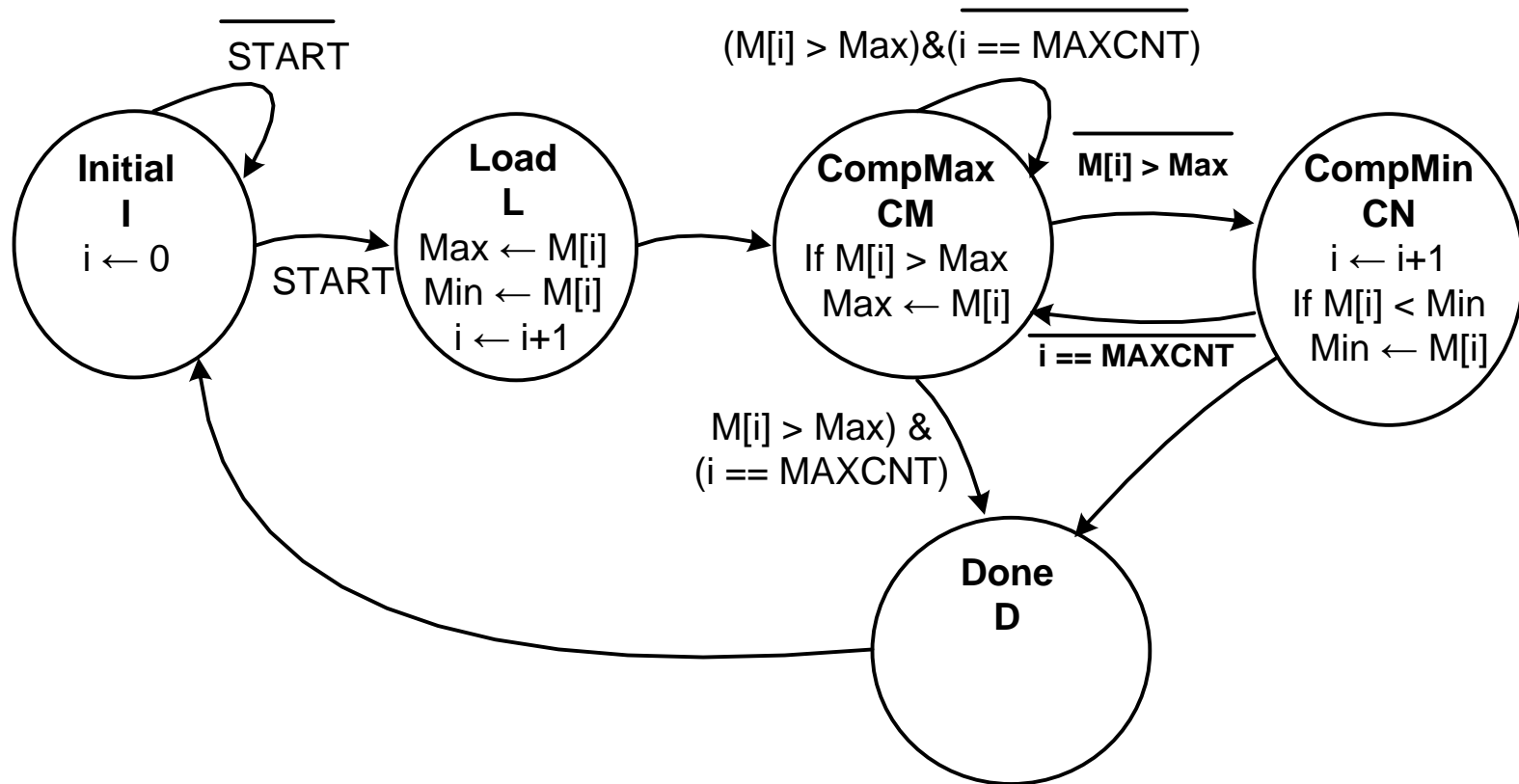


  
# Transition Conditions



- Is there any relationship between conditions associated with incoming transitions or outgoing transitions?
- Outgoing transitions must be
  - Mutually Exclusive (< 2 conditions true)
  - All-inclusive (> 0 conditions true)



# Example: Vote Counting Machine

  1.1 Majority vote for a 5-vote case: In your homework #8, you have designed a state machine to inspect *four votes* serially to find majority vote. This is a similar problem with **FIVE votes** *instead of FOUR votes*. Majority means **three YES** votes in the five-vote case also. The six states are:



- I = INITIAL
- C = COUNTING votes
- C1N = continuing COUNTING votes  
after seeing one (1) NO vote
- C2N = continuing COUNTING votes  
after seeing two (2) NO votes
- W = WON the majority vote
- L = LOST the majority vote



Complete the state diagram.
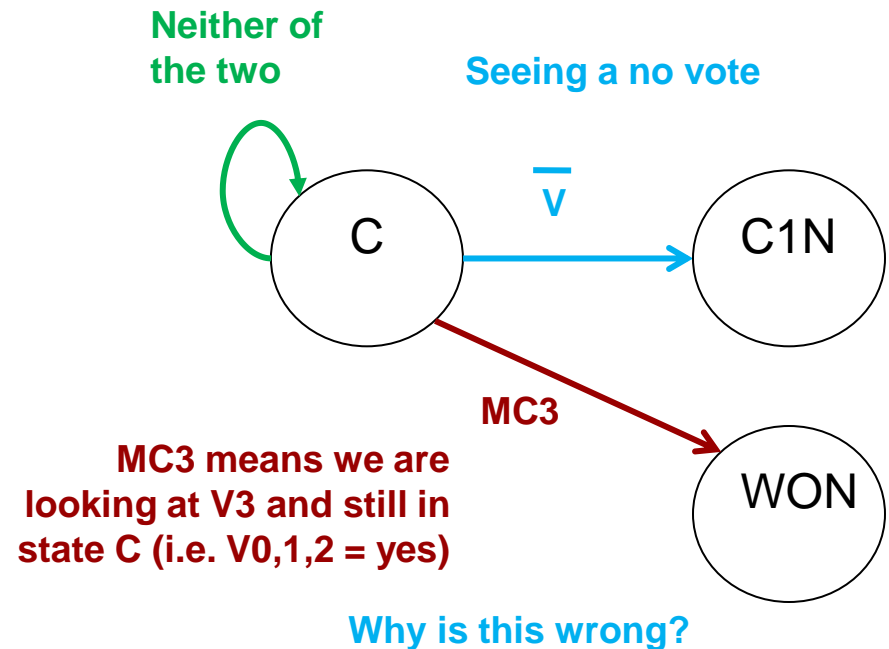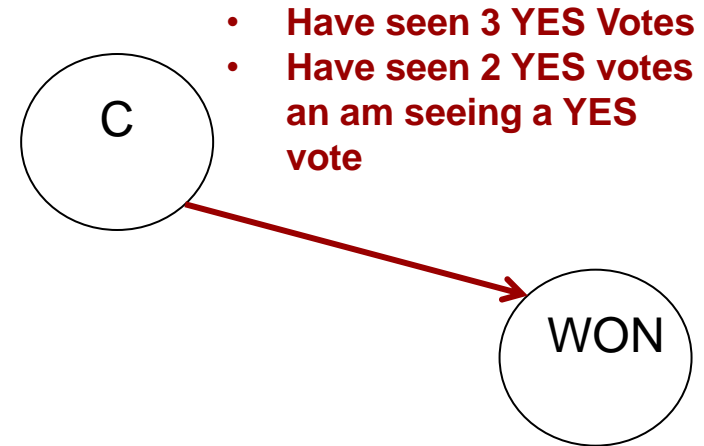
# Vote State Machine Conditions

- Remain in C until...
  - Find a NO vote...
    - ...then go to C1N
  - Have enough YES votes to guarantee victory...
    - ...then go to WON



# Control / Datapath Interaction

- We have used the analogy of the control unit as a manager and datapath as workers
- Consider the DPU as individual workers (plumbers, electricians,...) who need to be told what to do each hour (each clock cycle)
- The control unit uses the current state (updated each clock cycle) to determine what work (control signals) should be performed each hour (clock cycle)
- Control signals generated by state machines may fall into one of two sets:
  - Mealy-style outputs
  - Moore-style outputs

# Control Output Summary

- A Mealy-style output is conditioned upon the current state AND other input signals
- A Moore-style output is conditioned only upon the current state
- In synchronous digital systems, you must prepare a control signal during the clock so the effect takes place at the end of the clock (beginning of next clock)




# TRI-STATE OUTPUTS & BUSES

# Typical Logic Gate

- Gates can output two values: 0 & 1
  - Logic '1' ( $V_{dd} = 3V$ ), or Logic '0' ( $V_{ss} = GND$ )
- Analogy: a sink faucet
  - 2 possibilities: Hot ('1') or Cold ('0')
- Inputs cause *EITHER* a pathway from output to VDD *OR* VSS



Hot Water = Logic 1

Cold Water = Logic 0

  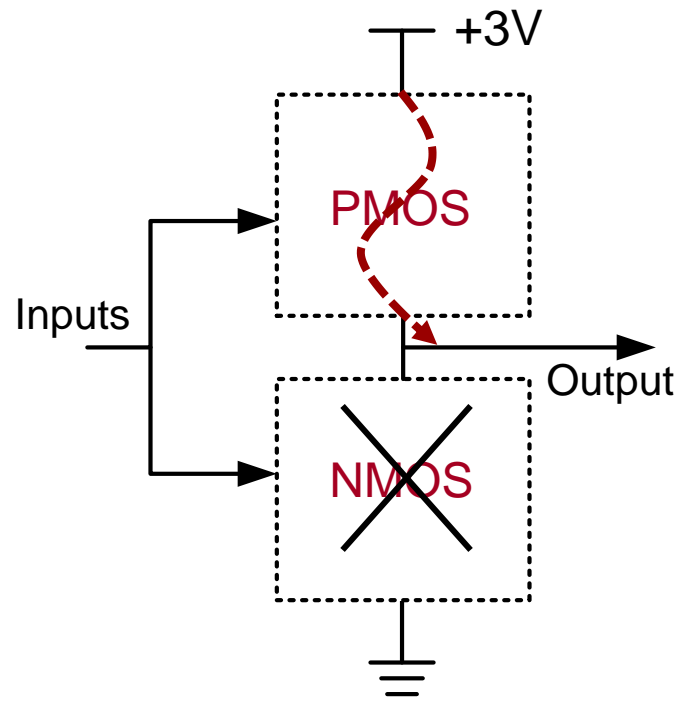
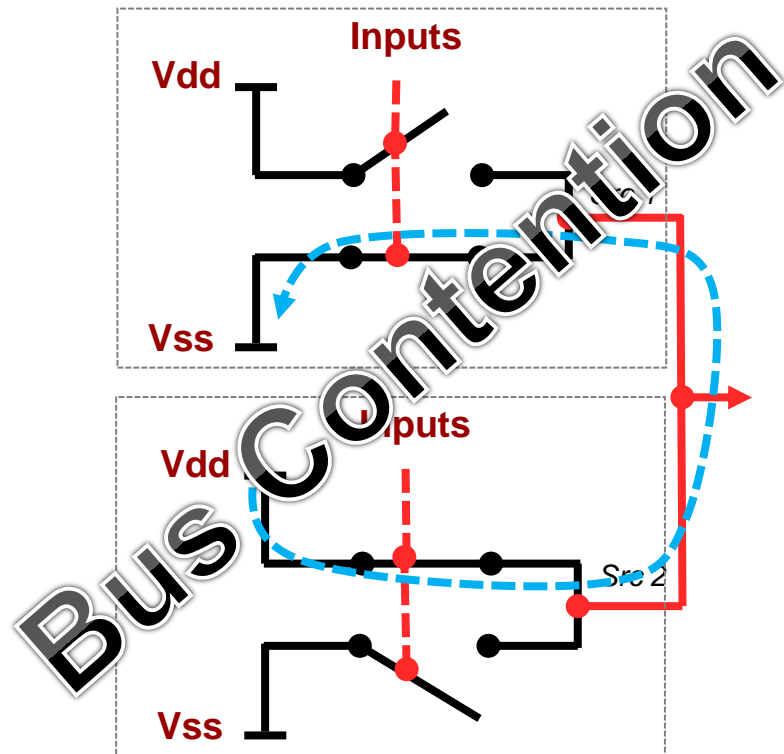 
# Output Connections


- Can we connect the output of two logic gates together?
- No! Possible short circuit (static, low-resistance pathway from Vdd to GND)
- We call this situation “bus contention”




 
# Tri-State Buffers

- Gates can output two values: 0 & 1
  1. Logic 0 = 0 volts
  2. Logic 1 = 5 volts
- Tristate buffers can output a third value:
  3. Z = High-Impedance  
(no connection to any voltage source)
- Analogy: a sink faucet
  - 3 possibilities:
    - 1.) Hot water,
    - 2.) Cold water,
    - 3.) NO water



**Hot Water = Logic 1**


**Cold Water = Logic 0**

**NO Water = Z (High-Impedance)**

# Tri-State Buffers

- Tri-state buffers have an extra enable input
- When disabled, output is Z
- When enabled, normal buffer


Tri-State Buffer

 

En	In	Out
0	x	Z
1	0	0
1	1	1

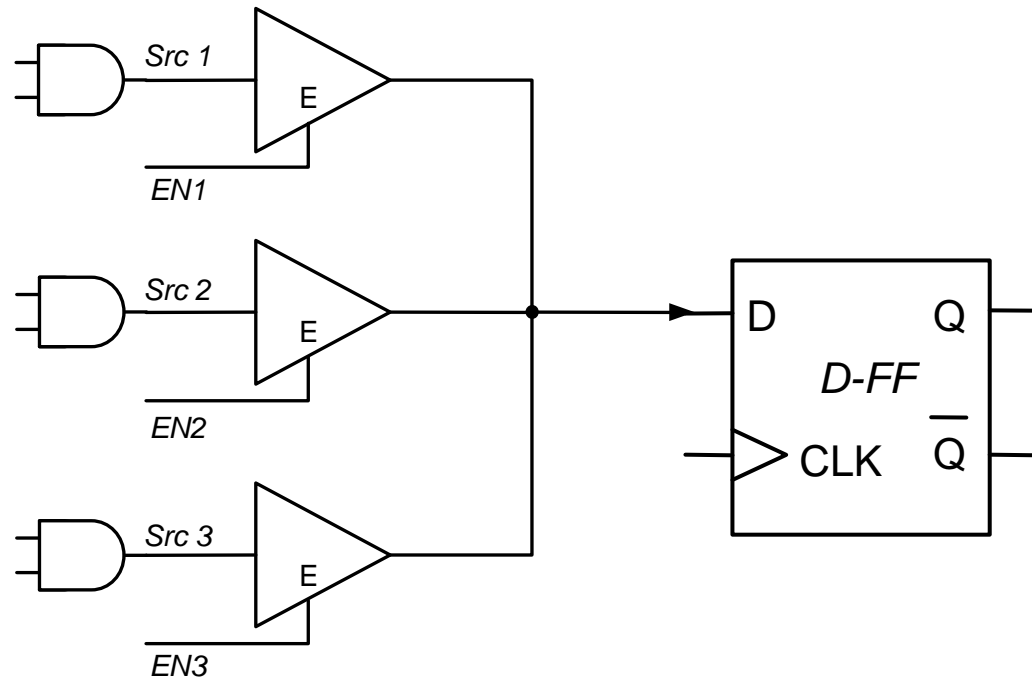
# Tri-State Buffers

- We use tri-state buffers to share one output amongst several sources
- Rule: Only 1 buffer enabled at a time


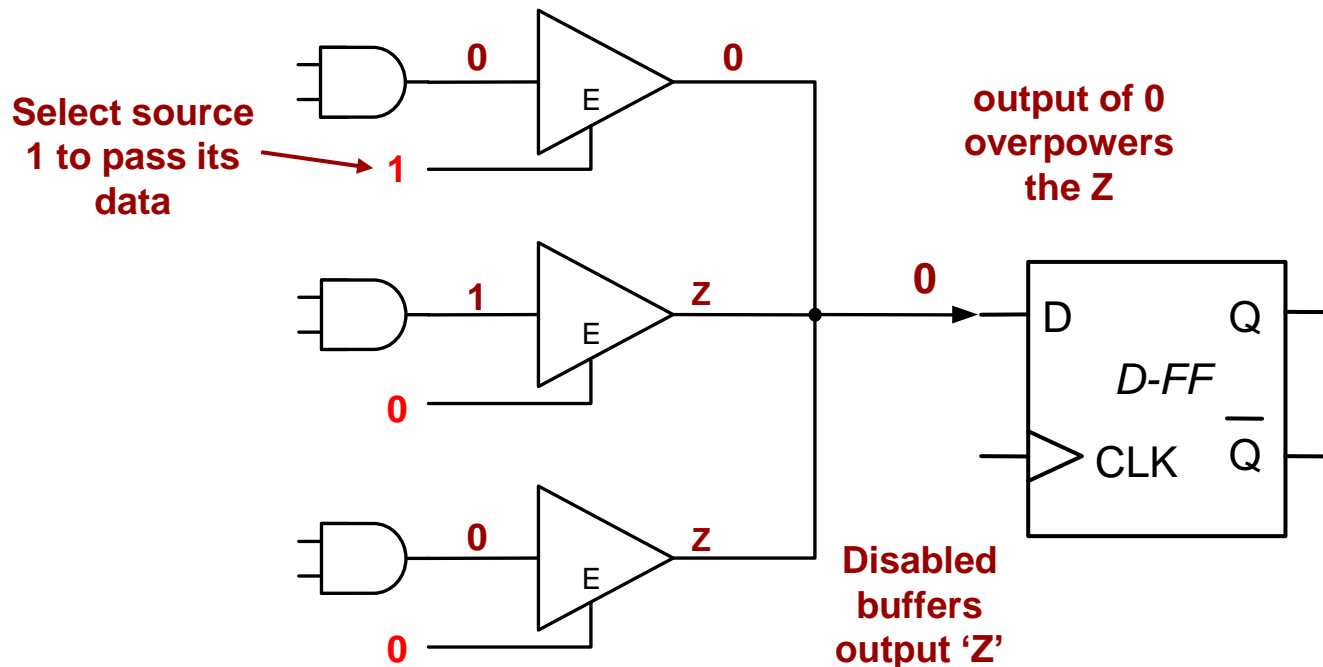
# Tri-State Buffers


- We use tri-state buffers to share one output amongst several sources
- Rule: Only 1 buffer enabled at a time
- When 1 buffer enabled, its output overpowers the Z's (no connection) from the other gates




# Communication Connections

- Multiple entities need to communicate
- We could use
  - Point-to-point connections
  - A shared bus (set of wires)

**Separate point to point connections**

 


**Shared Bus**

 
 
# Bidirectional Bus

- 1 transmitter (otherwise bus contention)
- N receivers
- Each device can send (though 1 at a time) or receive



# Tri-State Buffer / Bussing Summary


- Provide a 3<sup>rd</sup> output value: Z (high impedance)
- Allows multiple outputs to be wired together
- Only one bus driver can be enabled at a time

# MICROARCHITECTURE EXAMPLE



 
# Digital Design Goals

- Digital systems seek to optimize a design along these three axes:
  - Area (size)
  - Speed
  - Power Consumption
- Can often only optimize one or two of these without sacrificing the other(s)
  - Just as in software design, there is a classic time/space trade-off
  - Microarchitecture can determine where a design falls in this trade space




# Different Architectures

Single Bus

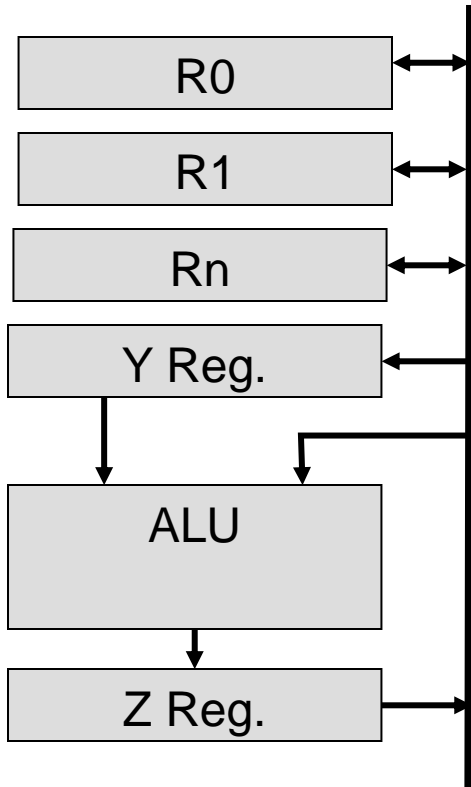


Clock 1:  $Y = R_{src1}$   
 Clock 2:  $Z = R_{src2} + Y$   
 Clock 3:  $R_{dst} = Z$

Two-Bus

 

Clock 1:  $Z = R_{src1} + R_{src2}$   
 Clock 2:  $R_{dst} = Z$

Three Bus

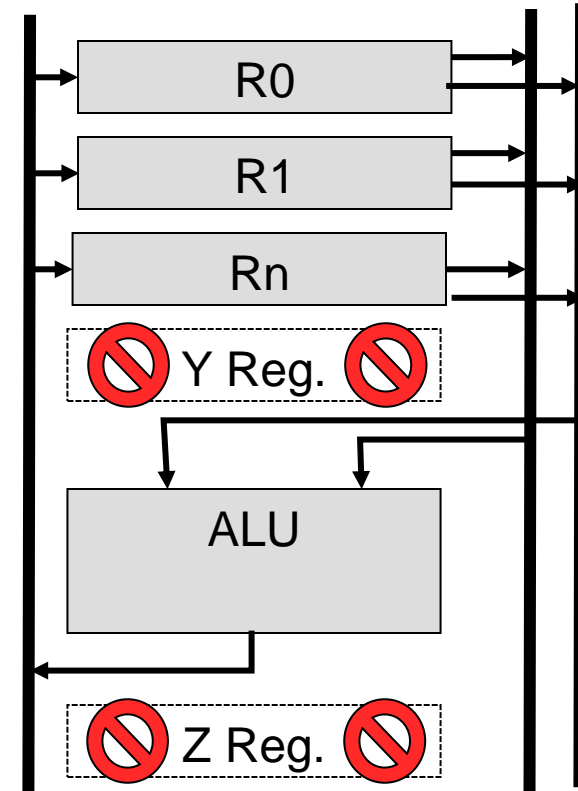

Clock 1:  $R_{dst} = R_{src1} + R_{src2}$

**General Implications: Less Resources => More Clock Cycles (Time)**