

EE 457 Unit 1

Overview of Digital System Design

Credits

- These slides were derived from Gandhi Puvvada's EE 457 Class Notes


Clocking Strategies

REGISTERS & DATA ENABLES

Registers

- A Register is a group of D-FF's tied to a common clock and clear (reset) input
 - Clear can be asynchronous or synchronous
- Used to store multiple bit values on each clock cycle


CLK	RST	D _i	Q _i *
1,0	X	X	Q _i
↑	1	X	0
↑	0	0	0
↑	0	1	1

 

4-bit Register


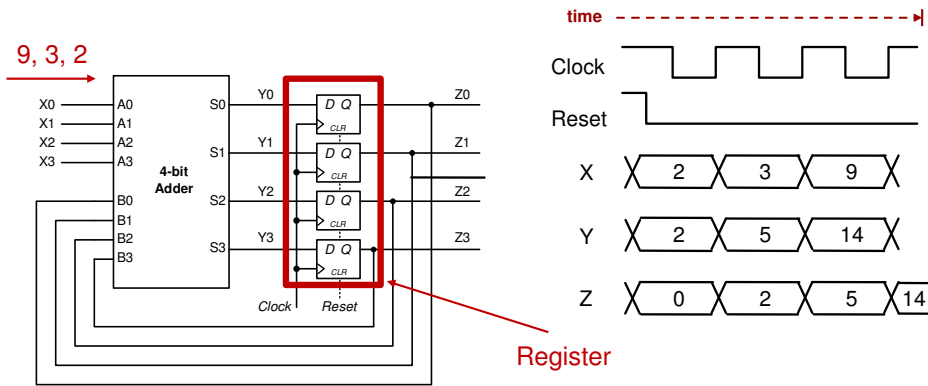
Example: Accumulator

- Sum a time-based sequence of numbers
- A register usually stores a single logic value (i.e. a number)




Synchronous vs. Asynchronous

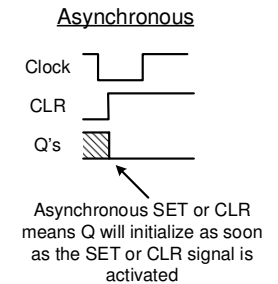 - The set/preset and clear inputs can be built to be **synchronous** or **asynchronous**
- These terms refer to when the initialization takes place
 - Asynchronous Reset (AR): Initialization of Q takes effect immediately regardless of the CLK
 - Synchronous Reset (SR): Initialization of Q takes effect only at an edge (clear must be active at the edge)





Registers

 - Whatever the D value is at the clock edge is sampled and passed to the Q output until the next clock edge





Selective Loading/Registering of Data

  - What if we only want a register to capture data on *selective* clocks (and not on *EVERY* clock)
 - Clocks are indicated with a "LOAD" signal





Clocking Option 1

  - Use Load as the clock signal
- **(Does/Doesn't) Work.**
- _____




Clocking Option 2

  - Use ~Load (inverted Load) as the clock signal
- **(Does/Doesn't) Work.**
- _____




Glitches

 - Temporary (transient) incorrect / toggling output values due to differing delay paths of the inputs
 - Eventually output settles to correct value
 - Unless a circuit is specially designed, glitches are possible on all circuits





Successive Loading Clocks

- If load is held high on two successive clock cycles will get _____ edge(s)

 


Option 3

- Gate the clock with the load signal
- Also susceptible to glitches

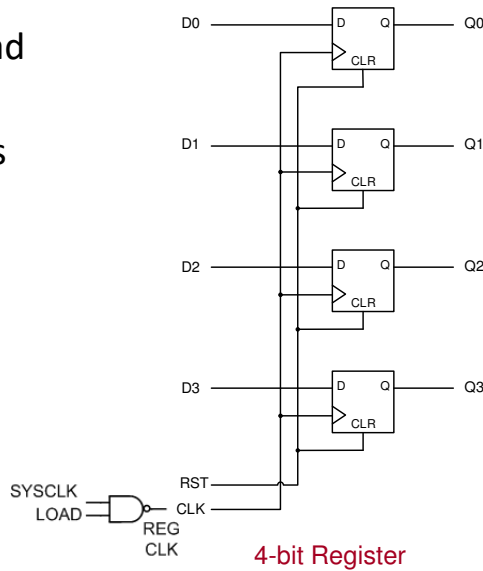 

Option 4: Feedback mux

 - Registers (D-FF's) will sample the D bit every clock edge and pass it to Q
- Sometimes we may want to hold the value of Q and ignore D even at a clock edge
- We can add an enable input and some logic in front of the D-FF to accomplish this




FF with Data Enable
(Always clocks, but selectively chooses old value, Q, or new value D)


CLK	AR	EN	D _i	Q _i *
X	1	X	X	0
0,1	0	X	X	Q _i
↑	0	0	X	Q _i
↑	0	1	0	0
↑	0	1	1	1

Registers w/ Enables

 - When EN=0, Q value is passed back to the input and thus Q will maintain its value at the next clock edge
- When EN=1, D value is passed to the input and thus Q will change at the edge based on D



 
When EN=0, Q is recycled back to the input



When EN=1, D input is passed to FF input


Registers w/ Enables

 - The D value is sampled at the clock edge only if the enable is active
- Otherwise the current Q value is maintained




Register With or Without An Enable

Free-Running Register

 

Register with Load (Data) Enable

 


When to use one vs. the other?

- Free-running register: Do you want to update the stored value EVERY edge
- Register w/ Enable: In all other cases...


Counters

- Increment (Add 1 to Q) at each clock edge
 - Up Counter: $Q^* = Q + 1$
- Standard counter components include other features
 - Enables: Will not count at edge if $EN=0$
 - Resets: Reset count to 0
 - Parallel Load Inputs: Can initialize count to a value P (i.e. $Q^* = P$ rather than $Q+1$)

 

Sample 4-bit Counter


- 4-bit Up Counter
 - RST: synchronous reset input
 - PE and P_i inputs: loads Q with P when PE is active
 - CE: Count Enable
 - Must be active for the counter to count up
 - TC (Terminal Count) output
 - Active when $Q=1111$ AND counter is enabled
 - $TC = EN \cdot Q_3 \cdot Q_2 \cdot Q_1 \cdot Q_0$
 - Indicates that on the next edge it will roll over to 0000
 - Used to create 8-, 12-, 16-bit, etc. counters from these 4-bit building blocks

 


CLK	RST	PE	CE	Q^*
0,1	X	X	X	Q
↑	1	X	X	0
↑				
↑				
↑				

Counter Design

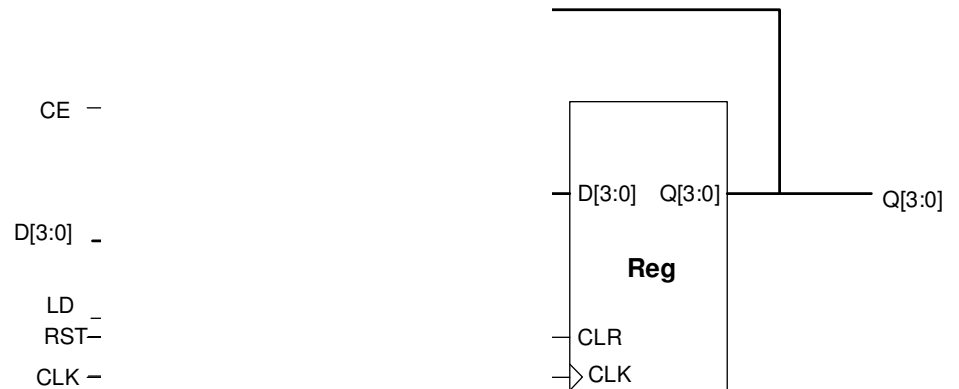- Sketch the design of the 4-bit counter presented on the previous slides



Counters

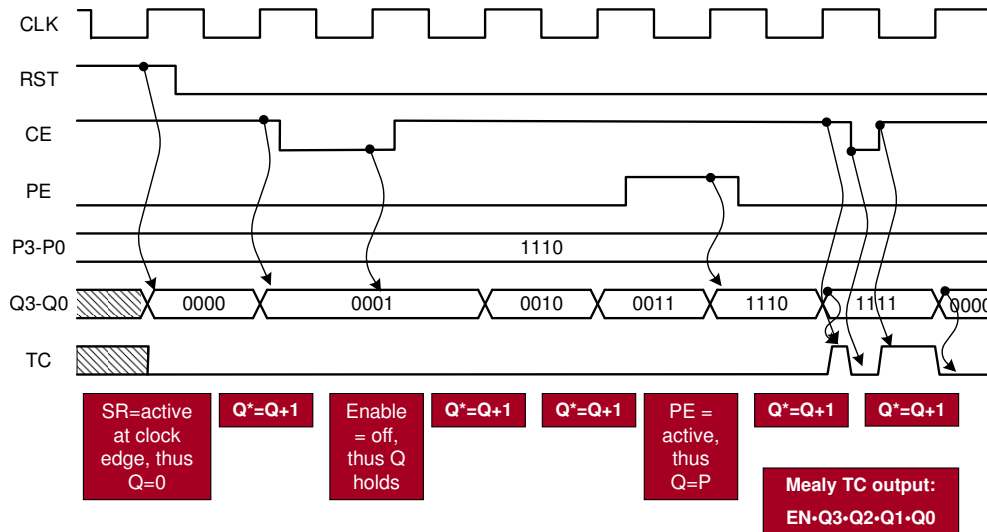

Reference Verilog

- Verilog description of a register with enable and counter with load and count enable

```

module reg16e(
  input clk,
  input reset,
  input en,
  input [15:0] d,
  output reg [15:0] q
);

always @(posedge clk)
begin
  if(reset)
    q <= 16'd0;
  else if(en)
    q <= d;
end
endmodule
    
```

16-bit Register w/ Enable

```

module cnt16ce(
  input clk,
  input reset,
  input load,
  input ce,
  input [15:0] d,
  output reg [15:0] q
);

always @(posedge clk)
begin
  if(reset == 1)
    q <= 16'd0;
  else if(load == 1)
    q <= d;
  else if(ce == 1)
    q <= q+1;
end
endmodule
    
```

16-bit Counter w/ Load and Count Enable

Data Register Summary


- Understand the operation of a free-running register, register w/ data/load enable, and a counter with count enables, etc.

Datapath and Control Unit Decomposition

SYNCHRONOUS SYSTEM DESIGN TECHNIQUES


Digital System Design

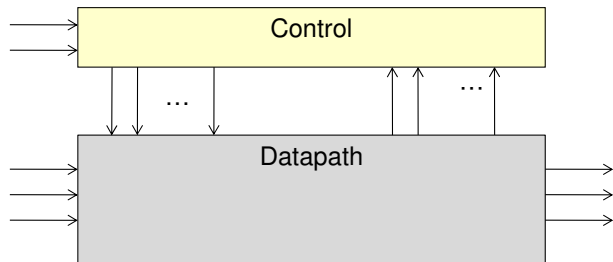- Control (CU) and Datapath Unit (DPU) paradigm
 - Separate logic into datapath elements that operate on data and control elements that generate control signals for datapath elements
 - Datapath: Adders, muxes, comparators, counters, registers (w/ enables), memories, FIFO's
 - Control Unit: State machines/sequencers



Datapath + Control

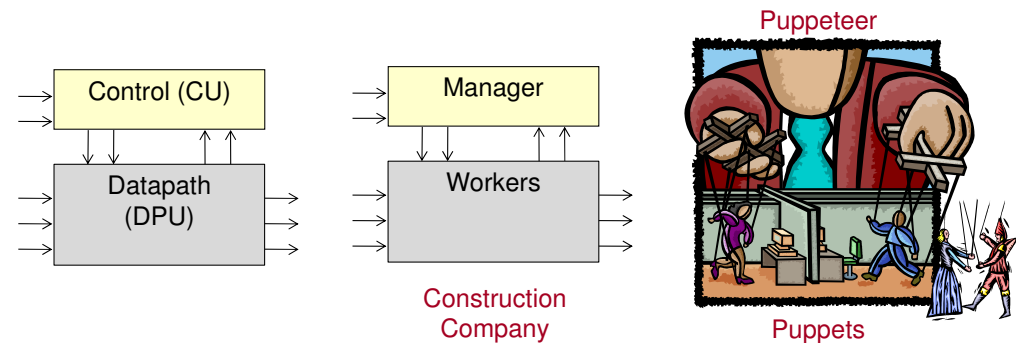- The control unit acts as scheduler and manager while the datapath "does" the work
 - Similar division of labor in many other areas
 - Control signals include: _____, _____, _____ enables, output enables, etc.




Identifying Control Signals

- Design a datapath to support the following RTL (Register Transfer Level) operations
 - Identify the control signals & other datapath components

Desired Operations:

 
$C \leftarrow A+B,$ if $F,G=0,0$
 $C \leftarrow A-B,$ if $F,G=0,1$
 $R \leftarrow P+Q,$ if $F,G=1,0$
 $R \leftarrow P-Q,$ if $F,G=1,1$



One-hot State Machine Design

STATE MACHINE (CONTROL UNIT) DESIGN

Digital System Representation

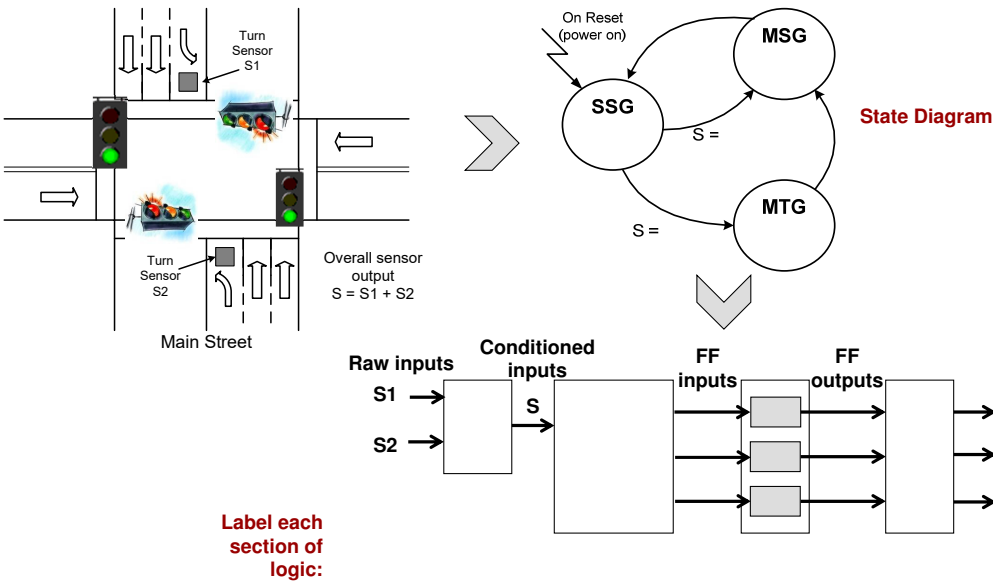


State Machine Review

State Diagrams

 
1. States
2. Transition Conditions
3. Outputs

State Machines require sequential logic to remember the current state (w/ just combo logic we could only look at the current value of X, but now we can take 4 separate actions when X=0)




State Machine

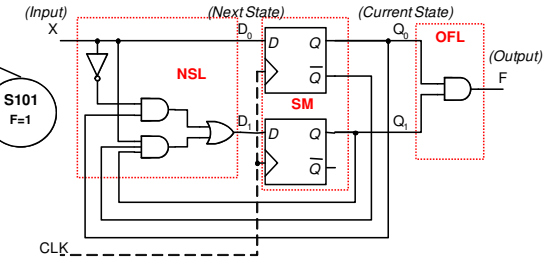1. State Memory => FF's
 - n-FF's => 2^n states
2. Next State Logic (NSL) + Input Function Logic (IFL)
 - combinational logic for FF inputs
3. Output Function Logic (OFL)
 - MOORE: f(state)
 - MEALY: f(state + inputs)




State Assignment

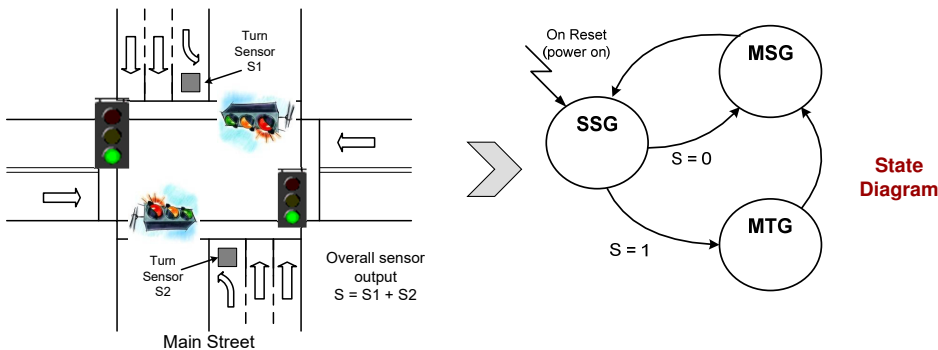- Design of the traffic light controller with main turn arrow
- Represent states with some binary code, but what kind?
 - Encoded: 3 States => 2 bit code: 00=SSG, 01=MSG, 10=MTG
 - One-hot: Separate FF per state: 100=SSG, 010=MSG, 001=MTG




NSL Implementation in 1-Hot Method

- In one-hot assignment, NSL is designed by simple observation
- For each state, examine each incoming transition
 - Each incoming arrow will be one case in our logic
 - We can just OR each condition together
- Describe each transition as a combination of what state it originates from & any associated conditions
- Ex. Two arrows converge on MS: "Q_{MS} should be '1' on the next clock when...
 - Current state is MT ...OR...
 - Current stat is SS AND S=0

 


	Q _{SS}	Q _{MT}	Q _{MS}
SS	1	0	0
MT	0	1	0
MS	0	0	1

One-hot State Assignment

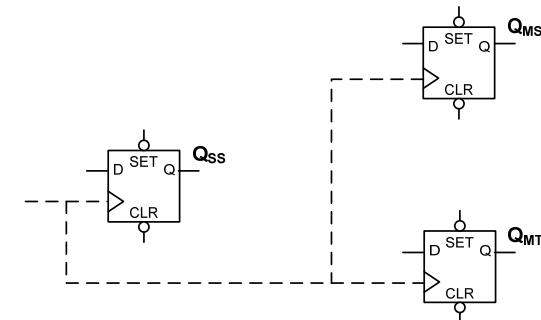

NSL Implementation in 1-Hot Method

 - Two arrows converge on MS: "Q_{MS} should be '1' on the next clock when..."
 - Current state is MT ...OR...
 - Current state is SS AND S=0



	Q _{SS}	Q _{MT}	Q _{MS}
SS	1	0	0
MT	0	1	0
MS	0	0	1


One-hot State Assignment

• $Q^*_{MS} = D_{MS} = Q_{MT} + Q_{SS} \bullet S'$

• $Q^*_{MT} = D_{MT} =$



• $Q^*_{SS} = D_{SS} =$

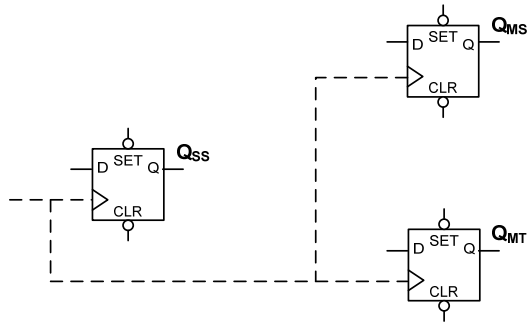- What about initial state? Preset the appropriate flop.




Illustrative Example

- Consider the following state diagram

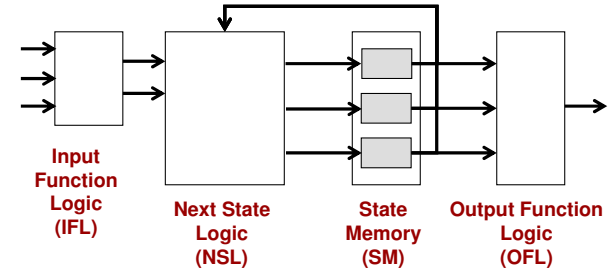 

State Assignment & NSL

 - Let us choose a one-hot state assignment (one FF per state)



- Next State Equations:


– $D_1 = Q_1^* =$

– $D_p = Q_p^* =$

– $D_d = Q_d^* =$



IFL, NSL, & OFL

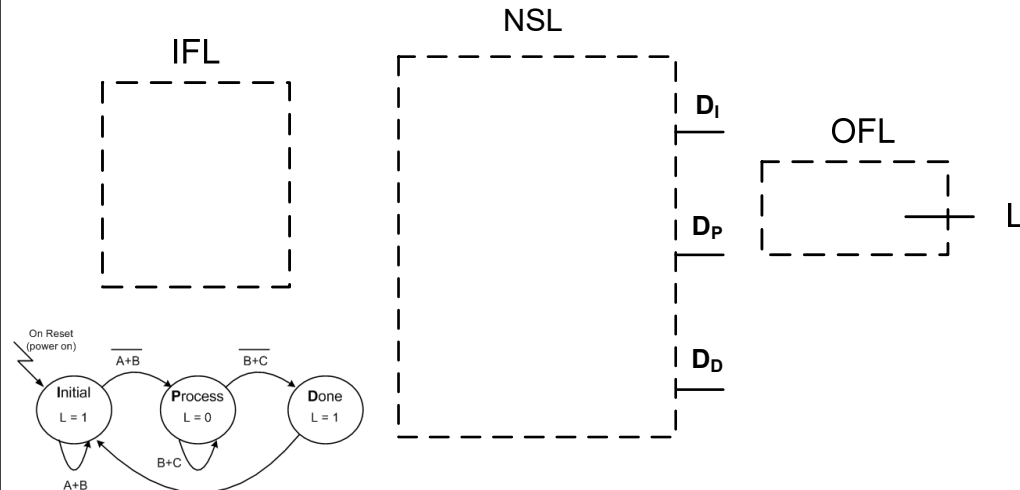- Now we can draw the logic for each section





Waveform

  - Recall, $X = A+B$ and $Y = B + C$
- L is a combinational function of the current state



State Assignment & NSL

  - Let us choose a one-hot state assignment (one FF per state)




- Next State Equations:

$$\begin{aligned}
 - D_I &= Q_I^* = Q_I \cdot (A+B) + Q_D \\
 - D_P &= Q_P^* = Q_P \cdot (B+C) + Q_I \cdot (A+B)' \\
 - D_D &= Q_D^* = Q_P \cdot (B+C)'
 \end{aligned}$$



IFL, NSL, & OFL

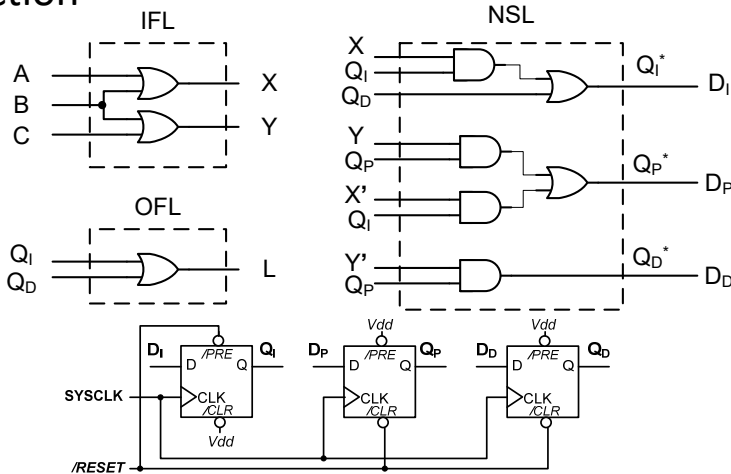- Now we can easily draw the logic for each section



Waveform

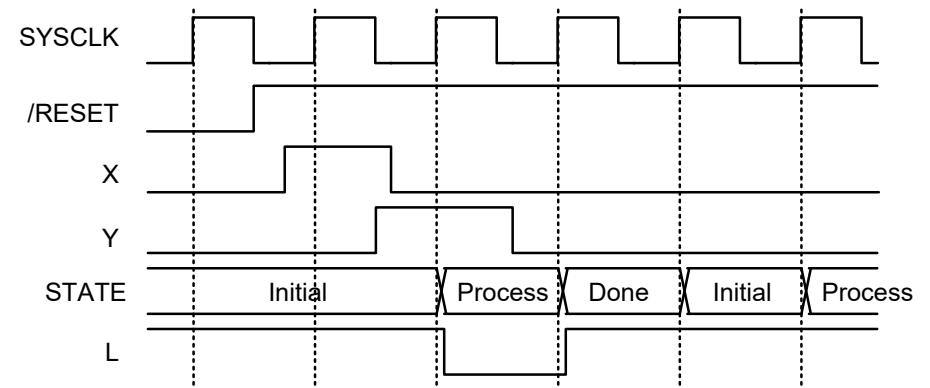 - Recall, $X = A+B$ and $Y = B + C$
- L is a combinational function of the current state



State Machine Summary

- 4 sections of state machine circuitry: _____
- In one-hot state encoding, a system with 5 states requires _____ flip-flops (_____ flip-flops per _____)
- In an encoded state encoding, a system with 5 states requires _____ flip-flops (_____ FF's for n states)
- When designing the NSL for a state, enumerate the conditions associated with the **(incoming/outgoing)** transitions to that state
- To implement the power-on reset condition in a one-hot state encoding, connect the RESET signal to the _____ input for the _____ FF associated with the initial state, and to the _____ signals of the other FF(s).

Mealy- vs. Moore-style outputs

STATE MACHINE OUTPUTS

State Machine Outputs

- State Machine outputs can be classified according to how the outputs are produced

– If $Outputs = f(current\ state, other\ inputs)...$


_____ -Style

– If $Outputs = f(current\ state)...$

_____ -Style

Moore-Style Outputs

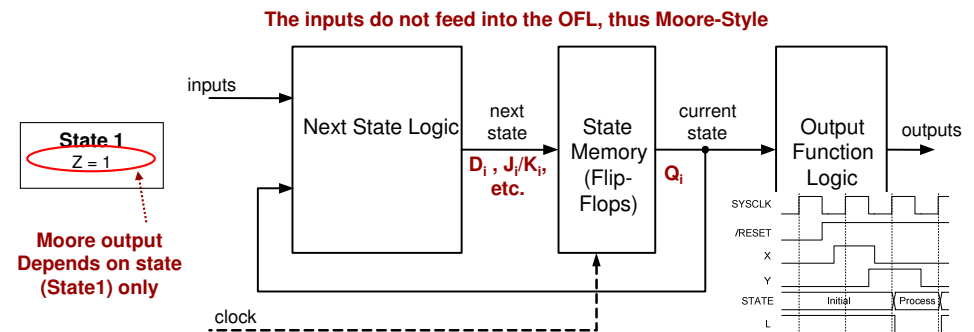
- Moore-style outputs only depend on the current state
- Thus, they are valid _____ in the clock cycle and **stay** _____ nearly the entire
- Often requires extra states compared to Mealy-style implementations



Mealy-Style Outputs

- Mealy-style outputs depend not only on the current state but the external inputs
- Thus, they may not be valid until _____ in the clock cycle and **may** _____ during the cycle if the inputs change

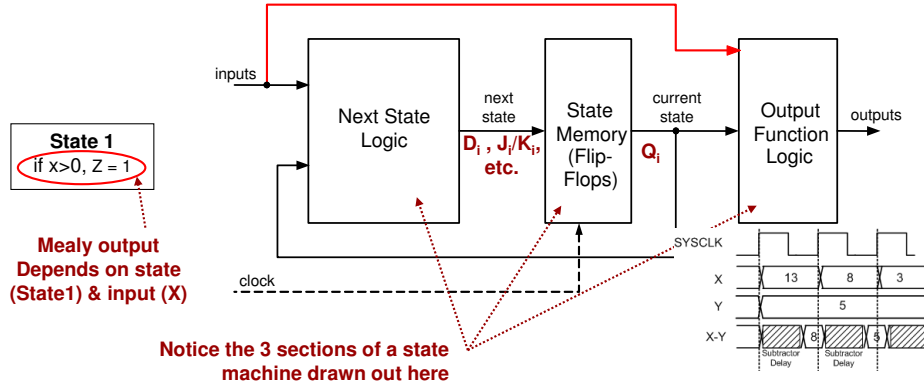The inputs feed into the output function logic, thus Mealy



Mealy vs. Moore Update

- Consider the update/loading of a register, X, with X-25
- Need to generate an X_LOAD signal
 - Can be Moore or Mealy-style




Divider

- Consider design of a sequential divider, (X / Y)
- Algorithm:
 - Repeatedly subtract Y from X while X-Y ≥ 0 (or really X ≥ Y).
 - Quotient, Q, is simply how many subtractions were performed (i.e. count how many times we performed X=X-Y)
 - Use a subtractor to compute X-Y (if subtractor needs to borrow, then we know X-Y < 0 (or really X < Y))
- Sample Operation: X = 13, Y = 5
 - Q = 0
 - X = X - Y = 13 - 5 = 8, Q = 1
 - X = X - Y = 8 - 5 = 3, Q = 2
 - Remainder = X = 3


Divider Datapath

- Datapath for Divider

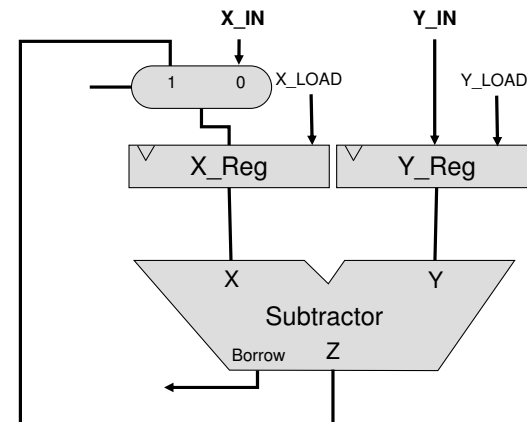

Divider Control Unit

 
- Complete the state diagram
 - What is the logic for X_Load



Mealy vs. Moore Comparison


Moore Implementation

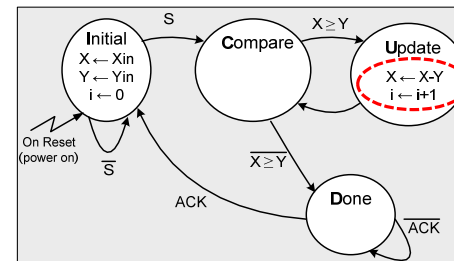- We need to compare X with Y to determine if we should increment our quotient and update X
- If we want Moore-style enable and increment signals, we need a separate compare & update state




Mealy Implementation

 - In a Mealy-style implementation we can compare and use the result to produce the enable and increment signals in the same clock



Mealy Timing

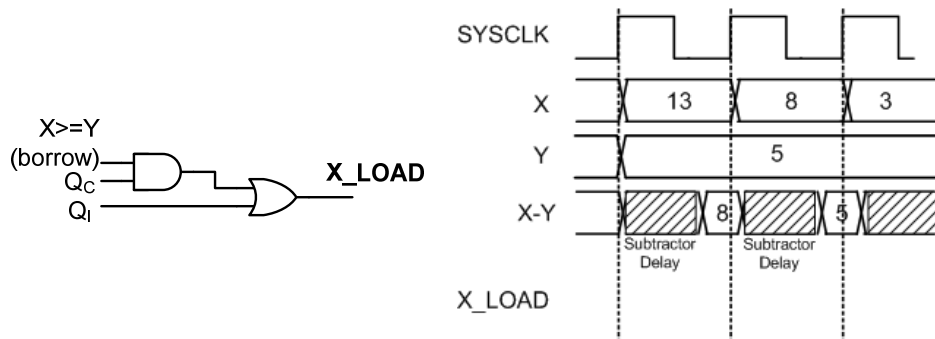- In Mealy-style implementation, we must ensure the clock is long enough for control signals to be produced



Control Signal Timing

- When identifying control signals in the datapath, be sure to consider if the signal should be valid

–“During the clock”

- Must be valid shortly after the beginning of the clock (e.g. mux selects, etc.)
- Usually must be produced as Moore-style output or fast, Mealy output

–“At the end of the clock”


- Must be valid by the end of the clock (e.g. register load enables)
- Can be produced by combo logic in datapath

Datapath Design Example

- Design a datapath to support the following RTL (Register Transfer Level) operations
 - Identify the control signals & other datapath components


Desired Operations:

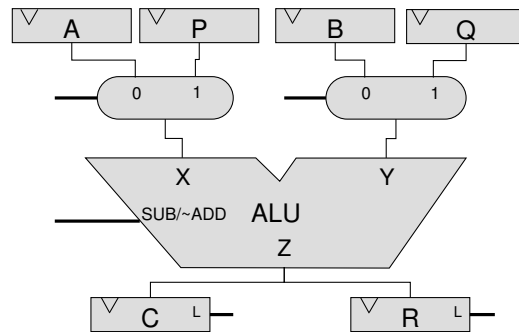- $C \leftarrow A+B$, if $F,G=0,0$
- $C \leftarrow A-B$, if $F,G=0,1$
- $R \leftarrow P+Q$, if $F,G=1,0$
- $R \leftarrow P-Q$, if $F,G=1,1$



Divider Datapath

- Datapath for Divider

 

MIN/MAX FINDER


- Sixteen 4-bit unsigned numbers are stored in a 16x4 (16 rows/addresses of 4-bits each)
- Iterate over all numbers and determine the maximum (largest) and minimum (smallest) number
- First implement assuming (2) 4-bit comparators are available
- Repeat the implementation assuming (1) 4-bit comparator is available
- Remember in HW we try to perform as many operations in parallel as possible to achieve speed (e.g. perform iteration counter increment in same clock as iteration)
- How many clocks do you think we need?

	0	1	2	3	4	5	6
data	30	51	52	53	54	10	21

```
int min = data[0];
int max = data[0];
for(int i=1; i < N; i++)
{
    if(data[i] < min)
        min = data[i];
    if(data[i] > max)
        max = data[i];
}
```

Datapath Components

 
- The datapath requires...
 - Two comparators (as per our first implementation description)
 - A 16x4 memory
 - _____
 - _____




Datapath Components

- Algorithm
 - After a START signal is applied, load the zero-th (0-th) number in the memory in both MAX and MIN registers.
 - Enter an iterative loop for the first thru fifteenth numbers with both the current known MAX and MIN values, updating the registers appropriately
 - When all iterations are done (or about to be done?) go to a DONE state
- Draw a flow chart or state diagram

Flow Chart

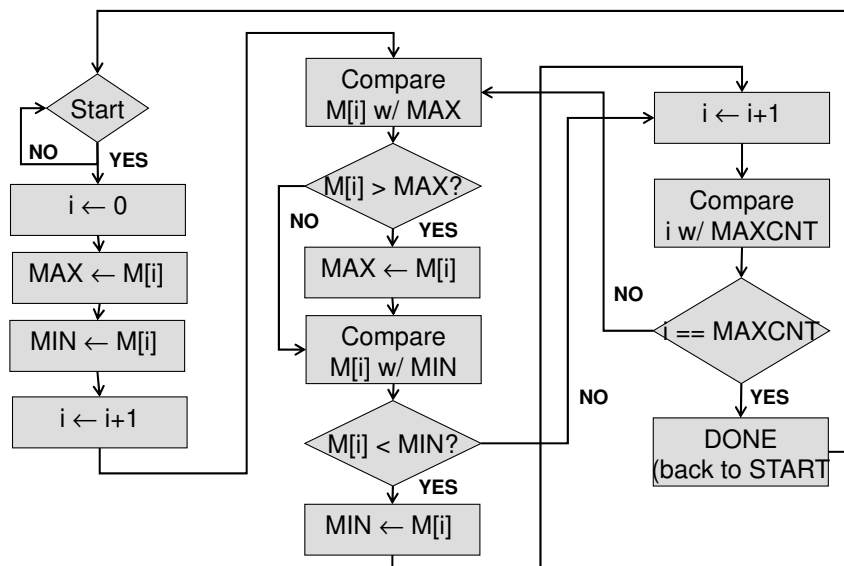

MinMax Control Unit

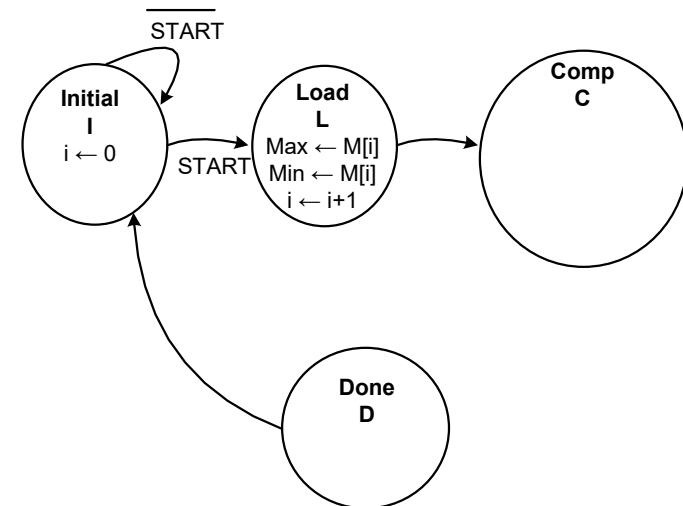


Add transition conditions Comp state operations

Control Signal Timing Example

- Consider the following statement of building a counter such that i increments ($i \leftarrow i+1$) on each clock
 - (During the clock / At the end of the clock) you enable the counter so that (during the clock / at the end of the clock) it actually increments
- Consider designing a minutes & seconds counter circuit with separate counters for each
 - Option 1:** After 60 seconds (during 61st second) enable the minutes counter
 - Option 2:** During the 60th second (after 59 seconds) enable the minutes counter


Early or Late?

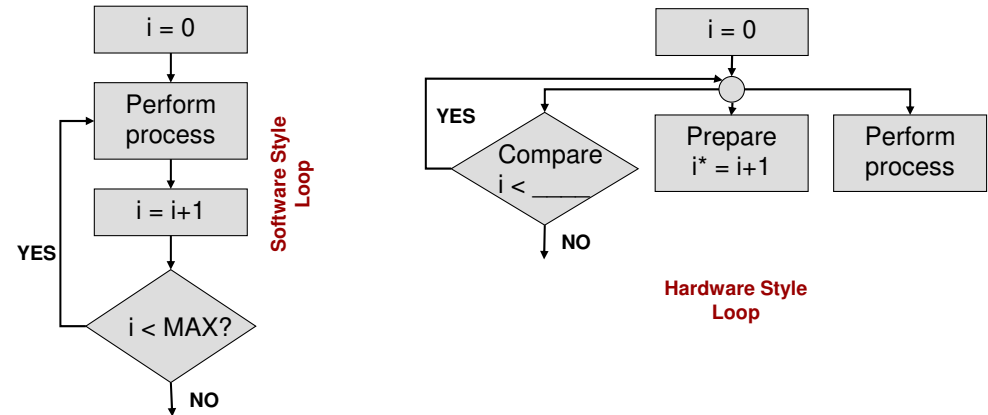- Consider a counting loop to iterate MAX times
- In hardware we try to perform as many operations in parallel as possible
- To iterate MAX times, what should we compare with i ?




1 Comparator Datapath

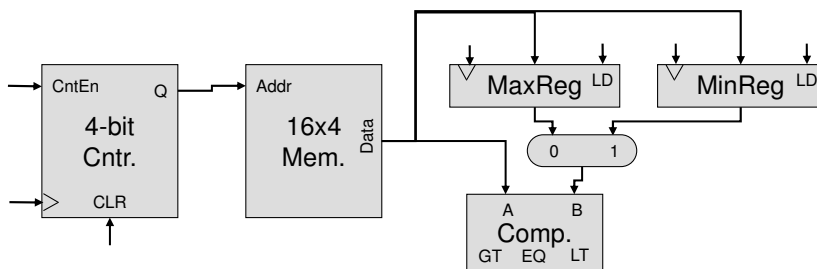- The datapath now requires...
 - One comparator
 - A 16x4 memory
 - (2) registers to store current min / max
 - (1) 4-bit counter to counter iterations & address memory




1-Comparator Implementation

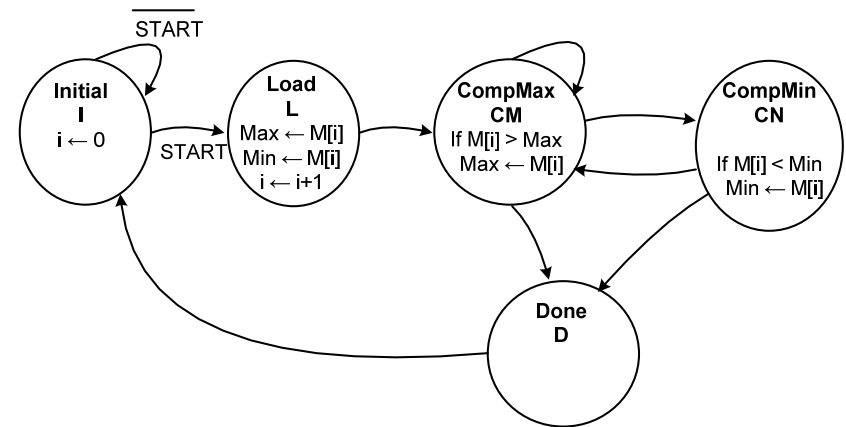

Add transition conditions and add counter increment statements

Transition Conditions


 
- Is there any relationship between conditions associated with incoming transitions or outgoing transitions?
- Outgoing transitions must be
 - _____ (____ conditions true)
 - _____ (____ conditions true)



Example: Vote Counting Machine

  1.1 Majority vote for a 5-vote case: In your homework #8, you have designed a state machine to inspect *four votes* serially to find majority vote. This is a similar problem with *FIVE votes* instead of *FOUR votes*. Majority means *three YES votes* in the five-vote case also. The six states are:


- I = INITIAL
- C = COUNTING votes
- C1N = continuing COUNTING votes after seeing one (1) NO vote
- C2N = continuing COUNTING votes after seeing two (2) NO votes
- W = WON the majority vote
- L = LOST the majority vote



Complete the state diagram.

Vote State Machine Conditions

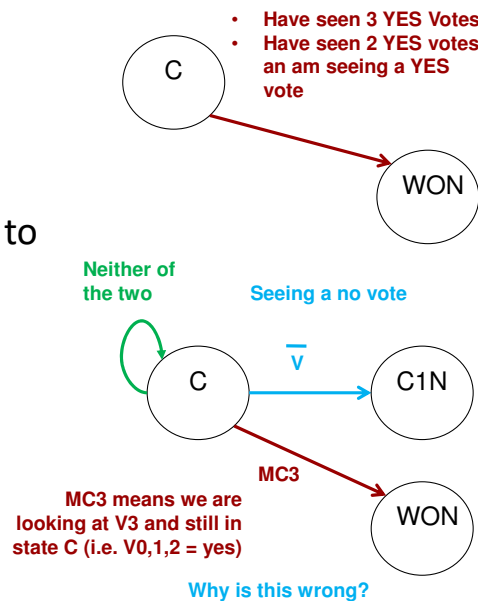- Remain in C until...
 - Find a NO vote...
 - ...then go to C1N
 - Have enough YES votes to guarantee victory...
 - ...then go to WON



Control / Datapath Interaction

- We have used the analogy of the control unit as a manager and datapath as workers
- Consider the DPU as individual workers (plumbers, electricians,...) who need to be told what to do each hour (each clock cycle)
- The control unit uses the current state (updated each clock cycle) to determine what work (control signals) should be performed each hour (clock cycle)
- Control signals generated by state machines may fall into one of two sets:
 - Mealy-style outputs
 - Moore-style outputs

Control Output Summary



- A _____-style output is conditioned upon the current state AND other input signals
- A _____-style output is conditioned only upon the current state
- In synchronous digital systems, you must prepare a control signal _____ so the effect takes place at the _____ (beginning of next clock)

TRI-STATE OUTPUTS & BUSES

Typical Logic Gate


- Gates can output two values: 0 & 1
 - Logic '1' (Vdd = 3V), or Logic '0' (Vss = GND)
- Analogy: a sink faucet
 - 2 possibilities: Hot ('1') or Cold ('0')
- Inputs cause *EITHER* a pathway from output to VDD *OR* VSS

Hot Water = Logic 1
Cold Water = Logic 0

 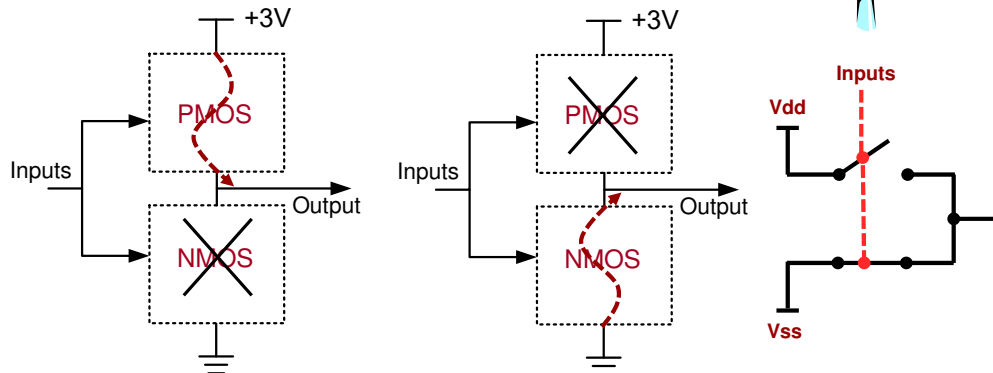


Output Connections

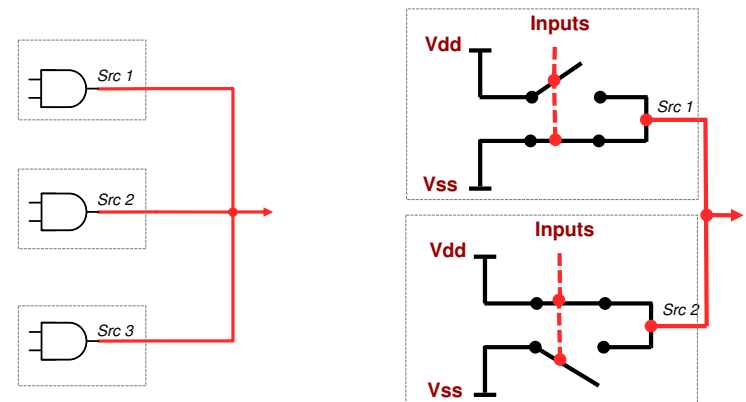- Can we connect the output of two logic gates together?




Tri-State Buffers

 - Gates can output two values: 0 & 1
 - Logic 0 = 0 volts
 - Logic 1 = 5 volts
- Tristate buffers can output a third value:
 - _____ = _____
(no connection to any voltage source)
- Analogy: a sink faucet
 - 3 possibilities:
 - Hot water,
 - Cold water,
 - _____



Tri-State Buffers

 
- Tri-state buffers have an extra enable input
- When disabled, output is Z
- When enabled, normal buffer



En	In	Out
0	x	Z
1	0	0
1	1	1


Tri-State Buffers

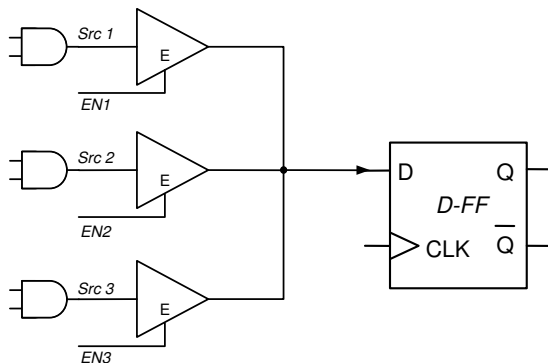- We use tri-state buffers to share one output amongst several sources
- Rule: _____



Tri-State Buffers

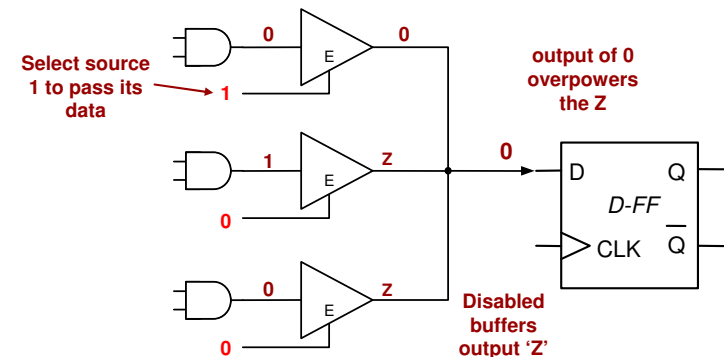
- We use tri-state buffers to share one output amongst several sources
- When 1 buffer enabled, its output overpowers the Z's (no connection) from the other gates



Communication Connections


- Multiple entities need to communicate
- We could use
 - Point-to-point connections
 - A _____

Separate point to point connections

 

Bidirectional Bus

 - ___ transmitter (otherwise bus contention)
- N receivers




Tri-State Buffer / Bussing Summary

- Provide a 3rd output value: _____
- Allows multiple outputs to be wired together
- Only _____ bus driver can be enabled at a time


MICROARCHITECTURE EXAMPLE

Digital Design Goals

 - Digital systems seek to optimize a design along these three axes:
 - Area (size)
 - Speed
 - Power Consumption
- Can often only optimize one or two of these without sacrificing the other(s)
 - Just as in software design, there is a classic time/space trade-off
 - Microarchitecture can determine where a design falls in this trade space



Different Architectures

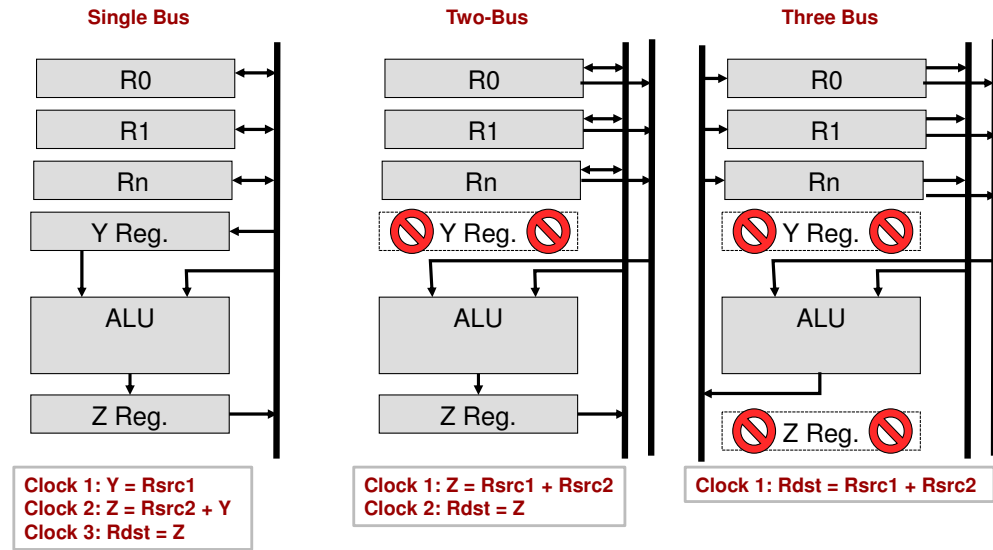

General Implications: Less Resources => More Clock Cycles (Time)