

# EE 457 Unit 5

## Single Cycle CPU Datapath and Control

1

# CPU Organization Scope

- We will build a CPU to implement our subset of the MIPS ISA
  - Memory Reference Instructions:
    - Load Word (LW)
    - Store Word (SW)
  - Arithmetic and Logic Instructions:
    - ADD, SUB, AND, OR, SLT
  - Branch and Jump Instructions:
    - Branch if equal (BEQ)
    - Jump unconditional (J)
- These basic instructions exercise a majority of the necessary datapath and control logic for a more complete implementation

2

# CPU Implementations

- We will go through two implementations
  - Single-cycle CPU ( $CPI = 1$ )
    - All instructions execute in a single, long clock cycle
  - Multi-cycle CPU ( $CPI = n$ )
    - Instructions can take a different number of *short* clock cycles to execute
- Recall that a program execution time is:
 
$$(\text{Instruction count}) \times (\text{CPI}) \times (\text{Clock cycle time})$$
  - In single-cycle implementation *cycle time* must be set for longest instruction thus requiring shorter instructions to wait
  - Multi-cycle implementation breaks logic into sub-operations each taking one *short clock cycle*; then each instruction takes only the number of *clocks* (i.e. *CPI*) it needs

3


# Single-Cycle Datapath

- To start, let us think about what operations need to be performed for the basic instructions
- All instructions go through the following steps:
  - Fetch: Use \_\_\_\_\_ to fetch instruction
  - Decode & Register/Operand Fetch: Determine instruction type and fetch any register operands needed
- Once decoded, different instructions require different operations
  - ALU instructions: Perform Add, Sub, etc. and write result back to register
  - LW / SW: Calculate address (\_\_\_\_) and perform memory access
  - BEQ / J: Update PC (possible based on \_\_\_\_\_)
- Let us start with fetching an instruction and work our way through the necessary components

4

 
# Instruction Ordering

- Identify which components each instruction type would use and in what order: ALU-Type, LW, SW, BEQ



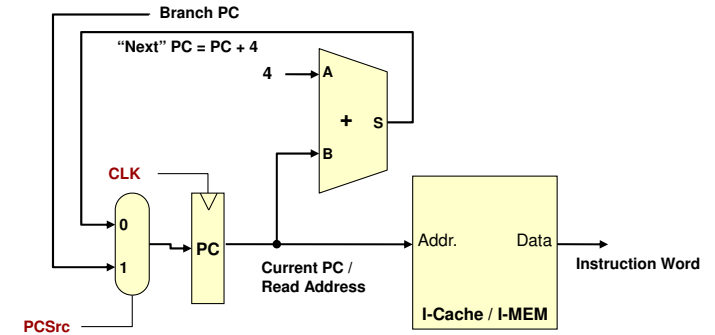
# Modified Fetch Datapath

- Below is the fetch datapath modified to support branch instructions



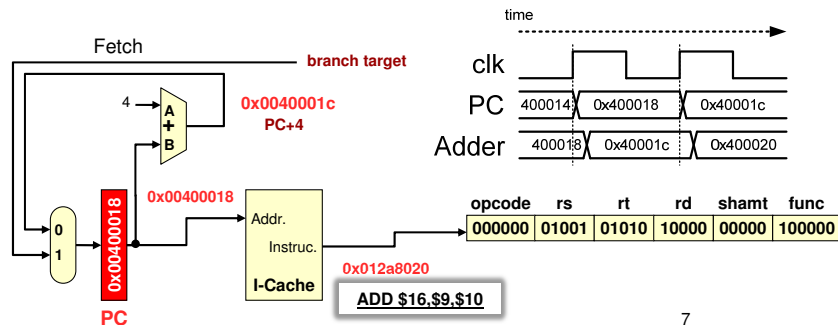
# Fetch

- Address in PC is used to fetch instruction while it is also incremented by 4 to point to the next instruction
- Remember, the PC doesn't update until the end of the clock cycle / beginning of next cycle
- Mux provides a path for branch target addresses



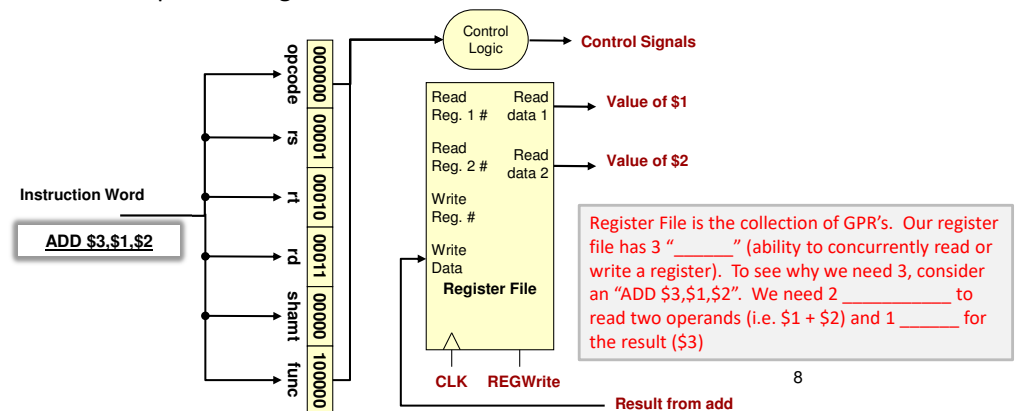
# Decode

- Opcode and func. field are decoded to produce other control signals
- Execution of an ALU instruction (ADD \$3,\$1,\$2) requires reading 2 register values and writing the result to a third
- REGWrite is an enable signal indicating the write data should be written to the specified register



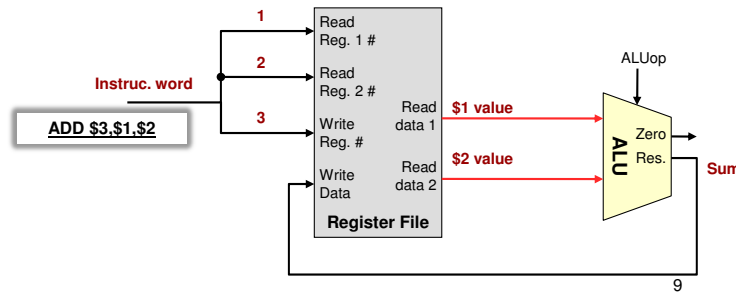
# Datapath for ALU instruction

- ALU takes inputs from register file and performs the add, sub, and, or, slt, operations
- Result is written back to dest. register



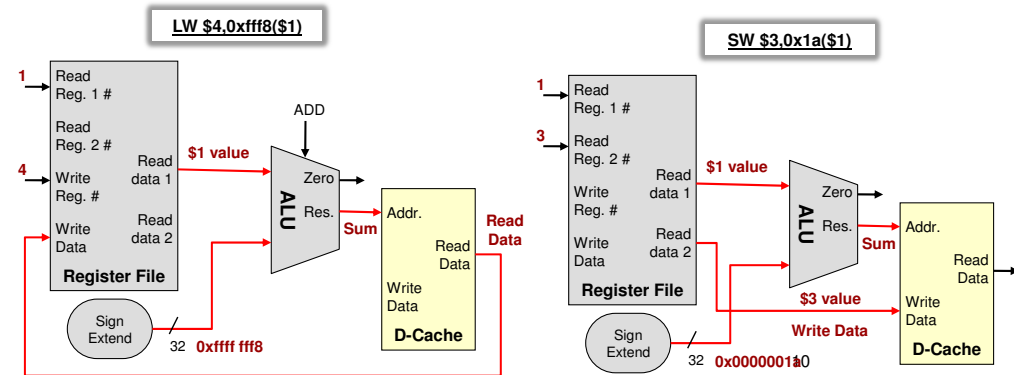
# Memory Access Datapath

- Operands are read from register file while offset is sign extended
- ALU calculates \_\_\_\_\_
- Memory access is performed
- If LW, \_\_\_\_\_


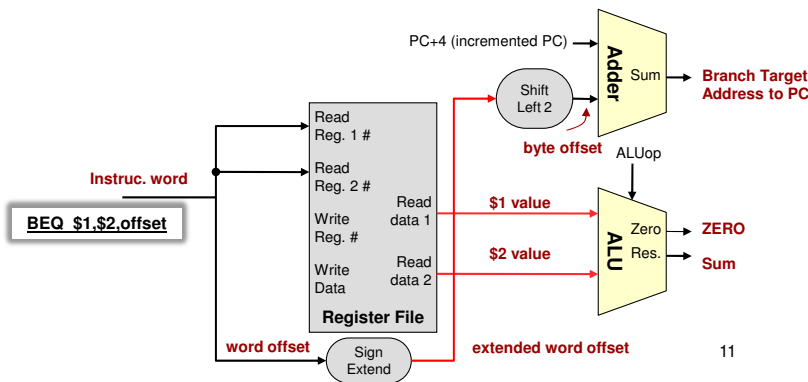
# Branch Datapath

- BEQ requires...
  - ALU for comparison (examine 'zero' output)
  - Sign extension unit for branch offset
  - Adder to add PC and offset
    - Need a separate adder since ALU is used to perform comparison




# Combining Datapaths

- Now we will take the datapaths for each instruction type and try to combine them into one
- Anywhere we have multiple options for a certain input we can use a mux to select the appropriate value for the given instruction
- Select bits must be generated to control the mux
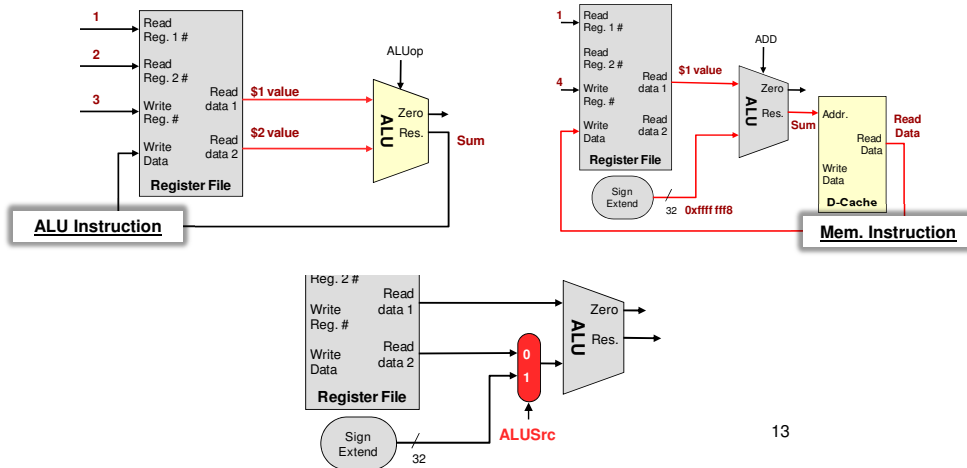
# ALUSrc Mux


- Mux controlling second input to ALU
  - ALU instruction provides Read Register 2 data to the 2<sup>nd</sup> input of ALU
  - LW/SW uses 2<sup>nd</sup> input of ALU as an offset to form effective address



13
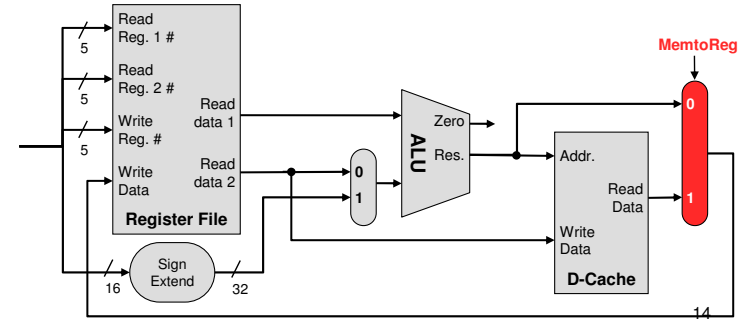
# MemtoReg Mux


- Mux controlling writeback value to register file
  - ALU instructions use the result of the ALU
  - LW uses the read data from data memory



14
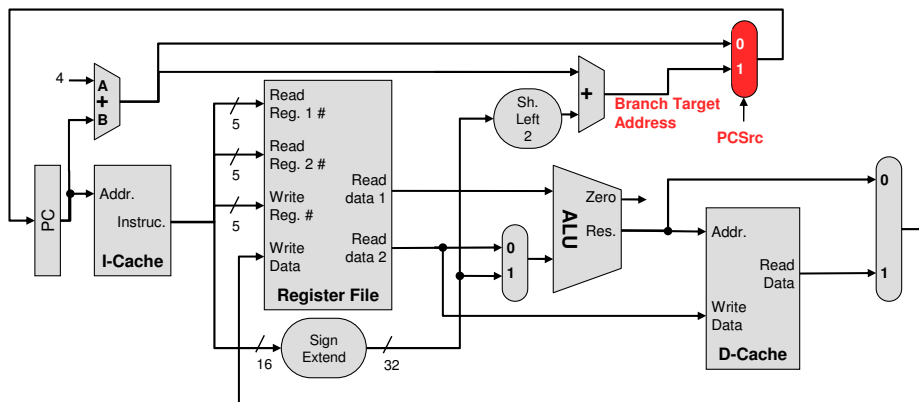
# PCSrc Mux



- Next instruction can either be at the next sequential address (PC+4) or the branch target address (PC+offset)




15
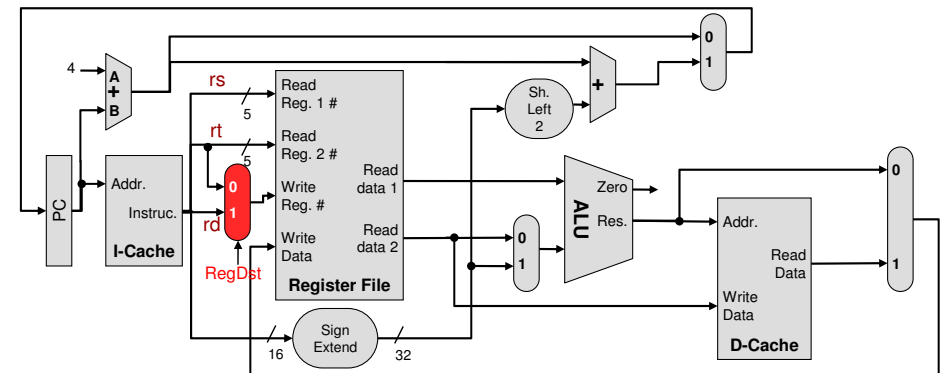 
# RegDst Mux


- Different destination register ID fields for ALU and LW instructions




# Single-Cycle CPU Datapath

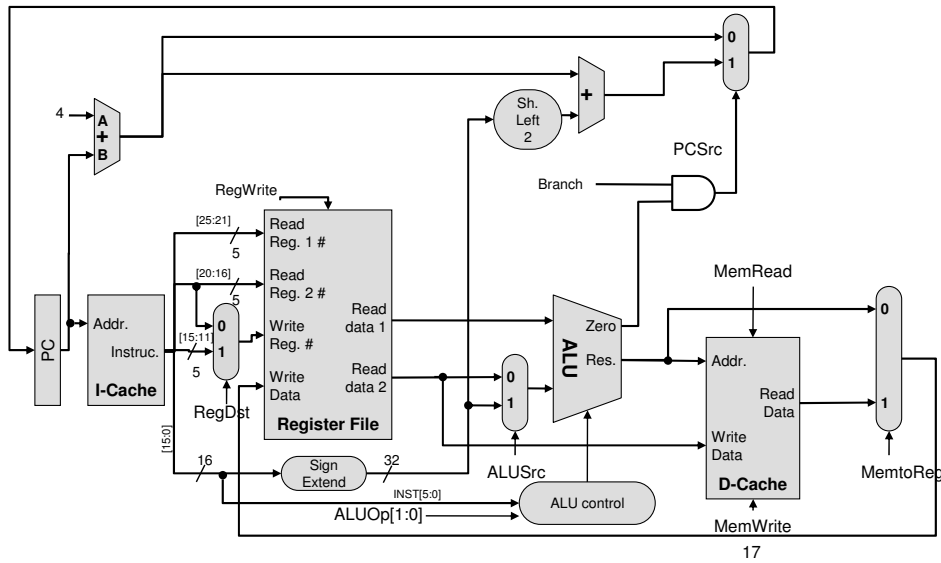

# Single-Cycle CPU Datapath

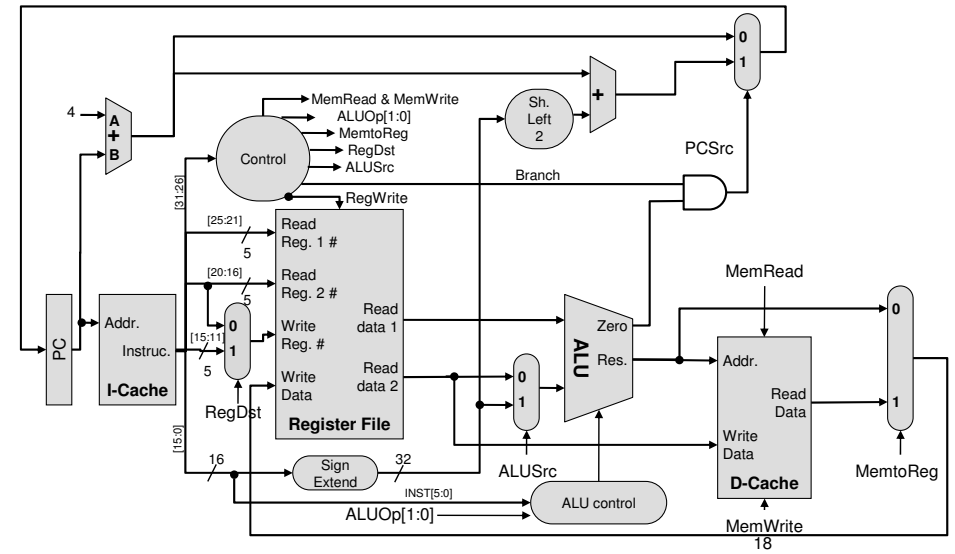


# Jump Instruc. Implementation

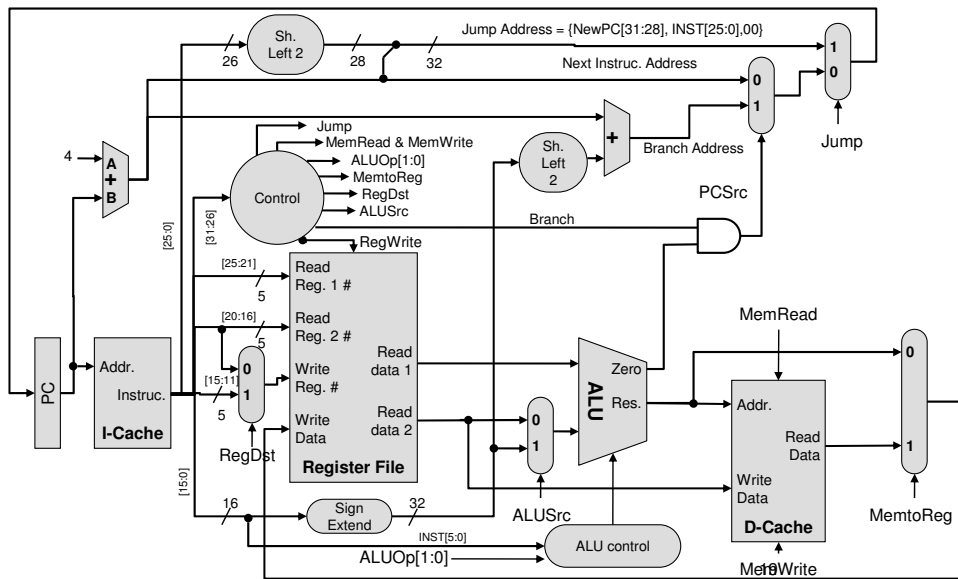


# SINGLE CYCLE CONTROL
 
## Control Unit Design for Single-Cycle CPU

- Control Unit: Maps instruction to control signals
- Traditional Control Unit
  - FSM: Produces control signals asserted at different times
  - Design NSL, SM, OFL
- Single-Cycle Control Unit
  - Every cycle we perform the same steps: Fetch, Decode, Execute
  - Signals are not necessarily time based but instruction based => only combinational logic



 
# of FF's in tightly-encoded state assignment:  
5-8 states: \_\_\_\_\_, 9-16 states: \_\_\_\_\_



Single-Cycle Control Unit  
Only 1 state => \_\_\_\_\_ FF's

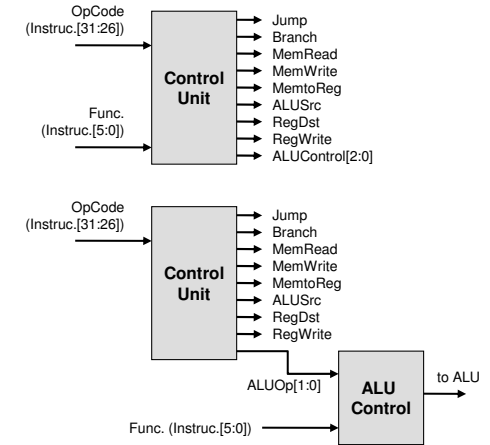
## Control Unit

- Most control signals are a function of the opcode (i.e. LW/SW, R-Type, Branch, Jump)
- ALU Control is a function of opcode AND function bits.


 
## ALU Control

- ALU Control needs to know what instruction type it is:
  - R-Type (op. depends on func. code)
  - LW/SW (op. = ADD)
  - BEQ (op. = SUB)
- Let main control unit produce ALUOp[1:0] to indicate \_\_\_\_\_, then use function bits if necessary to tell the ALU what to do



Instruction	ALUOp[1:0]
LW/SW	00
Branch	01
R-Type	10

Control unit maps instruction opcode to ALUOp[1:0] encoding

## ALU Control Truth Table



- ALUControl[2:0] is a function of: ALUOp[1:0] and Func.[5:0]

Instruc.	ALUOp[1:0]	Instruction Operation	Func.[5:0]	Desired ALU Action
LW	00	Load word	X	Add
SW	00	Store word	X	Add
Branch	01	BEQ	X	Subtract
R-Type	10	AND	100100	And
R-Type	10	OR	100101	Or
R-Type	10	Add	100000	Add
R-Type	10	Sub	100010	Subtract
R-Type	10	SLT	101010	Set on less than

Produce each ALUControl[2:0] bit from the ALUOp and Func. inputs

 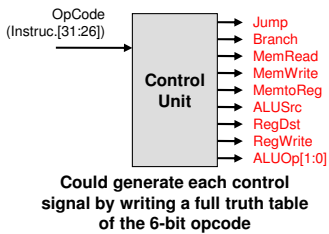
# Control Signal Generation

- Other control signals are a function of the opcode
- We could write a full truth table or (because we are only implementing a small subset of instructions) simply decode the opcodes of the specific instructions we are implementing and use those intermediate signals to generate the actual control signals




# Control Signal Truth Table

R-Type	LW	SW	BEQ	J	Jump	Branch	Reg Dst	ALU Src	Memto-Reg	Reg Write	Mem Read	Mem Write	ALU Op[1]	ALU Op[0]
1	0	0	0	0	0	0					0	0	1	0
0	1	0	0	0	0	0					1	0	0	0
0	0	1	0	0	0	0					0	1	0	0
0	0	0	1	0	0	1					0	0	0	1
0	0	0	0	1	1	X					0	0	X	X

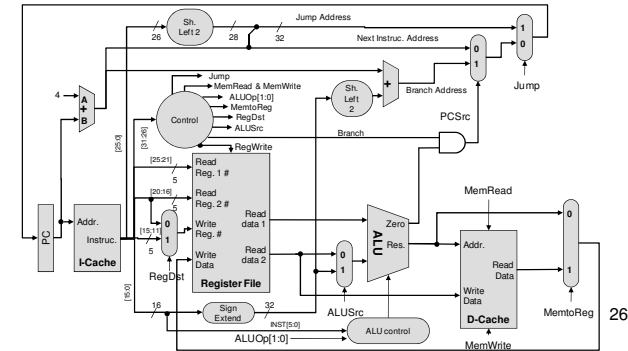


# Control Signal Logic

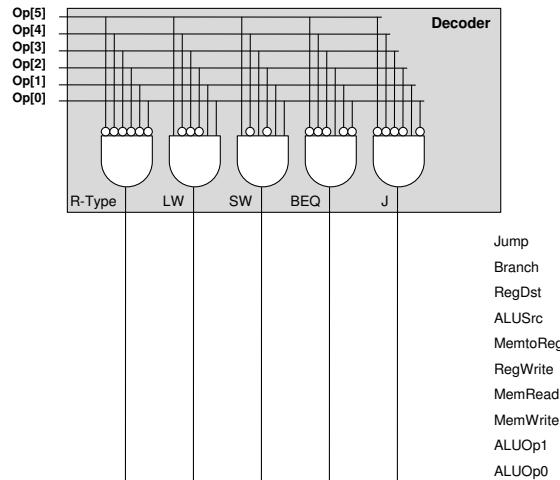

# DATAPATH QUESTIONS
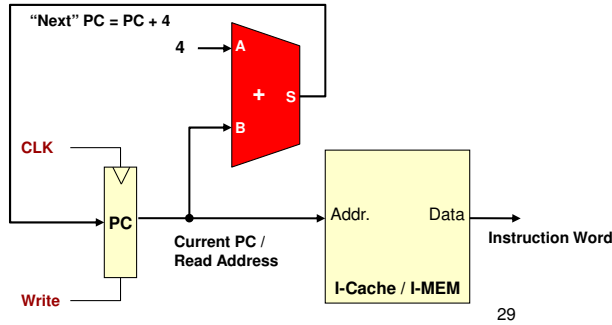
# Fetch Datapath Question 1


- Can the adder used to increment the PC be an ALU and be used/shared for ALU instructions like ADD/SUB/etc.
  - In a single-cycle CPU, \_\_\_\_\_



29
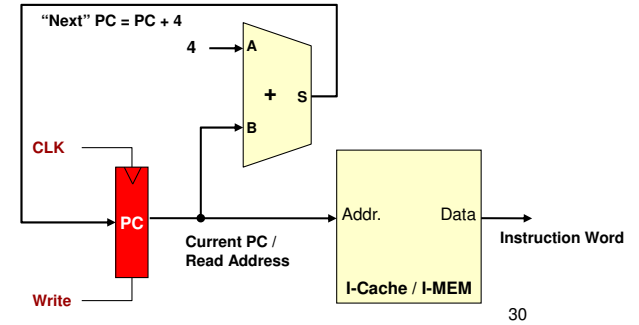
# Fetch Datapath Question 2


- Do we need the "Write" enable signal on the PC register for our single-cycle CPU?
  - In the single-cycle CPU, \_\_\_\_\_



30
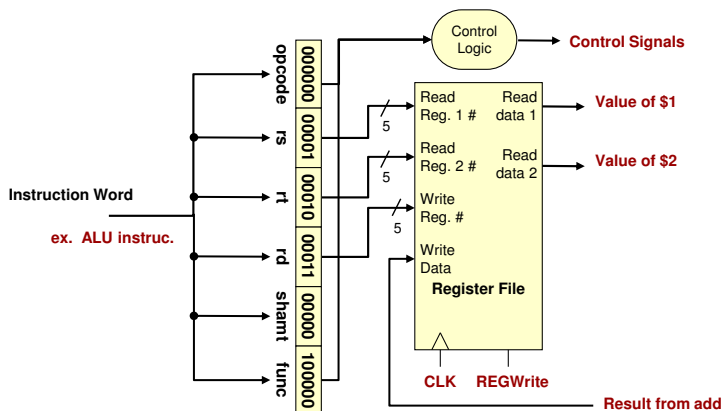
# RegFile Question 1


- Why do we need the write enable signal, REGWrite?



31
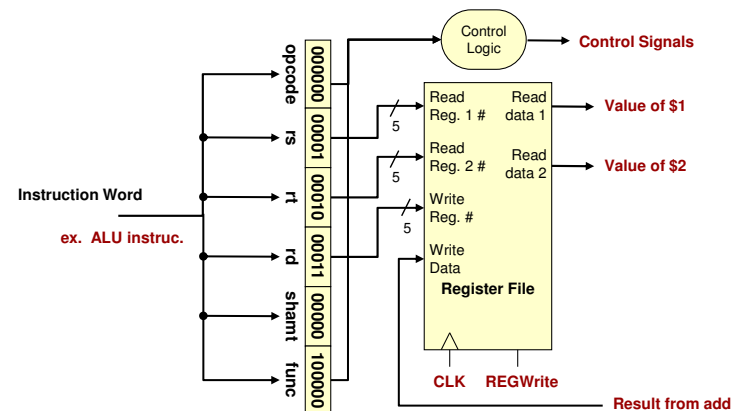
# RegFile Question 2

- Can write to registers be level sensitive or does it have to be edge-sensitive?




32


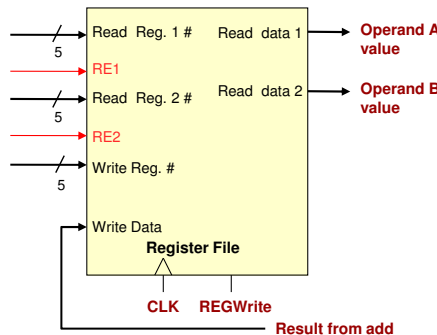
## RegFile Question 3


- Since we need a write enable, do we need read enables (i.e. RE1, RE2)



33
 
## Sign Extension Unit


- In a 'LW' or 'SW' instructions with their base register + offset format, the instruction only contains the offset as a 16-bit value
  - Example: LW \$4,-8(\$1)
  - Machine Code: 0x8c24fff8
    - 8 = 0xffff8
- The 16-bit offset must be extended to 32-bits before being added to base register



34
 
## Sign Extension Questions


- What logic is inside a sign-extension unit?
  - How do we sign extend a number?
  - Do you need a shift register?



35
 
## Data Memory Questions


- Do we need separate instruction and data memory or can we just use one (i.e. most personal computers only have one large set of RAM)?
- Do we need separate read/write address inputs or can we have just one address input used for both operations?
- Can we do away with the "read" control signal (similar to how we did away with read enables for register file)?



36
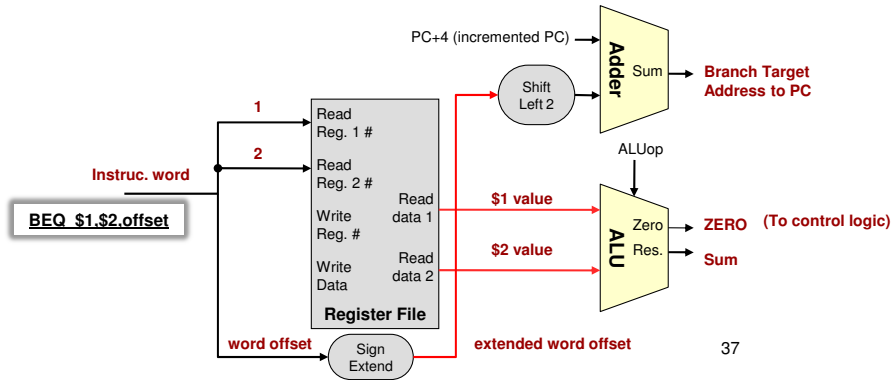
# Branch Datapath Question

- Is it okay to start adding branch offset even before determining whether the branch is taken or not?



# Credits

- These slides were derived from Gandhi Puvvada's EE 457 Class Notes