 


Design and Analysis of Testable Mutual Exclusion Elements

05/06/2015

Yang Zhang, Leandro S. Heck,
Matheus T. Moreira, David Zar, Mel Breuer,
Ney L. V. Calazans and Peter A. Beerel

- ❖ Introduction
 - ❖ MUTEX and Its Operation
 - ❖ Motivation
- ❖ Proposed Testable MUTEX (Full-Custom)
 - ❖ Structure
 - ❖ Fault Coverage
 - ❖ Testable Metastability Filter
- ❖ Proposed Testable MUTEX (Standard-Cell)
 - ❖ Structure
 - ❖ Fault Coverage
 - ❖ Testable Metastability Filter
- ❖ Experimental Results and MetaACE Analysis of Settling Times




❖ Operation

- ❖ Mutually exclusively raise grant (G0 or G1) in response to requests (R0 and R1)

❖ Metastability (MS)

- ❖ Outputs of NAND gates may stay close to $V_{dd}/2$ for an unbounded amount of time



Metastability Filter

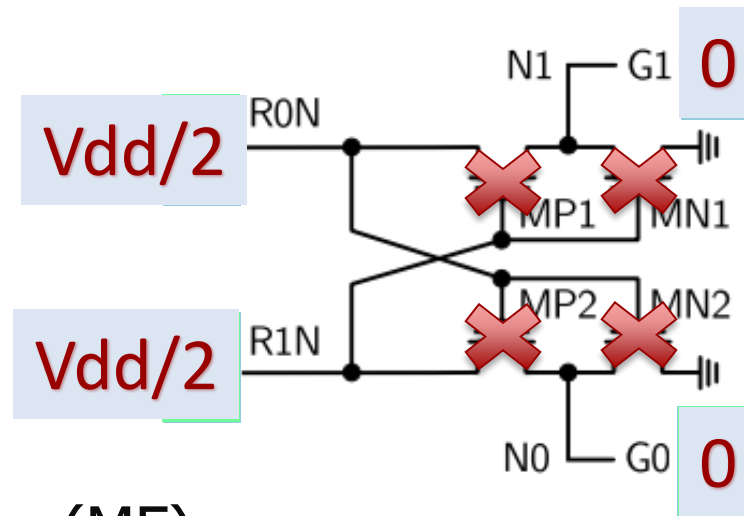

❖ Metastability Filter (MF)


- ❖ Guarantee grant outputs (G0 and G1) remain stable 0 until MS is resolved
- ❖ G0 to 1 only when R0N and R1N differ by more than V_t of PMOS transistors MP1/MP2

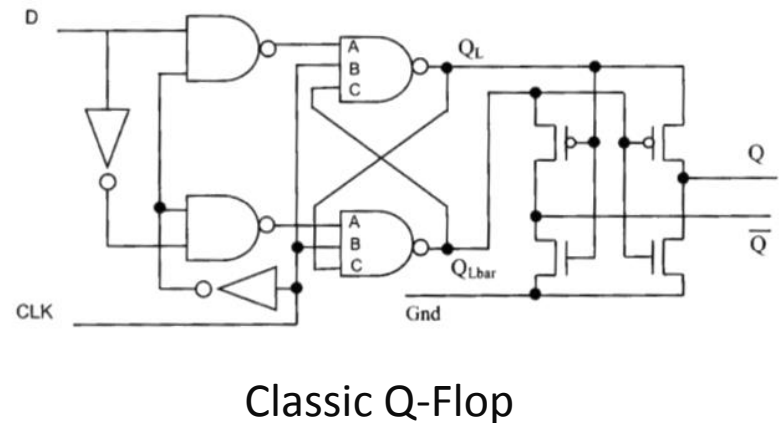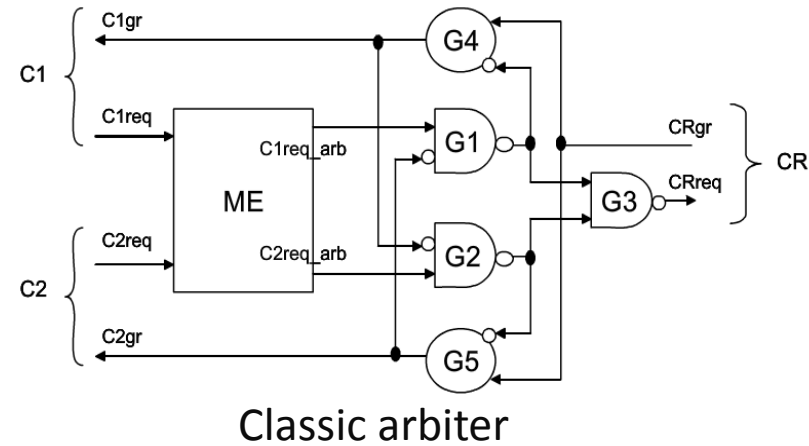- ❖ Pausable Clocking Circuits
 - ❖ Arbitrate b/w clock and pause signals
- ❖ Asynchronous Crossbar / NoC routers
 - ❖ Typically contains arbiters to decide the access to output ports
 - ❖ Arbiters contains MUTEXes
- ❖ Asynchronous Resilient Computing (Blade)
 - ❖ Relies on Q-Flop to sample error signal
 - ❖ Q-Flop contains a MUTEX
 - ❖ Async control waits for MS to resolve




- ❖ Possible outcomes of metastability
 - ❖ Metastability can delay outputs significantly
 - ❖ Failure in Metastability Filter may allow metastability to propagate
- ❖ Functional testing is not sufficient
 - ❖ Hard to guarantee testing metastability due to fs-timing required
 - ❖ Miss testing key behavior of control circuits driven by MUTEXes

Drawback 1: Undetectable Stuck-At Faults

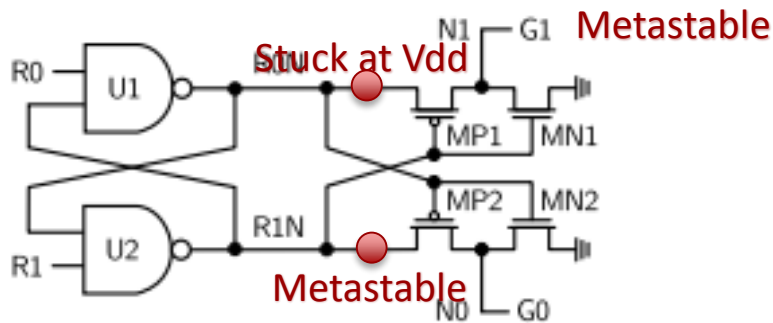

Full-custom MUTEX design

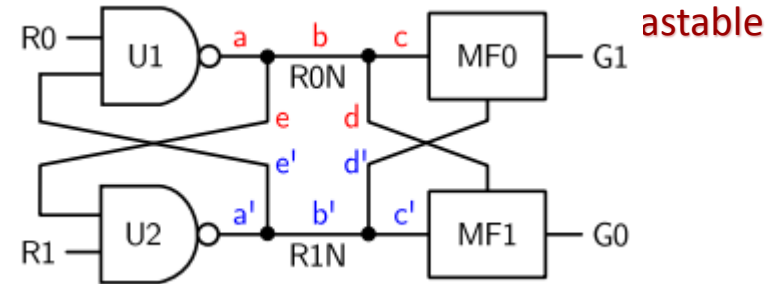


Gate-level model

Node	Test	Detectable	Test Vector {R0, R1}	Fault-free Output {G0, G1}	Faulty Output {G0, G1}
R0	SA0	Yes	{1, 0}	{1, 0}	{0, 0}
R0	SA1	Yes	{0, 0}	{0, 0}	{1, 0}
c	SA0	Yes	{0, 1}	{0, 1}	{0, 0}
c	SA1	No	-	-	-
c'	SA0	Yes	{1, 0}	{1, 0}	{0, 0}
c'	SA1	No	-	-	-
⋮					


Stuck-At Fault Analysis for FC-MUTEX

- ❖ Two SAFs not detected
- ❖ Nodes c and c' stuck-at-1

Drawback 2: Non-testable MS Filter

 


Full-custom MUTEX design

 


Gate-level Model

- ❖ No single test vector generates prolonged metastability
- ❖ Test vector pair $(R0, R1) = (0,0) \rightarrow (1,1)$
 - ❖ May generate MS but depends on exact input timing
 - ❖ May be short-lived

Proposed Testable MUTEX (Full-Custom)

 


 - ❖ Two inverters U5 and U6 added
- ❖ Isolates MS nodes
- ❖ Two PMOS MP5 and MP6 added
- ❖ Helps test metastability filter



Layout (STM 65nm)

- ❖ Forces MS when $R0=R1=M=0$

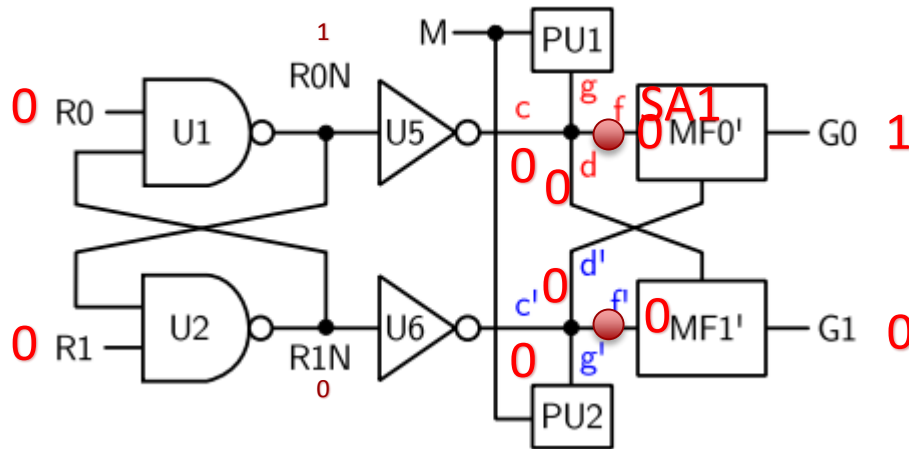


- ❖ The marked SA1 faults are undetectable in classic MUTEX
- ❖ Now they become testable!

Node	Test	Detectable	Test Vector {R0, R1, M}	Fault-free Output {G0, G1}	Faulty Output {G0, G1}
R0	SA0	Yes	{1, 0, 1}	{1, 0}	{0, 0}
R0	SA1	Yes	{0, 0, 1}	{0, 0}	{1, 0}
f	SA0	Yes	{1, 0, 1}	{1, 0}	{0, 0}
f	SA1	Yes	{0, 0, 1}	{0, 0}	{1, 0}
f'	SA0	Yes	{0, 1, 1}	{0, 1}	{0, 0}
f'	SA1	Yes	{0, 0, 1}	{0, 0}	{0, 1}

⋮

Floating Output Problem and Solution

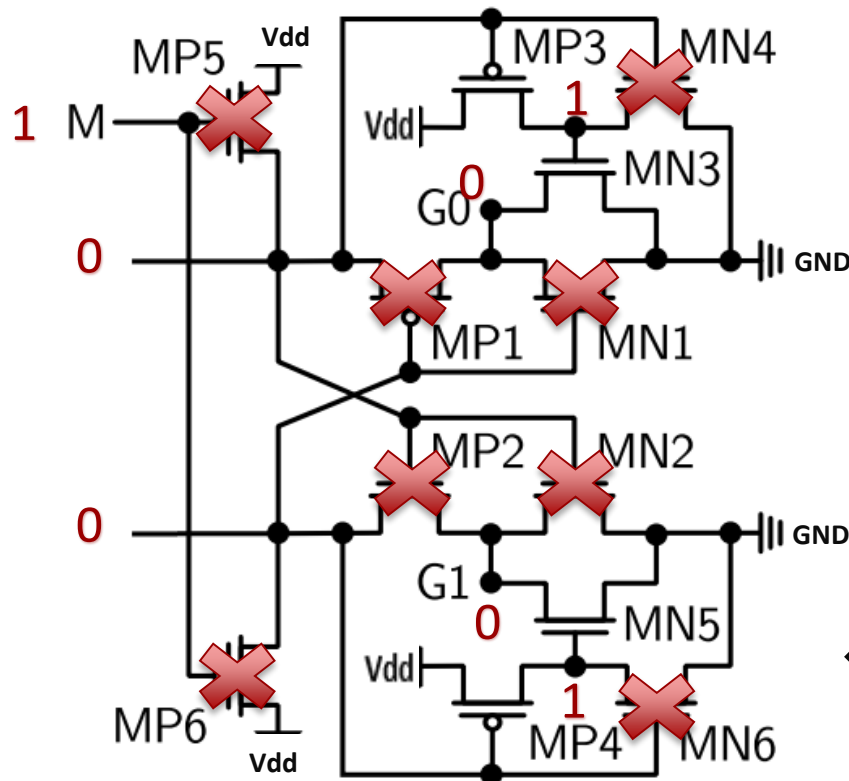

- ❖ The Problem: G0 and G1 may float

- ❖ $\{R0, R1, M\} = \{0, 0, 1\}$

- ❖ MF inputs are 0

- ❖ MP1, MN1, MP2, MN2 are in cut-off state

- ❖ G0 and G1 float


- ❖ The Solution for floating G0

- ❖ Add MP3, MN3 and MN4

- ❖ Forces a strong 0 on G0


- ❖ Same solution for node G1

Testable Metastability Filter

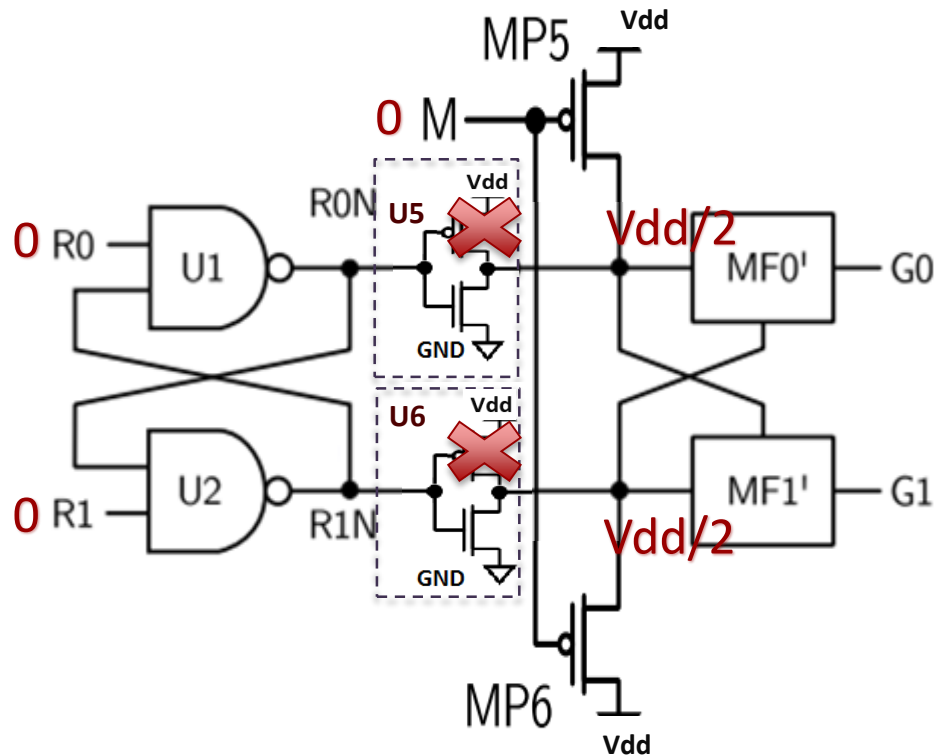


❖ The input of MS filter is $\sim V_{dd}/2$ when $M = 0$ and input of $U5 = 1$

Proposed Testable MUTEX (Standard-Cell)

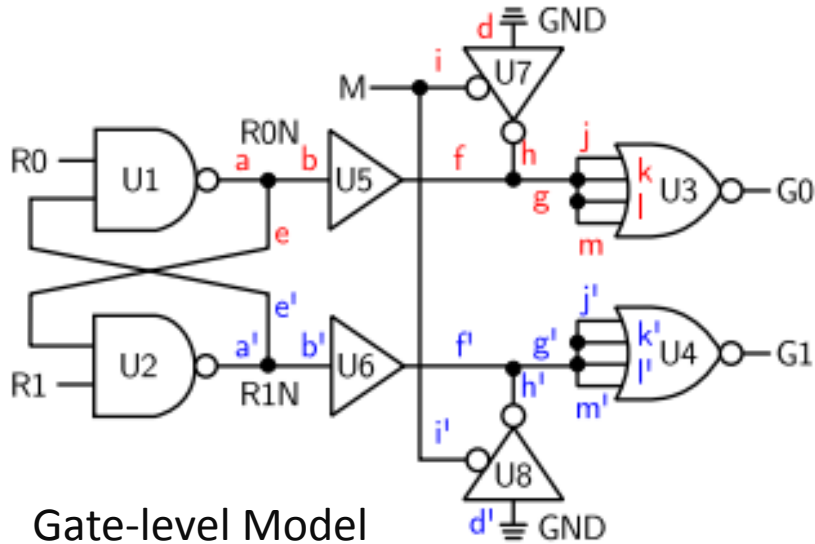


 - ❖ Two tri-state inverters U7 and U8 added
 - ❖ Help test metastability filter
- ❖ Two buffers U5 and U6 added
 - ❖ Isolate metastable nodes
 - ❖ Help test metastability filter



Layout (STM 65nm)

Fault Coverage


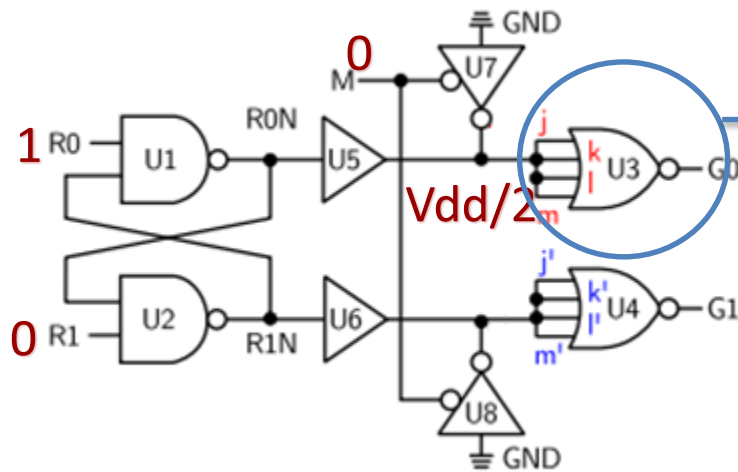


Stuck at 0

Vdd/2

Vdd/2

Vdd/2

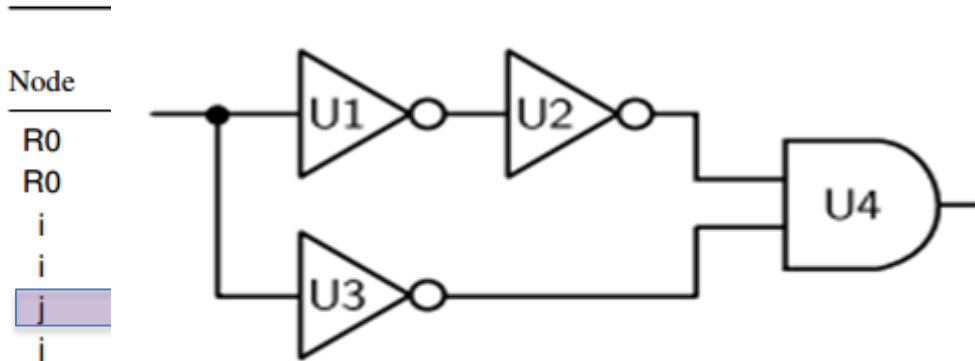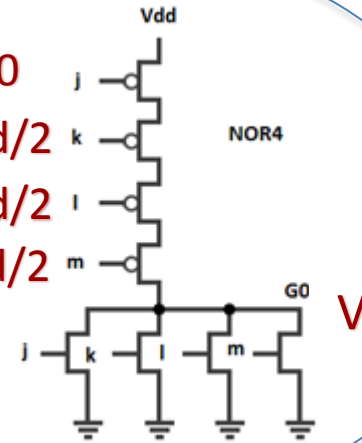


Metastability Detector [Ernst, 2003]

Node	Output
R0	0, G1
R0	0, 0
i	1, 0
i	0, 0
j	1, 0
j	V, 0
j	0, 0

- ❖ G0=0 when NOR4 inputs are Vdd/2
- ❖ If one of inputs is SA0, voltage of G0 will increase
- ❖ May be detected by a metastability detector

Standard Cell
Testable MUTEX

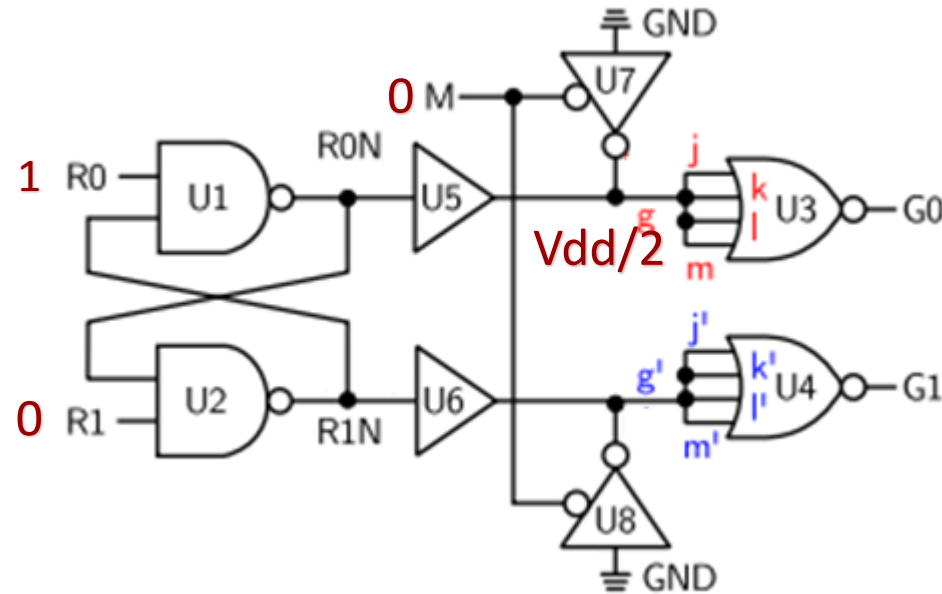

- ❖ The input of MS filter (NOR4) is $\sim V_{dd}/2$ when $M=0$ and input of $U5=0$

Experimental Results - Overheads

ENERGY, LEAKAGE POWER, DELAY AND AREA TRADE-OFFS FOR MUTEXES.

Designs	Avg EPT	Avg Leak. Power	Avg t_{pd}	Avg Tran. Delay	Area
FC-MUTEX	4.81 fJ	117.83 nW	48.77 ps	16.64 ps	9.36 μm^2
DFT-FC-MUTEX	5.99 fJ	231.59 nW	44.53 ps	32.64 ps	13.52 μm^2
<i>Overhead</i>	<i>25%</i>	<i>97%</i>	<i>-9%</i>	<i>96%</i>	<i>44%</i>
SC-MUTEX	3.02 fJ	71.45 nW	61.09 ps	70.96 ps	9.88 μm^2
DFT-SC-MUTEX	5.76 fJ	163.81 nW	86.33 ps	72.80 ps	17.16 μm^2
<i>Overhead</i>	<i>91%</i>	<i>130%</i>	<i>41%</i>	<i>2%</i>	<i>74%</i>

- ❖ Proposed design introduces overheads because of added transistors
- ❖ DFT-FC-MUTEX has a smaller propagation delay than original
- ❖ DFT-SC-MUTEX has a larger propagation delay than original

Experimental Results and MTBF Analysis

Mean Time Between
Failure (MTBF) Analysis

$$MTBF = \frac{e^{t_s/\tau}}{t_w f_c f_d}$$

- τ is the resolution time constant
- t_s is the settling time in which metastability should resolve to a valid logic value
- t_w is the time window during which the MUTEX is vulnerable to metastability
- f_c and f_d are respectively the clock and data rates

*Async circuits with MUTEXes typically do not “fail”
but do instantaneously slow down*

Experimental Results - MTBF

VARIATION OF MTBF FOR SEVERAL VALUES OF t_s (TT CORNER, 1.0V AND 25°C, $f_c = 200$ MHz AND $f_d = 133$ MHz).

Designs	t_w	MTBF (years) when $t_s = N \times t_{pd}$				
		$N = 1.5$	$N = 2$	$N = 3$	$N = 5$	$N = 10$
FC-MUTEX	60.0e-12	2.2e-11	1.8e-10	1.2e-08	5.2e-05	6.7e+04
DFT-FC-MUTEX	61.2e-12	1.7e-11	1.3e-10	7.3e-09	2.4e-05	1.5e+04
SC-MUTEX	54.5e-12	1.0e-10	1.3e-09	2.4e-07	7.3e-03	1.2e+09
DFT-SC-MUTEX	40.0e-12	3.1e-09	1.2e-07	1.7e-04	3.4e+02	2.0e+18

- ❖ Mean Time Between Failures (MTBF) analyzed using Blendics's MetaAce
- ❖ Consider t_s values of 1.5, 2, 3, 5 and 10 times t_{pd} , where t_{pd} is the nominal delay of the MUTEX under analysis

Metastability resolves close to as fast as original MUTEXes

Experimental Results – PVT Analysis

ANALYSIS OF THE CHANGES IN τ (ps) DUE TO P, V, AND T VARIATIONS.

Designs	τ (ps) for 1.0V, 25°C varying process (P)			τ (ps) for TT, 25°C varying voltage (V)			τ (ps) for TT, 1.0V varying temperature (T)		
	SS	TT	FF	0.9V	1.0V	1.1V	-55°C	25°C	120°C
FC-MUTEX	14.3	11.6	9.64	13.9	11.6	10.3	9.81	11.6	13.7
DFT-FC-MUTEX	13.9	10.9	9.12	13.5	10.9	9.78	9.48	10.9	13.0
SC-MUTEX	14.7	11.8	9.83	14.1	11.8	10.4	9.94	11.8	13.9
DFT-SC-MUTEX	14.6	11.8	9.84	14.1	11.8	10.5	10.0	11.8	13.9

The proposed MUTEXes have similar τ values to classic ones, even under PVT variation

- ❖ New structures for testable MUTEXes proposed
 - ❖ Both full-custom and standard-cell versions
 - ❖ Layout created and analyzed

- ❖ Key Features
 - ❖ Improve fault coverage to 100%
 - ❖ Enable testing of Metastability Filters
 - ❖ Metastability resolution times not adversely effected

- ❖ Performance and power overheads analyzed

- ❖ Scrutinize impact of **local** PVT variations on MTBF of new MUTEXes
- ❖ Tri-state buffers may not be available in all standard-cell libraries
 - ❖ Explore alternatives for semi-custom testable MUTEXes
- ❖ Test proposed MUTEXes in silicon

Thank You!

