

Verilog HDL

Mark Redekopp

Purpose

- HDL's were originally used to model and simulate hardware before building it
- In the past 20 years, synthesis tools were developed that can essentially build the hardware from the same description

Differences from Software

- Software programming languages are inherently sequential
 - Operations executed in sequential order (next, next, next)
- Hardware blocks always run in parallel (at the same time)
 - Uses event-driven paradigm (change in inputs causes expression to be evaluated)
- HDL's provide constructs for both parallel & sequential operation

Software
Perform x+y and when that is done assign d-c to tmp

```
var = x+y;
tmp = d-c;
```


Hardware
This description models 2 gates working at the same time

```
f = a & b;
g = a | b;
```

Event Driven Paradigm:
If a or b changes, f and g will be re-evaluated

Modules

 
- Each Verilog designs starts as a block diagram (called a "module" in Verilog)
- Start with input and output signals, then describe how to produce outputs from inputs



Software analogy: Modules are like functions, but also like classes in that they are objects that you can instantiate multiple times.

Ports

 - Input and output signals of a module are called “ports” (similar to parameters/arguments of a software function)
- Unlike software, ports need to be declared as “input” or “output”
- Vectors declared using [MSB : LSB] notation



Signal Types

- Signals represent the inputs, outputs, and internal values
- Signals need to be typed
 - Similar to variables in software (e.g. int, char)
- 2 basic types
 - **Wire**: Represents a node connecting two logic elements
 - Only for modeling combinational logic
 - Used in “assign” statements
 - Use for signals connecting outputs of instantiated modules (structural modeling)
 - **Reg(ister)**: Used for signals that are described behaviorally
 - Used to model combinational & sequential logic
 - Used for anything produced by an “always” or “initial” block

```

module m1 (x, y, z, f, g) ;
input  x, y;
input  [2:0] z;
output f;
output reg [1:0] g;

wire  n1, n2;
reg   n3, n4;
...
endmodule
    
```

Inputs are always type 'wire'. Outputs are assumed 'wire' but can be redefined as 'reg'.

Constants

- Multiple bit constants can be written in the form:
 - [size] `base value
 - *size* is number of bits in constant
 - *base* is o or O for octal, b or B for binary, d or D for decimal, h or H for hexadecimal
 - *value* is sequence of digits valid for specified *base*
 - Values a through f (for hexadecimal base) are case-insensitive
- Examples:
 - 4'b0000 // 4-bits **binary**
 - 6'b101101 // 6-bits **binary**
 - 8'hfC // 8-bits in **hex**
 - Decimal is default
 - 17 // 17 decimal converted to appropriate # of unsigned bits

Structural vs. Behavioral Modeling

Structural



- Starting with primitive gates, build up a hierarchy of components and specify how they should be connected

Behavioral

- Describe behavior and let synthesis tools select internal components and connections

Structural Modeling

  - Starting with primitive gates, build up a hierarchy of components and specify how they should be connected



Use HA's to structurally describe incrementer

```

module ha(x,y,s,co);
  input  x,y;
  output s,co;


  xor i1(s,x,y);
  and i2(co,x,y);
endmodule

module incrementer(a,z);
  input  [3:0] a;
  output [3:0] z;
  wire   [3:1] c;

  ha ha0(a[0],1,z[0],c[1]);
  ha ha1(a[1],c[1],z[1],c[2]);
  ha ha2(a[2],c[2],z[2],c[3]);
  ha ha3(a[3],c[3],z[3], );
endmodule
    
```

Structural Modeling of Logic Gates

 - Modules and primitive gates can be instantiated using the following format:
module_name instance_name(output, input1, input2,...)
- Input and outputs must be wire types
- Supported Gates: *and, or, not, nand, nor, xor, xnor*



```

module m1(c16,c8,c4,f);
  input  c16,c8,c4;
  output f;
  wire   n1;

  or  i1(n1,c8,c4);
  nand i2(f,c16,n1);
endmodule
    
```

Verilog Description

Instantiating User-Defined Modules

- Format: **module_name instance_name(port1, port2, port3, ...)**
- Positional mapping
 - Signals of instantiation ports are associated using the order of module's port declaration (i.e. order is everything)
- Named mapping
 - Signals of instantiation ports are explicitly associated with module's ports (i.e. order is unimportant)
 - module_name instance_name(.module_port_name(signal_name),...);**

```

module ha(x,y,s,co);
  ...
endmodule

module incrementer(a,z);
  ha ha0(a[0],1,z[0],c[1]);
  ...
endmodule
    
```

Positional mapping

```

module ha(x,y,s,co);
  ...
endmodule

module incrementer(a,z);
  ha ha0(.x(a[0]),
        .s(z[0]),
        .y(1),
        .co(c[1]) );
  ...
endmodule
    
```

Named Mapping


Internal Signals

- Define signals (wire or reg) for each internal signal/wire

```

module m2(x,y,z,f);
  input  x,y,z;
  output f;
  wire  n1,n2,n3;

   and u1(n1,x,z); // instance names need
  and u2(n2,x,y); // not be declared
  not u3(n3,z);
  or  u4(f,n1,n2,n3);
endmodule
    
```



Behavioral Modeling

- Describe behavior and let synthesis tools select internal components and connections
- Advantages:
 - Easier to specify
 - Synthesis tool can pick appropriate implementation (for speed / area / etc.)

```
module incremter(a, z);
  input  [3:0] a;
  output [3:0] z;

  assign z = a + 1'b1;
endmodule
```

Could instantiate a ripple-carry adder, a fast carry-lookahead adder, etc. as needed


Use higher level operations and let synthesis tools infer the necessary logic

Operators

- Operator types
 - Non-blocking / Blocking assignment (<=, =)
 - Arithmetic (+, -, *, /, %)
 - Relational (<, <=, >, >=)
 - Equality (=, !=, ==, !==)
 - Logical (&&, ||, !)
 - Bitwise (~, &, |, ^, ~^)
 - Reduction (&, ~&, |, ~|, ^, ~^)
 - Shift (<<, >>)
 - Conditional (? :)
 - Concatenation and replication

Assign Statement

- Used for combinational logic expressions (must output to a 'wire' signal type)
- Can be used anywhere in the body of a module's code
- All 'assign' statements run in parallel
- Change of any signal on RHS (right-hand side) triggers re-evaluation of LHS (output)
- Format:
 - assign output = expr;**
 - '&' means AND
 - '|' means OR
 - '~' means NOT
 - '^' means XOR

 

```
module m1(c16, c8, c4, f);
  input  c16, c8, c4;
  output f;
  wire  n1;

  or    i1(n1, c8, c4);
  nand  i2(f, c16, n1);
endmodule
```

```
module m1(c16, c8, c4, f);
  input  c16, c8, c4;
  output f;

  assign f = ~(c16 & (c8 | c4));
endmodule
```

Multi-bit (Vector) Signals

- Reference individual bits or groups of bits by placing the desired index in brackets (e.g. x[3] or x[2:1])
- Form vector from individual signals by placing signals in brackets (i.e. { }) and separate with commas

```
module m1(x, f);
  input [2:0] x;
  output  f;

  // f = minterm 5
  assign f = x[2] & ~x[1] & x[0];
endmodule
```

```
module incremter(a, x, y, z);
  input [2:0] a;
  output x, y, z;

  assign {x, y, z} = a + 1;
endmodule
```

More Assign Statement

- Can be used with other operators besides simple logic functions
 - Arithmetic (+, -, *, /, %=modulo/remainder)
 - Shifting (<<, >>)
 - Relational (<, <=, >, >=, !=, ==)
 - Produces a single bit output ('1' = true / '0' false)
 - Conditional operator (? :)
 - Syntax:
condition ? statement_if_true : statement_if_false;

```
module m1(x,y,sub,s,cout,d,z,f,g);
input  [3:0] x,y;
input  sub;
output [3:0] s,d;
output [3:0] z;
output  cout,f,g;

assign {cout,s} = {0,x} + {0,y};
assign d = x - y;
assign f = (x == 4'h5);
assign g = (y < 0);
assign z = (sub==1) ? x-y : x+y;
endmodule
```

Sample "Assign" statements

Always Block (Combinational)

- Primary unit of parallelism in code
 - 'always' and 'assign' statements run in parallel
 - Statements w/in always blocks are executed sequentially
- Format
 - always @(sensitivity list)
 - begin
 - statements
 - end
- Always blocks are "executed" when there is a change in a signal in the sensitivity list
- When modeling combinational logic, sensitivity lists should include ALL inputs (i.e. all signals in the RHS's)
- Generation of a signal must be done within a single always block (not spread across multiple always blocks)
 - Signals generated in an always block must be declared type 'reg'

```
module addsub(a,b,sub,s);
input [3:0] a,b;
input sub;
output reg [3:0] s;
reg [3:0] newb;

always @(b,sub)
begin
if(sub == 1)
newb = ~b;
else
newb = b;
end

always @*
s = a + newb + sub;
end
endmodule
```

Always Block (Sequential)

- Flip-flops (sequential logic) are modeled using an always block sensitive to the edge (posedge or negedge) of the clock
 - block will only be executed on the positive edge of the clock
- Use the non-blocking assignment operator (<=) in clocked "always" blocks

```
module accumulator(x,z,clk,rst);
input [3:0] x;
input clk,rst;
output [3:0] z;
reg [3:0] z;

always @(posedge clk)
begin
if(rst == 1)
z <= 4'b0000;
else
z <= z + x;
end
endmodule
```

Procedural Statements

- Must appear inside an *always* or *initial* block
- Procedural statements include
 - if...else if...else...
 - case statement
 - for loop (usually unnecessary for describing logic)
 - while loop (usually unnecessary for describing logic)

If...Else If...Else Statements

- Syntax

```
if(expr)
begin
statements;
end
else if(expr)
statement;
else
statement;
```

```
// 4-to-1 mux description
always @(i0,i1,i2,i3,sel)
begin
if(sel == 2'b00)
y <= i0;
else if(sel == 2'b01)
y <= i1;
else if(sel == 2'b10)
y <= i2;
else
y <= i3;
end
...
```

- If multiple statements as the body of *if...else if...else* then enclose in *begin...end* construct

Case Statements

- Syntax

```
case(expr)
option 1: begin
statements;
end
option 2: statement;
[default: statement;]
endcase
```

```
// 4-to-1 mux description
always @(i0,i1,i2,i3,sel)
begin
case(sel)
2'b00: y <= i0;
2'b01: y <= i1;
2'b10: y <= i2;
default: y <= i3;
endcase
end
```

- Default statement is optional
- If multiple statements as the body of an option then enclose in *begin...end* construct

Traffic Light State Machine

```
module trafficlight(s1, s2, clk, rst, msg, ssg, mtg,
msr, ssr, mtr);
input s1, s2, clk, rst;
output msg, ssg, mtg, msr, ssr, mtr;

reg msg, ssg, mtg, msr, ssr, mtr;

reg [1:0] state;
reg [1:0] state_d;
wire s;
parameter MT = 2'b11;
parameter MS = 2'b10;
parameter SS = 2'b00;

assign s = s1 | s2;
always @(state, s)
begin
if(state == MS)
state_d <= SS;
else if(state == SS)
if(s == 1)
state_d <= MT;
else
state_d <= MS;
else // state == MT
state_d <= MS;
end
end

always @(posedge clk)
begin
if(rst == 1)
state <= SS;
else
state <= state_d;
end

always @(state)
begin
mtg <= 0; msg <= 0; ssg <= 0;
mtr <= 0; msr <= 0; ssr <= 0;
case(state)
MT:
begin
mtg <= 1; ssr <= 1; msr <= 1;
end
MS:
begin
msg <= 1; ssr <= 1; mtr <= 1;
end
SS:
begin
ssg <= 1; msr <= 1; mtr <= 1;
end
endcase
end
endmodule
```

Understanding Simulation Timing

- When expressing parallelism, an understanding of how time works is crucial
- Even though 'always' and 'assign' statements specify operations to be run in parallel, simulator tools run on traditional computers that can only execute sequential operations
- To maintain the appearance of parallelism, the simulator keeps track of events in a sorted event queue and updates signal values at appropriate times, triggering more statements to be executed

Explicit Time Delays

- In testbenches, explicit delays can be specified using '# delay'
 - When this is done, the RHS of the expression is evaluated at time t but the LHS is not updated until $t+delay$

```
module m1_tb;
  reg a,b,c;
  wire w,x,y,z;
  assign a = 1;
  #5 // delay 5 ns (ns = default)
  assign a = 0;
  assign b = 0;
  #2 // delay 2 more ns
  assign a = 1;
endmodule
```

Simulator Event Queue

Time	Event
0 ns	a = 1
5 ns	a = 0
5 ns	b = 0
7 ns	a = 1

Explicit Time Delays

- Assignments to the same signal without an intervening delay will cause only the last assignment to be seen

```
module m1_tb;
  reg a,b,c;
  wire w,x,y,z;
  assign a = 1;
  #5 // delay 5 ns (ns = default)
  assign a = 0;
  assign a = 1;
endmodule
```

Simulator Event Queue

Time	Event
0 ns	a = 1
5 ns	a = 0 → 1
5 ns	b = 0
7 ns	a = 1

Explicit Propagation Delay

- When modeling logic, explicit propagation delays can be inserted
 - Normally behavioral descriptions should avoid this since the delays will be determined by the synthesis tools
- Verilog supports different propagation delay paradigms
- One paradigm is to specify the delay with the RHS of an assignment in an always block.
- When this is done, the RHS of the expression is evaluated at time t but the LHS is not updated until $t+delay$
- This is called "transport" delay since we are specifying the time to transport the value from inputs to output

```
module m1(a,b,c,w,x,y,z);
  input a,b,c;
  output w,x,y,z;
  always @(a,b,c)
  begin
    w <= #4 a ^ b;
    x <= #5 b | c;
  end
endmodule
```

Simulator Event Queue

Time	Event
0 ns	a,b,c = 0,0,1
4 ns	w = 0
5 ns	x = 1

Implicit Time Delays

- Normal behavioral descriptions don't model propagation delay until the code is synthesized
- To operate correctly the simulators event queue must have some notion of what happens first, second, third, etc.
- Delta (δ) time is used
 - Delta times are purely for ordering events and all occur in "0 time"
 - The first event(s) occur at time 0 ns
 - Next event(s) occur at time $0 + \delta$
 - Next event(s) occur at time $0 + 2\delta$

```
always @(a,b,c,w,x,y)
begin
  w <= a ^ b;
  x <= b | c;
  y <= w & x;
  z <= ~y;
end
```

Equivalent Implementations

```
assign w = a ^ b;
assign x = b | c;
assign y = w & x;
assign z = ~y;
```

Simulator Event Queue

Time	Event	Triggers
0 ns	a,b,c = 0,0,1	w and x assigns
$0 + \delta$	w=0, x=1	y assign
$0 + 2\delta$	y = 0	z assign
$0 + 3\delta$	z = 1	Anything sensitive to z

Synthesized Logic & Timing

- Synthesis tools have to determine whether you are describing combinational or sequential logic in an *always* block
- If we reach the end of a block attempting to model combinational logic without assigning a signal then it infers that the signal should be remembered (i.e. sequential logic) and a latch results (usually undesired)
- When modeling combinational logic ALWAYS:
 - Provide a default assignment or
 - Provide an else/default case

```
// 2-to-1 mux description
always @(i0,i1,sel)
begin
  y = i1;
  if(sel == 0)
    y = i0;
end
```

Default assignment of y overwritten if necessary


```
// 2-to-1 mux description
always @(i0,i1,sel)
begin
  if(sel == 0)
    y = i0;
  else
    y = i1;
endcase
end
```

Else case acts as a catch-all / default case.

TESTBENCHES

Testbenches

- Generate input stimulus (values) to your design over time
- Simulator will run the inputs through the circuit you described and find what the output from your circuit would be
- Designer checks whether the output is as expected, given the input sequence
- Testbenches consist of code to generate the inputs as well as instantiating the design/unit under test and possibly automatically checking the results

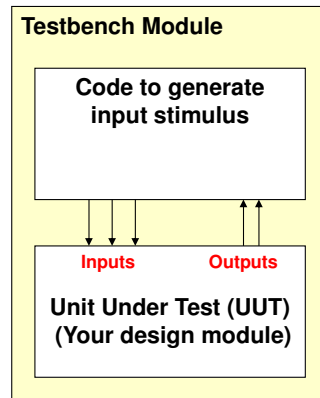

Testbench Modules

- Declared as a module just like the design circuit
- No inputs or outputs

```
module my_tb;
  // testbench code
endmodule
```


Testbench Signals

- Declare signals in the testbench for the inputs and outputs of the design under test
 - inputs to your design should be declared type 'reg' in the testbench (since you are driving them and their value should be retained until you change them)
 - outputs from your design should be declared type 'wire' since your design is driving them

```
module m1(x,y,z,f,g);
    input x,y,z;
    output f,g;
    ...
endmodule
```

Unit Under Test

```
module my_tb;
    reg x,y,z;
    wire f,g;
endmodule
```

Testbench

UUT Instantiation

- Instantiate your design module as a **component** (just like you instantiate a gate in your design)
- Pass the input and output signals to the ports of the design
- For designs with more than 4 or 5 ports, use named mapping rather than positional mapping

```
module m1(x,y,z,f,g);
    input x,y,z;
    output f,g;
    ...
endmodule
```

Unit Under Test

```
module my_tb;
    reg x,y,z;
    wire f,g;
    m1 uut(x,y,z,f,g);
    /* m1 uut(.x(x), .y(y),
              .z(z), .f(f),
              .g(g));
    */
endmodule
```

Testbench

Generating Input Stimulus (Values)

- Now use Verilog code to generate the input values over a period of time

```
module m1(x,y,z,f,g);
    input x,y,z;
    output f,g;
    ...
endmodule
```

Unit Under Test

```
module my_tb;
    reg x,y,z;
    wire f,g;
    m1 uut(x,y,z,f,g);
    /* m1 uut(.x(x), .y(y),
              .z(z), .f(f),
              .g(g));
    */
endmodule
```

Testbench

Initial Block Statement

- Tells the simulator to run this code just once (vs. always block that runs on changes in sensitivity list signals)
- Inside the "initial" block we can write code to generate values on the inputs to our design
- Use "begin...end" to bracket the code (similar to { .. } in C or Java)

```
module my_tb;
    reg x,y,z;
    wire f,g;
    m1 uut(x,y,z,f,g);
    initial
    begin
        // input stimulus
        // code
    end
endmodule
```

Testbench

Assignment Statement

- Use '=' to assign a signal a value
 - Can assign constants
 - $x = 0$; $y = 1$;
 - Can assign logical relationships
 - $x = \sim x$ // $x = \text{not } x$
 - $x = y \ \& \ z$ // $x = y \ \text{and } z$

```

module my_tb;

  reg  x,y,z;
  wire f,g;

  m1 uut(x,y,z,f,g);

  initial
  begin
    x = 0;
  end
endmodule
    
```

Testbench

Aggregate Assignment Statement

- Can assign multiple signals at once
- Place signals in brackets (i.e. { }) and separate with commas
- Multiple bit constants can be written in the form:
 - num_bits '{b,o,d,h}' value
 - 4'b0000 // 4-bits binary
 - 6'b101101 // 6-bits binary
 - 8'hFF // 8-bits in hex
 - Decimal is default
 - 17 // 17 decimal

```

module my_tb;

  reg  x,y,z;
  wire f,g;

  m1 uut(x,y,z,f,g);

  initial
  begin
    {x,y,z} = 3'b000;
  end
endmodule
    
```

Testbench

Time

- We must explicitly indicate when and how much time should pass between assignments
- Statement ('#' indicates a time delay):
 - # 10; // wait 10 ns;
 - # 50; // wait 50 ns;
- Default timescale is nanoseconds (ns)

```

module my_tb;

  reg  x,y,z;
  wire f,g;

  m1 dut(x,y,z,f,g);

  initial
  begin
    {x,y,z} = 3'b000;
    #10;
    {x,y,z} = 3'b001;
    #25;
  end
endmodule
    
```

Testbench

Integer Signal Type

- To model a collection of bits representing a number, declare signals as type 'integer'
- Assigning an integer to a bit or group of bits will cause them to get the binary equivalent
- Assigning an integer value too large for the number of bits will cause just the LSB's of the number to be assigned
 - Assigning $8_{10} = 1000_2$ to a 3-bit value will cause the 3-bit value to be 000 (i.e. the 3 LSB's of 1000)

```

module my_tb;

  reg  w,x,y,z;
  integer num;

  initial
  begin
    num = 15;
    {w,x,y,z} = num;
    // assigns
    // w,x,y,z = 1111
    #10;
    num = num+1;
    // num = 16
    {w,x,y,z} = num;
    // w,x,y,z = 0000
  end
endmodule
    
```

Testbench

For loop

- Integers can also be used as program control variables
- Verilog supports 'for' loops to repeatedly execute a statement
- Format:
 - for(initial_condition; end_condition; increment statement)

```

module my_tb;
  reg    a,b;
  integer i;
  initial
    begin
      for (i=0; i<4; i=i+1)
        begin
          {a,b} = i;
        end
      end
    endmodule
    
```

You can't do "i++" as in C/C++ or Java

a,b = 00, then 01, then 10, then 11

Here, 'i' acts as a counter for a loop. Each time through the loop, i is incremented and then the decimal value is converted to binary and assigned to a and b

For loop

- Question:** How much time passes between assignments to {a,b}
- Answer:** 0 time...in fact if you look at a waveform, {a,b} will just be equal to 1,1...you'll never see any other combinations
- We must explicitly insert time delays!

```

module my_tb;
  reg    a,b;
  integer i;
  initial
    begin
      for (i=0; i<4; i=i+1)
        begin
          {a,b} = i;
          #10;
        end
      end
    endmodule
    
```

Now, 10 nanoseconds will pass before we start the next iteration of the loop

Generating Sequential Stimulus


- Clock Generation
 - Initialize in an initial block
 - Continue toggling via an always process
- Reset generation
 - Activate in initial block
 - Deactivate after some period of time
 - Can wait for each clock edge via @(posedge clk)

```

module my_tb;
  reg    clk, rst, s;

  always #5 clk = ~clk;

   initial begin
    clk = 1; rst = 1; s=0;
    // wait 2 clocks
    @(posedge clk);
    @(posedge clk);
    rst = 0;
    s=1;
    @(posedge clk);
    s=0;
  end
endmodule
    
```



Generated stimulus