

## EE 457 Unit 2b

Fast Adders  
(Carry-Lookahead Adder)


Carry-Lookahead Adders

## FAST ADDERS
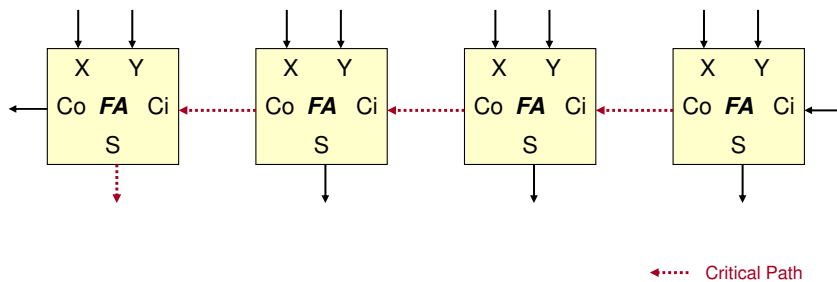
## Ripple Carry Adder Critical Path


- Critical Path = Longest possible delay path

Assume  $t_{sum} = 5 \text{ ns}$ ,  
 $t_{carry} = 4 \text{ ns}$


 
## Ripple Carry Adders

- Ripple-carry adders (RCA) are slow due to carry propagation
  - At least    levels of logic per full adder
  - Total delay for n-bit adder =    \*  $T_{fa}$



## Fast Adders

- Recall that any logic function can be implemented as a \_\_\_\_\_ implementation
  - SOP (AND-OR / NAND-NAND) implementation
  - POS (OR-AND / NOR-NOR) implementation
- Rather than waiting for the previous carry,  $[C_{i+1} = \underline{\hspace{2cm}}]$  can we compute the carry as a function of just the inputs
  - $C_{i+1} = f(X_i, X_{i-1}, \dots, X_0, Y_i, Y_{i-1}, \dots, Y_0)$
  - This requires gates with many inputs which is infeasible in modern technologies above 4 or 5 inputs
  - But, we can try to use this idea of generating multiple \_\_\_\_\_ by looking at many inputs


## Fast Adders

- To produce multiple carries in parallel, let us define some new signals for each column of addition that indicate information about the carry-out regardless of carry-in:
  - $g_i = \underline{\hspace{2cm}}$ : This column will generate a carry-out whether or not \_\_\_\_\_  
 $g_i$  is true when  $A_i$  and  $B_i$  is 1  $\Rightarrow g_i = A_i \cdot B_i$
  - $p_i = \underline{\hspace{2cm}}$ : This column will propagate a carry-in (if there is one) to the carry-out.  
 $p_i$  is true when  $A_i$  or  $B_i$  is 1  $\Rightarrow p_i = A_i + B_i$
- Using these signals, we can define the carry-out ( $c_{i+1}$ ) as:

$$C_{i+1} = \underline{\hspace{2cm}}$$
 
## Carry Lookahead Analogy

- Consider the carry-chain like a long tube broken into segments. Each segment is controlled by a valve (propagate signal) and can insert a fluid into that segment (generate signal)
- The carry-out of the diagram below will be true if  $g_1$  is true or  $p_1$  is true and  $g_0$  is true, or  $p_1, p_0$  and  $c_1$  is true



## Carry Lookahead Logic

- Define each carry in terms of  $p_i, g_i$  and the initial carry-in ( $c_0$ ) and not in terms of \_\_\_\_\_
- $c_1 = g_0 + p_0 c_0$
- $c_2 = g_1 + p_1 c_1 = \underline{\hspace{2cm}}$
- $c_3 = \underline{\hspace{2cm}}$
- $c_4 = \underline{\hspace{2cm}}$


## 4-Bit CLA

- At this point we should probably stop as we have a \_\_\_\_\_ gate in our equation
- Let's take our logic and build a 4-bit carry lookahead adder (CLA)

Delay to produce  $s_2$

- Delay for  $p_i, g_i = \underline{\hspace{1cm}}$
- Delay to produce  $c_2 = \underline{\hspace{1cm}}$
- Delay to produce  $s_2 = \underline{\hspace{1cm}}$

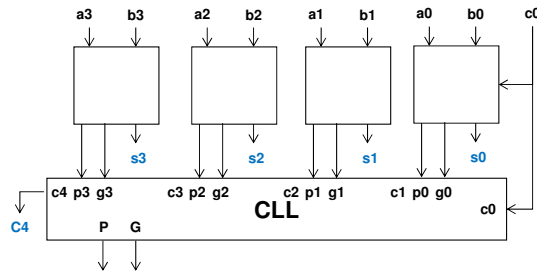
$= \underline{\hspace{1cm}}$  gates  
(Compare to 8 gate delays for RCA)



Is  $S_3$  produced later than  $S_2$ ?  
Is  $C_3$  the last signal produced?

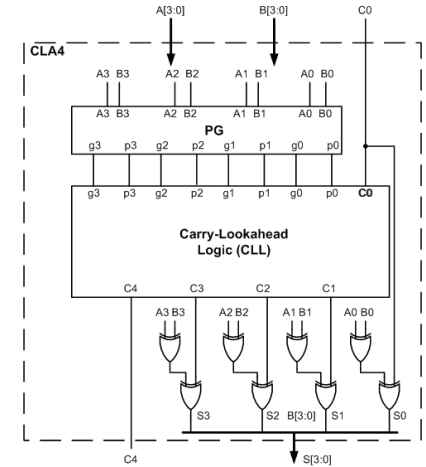
## Carry Lookahead Adder

- Use carry-lookahead logic to generate all the carries in one shot and then create the sum
- Example 4-bit CLA shown below


 
## 16-Bit CLA

- At this point we should probably stop as we have a 5-input gate in our equation



16-bit RCA Delay = \_\_\_\_\_ = \_\_\_\_\_ gate delays  
Delay of the above adder design = \_\_\_\_\_ = \_\_\_\_\_ gates  
Let us improve by looking ahead at a higher level to produce  $C_{16}, C_{12}, C_8, C_4$  in \_\_\_\_\_

Define P and G as the overall Propagate and Generate signals for a set of 4 bits

$P = \underline{\hspace{2cm}}$

$G = \underline{\hspace{2cm}}$


What's the difference between the equation for G here and C4 on the previous slides

## 16-bit CLA Closer Look

- Each 4-bit CLA only propagates its overall carry-in if each of the 4 columns propagates:
  - $P_0 = p_3 \cdot p_2 \cdot p_1 \cdot p_0$
  - $P_1 = p_7 \cdot p_6 \cdot p_5 \cdot p_4$
  - $P_2 = p_{11} \cdot p_{10} \cdot p_9 \cdot p_8$
  - $P_3 = p_{15} \cdot p_{14} \cdot p_{13} \cdot p_{12}$
- Each 4-bit CLA generates a carry if any column generates and the more significant columns propagate
  - $G_0 = g_3 + (p_3 \cdot g_2) + (p_3 \cdot p_2 \cdot g_1) + (p_3 \cdot p_2 \cdot p_1 \cdot g_0)$
  - ...
  - $G_3 = g_{15} + (p_{15} \cdot g_{14}) + (p_{15} \cdot p_{14} \cdot g_{13}) + (p_{15} \cdot p_{14} \cdot p_{13} \cdot g_{12})$
- The higher order CLL logic (producing  $C_4, C_8, C_{12}, C_{16}$ ) then is realized as:
  - $(C_4) \Rightarrow C_1 = G_0 + (P_0 \cdot c_0)$
  - ...
  - $(C_{16}) \Rightarrow C_4 = G_3 + (P_3 \cdot G_2) + (P_3 \cdot P_2 \cdot G_1) + (P_3 \cdot P_2 \cdot P_1 \cdot G_0) + (P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot c_0)$
- These equations are exactly the same CLL logic we derived earlier


# 16-Bit CLA

- Understanding 16-bit CLA hierarchy...

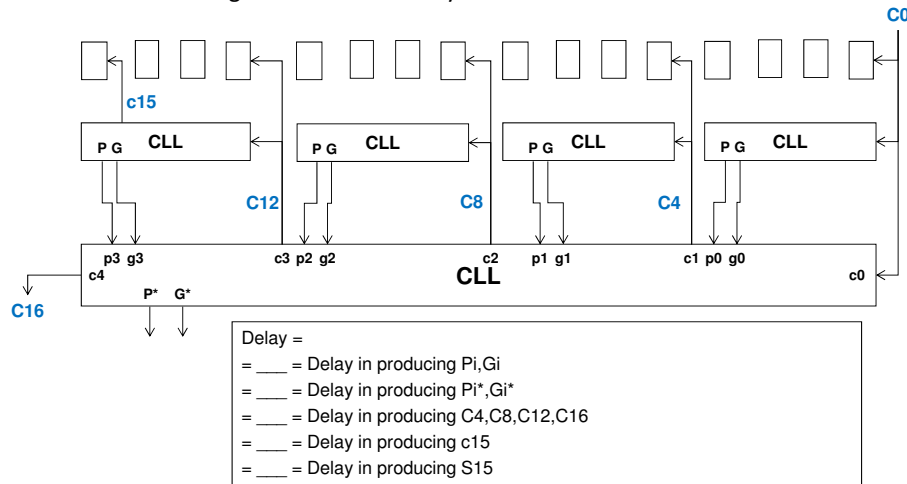
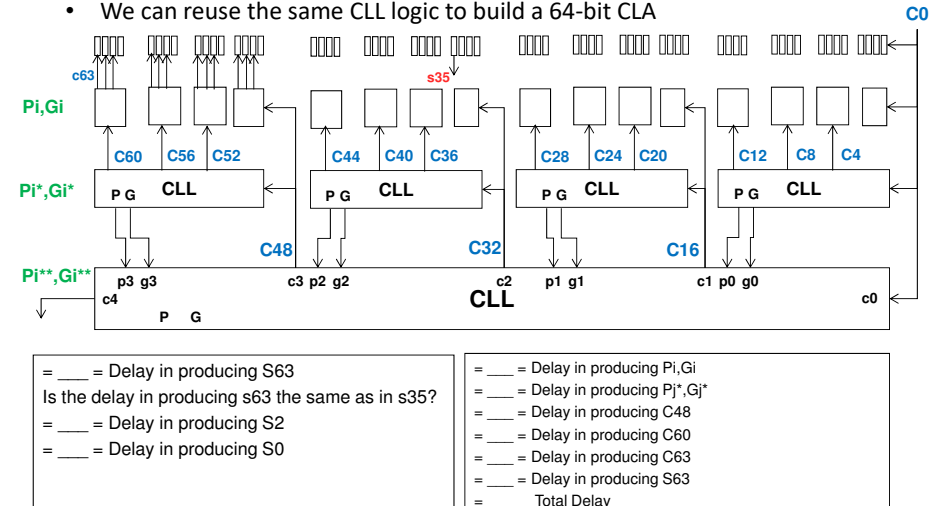
# 64-Bit CLA

- We can reuse the same CLL logic to build a 64-bit CLA



# Extrapolating CLA Logic Levels

- In the above designs we've assumed 5-input AND and OR gates are reasonable allowing us to group in blocks of 4
  - Define  $b$  = blocking factor = number of carries produced in parallel
- The greater the blocking factor the smaller the depth of logic (and vice-versa)
- This leads us to reason that the delay of a CLA is  $O(\log_b n)$
- If we could only use 3-input gates we'd need a blocking factor of 2

# Blocking factor of 2

- Each A box generates
  - $p_i = a_i + b_i$
  - $g_i = a_i \bullet b_i$
  - $s_i = a_i \oplus b_i$
- Each B box generates
  - $P_i = p_i \bullet p_{i-1}$
  - $G_i = g_i + p_i \bullet g_{i-1}$
  - $c_{i+1} = G_i + (P_i \bullet c_i)$

 


FIGURE A.13 Complete carry-lookahead tree adder. This is the combination of Figures A.11 and A.12. The numbers to be added enter at the top, flow to the bottom to combine with  $c_0$ , and then flow back up to compute the sum bits.

- Key lesson: In logic design trees are better than chains!

## Credits

- These slides were derived from Gandhi Puvvada's EE 457 Class Notes