

# Introduction to Digital Logic

## Lecture 10: Implementing Logic Functions w/ Memories Decoders

# Building Larger Functions/Circuits


- Scalability issues
  - K-Maps: Up to 6 inputs
  - Decoders: 6-8 inputs
    - But larger decoders can be built from smaller ones
  - Multiplexers: Can be decomposed to multiple levels
    - Use Shannon's Theorem
  - Memories: 12-13 inputs (4K – 8K rows)
- Building Block Methodology
  - Decompose circuits into smaller units
  - Design the smaller units using any of the above methods
  - Use those smaller circuits as building blocks to construct arbitrarily large functions/circuits

# Combinational Building Blocks

- Fundamental blocks that other combinational structures can be built from
  - Decoders
  - Encoders
  - Multiplexers
  - Demultiplexers
  - Adders (Multipliers)
  - Comparators
  - Shifters


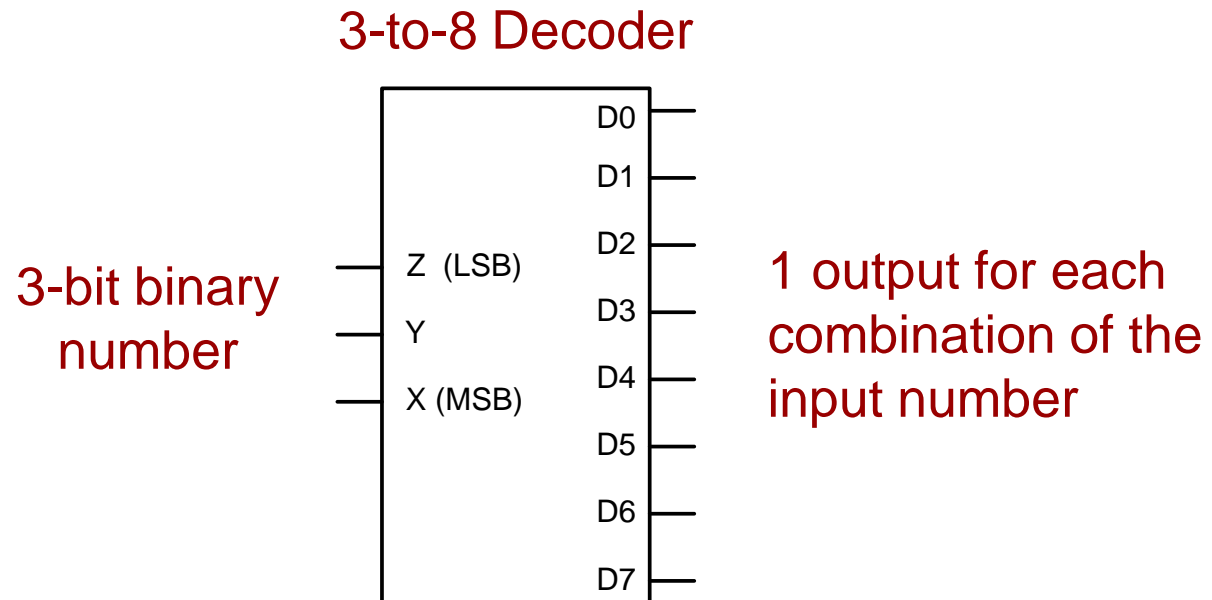
# Decoders

- A decoder is a building block that:
  - Takes in an  $n$ -bit binary number as input
  - Decodes that binary number and activates the corresponding output
  - Individual outputs for EVERY input combination (i.e.  $2^n$  outputs)




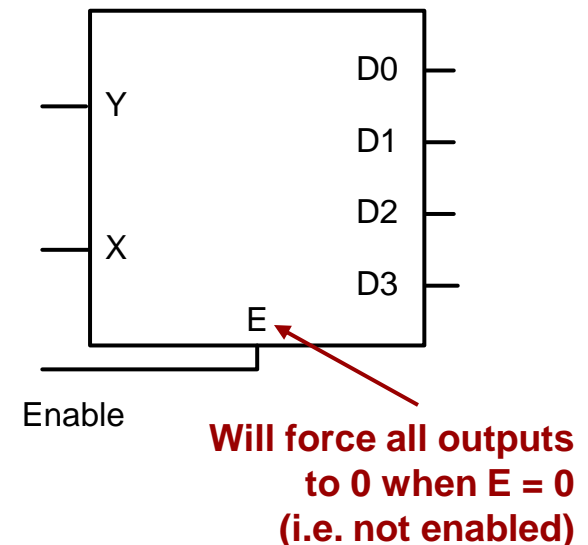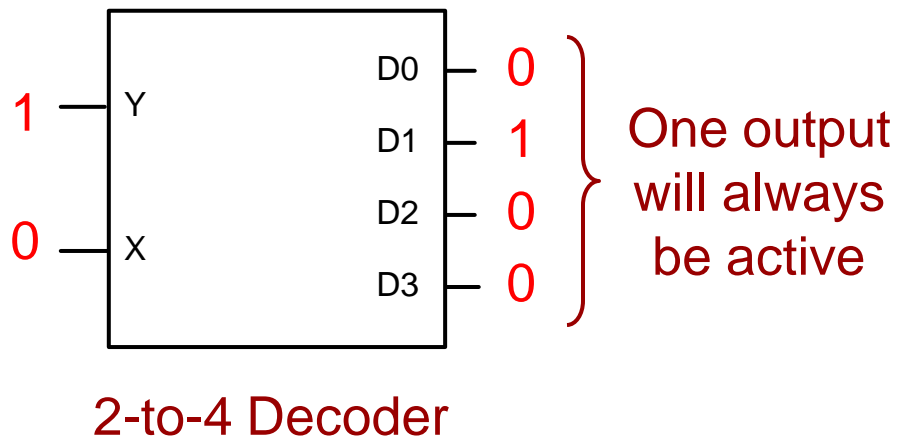
# Enables

- Exactly one output is active at all times
- It may be undesirable to always have an active output
- Add an extra input (called an enable) that can independently force all the outputs to their inactive values




# Enables

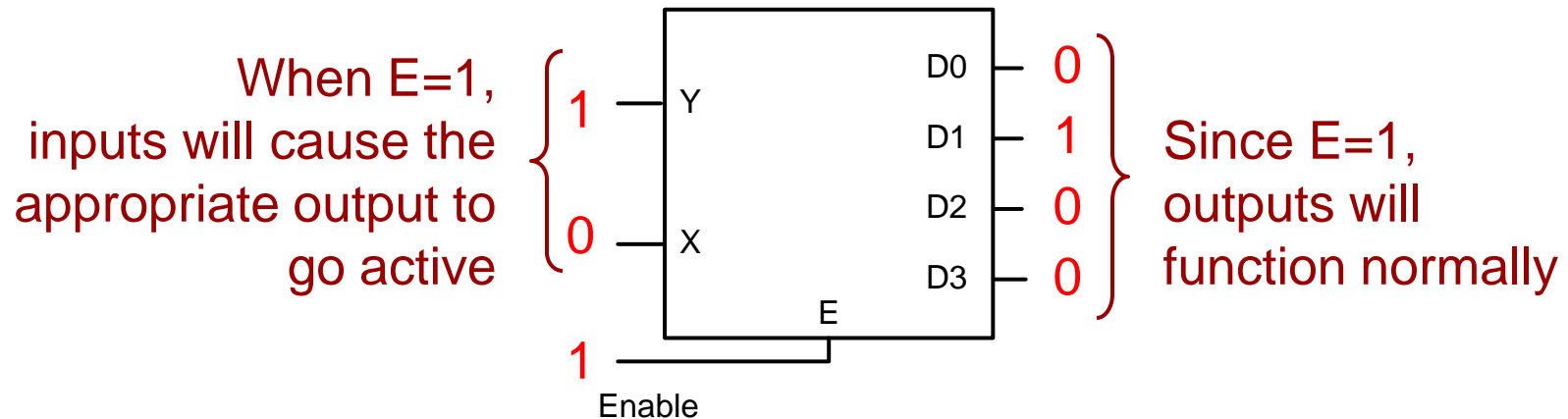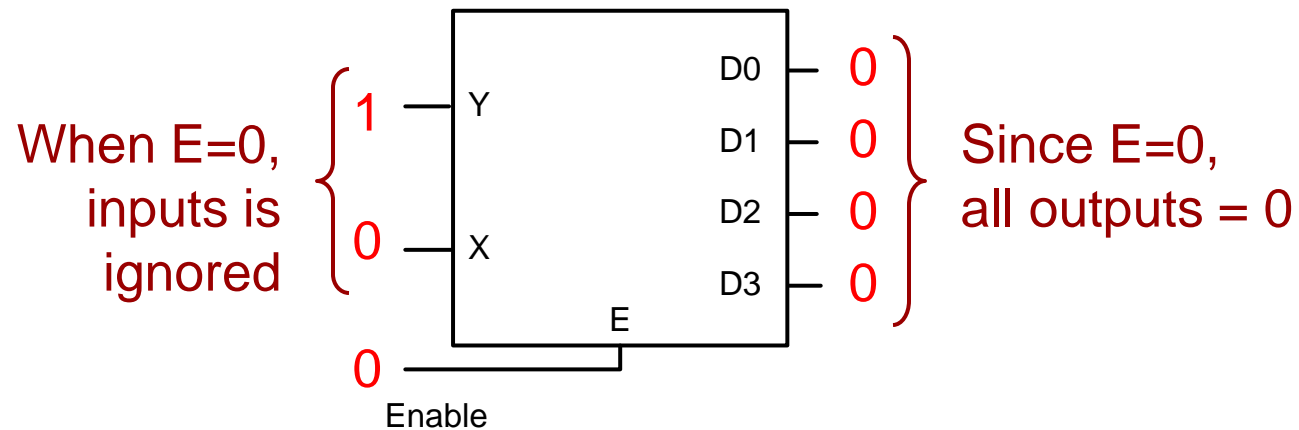

# Implementing Enables

- Original 2-to-4 decoder

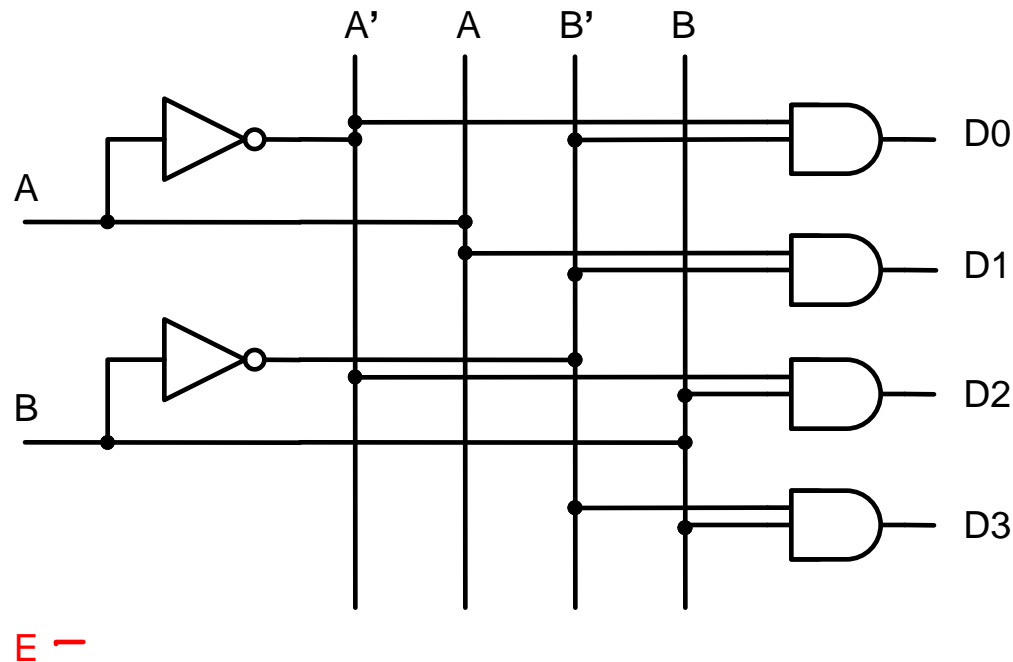


When  $E=0$ , force all outputs = 0

When  $E=1$ , outputs operate as they did originally
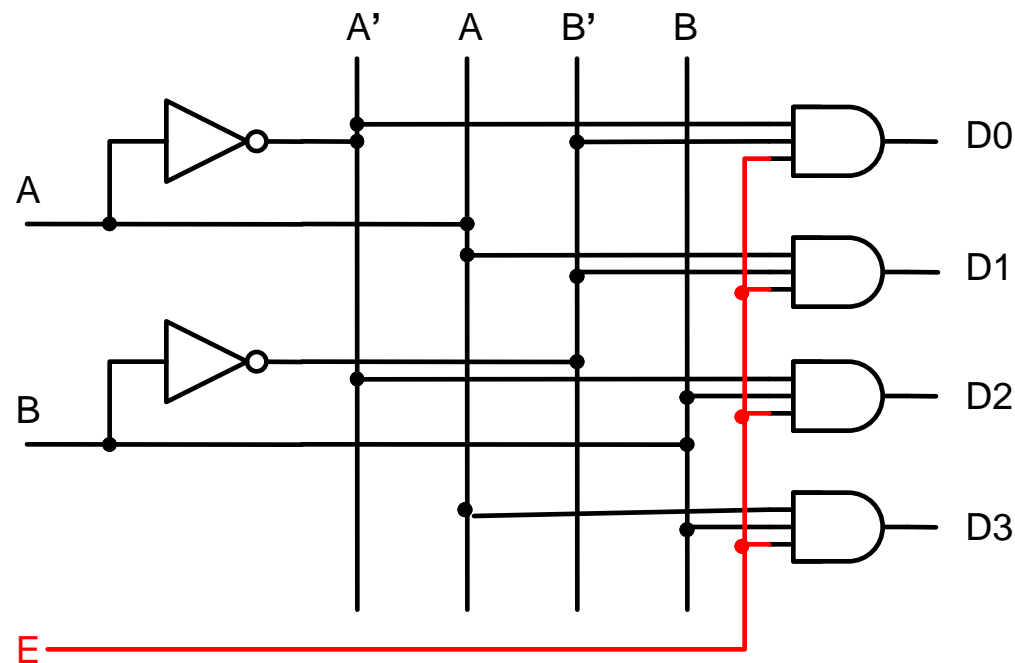
# Enables

- Enables can be implemented by connecting it to each AND gate of the decoder




When  $E=0$ ,  $0 \text{ AND anything} = 0$

When  $E=1$ ,  $1 \text{ AND anything} = \text{that anything}$ , which was the normal decoding logic




# Active-Lo Outputs

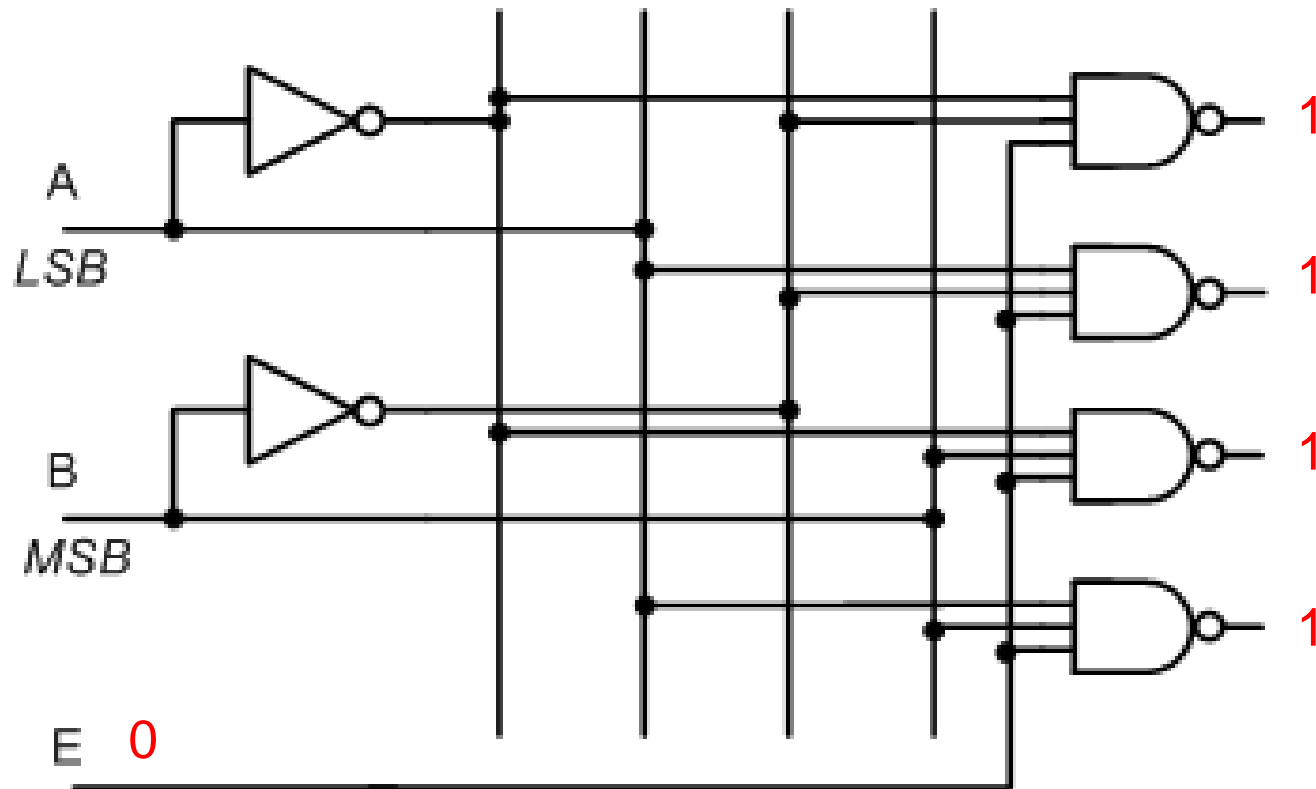

When E=inactive (inactive means 0), Outputs turn off (off means 1)

When E=active (active means 1), Selected outputs turn on (on means 0)


# Active-Lo Outputs

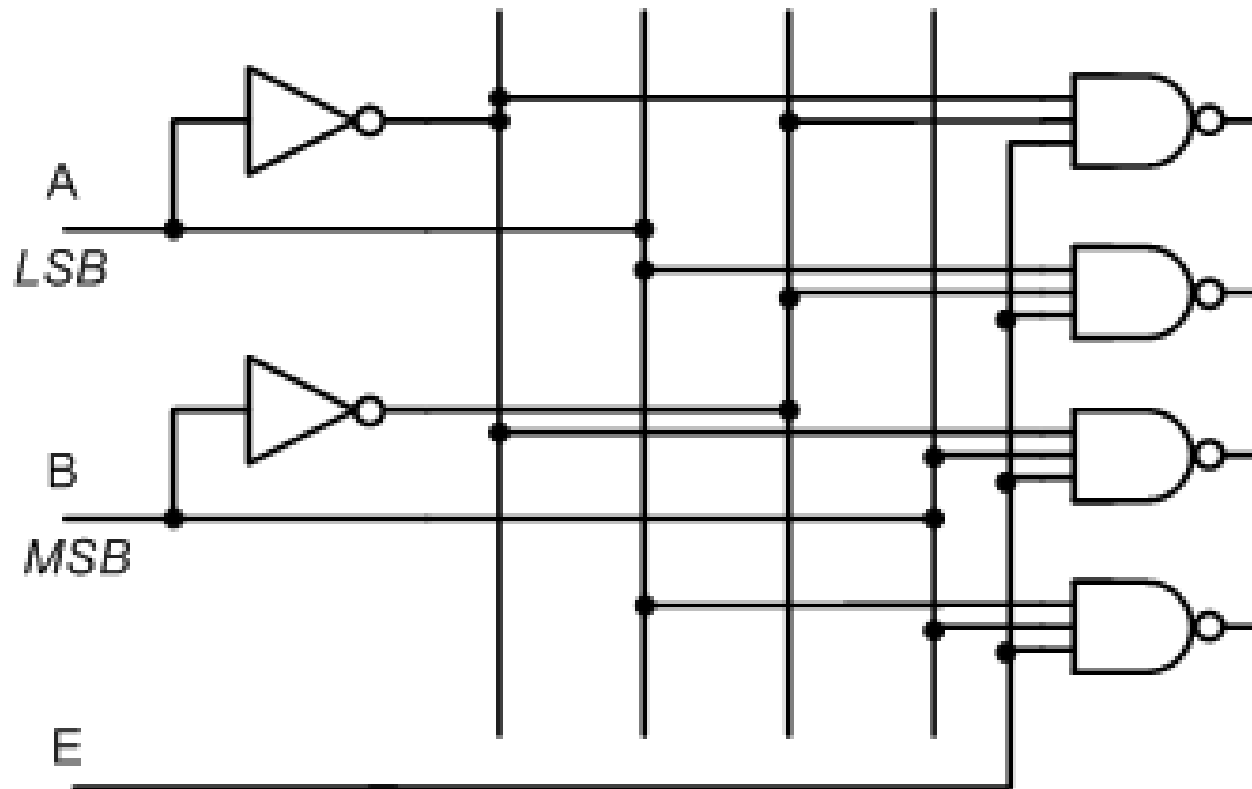

When E=inactive (inactive means 0), Outputs turn off (off means 1)

When E=active (active means 1), Selected outputs turn on (on means 0)

# Active-Lo Enable

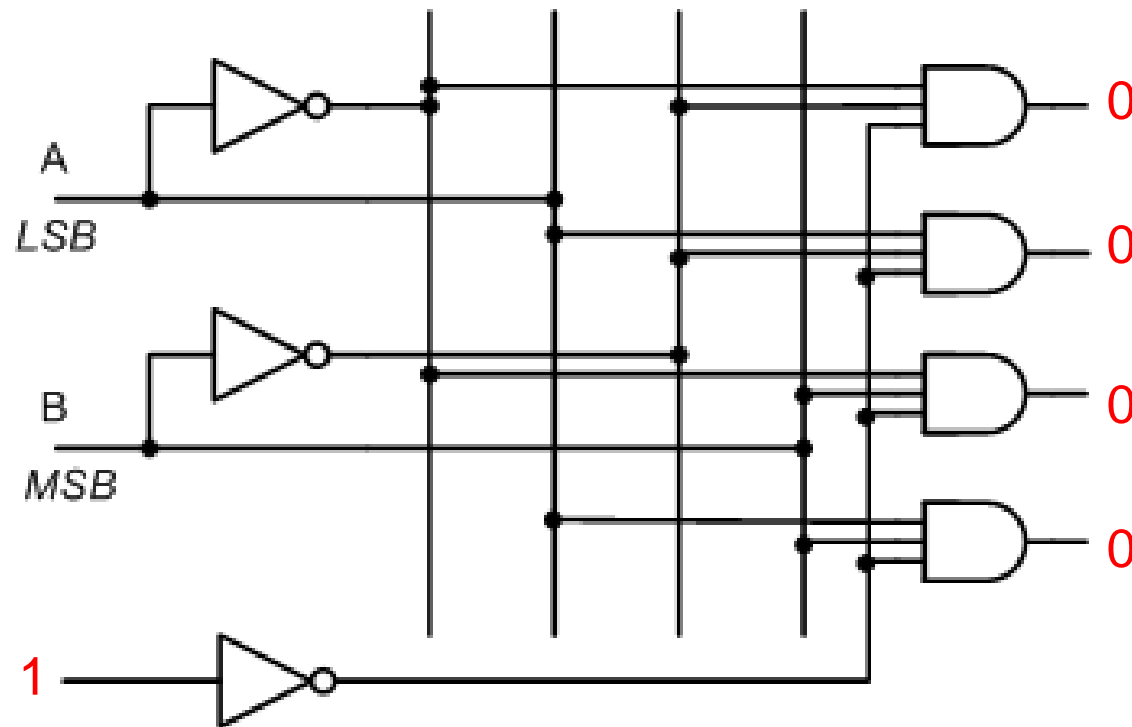


When E=inactive (inactive means 1), Outputs turn off (off means 0)

When E=active (active means 0), Selected outputs turn on (on means 1)

**When E=active (active means 0), Selected outputs turn on (on means 1)**


# Active-Lo Enable

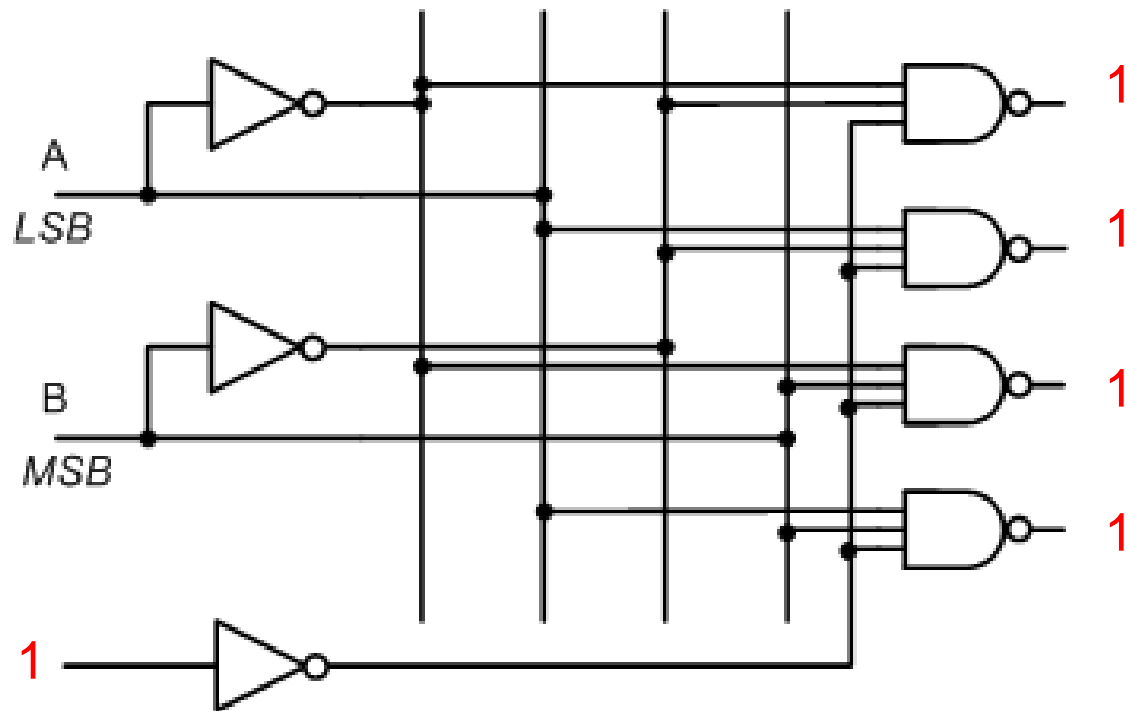

When E=inactive (inactive means 1), Outputs turn off (off means 1)

When E=active (active means 0), Selected outputs turn on (on means 0)

# Active-Lo Enable

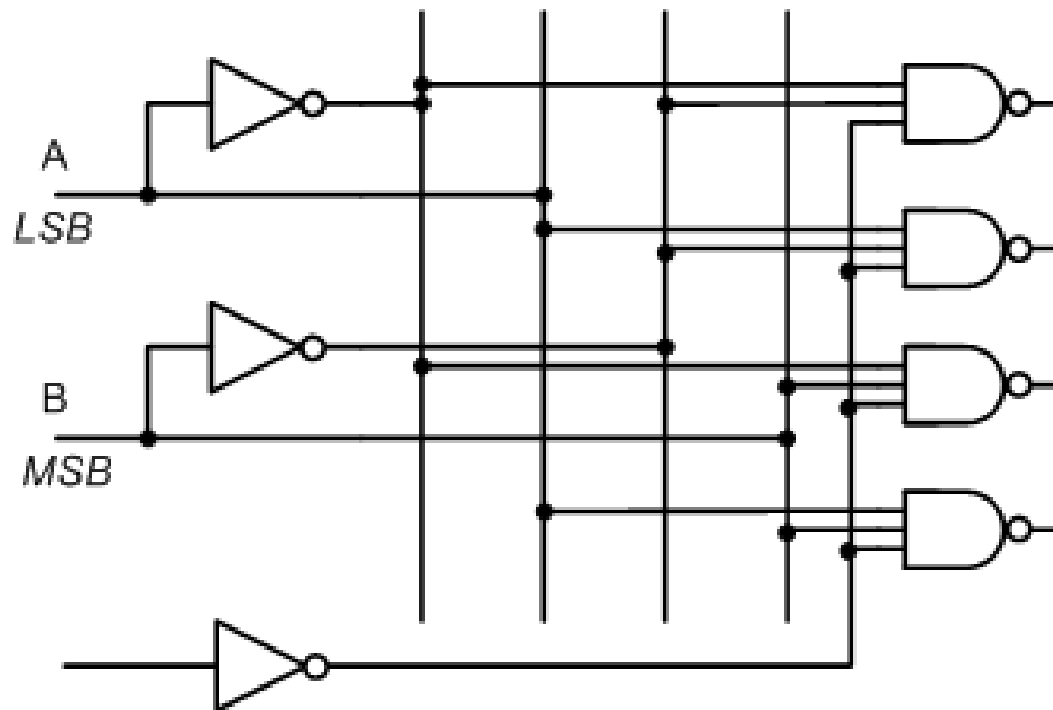

When E=inactive (inactive means 1), Outputs turn off (off means 1)

When E=active (active means 0), Selected outputs turn on (on means 0)