

Introduction to Digital Logic

Lecture 11:
Cascading Decoders
Implementing Functions w/ Decoders
Encoders & Priority Encoders

Building Larger Functions/Circuits


- Scalability issues
 - K-Maps: Up to 6 inputs
 - Decoders: 6-8 inputs
 - But larger decoders can be built from smaller ones
 - Multiplexers: Can be decomposed to multiple levels
 - Use Shannon's Theorem
 - Memories: 12-13 inputs (4K – 8K rows)
- Building Block Methodology
 - Decompose circuits into smaller units
 - Design the smaller units using any of the above methods
 - Use those smaller circuits as building blocks to construct arbitrarily large functions/circuits

Combinational Building Blocks

- Fundamental blocks that other combinational structures can be built from
 - Decoders
 - Encoders
 - Multiplexers
 - Demultiplexers
 - Adders (Multipliers)
 - Comparators
 - Shifters



Decoders

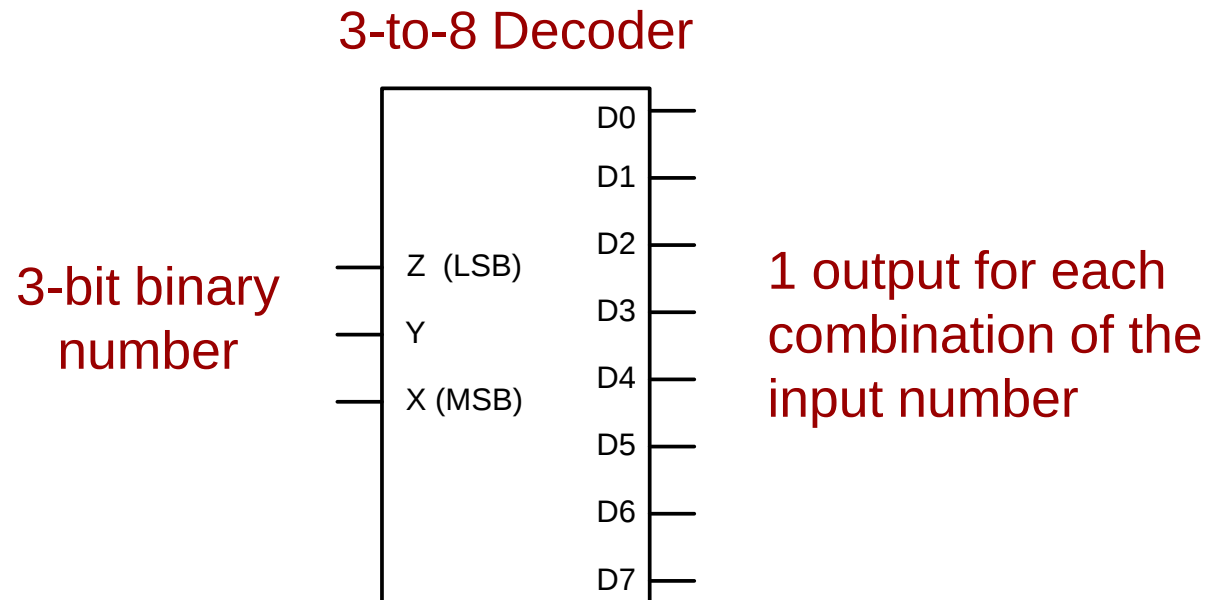- A decoder is a building block that:
 - Takes in an n -bit binary number as input
 - Decodes that binary number and activates the corresponding output
 - Individual outputs for EVERY input combination (i.e. 2^n outputs)





Enables

 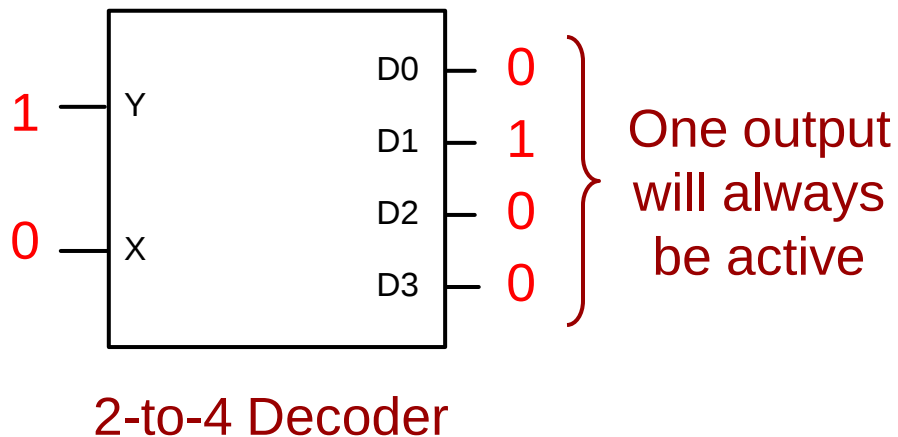- Exactly one output is active at all times
- It may be undesirable to always have an active output
- Add an extra input (called an enable) that can independently force all the outputs to their inactive values




Enables

  

Implementing Enables

- Original 2-to-4 decoder

 


When $E=0$, force all outputs = 0

When $E=1$, outputs operate as they did originally

Enables

 - Enables can be implemented by connecting it to each AND gate of the decoder



When $E=0$, $0 \text{ AND anything} = 0$

When $E=1$, $1 \text{ AND anything} = \text{that anything}$, which was the normal decoding logic


Active-hi vs. Active-low

- Active-hi convention
 - 1 = on/true/active
 - 0 = off/false/inactive
- Active-low convention
 - 0 = on/true/active
 - 1 = off/false/inactive
- To convert between conventions
 - INVERT!!!

Why Active-low

- Some digital circuits are better at “sinking” (draining/sucking) electric current than “sourcing” (producing) current


Active-Lo Outputs

 

When E=inactive (inactive means 0), Outputs turn off (off means 1)

When E=active (active means 1), Selected outputs turn on (on means 0)


Active-Lo Outputs

 

When E=inactive (inactive means 0), Outputs turn off (off means 1)

When E=active (active means 1), Selected outputs turn on (on means 0)


Active-Lo Enable

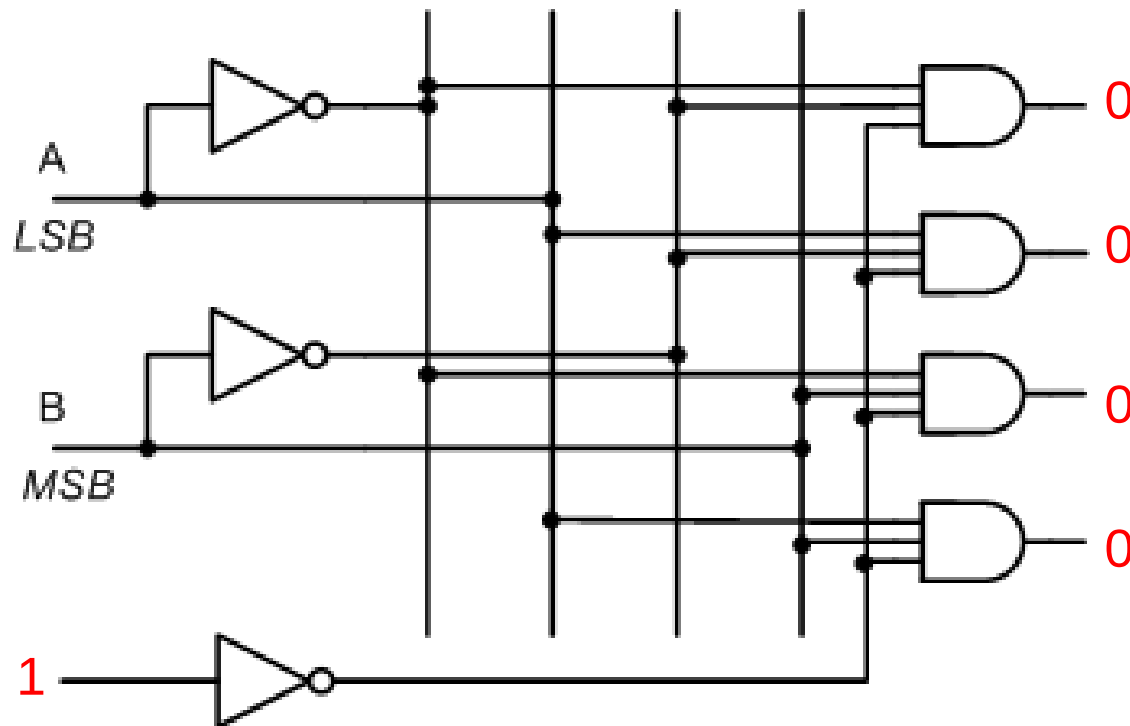

When E=inactive (inactive means 1), Outputs turn off (off means 0)

When E=active (active means 0), Selected outputs turn on (on means 1)


Active-Lo Enable

 

When E=inactive (inactive means 1), Outputs turn off (off means 0)

When E=active (active means 0), Selected outputs turn on (on means 1)


Active-Lo Enable

 

When E=inactive (inactive means 1), Outputs turn off (off means 1)

When E=active (active means 0), Selected outputs turn on (on means 0)

Active-Lo Enable

 


When E=inactive (inactive means 1), Outputs turn off (off means 1)

When E=active (active means 0), Selected outputs turn on (on means 0)

Decoder w/ Multiple Enables


- When a decoder has multiple enables, all enables ***must be active*** for the decoder to be enabled

 3 Enables
 /G1 must equal 0
 /G2 must equal 0
 and E must equal 1




Implementing Logic Functions

 - $F = \Sigma_{MNO}(2,3,4,6)$
 $= m_2 + m_3 + m_4 + m_6$
- Since decoders are just minterm generators, just OR together the appropriate minterms



Implementing Logic Functions

 - $F = \Sigma_{MNO}(2,3,4,6)$
 $= m_2 + m_3 + m_4 + m_6$
- If we have active-low outputs just invert back to active-hi
- OR gate becomes NAND gate



Key: w/ active-lo outputs use NAND gates

Add another level
of bubbles to
cancel the active-
low outputs

Decoder/Logic Function Summary

- To produce F ...


	Active-hi outputs	Active-lo outputs
Fewer minterms in F	Implement F with OR gate	Implement F with NAND gate
Fewer minterms in F'	Implement F' with NOR gate	Implement F' with AND gate

Building Larger Decoders

- Using the “building-block methodology”, cascade smaller decoders to build larger ones
- We’ll use stages of decoders
 - Start at the last stage (outputs) using as many small decoders as necessary to make the desired number (i.e. 2^n) of outputs
 - Connect enables of one stage to outputs of previous stage
 - All decoders in a stage should decode the same bit(s) of the input [usually MSB to first stage, LSB to last]


Cascading Decoders

 - Connect outputs of first stage to enables of next stage
- Usually, MSB's are connected to the first stage, LSB's to the following stages



Cascading Decoders

 - Connect outputs of first stage to enables of next stage
- Usually, MSB's are connected to the first stage, LSB's to the following stages



Cascading Decoders


- To understand how this works think of the process of elimination
 - Given a 2-bit number X, Y ($X = \text{MSB}$)
 - If I tell you $X=1$, what are the possible numbers we can have...2 or 3
 - If I then tell you $Y=0$, then you know the number is 2
- By decoding one bit at a time we can eliminate half of the possibilities until we get down to the actual number

Cascading Decoders

Example:
 $X=1, Y=0$

w/ $X=1$ we can narrow it down to D_2 or D_3 ...and you see that the lower decoder in the second stage is the one that is enabled

E	X	Y	D0	D1	D2	D3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 


Cascading Decoders

Example:
 $X=1, Y=0$

The top decoder is disabled so its outputs are forced to 0

The bottom decoder decodes the Y bit and outputs its D_0 (really D_2)


E	X	Y	D0	D1	D2	D3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 


Rules for Making Larger Decoders

- Rule 1: Outputs of one stage should connect to the enables of the next stage
- Rule 2: All decoders in a stages should decode the same bit(s)
 - Usually, the MSB is connected to the first stage and LSB to the last stage

Build a 3-to-8 Decoder

 


Cascading Decoders

 

G	A ₂	A ₁	A ₀	Active Output
0	X	X	X	None
1	0	0	0	D ₀
1	0	0	1	D ₁
1	0	1	0	D ₂
1	0	1	1	D ₃
1	1	0	0	D ₄
1	1	0	1	D ₅
1	1	1	0	D ₆
1	1	1	1	D ₇

Cascading Decoders


Decode the MSB...possible combos = 4-7

 

G	A ₂	A ₁	A ₀	Active Output
0	X	X	X	None
1	0	0	0	D ₀
1	0	0	1	D ₁
1	0	1	0	D ₂
1	0	1	1	D ₃
1	1	0	0	D ₄
1		0	1	D ₅
1		1	0	D ₆
1		1	1	D ₇

Cascading Decoders


Decode the A_1 ...possible combos = 5-6

 

G	A_2	A_1	A_0	Active Output
0	X	X	X	None
1	0	0	0	D_0
1	0	0	1	D_1
1	0	1	0	D_2
1	0	1	1	D_3
1	1	0	0	D_4
1			1	D_5
1			0	D_6
1			1	D_7



Cascading Decoders

Decode the LSB...combo = 5

 

G	A ₂	A ₁	A ₀	Active Output
0	X	X	X	None
1	0	0	0	D ₀
1	0	0	1	D ₁
1	0	1	0	D ₂
1	0	1	1	D ₃
1	1	0	0	D ₄
1			1	D ₅
1			0	D ₆
1			1	D ₇

Build a 3-to-8 Decoder

  

X0 —


X1 —

X2 —

SIMPLE & PRIORITY ENCODERS


Encoders

 - Opposite function of decoders
- Takes in 2^n inputs and produces an n-bit number



Encoders

 
- Assumption: Only one input will be active at a time



Encoders

- What's inside an encoder?

I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	Y_2	Y_1	Y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

Deriving equations for Y_0 , Y_1 , Y_2 is made simpler because of the assumption that only 1 input can be active at a time. Rather than having 256 rows in our truth table we only have 8


Encoders

- What's inside an encoder?

I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	Y_2	Y_1	Y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$Y_2 = 1$ when $I_4 = 1$ or $I_5 = 1$ or $I_6 = 1$ or $I_7 = 1$...

$$Y_2 = I_4 + I_5 + I_6 + I_7$$

 

Encoders


- What's inside an encoder?

I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	Y_2	Y_1	Y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$Y_2 = I_4 + I_5 + I_6 + I_7$$


$$Y_1 = I_2 + I_3 + I_6 + I_7$$

$$Y_0 = I_1 + I_3 + I_5 + I_7$$

 

Encoders

 - A simple binary encoder can be made with just OR gates




Problems

- There is a problem...
 - Our assumption is that only 1 input can be active at a time
 - What happens if 2 or more inputs are active or if 0 inputs are active

2 or More Active Inputs

 - What if I5 and I2 are active at the same time?
 - Substitute values into equation
- Output will be '111' = 7
- Output is neither 2 nor 5, it's something different, 7





$$Y_2 = I_4 + I_5 + I_6 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$

$$Y_0 = I_1 + I_3 + I_5 + I_7$$


0 Active Inputs

  - What if no inputs are active?
 - Substitute values into equation
- Output will be '000' = 0
- Problem: '000' means that input 0 was active
 - Can't tell the difference between when '000' means input 0 was active or no inputs was active




Priority Encoders

 - Fix the 2 problems seen above
- Problem of more than 2 active inputs
 - Assign priority to inputs and only encode the highest priority active input
- Problem of zero active inputs
 - Create an extra output to indicate if any inputs are active
 - We will call this output the “Valid” output (/V)




Priority Encoders

 - Fix the 2 problems seen above
- Problem of more than 2 active inputs
 - Assign priority to inputs and only encode the highest priority active input
- Problem of zero active inputs
 - Create an extra output to indicate if any inputs are active




Encoder Application: Interrupts

 - I/O Devices in a computer need to request attention from the CPU...they need to “interrupt” the processor
- CPU cannot have a dedicated line to each I/O device (too many inputs and outputs) plus it can only service one device at a time




Encoder Application: Interrupts

 - Solution: Priority Encoder
- /INT input of CPU indicates SOME device is requesting attention
- INT_ID inputs identify who is requesting attention




Encoder Application: Interrupts

 - Example: Sound and Network request interrupt at the same time
- Network is highest priority and is encoded
- After network is handled, sound will cause interrupt




Multiplexers

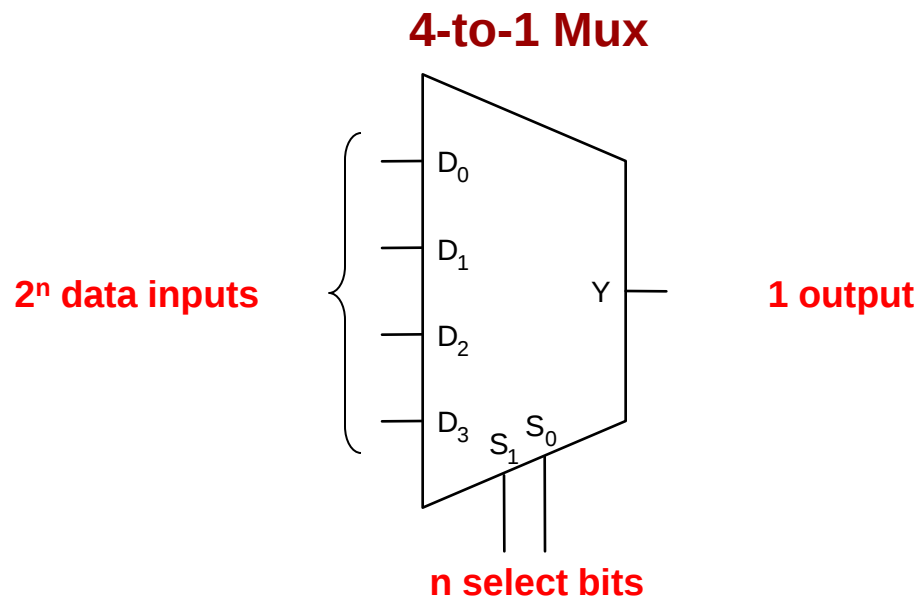- Along with adders, multiplexers are most used building block
- 2^n data inputs, n select bits, 1 output
- A multiplexer (“mux” for short) selects one data input and passes it to the output




Multiplexers

 ② Thus, D₂ is selected and passed to the output



① Select bits = $10_2 = 2_{10}$.


Multiplexers

 

**D2 is being selected and passed.
So if it changes the output
changes as well.**

Multiplexers

 ② Thus, D0 is selected and passed to the output




① Select bits = $00_2 = 0_{10}$.

Building a Mux

- To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.


$S_1 S_0 = 01$

 

Building a Mux


- To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.

$S_1 S_0 = 11$

 


Adding Enables to Muxes

 - When Enable = inactive, $Y = \text{inactive}$
- When Enable = active, normal mux




$/E$ = inactive forces
output to 0

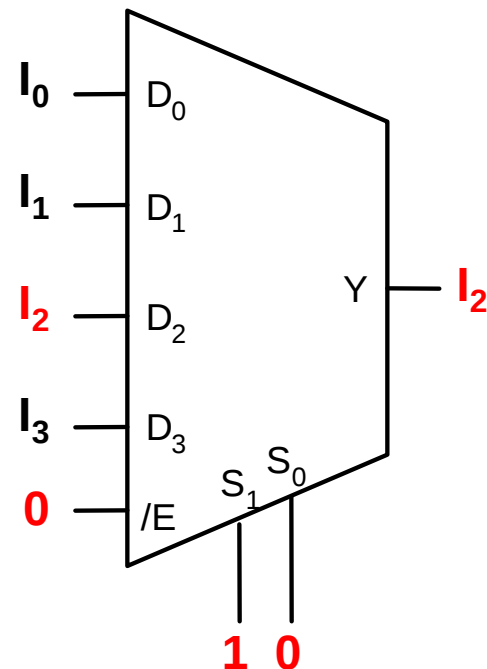


$/E$ = active allows
normal mux function

Adding Enables to Muxes

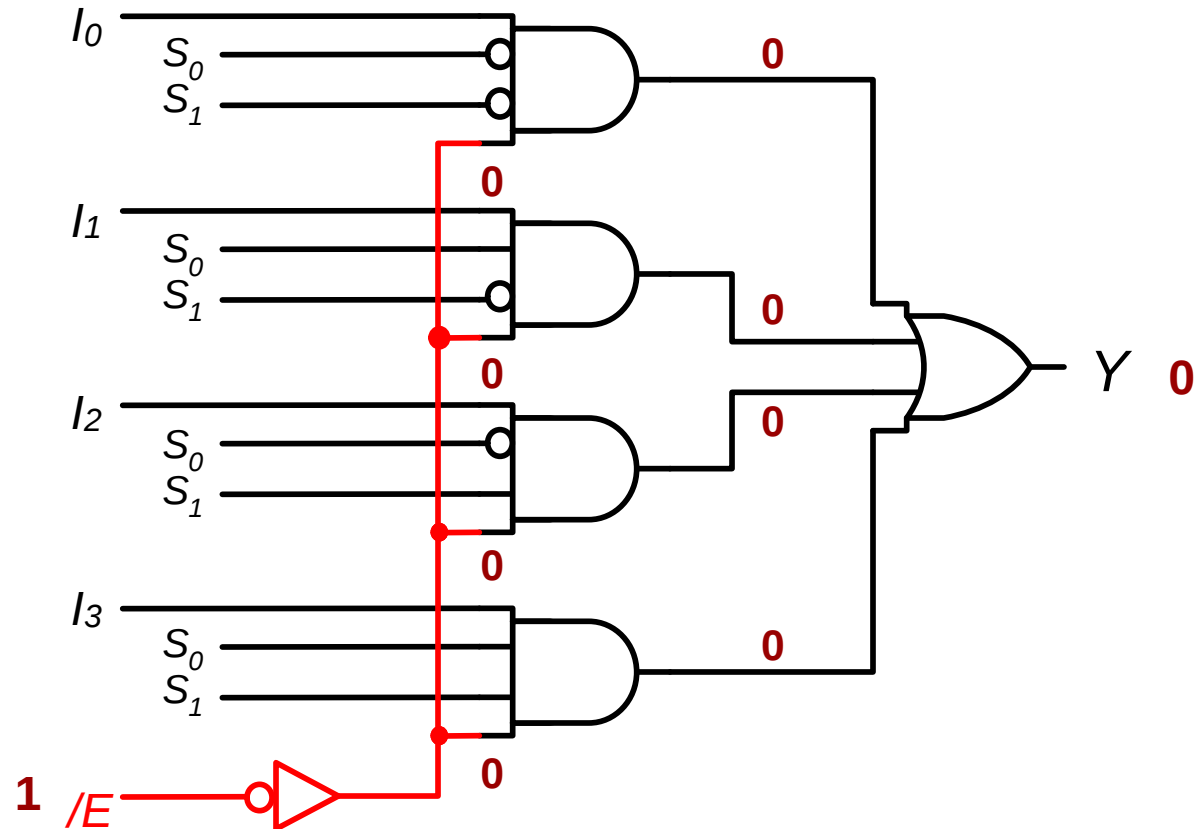


Building Wide Muxes

 - So far muxes only have single bit inputs...
 - I_0 is only 1-bit
 - I_1 is only 1-bit
- What if we still want to select between 2 inputs but now each input is a 4-bit number
- Use a 4-bit wide 2-to-1 mux



1-bit wide 2-to-1
mux

 

Pass all 4 bits
of I_0 or I_1

4-bit wide 2-to-1
mux

When we select I_0
or I_1 we want all
4-bits of that
input to be
passed

Building Wide Muxes

- To build a 4-bit wide 2-to-1 mux, use 4 separate 2-to-1 muxes
- When $S=0$, all muxes pass their I_0 inputs which means all the A bits get through
- When $S=1$, all muxes pass their I_1 inputs which means all the B bits get through
- In general, to build an **m-bit wide n-to-1 mux**, use **m individual (separate) n-to-1 muxes**

