

# Introduction to Digital Logic

Lecture 13:

Demuxes

Adders

Overflow


Carry-Lookahead Adders

# DEMULTIPLEXERS




# Demultiplexers

- Perform opposite function of multiplexers
- Pass the input to one selected output
- In general
  - 1 input
  - $2^n$  outputs
  - $n$  select bits


$S_1$	$S_0$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

 


# Demultiplexers

   

# Demultiplexer Design

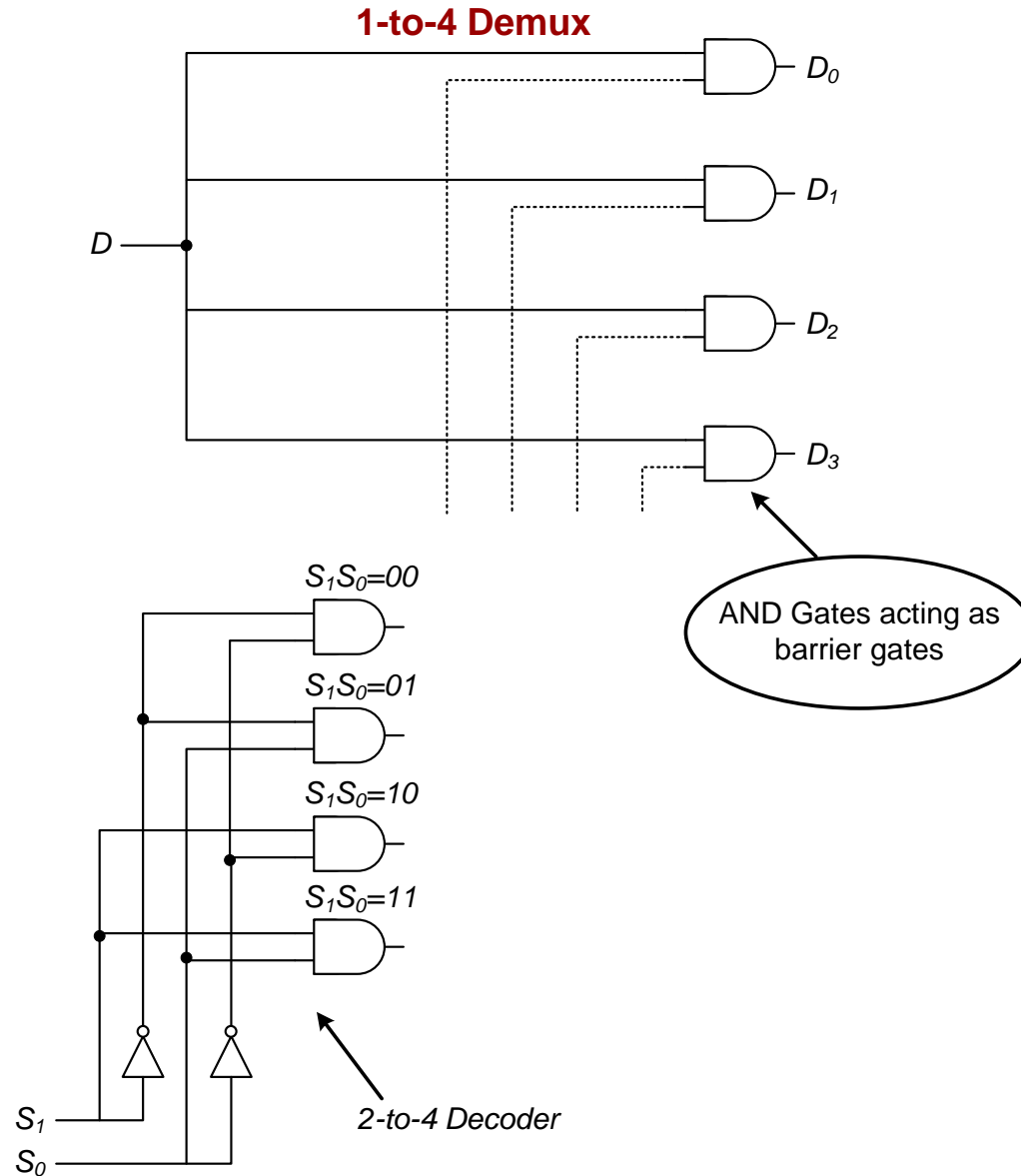


# Demultiplexer Design

 

1-to-4 Demux

# Demultiplexer Design


Notice D runs to all 4 output AND gates

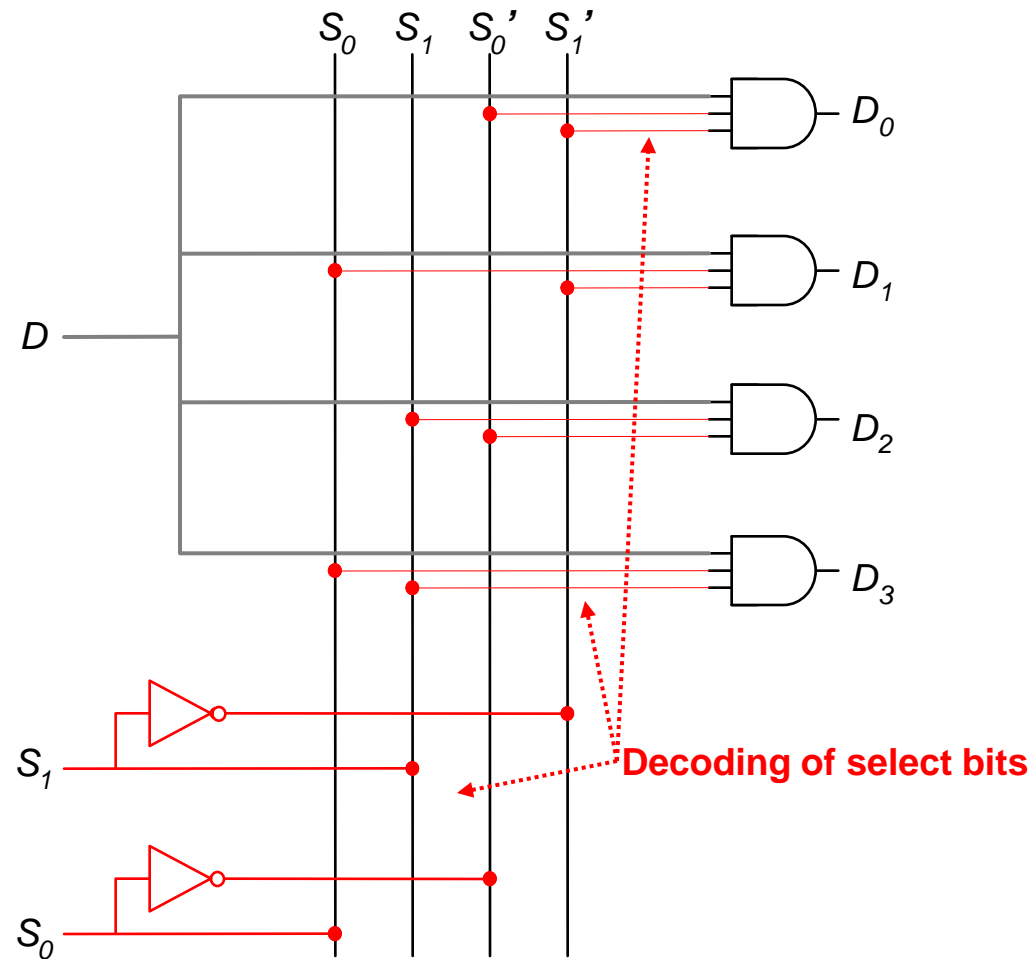

1-to-4 Demux

# Demultiplexer Design

Notice D runs to all 4 output AND gates

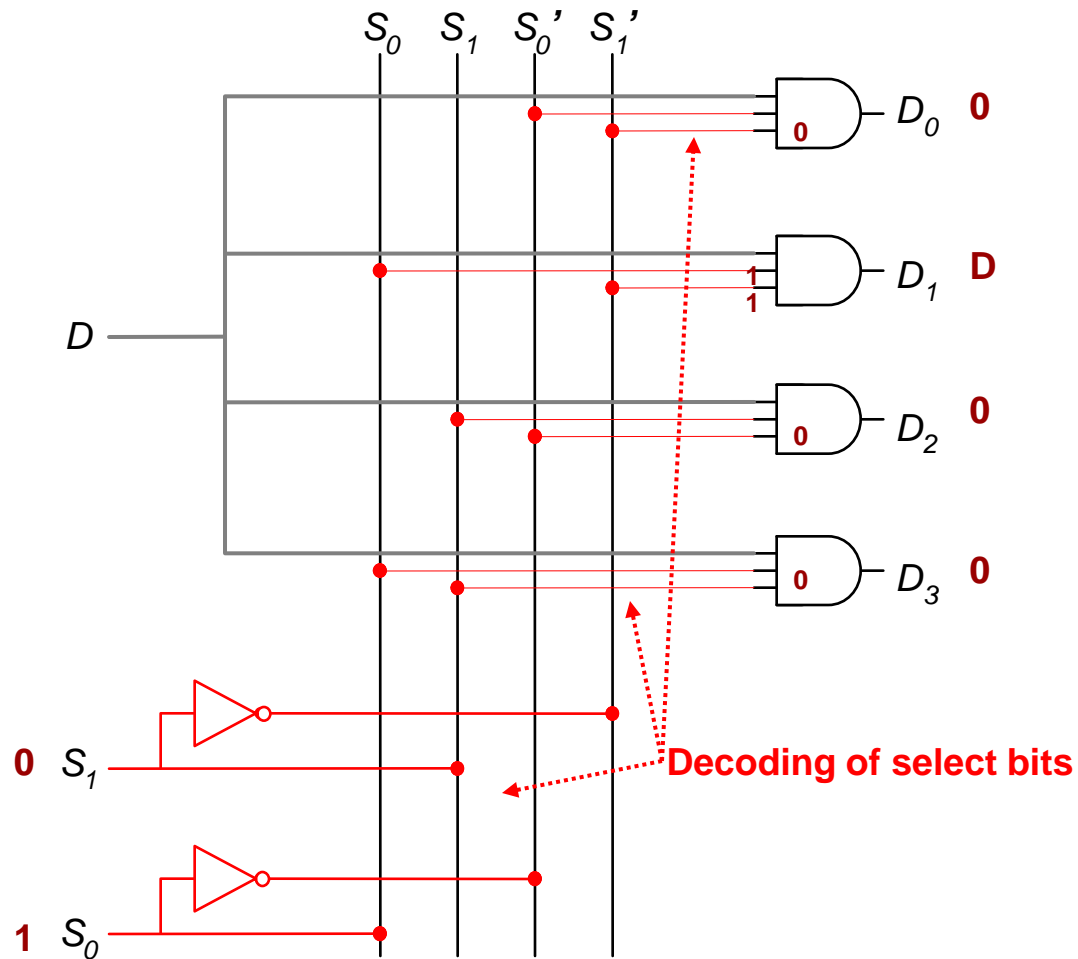


1-to-4 Demux



 
# Demultiplexers and Decoders

- Demultiplexers are actually just decoders w/ an enable (must have an enable)



1-to-4 Demux

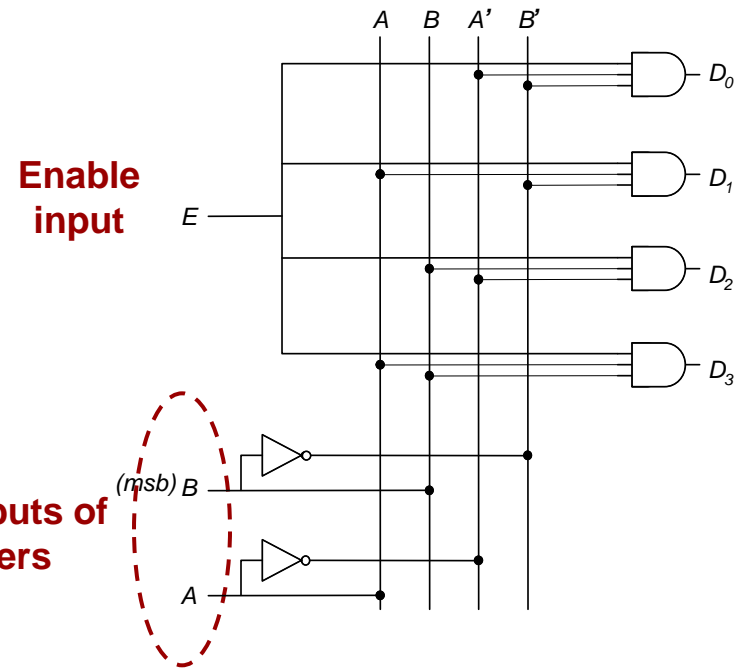


2-to-4 Decoder w/ Enable


= Binary inputs of Decoders
 
# Mux Active Levels


- We don't think of mux inputs/outputs as active or inactive
- Instead we count how many inversions “a single path” hits from input to output (don't count total inversions) and list the mux as “inverting” (odd # of inversions) or non-inverting (even # of inversions)




**Non-Inverting  
Mux**

 

**Inverting Mux**

 


**Inverting Mux**

 


**Non-Inverting  
Mux**


# Demux Active Levels

 


**Non-Inverting  
Demux**

 

**Inverting  
Demux**

 

**Inverting  
Demux**

 

**Non-Inverting  
Demux**


# ADDERS

# Addition – Half Adders

- Addition is done in columns
  - Inputs are the bit of X, Y
  - Outputs are the Sum Bit and Carry-Out ( $C_{out}$ )
- Design a Half-Adder (HA) circuit that takes in X and Y and outputs S and  $C_{out}$

X	Y	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
 
$$\begin{array}{r}
 C_{out} \\
 110 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101 \\
 \text{Sum}
 \end{array}$$



# Adder Intro


- Design a circuit to add two 4-bit numbers,  $X[3:0]$  and  $Y[3:0]$ 
  - How many inputs?
  - Can we use K-Maps or Minterms or decoders + an OR gate, etc?

$$\begin{array}{rcl}
 0110 & = & X \\
 + 0111 & = & Y \\
 \hline
 1101 & & 
 \end{array}$$
 
# Addition – Half Adders

- We'd like to use one adder circuit for each column of addition
- Problem:
  - No place for Carry-out of last adder circuit
- Solution
  - Redesign adder circuit to include an input for the carry

$$\begin{array}{r}
 110 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$




# Addition – Full Adders

- Add a Carry-In input( $C_{in}$ )
- New circuit is called a Full Adder (FA)

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{array}{r}
 \phantom{+} 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$

Diagram illustrating the addition of two 4-bit numbers, X (0110) and Y (0111), resulting in a 4-bit sum (1101) and a carry-out (1). The carry-in ( $C_{in}$ ) is 0. The carry-out ( $C_{out}$ ) is 1. The sum is 1101.

 





# Addition – Full Adders

- Find the minimal 2-level implementations for  $C_{out}$  and  $S$ ...

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1
  
# Full Adder Logic


- $S = X \text{ xor } Y \text{ xor } C_{in}$ 
  - Recall: XOR is defined as true when ODD number of inputs are true...exactly when the sum bit should be 1
- $C_{out} = XY + XC_{in} + YC_{in}$ 
  - Carry when sum is 2 or more (i.e. when at least 2 inputs are 1)
  - Circuit is just checking all combinations of 2 inputs


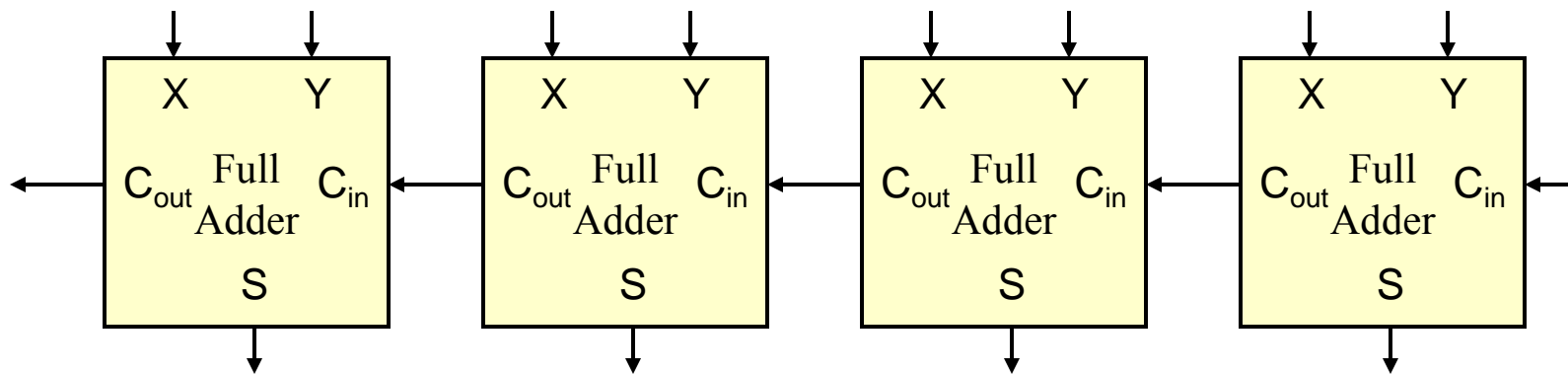
# Addition – Full Adders

- Use 1 Full Adder for each column of addition

$$\begin{array}{r} 0110 \\ + 0111 \\ \hline \end{array}$$




# Addition – Full Adders

- Connect bits of top number to X inputs

0110

+ 0111


---

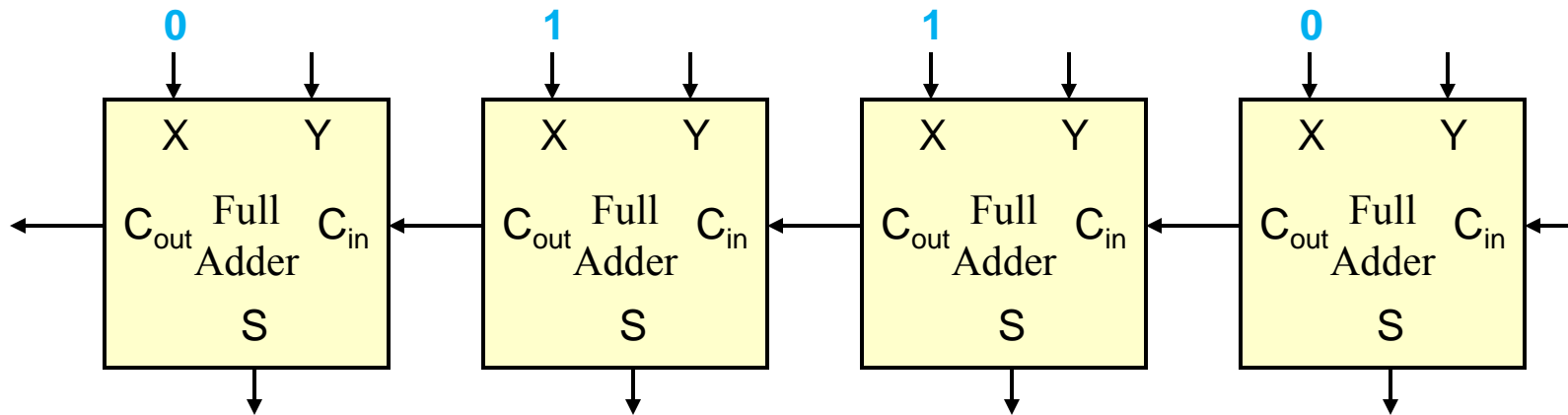
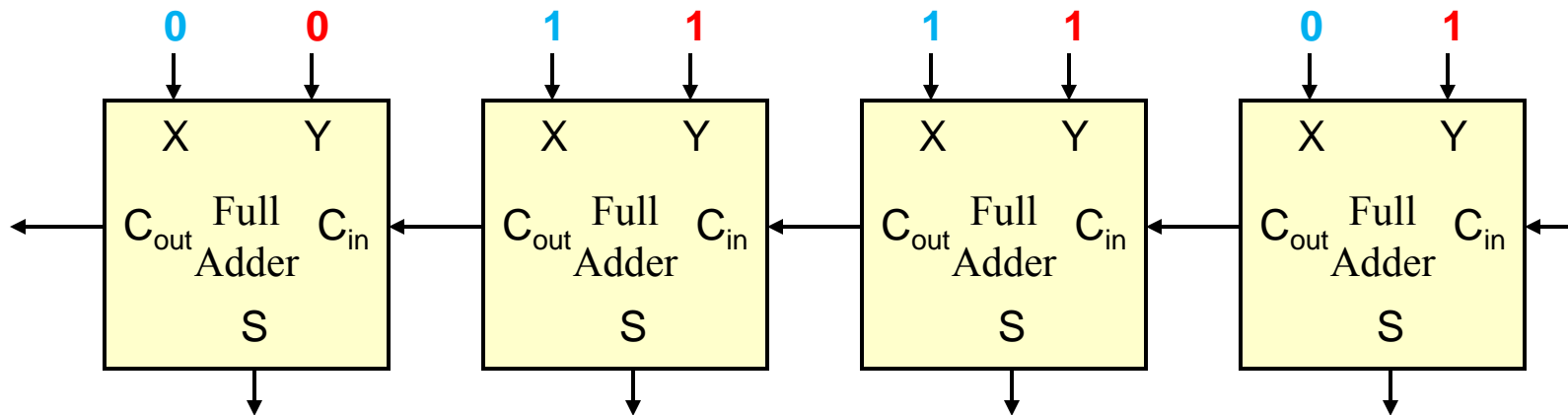
# Addition – Full Adders

- Connect bits of bottom number to Y inputs


$$\begin{array}{r} 0110 = X \\ + 0111 = Y \\ \hline \end{array}$$


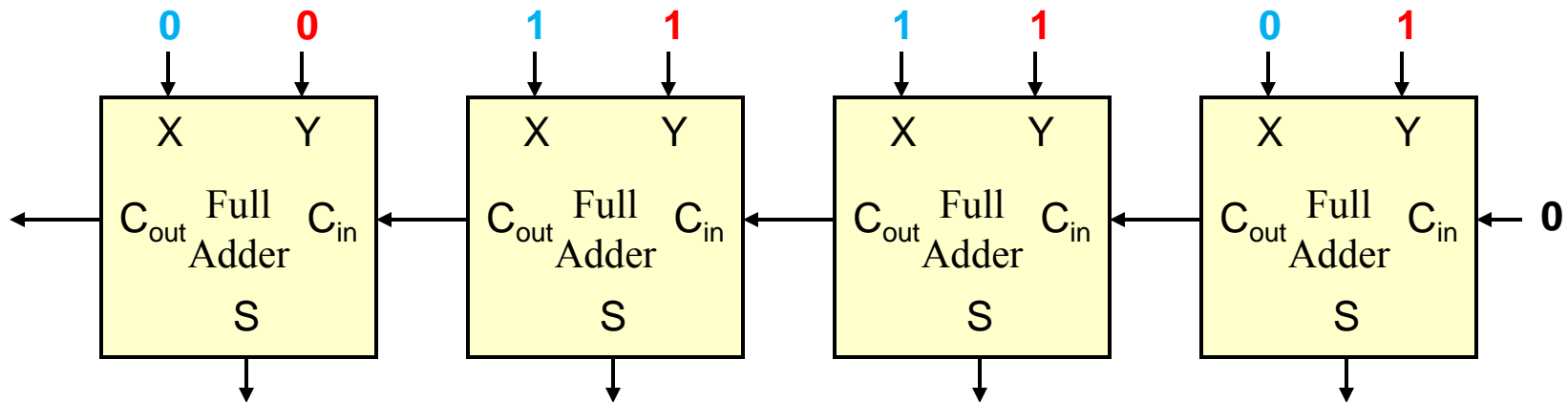
# Addition – Full Adders

- Be sure to connect first  $C_{in}$  to 0


$$\begin{array}{r} 0110 = X \\ + 0111 = Y \\ \hline \end{array}$$


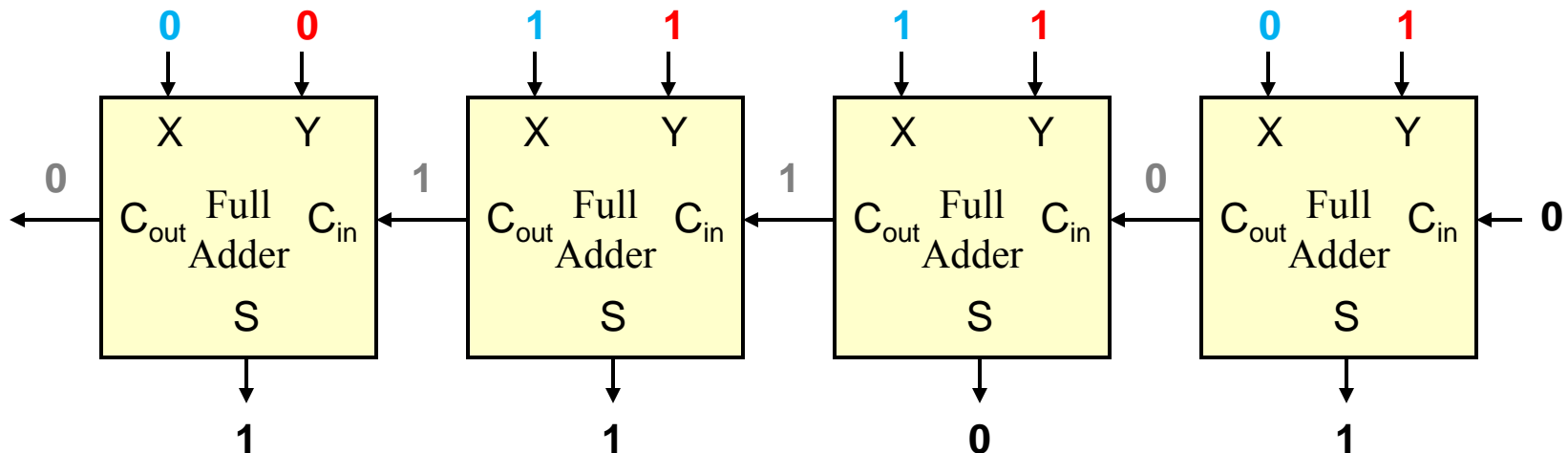
# Addition – Full Adders

- Use 1 Full Adder for each column of addition


$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$


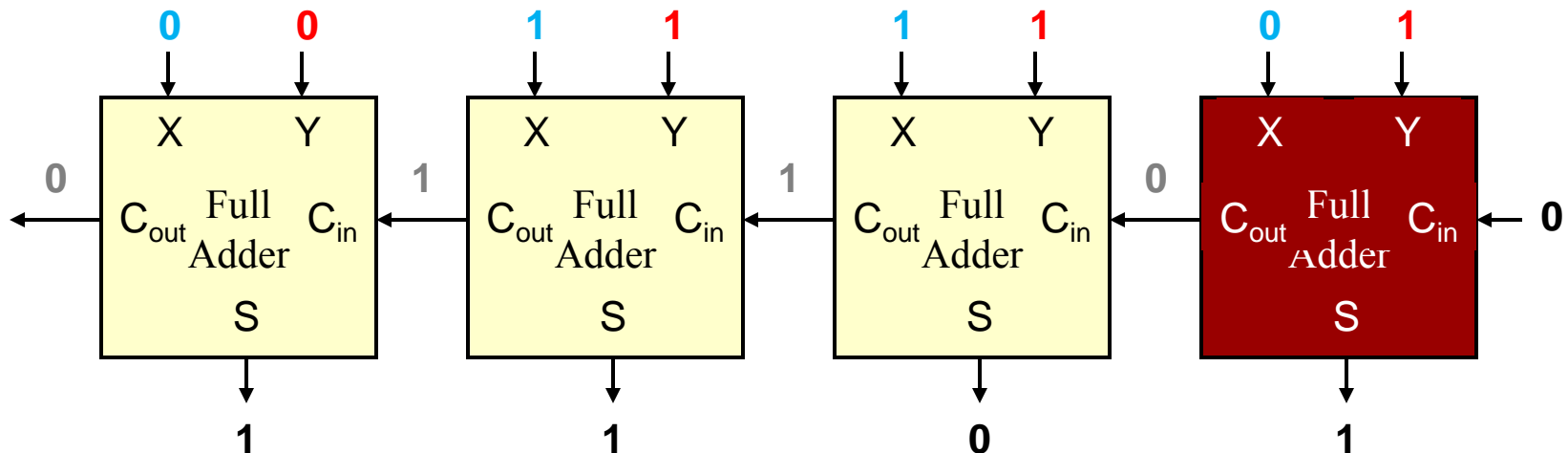
# Addition – Full Adders

- Use 1 Full Adder for each column of addition

$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$





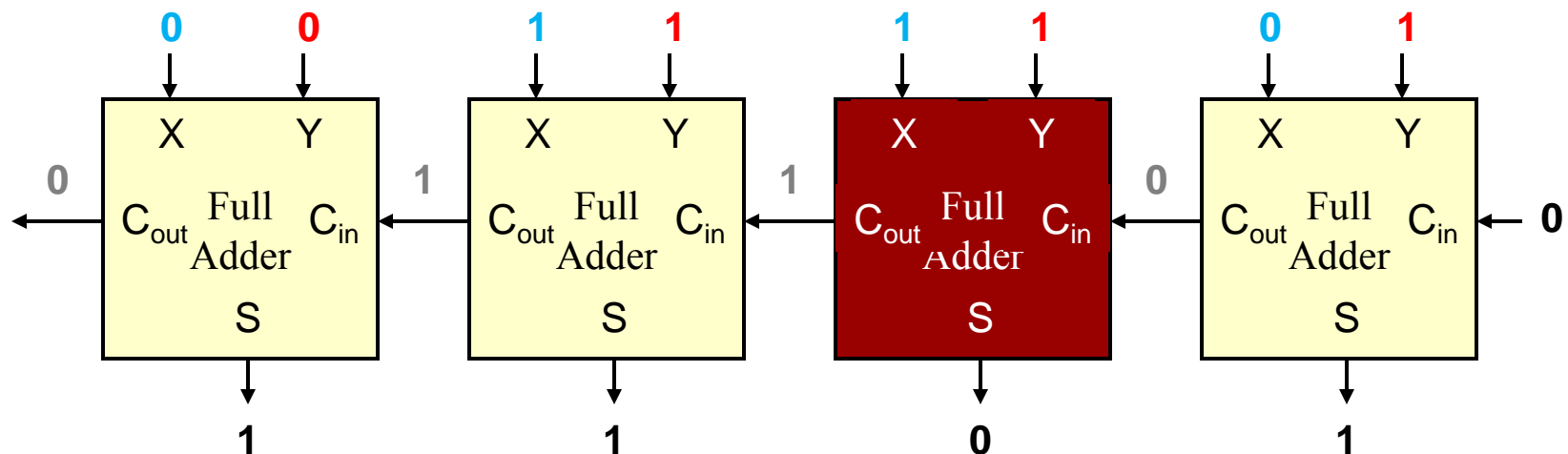
# Addition – Full Adders

- Use 1 Full Adder for each column of addition


$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$


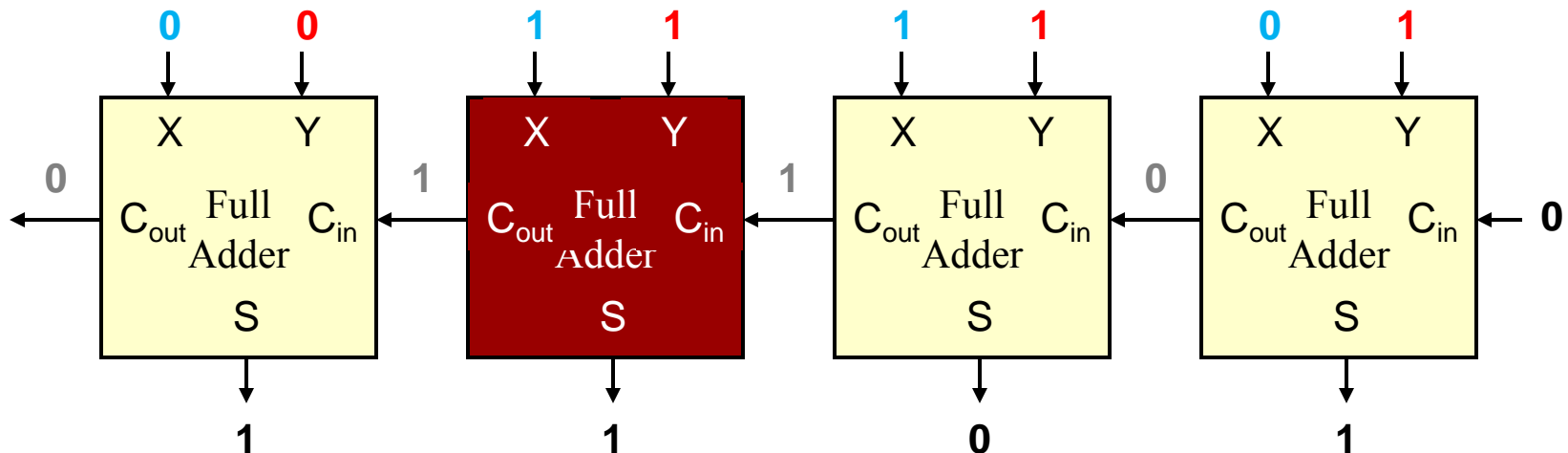
# Addition – Full Adders

- Use 1 Full Adder for each column of addition


$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$


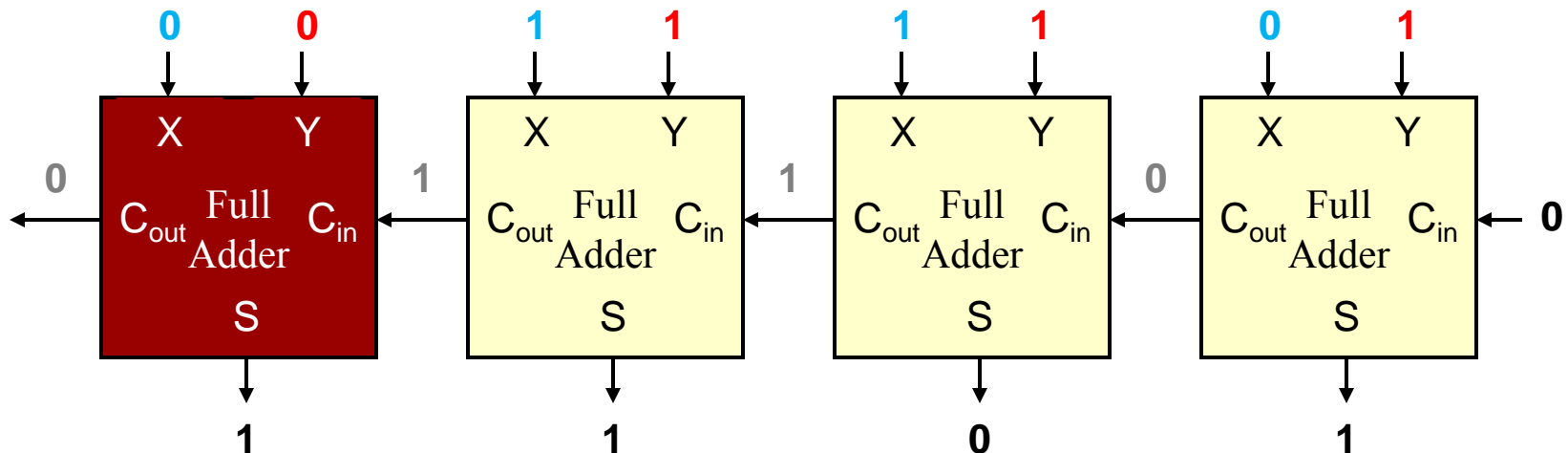
# Addition – Full Adders

- Use 1 Full Adder for each column of addition


$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$


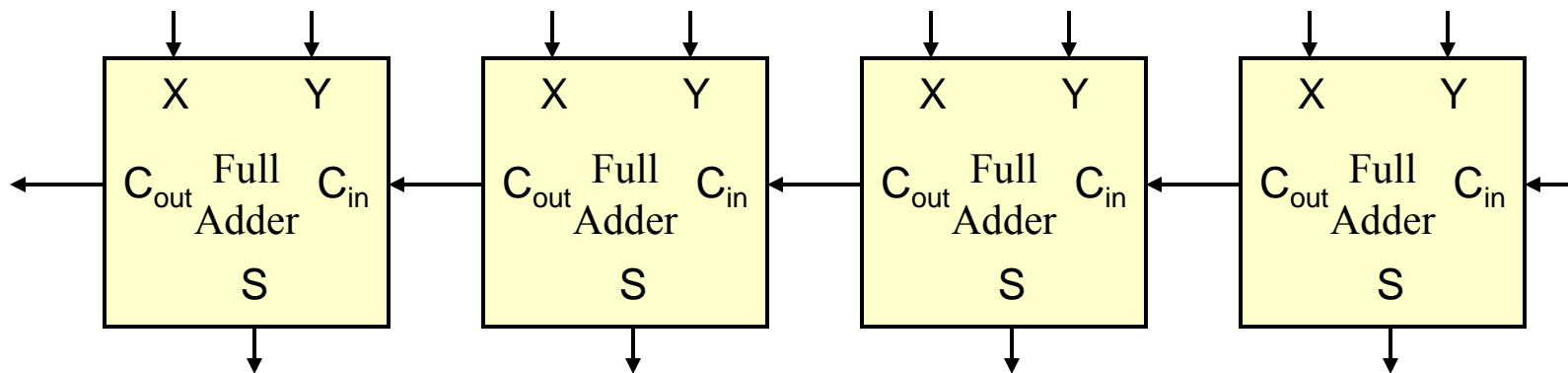
# Performing Subtraction w/ Adders

- To subtract
  - Flip bits of Y
  - Add 1


$$\begin{array}{r}
 0101 = X \\
 - 0011 = Y \\
 \hline
 0010
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1100 \\
 + 1 \\
 \hline
 0010
 \end{array}$$


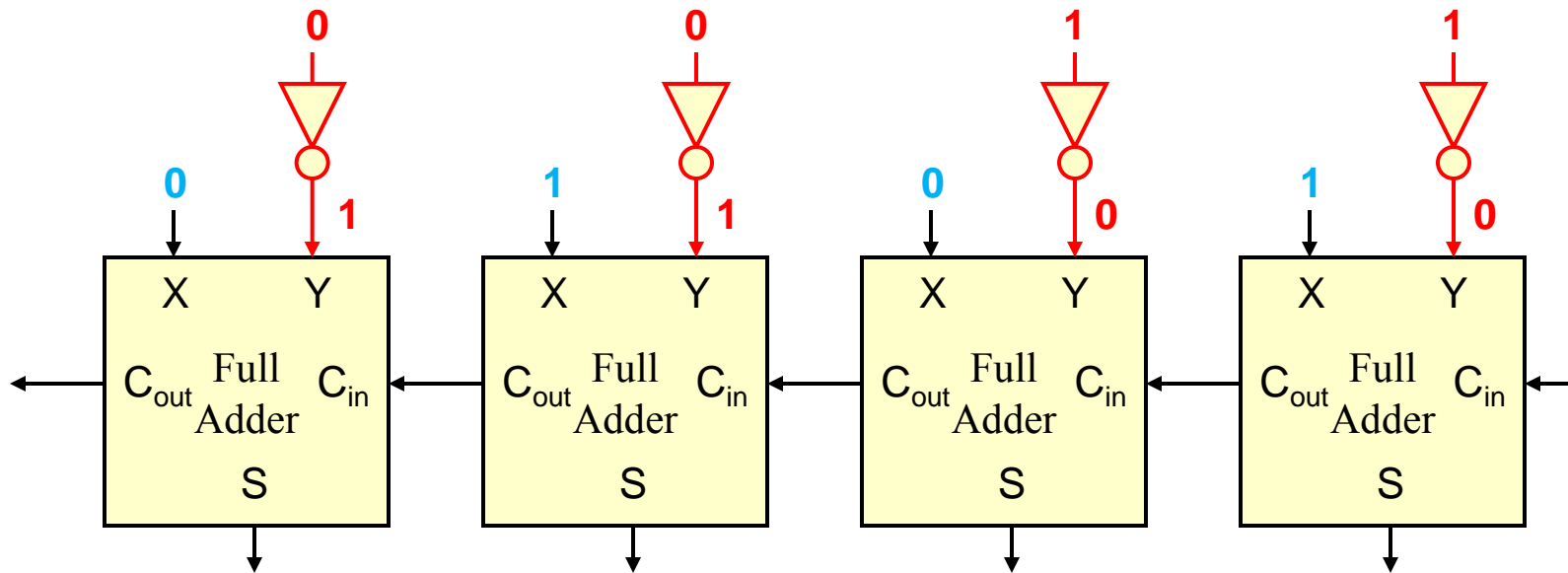
# Performing Subtraction w/ Adders

- To subtract
  - Flip bits of Y
  - Add 1


$$\begin{array}{r}
 0101 = X \\
 - 0011 = Y \\
 \hline
 0010
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1100 \\
 + 1 \\
 \hline
 0010
 \end{array}$$


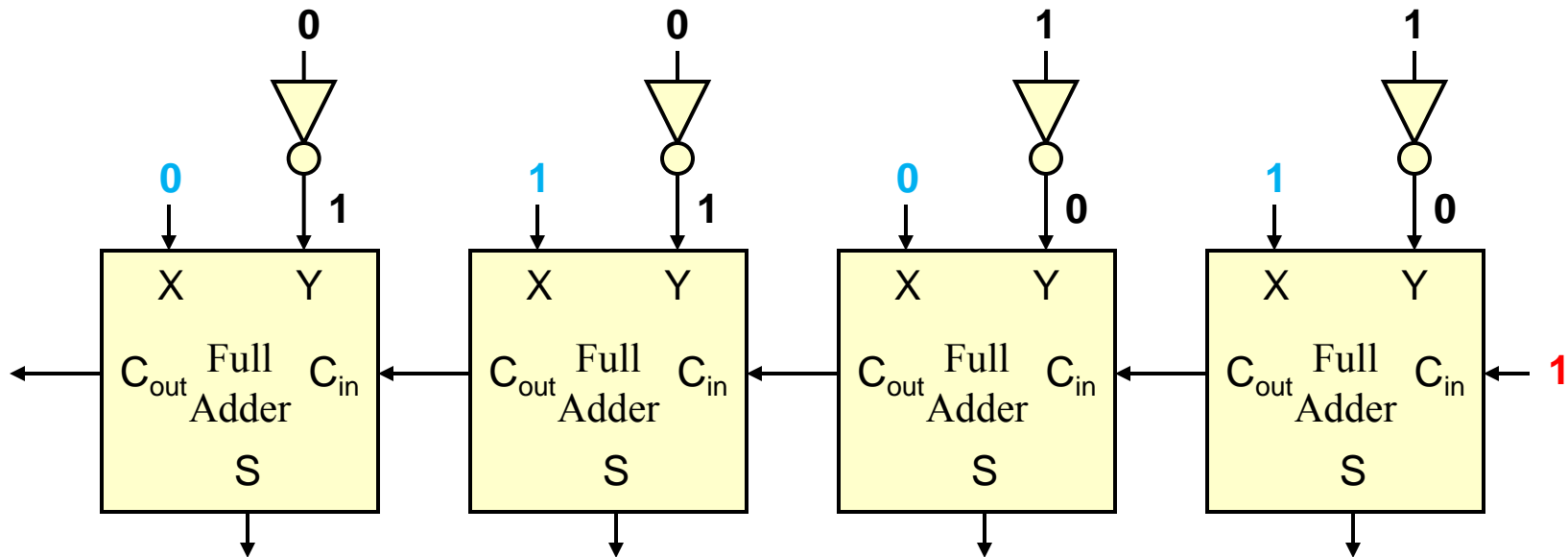
# Performing Subtraction w/ Adders

- To subtract
  - Flip bits of Y
  - Add 1


$$\begin{array}{r}
 0101 = X \\
 - 0011 = Y \\
 \hline
 0010
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1100 \\
 \hline
 1 \\
 0010
 \end{array}$$


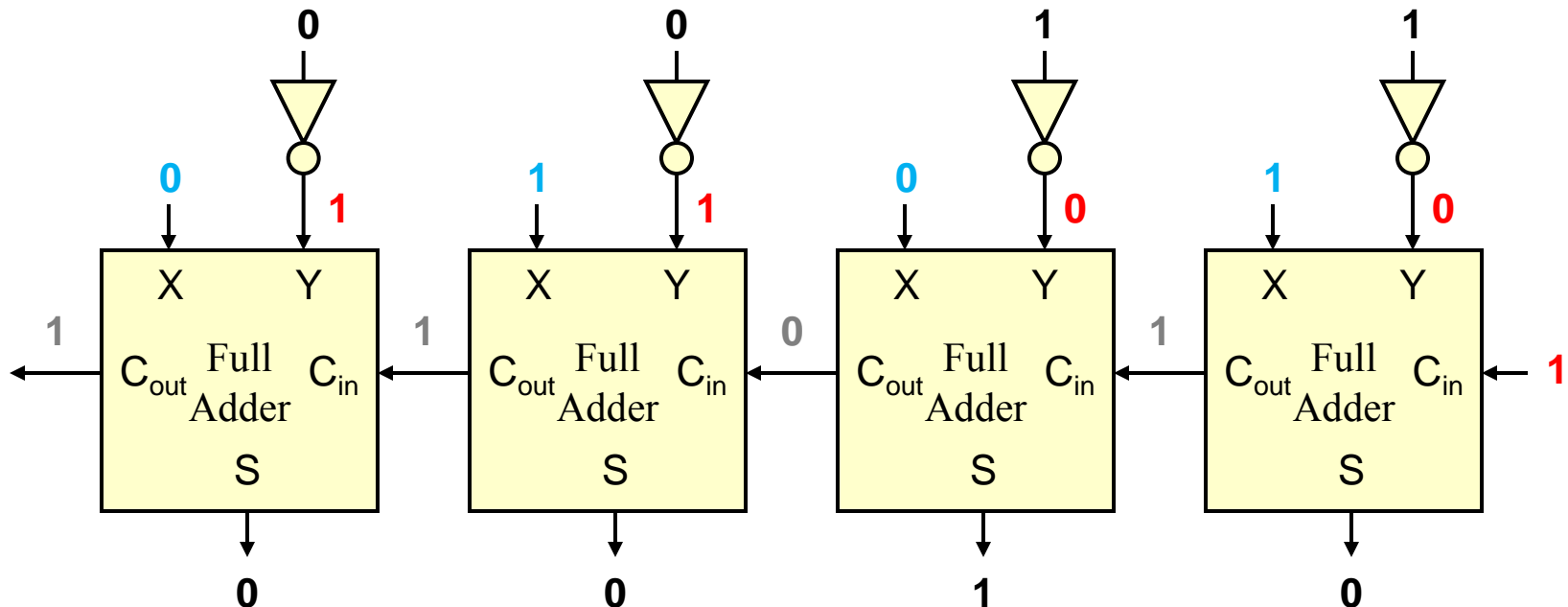
# Performing Subtraction w/ Adders

- To subtract
  - Flip bits of Y
  - Add 1

$$\begin{array}{r}
 0101 = X \\
 - 0011 = Y \\
 \hline
 0010
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1100 \\
 \hline
 1 \\
 0010
 \end{array}$$



# OVERFLOW



# Overflow


- Overflow occurs when the result of an arithmetic operation is too large to be represented with the given number of bits
  - Unsigned overflow occurs when adding or subtracting unsigned numbers
  - Signed (2's complement overflow) overflow occurs when adding or subtracting 2's complement numbers

# Unsigned Overflow

Overflow occurs when you cross  
this discontinuity

$$10 + 7 = 17$$

 With 4-bit *unsigned* numbers we  
can only represent 0 – 15. Thus,  
we say overflow has occurred.




# 2's Complement Overflow

$$5 + 7 = +12$$

$$-6 + -4 = -10$$

 With 4-bit 2's complement numbers we can only represent -8 to +7. Thus, we say overflow has occurred.



Overflow occurs when you cross this discontinuity

# Testing for Overflow

- Most fundamental test
  - Check if answer is wrong (i.e. Positive + Positive yields a negative)
- Unsigned overflow test
  - If carry-out of final position equals '1'
- Signed (2's complement) overflow test
  - Only occurs if two positives are added and result is negative or two negatives are added and result is positive
  - Alternate test: if carry-in and carry-out of final position are different

# Testing for Unsigned Overflow

- Unsigned Overflow test
  - Unsigned Addition: If final carry-out = 1

$$\begin{array}{r} 1011 \\ + 0110 \\ \hline \end{array}$$

$$\begin{array}{r} 1011 \\ + 0011 \\ \hline \end{array}$$

# Testing for Unsigned Overflow

- Unsigned Overflow test
  - Unsigned Addition: If final carry-out = 1

Final carry-out = 1,  
thus overflow

$$\begin{array}{r}
 \text{1} \quad \text{1} \quad \text{1} \\
 \phantom{1} \phantom{1} \phantom{1} \phantom{1} \\
 1011 \\
 + 0110 \\
 \hline
 0001
 \end{array}$$

Final carry-out = 0,  
thus no overflow

$$\begin{array}{r}
 \text{0} \quad \text{0} \quad \text{1} \quad \text{1} \\
 \phantom{0} \phantom{0} \phantom{1} \phantom{1} \phantom{1} \phantom{1} \\
 1011 \\
 + 0011 \\
 \hline
 1110
 \end{array}$$

# Testing for 2's Comp. Overflow

- 2's Complement Overflow Occurs If...
  - Test 1: If pos. + pos. = neg. or neg. + neg. = pos.
  - Test 2: If carry-in to MSB position and carry-out of MSB position are different

$$\begin{array}{r} 0101 \quad (5) \\ + 0110 \quad (6) \\ \hline \end{array}$$

$$\begin{array}{r} 1100 \quad (-4) \\ + 1001 \quad (-7) \\ \hline \end{array}$$

$$\begin{array}{r} 0011 \quad (3) \\ + 0010 \quad (2) \\ \hline \end{array}$$

$$\begin{array}{r} 1110 \quad (-2) \\ + 1010 \quad (-6) \\ \hline \end{array}$$

# Testing for 2's Comp. Overflow

- 2's Complement Overflow Occurs If...
  - Test 1: If pos. + pos. = neg. or neg. + neg. = pos.
  - Test 2: If carry-in to MSB position and carry-out of MSB position are different

Carry-in to MSB and carry-out of MSB position are *different...Overflow!*

$$\begin{array}{r}
 \text{0 1} \nearrow \\
 0101 \quad (5) \\
 + 0110 \quad (6) \\
 \hline
 1011 \quad (-5)
 \end{array}$$

Carry-in to MSB and carry-out of MSB position are *different...Overflow!*

$$\begin{array}{r}
 \text{1 0} \nearrow \\
 1100 \quad (-4) \\
 + 1001 \quad (-7) \\
 \hline
 0101 \quad (+5)
 \end{array}$$

Carry-in to MSB and carry-out of MSB position are *same...No Overflow!*

$$\begin{array}{r}
 \text{0 0} \nearrow \\
 0011 \quad (3) \\
 + 0010 \quad (2) \\
 \hline
 0101 \quad (5)
 \end{array}$$


Carry-in to MSB and carry-out of MSB position are *same...No Overflow!*

$$\begin{array}{r}
 \text{1 1} \nearrow \\
 1110 \quad (-2) \\
 + 1010 \quad (-6) \\
 \hline
 1000 \quad (-8)
 \end{array}$$


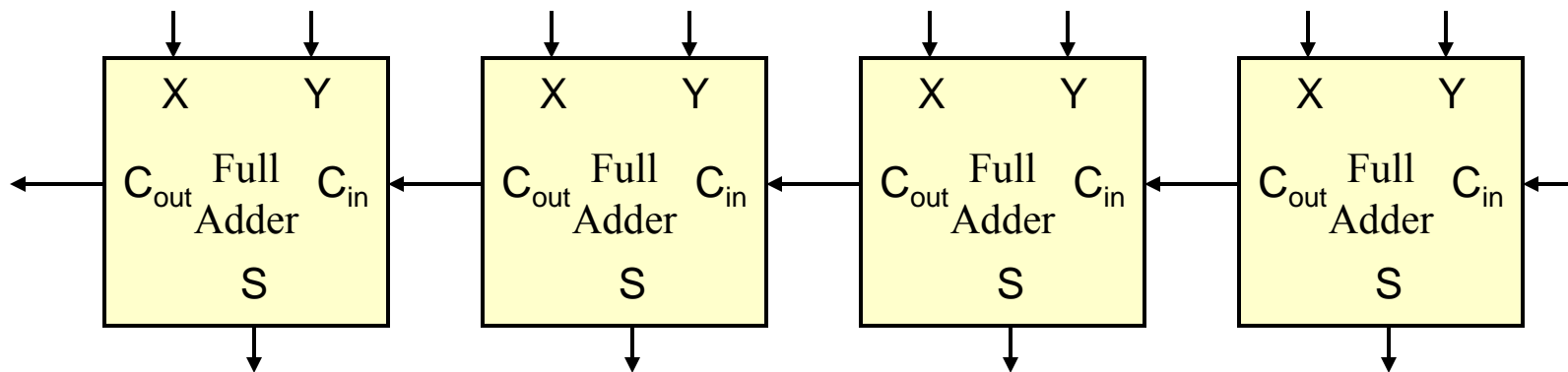
# Checking for Overflow


- Produce additional outputs to indicate if unsigned (UOV) or signed (SOV) overflow has occurred



# ADDER DELAY
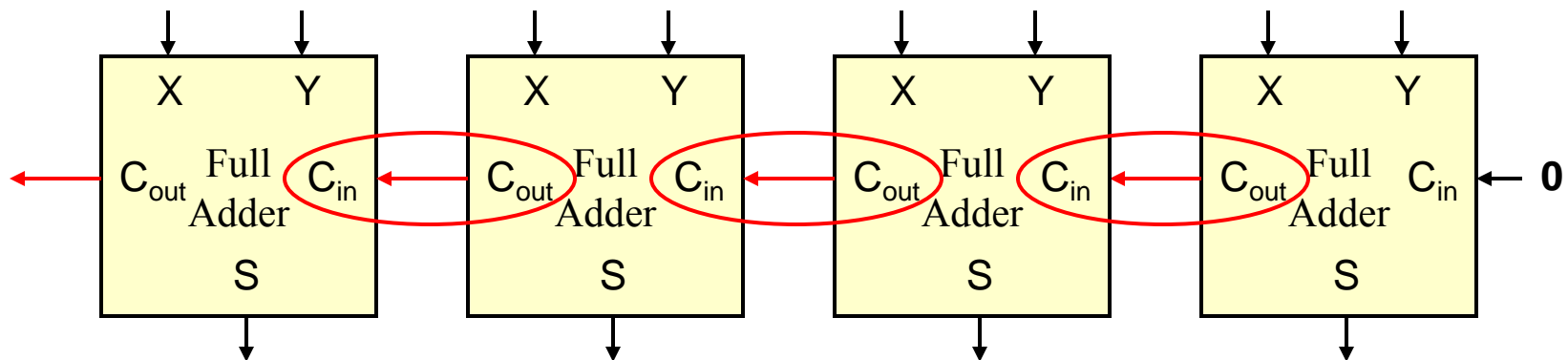
# Timing

- A chain of full adders presents an interesting timing analysis problem
- To correctly compute its own Sum and Carry-out, each full adder requires the carry-in bit from the previous full adder
- Because hardware works in parallel, the full adders further down the chain may momentarily produce the wrong outputs because the carry has not had time to propagate to them



# Timing Example

- Assume that we were adding one set of inputs and then change to a new set of inputs:

Old inputs:

0000

0010 = X

+ 0001 = Y

0011

New inputs:


1111

1111 = X

+ 0001 = Y

0000

Old inputs:

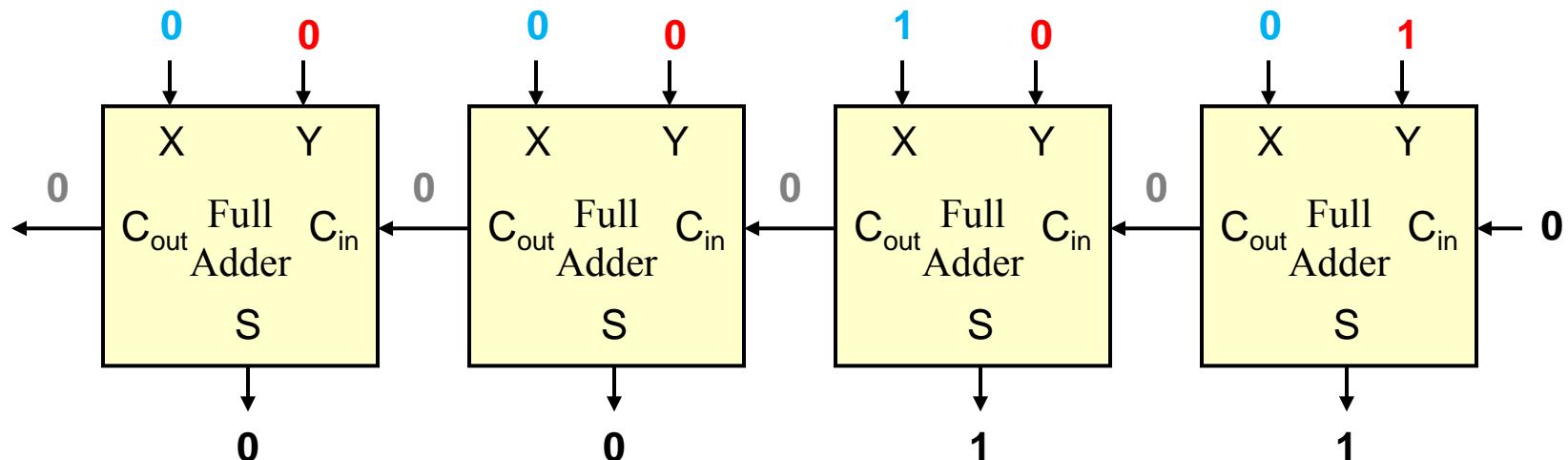

# Timing

- At the time just before we enter the new input values, all carries are 0's

New inputs:

0000


0010 = X

+ 0001 = Y

0011

Time  
-1

Old inputs:

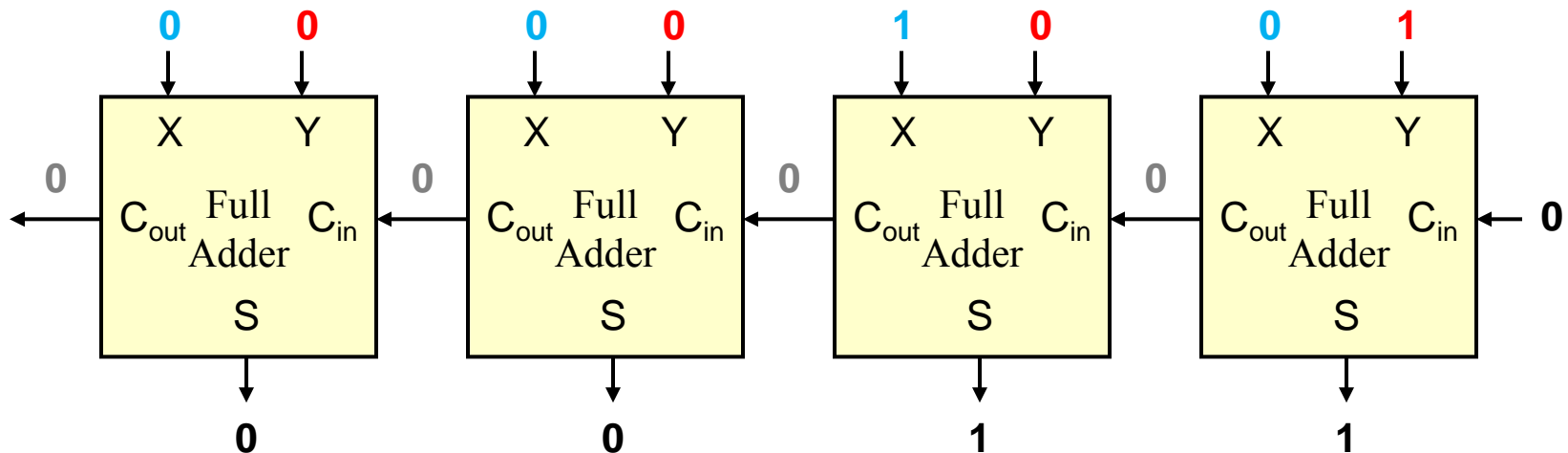


# Timing

- Now we enter the new inputs and all the FA's starting adding their respective inputs

$$\begin{array}{r}
 1111 \\
 1111 = X \\
 + 0001 = Y \\
 \hline
 0000
 \end{array}$$

Time  
0

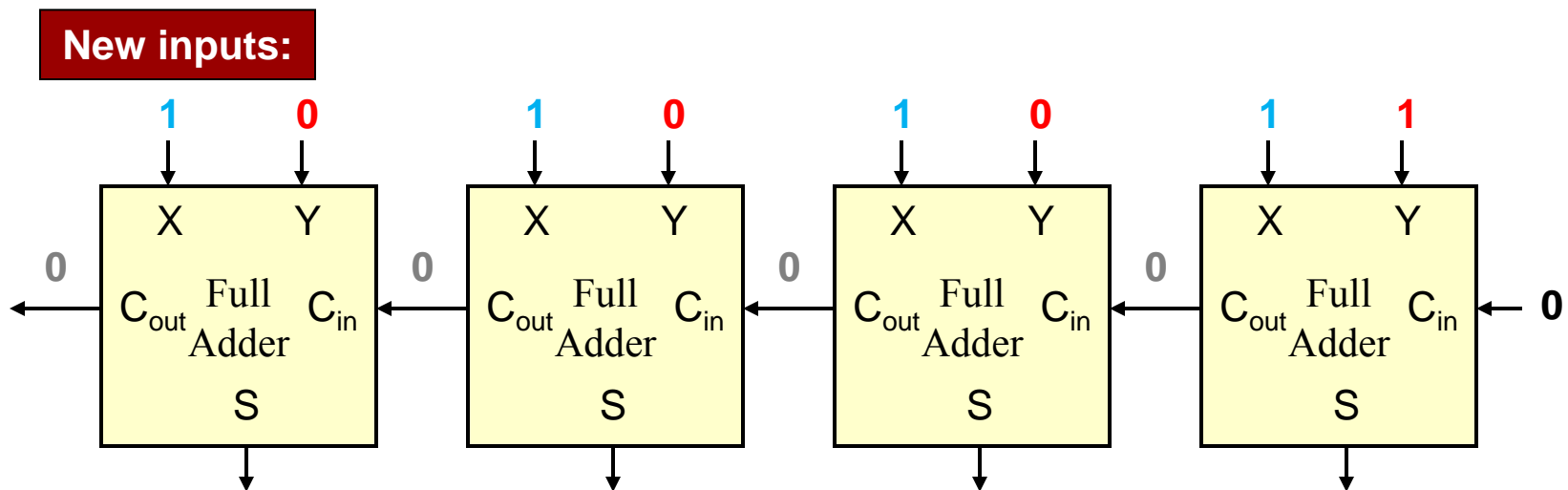

**Due to propagation delay, the carries are still from the old inputs**

# Timing

- Each adder computes from the current inputs (notice the sum of 1110 is incorrect at this point)


1111

1111 = X

+ 0001 = Y

0000

Time  
1

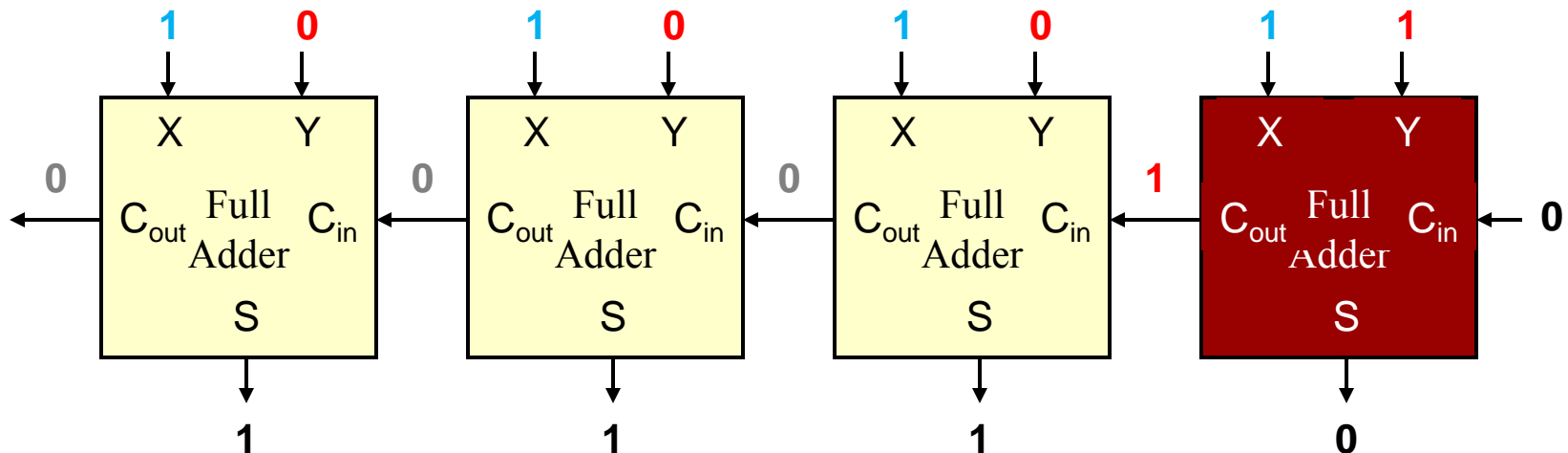


Now the carries are all based off the new inputs

# Timing

- The carry is “rippling” through each adder

$$\begin{array}{r}
 1111 \\
 1111 = X \\
 + 0001 = Y \\
 \hline
 0000
 \end{array}$$

Time  
2

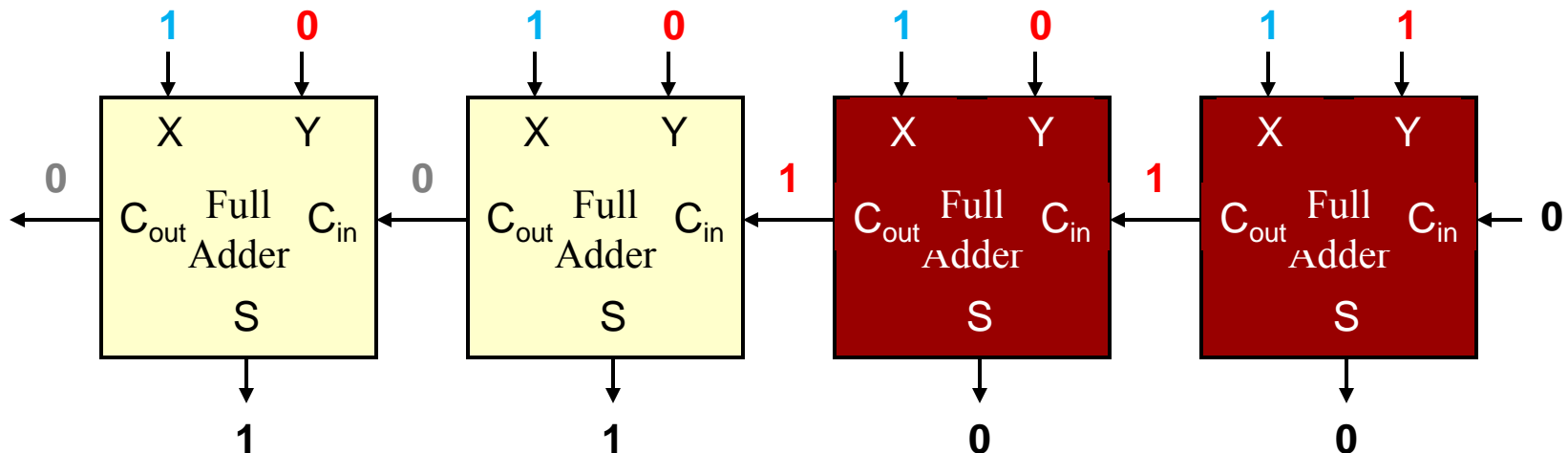




# Timing

- The carry is “rippling” through each adder

$$\begin{array}{r}
 1111 \\
 1111 = X \\
 + 0001 = Y \\
 \hline
 0000
 \end{array}$$

Time  
3

 

# Timing

- Only after the carry propagates through all the adders is the sum valid and correct


1111

1111 = X



+ 0001 = Y

0000

Time  
4

 


  - The longest path through a chain of full adders is the carry path
- We say that the carry “ripples” through the adder


 
# Ripple Carry Adder Delay

- An n-bit ripple carry adder has a worst case delay proportional to n (i.e. n-bits => n columns of addition => n-full adders)





# Glitches

- Transient, incorrect output values due to differing arrival times of gate inputs
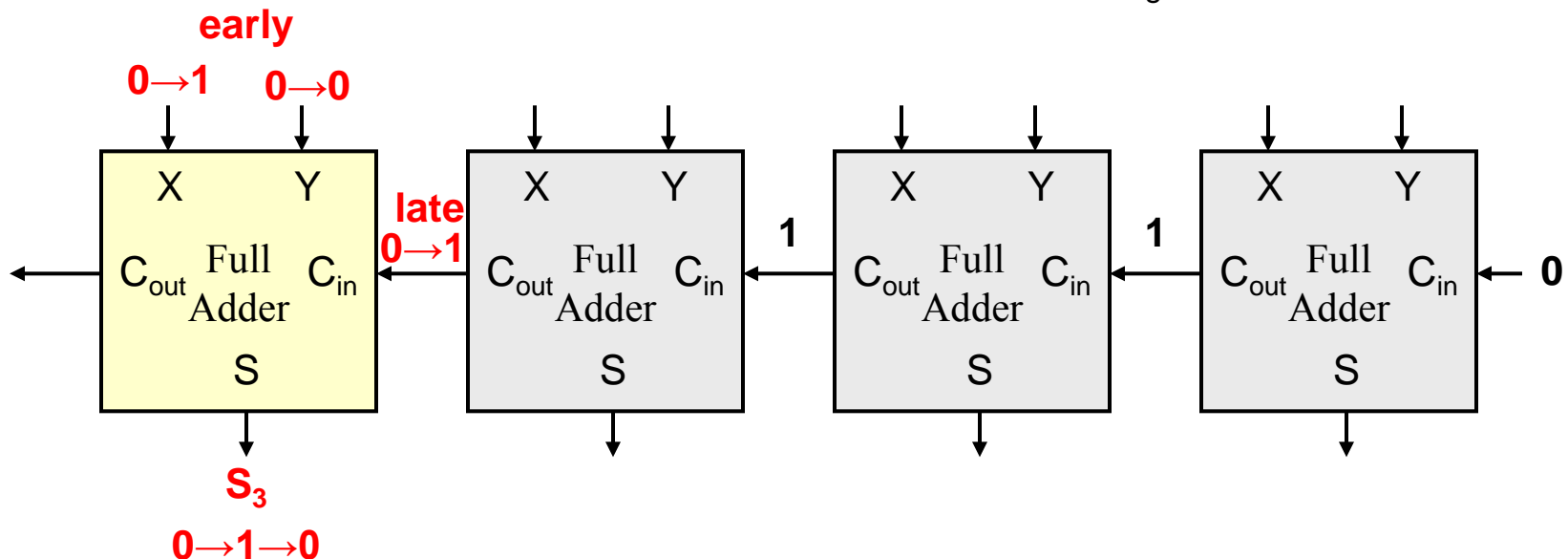 
# Output Glitches

- Delay of the carry causes glitches on the sum bits
- Glitch = momentarily, incorrect output value




# Critical Path

- Critical Path = Longest possible delay path

Assume  $t_{\text{sum}} = 5 \text{ ns}$ ,


$t_{\text{carry}} = 4 \text{ ns}$

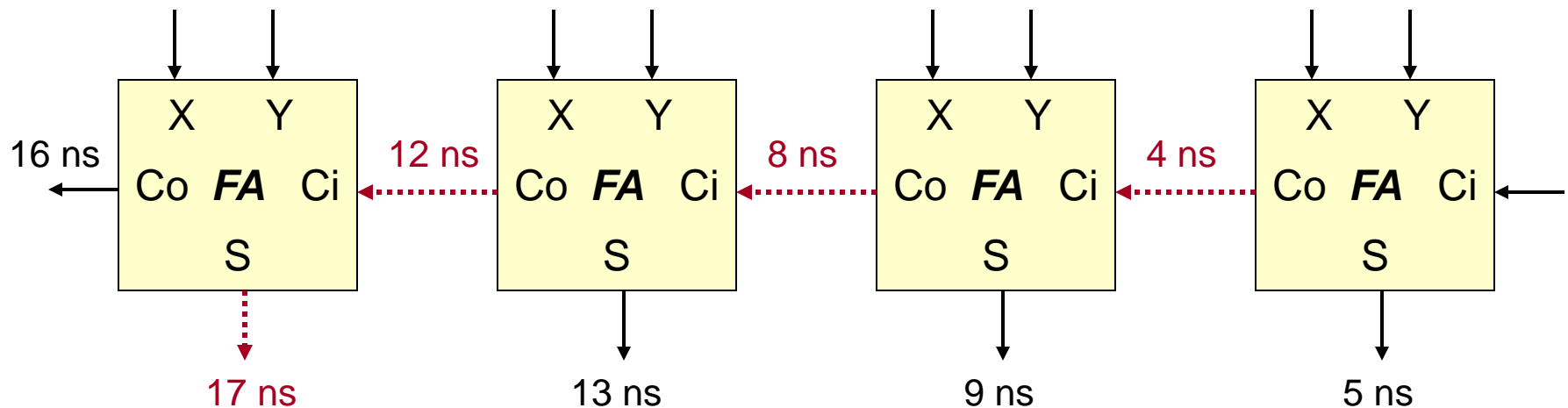

←..... Critical Path
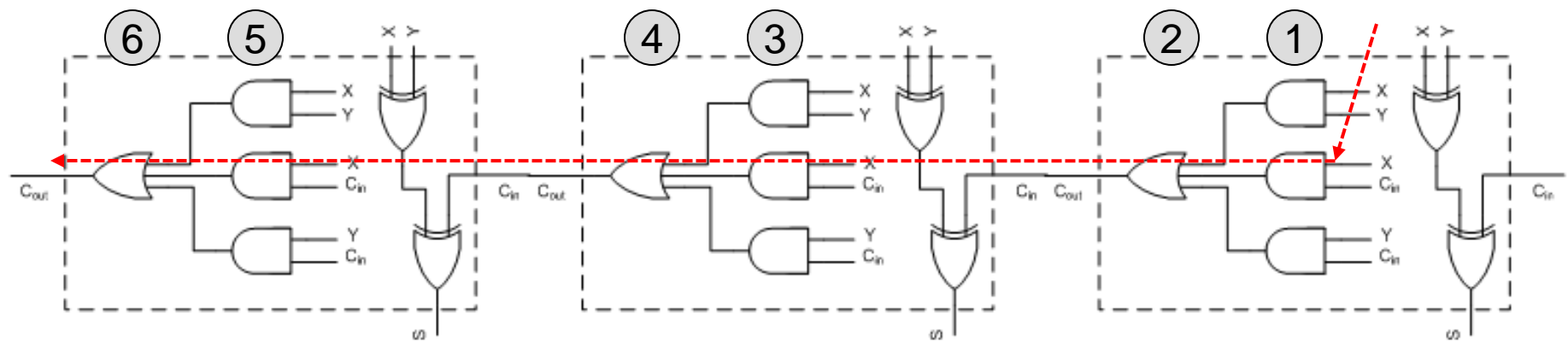
# Ripple Carry Adders

- Ripple-carry adders (RCA) are slow due to carry propagation
  - At least 2 levels of logic per full adder





# Fast Adders

- Rather than calculating one carry at a time and passing it down the chain, can we compute a group of carries at the same time
- To do this, let us define some new signals for each column of addition:
  - $p_i$  = Propagate: This column will propagate a carry-in (if there is one) to the carry-out.  
 $p_i$  is true when  $A_i$  or  $B_i$  is 1  $\Rightarrow p_i = A_i + B_i$
  - $g_i$  = Generate: This column will generate a carry-out whether or not the carry-in is '1'  
 $g_i$  is true when  $A_i$  and  $B_i$  is 1  $\Rightarrow g_i = A_i \cdot B_i$
- Using these signals, we can define the carry-out ( $c_{i+1}$ ) as:

$$c_{i+1} = g_i + p_i c_i$$

# Carry Lookahead Logic


- Define each carry in terms of  $p_i$ ,  $g_i$  and the initial carry-in ( $c_0$ ) and not in terms of carry chain (intermediate carries:  $c_1, c_2, c_3, \dots$ )
- $c_1 =$
- $c_2 =$
- $c_3 =$
- $c_4 =$


# Carry Lookahead Logic

- Define each carry in terms of  $p_i$ ,  $g_i$  and the initial carry-in ( $c_0$ ) and not in terms of carry chain (intermediate carries:  $c_1, c_2, c_3, \dots$ )
- $c_1 = g_0 + p_0 c_0$
- $c_2 = g_1 + p_1 c_1 = g_1 + p_1 g_0 + p_1 p_0 c_0$
- $c_3 = \dots$
- $c_4 = \dots$
 
# Carry Lookahead Analogy


- Consider the carry-chain like a long tube broken into segments. Each segment is controlled by a valve (propagate signal) and can insert a fluid into that segment (generate signal)
- The carry-out of the diagram below will be true if  $g_1$  is true or  $p_1$  is true and  $g_0$  is true, or  $p_1$ ,  $p_0$  and  $c_0$  is true



 

 
# Carry Lookahead Adder

- Use carry-lookahead logic to generate all the carries in one shot and then create the sum
- Example 4-bit CLA shown below


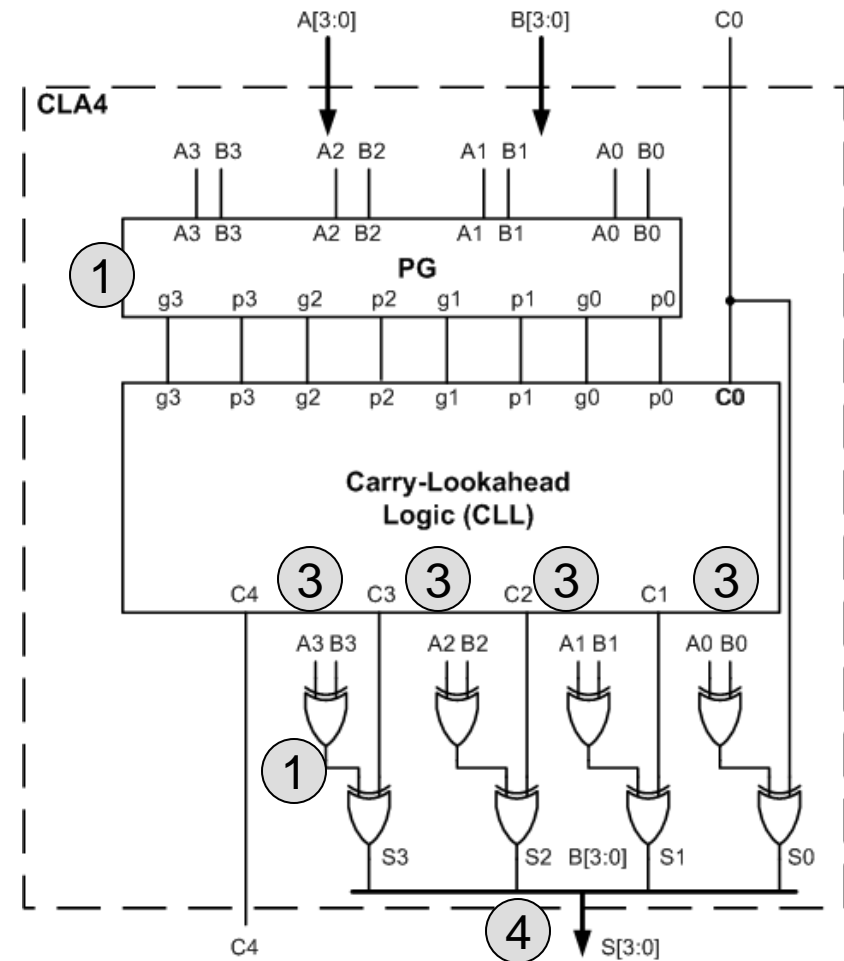
# Carry Lookahead Adder


- Use carry-lookahead logic to generate all the carries in one shot and then create the sum
- Example 4-bit CLA shown below


 
# 4-bit Adders

- 74LS283 chip implements a 4-bit adder using CLA methodology


$$\begin{array}{r}
 A_3 A_2 A_1 A_0 = A \\
 + B_3 B_2 B_1 B_0 = B \\
 \hline
 S_4 S_3 S_2 S_1 S_0 = S
 \end{array}$$




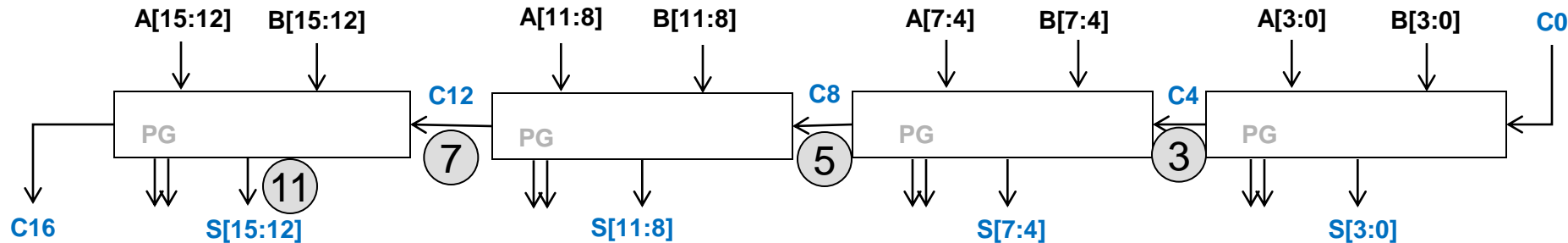
# 16-Bit CLA

- At this point we should probably stop as we have a 5-input gate in our equation



16-bit RCA Delay =  $16 \times 2 = 32$  gate delays

Delay of the above adder design =  $3 + 2 + 2 + 4 = 11$  gates

Let us improve by looking ahead at a higher level to produce C16, C12, C8, C4 in parallel

What's the difference between the equation for G here and C4 on the previous slides

Define P and G as the overall Propagate and Generate signals for a set of 4 bits

$$P = p_3 \bullet p_2 \bullet p_1 \bullet p_0$$


$$G = g_3 + p_3 \bullet g_2 + p_3 \bullet p_2 \bullet g_1 + p_3 \bullet p_2 \bullet p_1 \bullet g_0$$

# 16-bit CLA Closer Look

- Each 4-bit CLA only propagates its overall carry-in if each of the 4 columns propagates:
  - $P0 = p3 \bullet p2 \bullet p1 \bullet p0$
  - $P1 = p7 \bullet p6 \bullet p5 \bullet p4$
  - $P2 = p11 \bullet p10 \bullet p9 \bullet p8$
  - $P3 = p15 \bullet p14 \bullet p13 \bullet p12$
- Each 4-bit CLA generates a carry if any column generates and the more significant columns propagate
  - $G0 = g3 + (p3 \bullet g2) + (p3 \bullet p2 \bullet g1) + (p3 \bullet p2 \bullet p1 \bullet g0)$
  - ...
  - $G3 = g15 + (p15 \bullet g14) + (p15 \bullet p14 \bullet g13) + (p15 \bullet p14 \bullet p13 \bullet g12)$
- The higher order CLL logic (producing C4,C8,C12,C16) then is realized as:
  - $(C4) \Rightarrow C1 = G0 + (P0 \bullet c0)$
  - ...
  - $(C16) \Rightarrow C4 = G3 + (P3 \bullet G2) + (P3 \bullet P2 \bullet G1) + (P3 \bullet P2 \bullet P1 \bullet G0) + (P3 \bullet P2 \bullet P1 \bullet P0 \bullet c0)$
- These equations are exactly the same CLL logic we derived earlier

# 16-Bit CLA

- Understanding 16-bit CLA hierarchy...

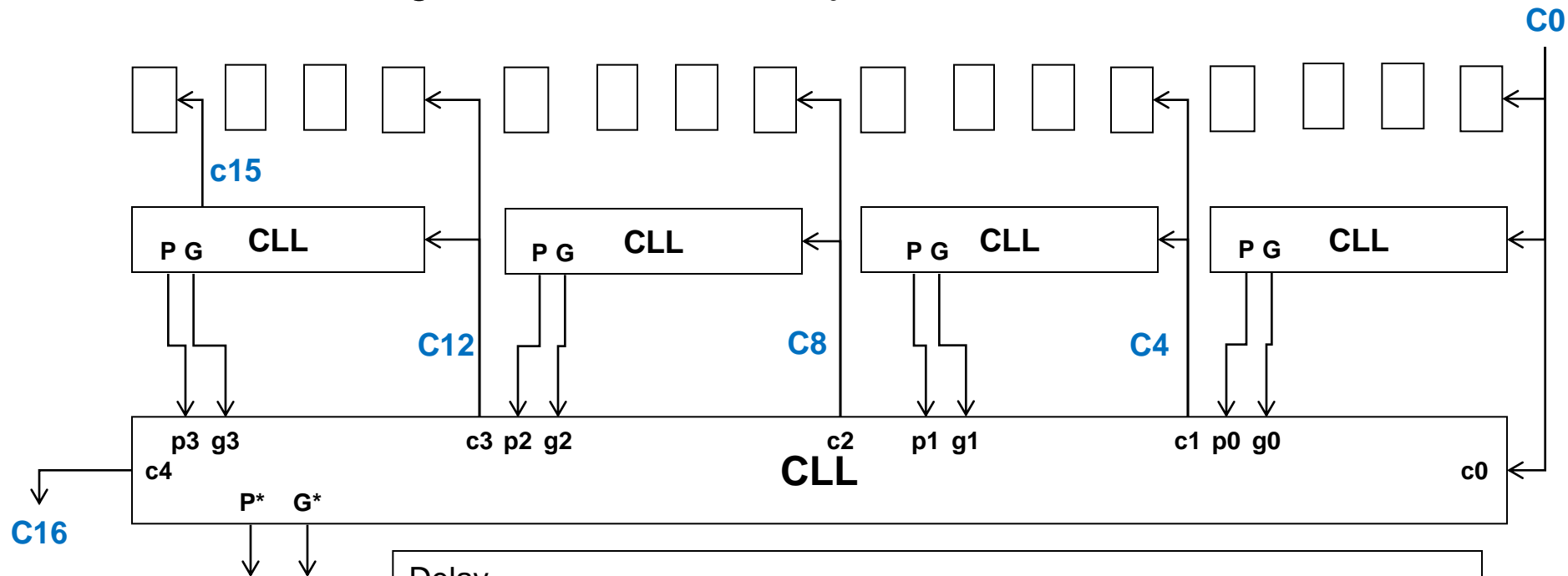

Delay =

= \_\_\_\_ = Delay in producing  $p_i, g_i$

= \_\_\_\_ = Delay in producing  $P_i^*, G_i^*$


= \_\_\_\_ = Delay in producing  $C_4, C_8, C_{12}, C_{16}$

= \_\_\_\_ = Delay in producing  $c_{15}$

= \_\_\_\_ = Delay in producing  $S_{15}$
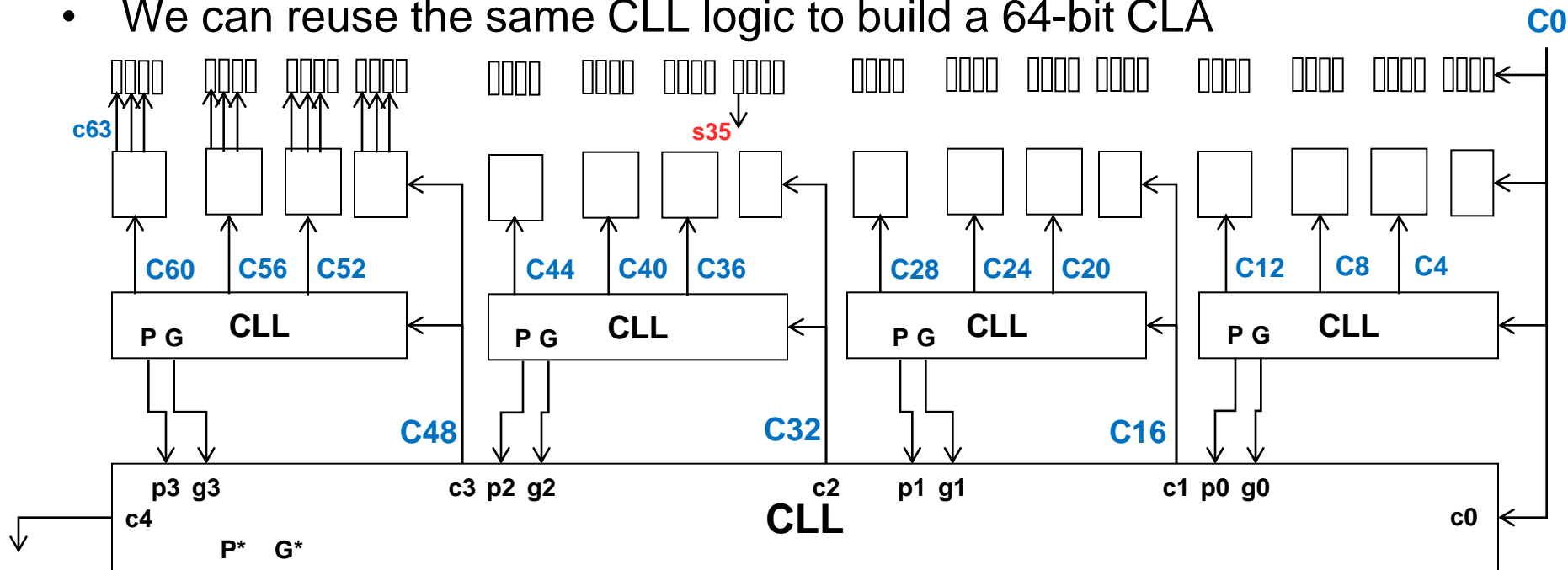
# 64-Bit CLA

- We can reuse the same CLL logic to build a 64-bit CLA



= \_\_\_\_ = Delay in producing S63  
Is the delay in producing s63 the same as in s35?  
= \_\_\_\_ = Delay in producing S2  
= \_\_\_\_ = Delay in producing S0

= \_\_\_\_ = Delay in producing  $p_i^*, g_i^*$   
= \_\_\_\_ = Delay in producing  $P_j^{**}, G_j^{**}$   
= \_\_\_\_ = Delay in producing C48  
= \_\_\_\_ = Delay in producing C60  
= \_\_\_\_ = Delay in producing C63  
= \_\_\_\_ = Delay in producing S63  
= \_\_\_\_ Total Delay