

Introduction to Digital Logic

Lecture 9:

Implementing Logic Functions w/ Decoder, Multiplexers, and Memories


Logic Function Synthesis

- Given a function description as a T.T. or canonical form, how can we arrive at a circuit implementation or equation (i.e. perform logic synthesis)?
- 5 methods to be discussed
 - Canonical sum/product + Simplification w/ theorems
 - Karnaugh Maps
 - Decoders + 1 gate per output
 - Multiplexers
 - Memories (used as Look-Up-Tables [LUT's])

Decoders


- A decoder is a building block that:
 - Takes in an n -bit binary number as input
 - Decodes that binary number and activates the corresponding output
 - Individual outputs for EVERY input combination (i.e. 2^n outputs)

3-to-8 Decoder

 


Decoders

 - A decoder is a building block that:
 - Takes a binary number as input
 - Decodes that binary number and activates the corresponding output
 - Put in 6=110, Output 6 activates ('1')
 - Put in 5=101, Output 5 activates ('1')




Decoders

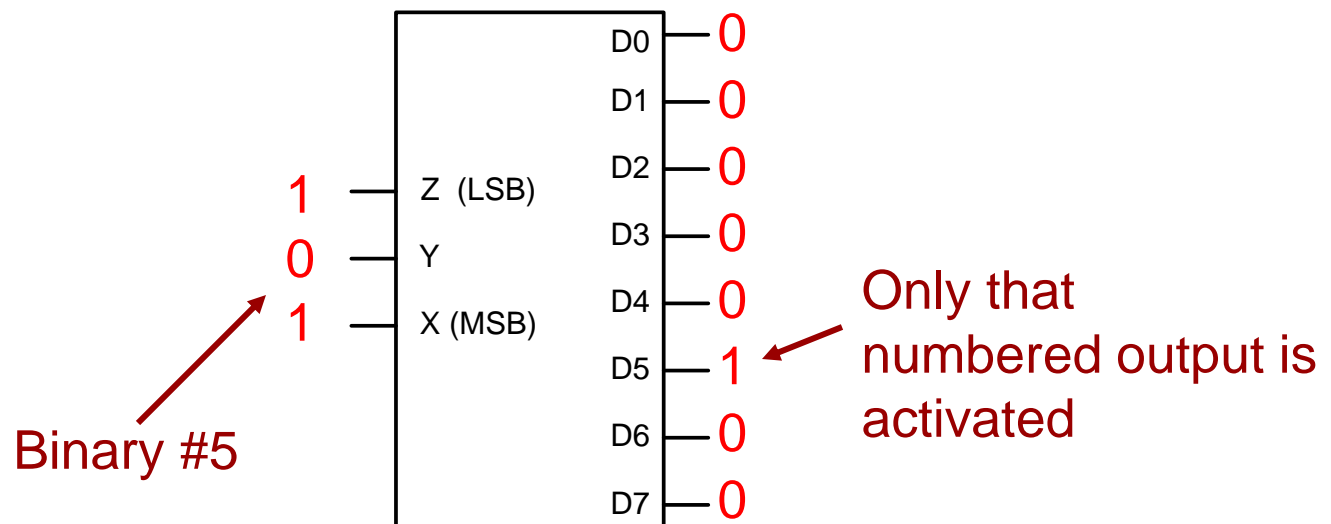- A decoder is a building block that:
 - Takes a binary number as input
 - Decodes that binary number and activates the corresponding output
 - Put in 6=110, Output 6 activates ('1')
 - Put in 5=101, Output 5 activates ('1')




Decoder Sizes

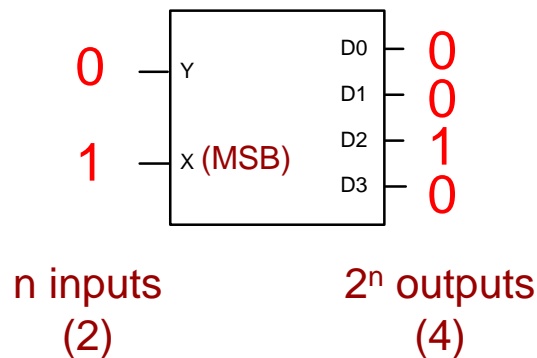- A decoder w/ an **n-bit input** has **2^n outputs**
 - 1 output for every combination of the n-bit input




2-to-4
Decoder

 

3-to-8
Decoder



Building Decoders

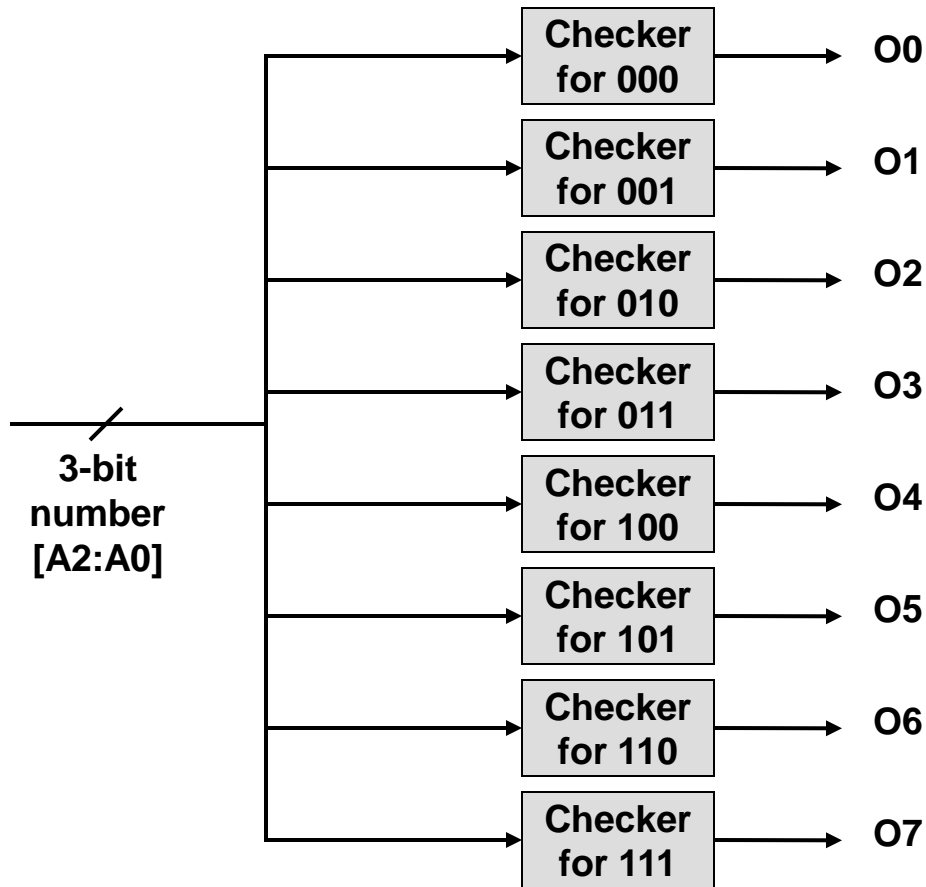

Building Decoders

| X | Y | D0 | D1 | D2 | D3 |
|---|---|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

$$D0 = X' \cdot Y'$$

 
 


Building Decoders

| X | Y | D0 | D1 | D2 | D3 |
|---|---|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

$$D0 = X' \cdot Y'$$

$$D1 = X' \cdot Y$$

  

Building Decoders



| X | Y | D0 | D1 | D2 | D3 |
|---|---|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

$$D0 = X' \cdot Y'$$

$$D1 = X' \cdot Y$$


$$D2 = X \cdot Y'$$

$$D3 = X \cdot Y$$

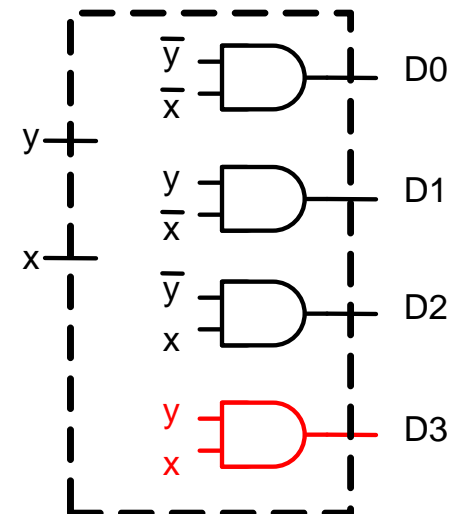 

Building Decoders

| X | Y | D0 | D1 | D2 | D3 |
|---|---|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

 


$$D0 = X' \cdot Y' = m_0$$

$$D1 = X' \cdot Y = m_1$$

$$D2 = X \cdot Y' = m_2$$

$$D3 = X \cdot Y = m_3$$

Notice output n is just minterm, m_n

 


Building Decoders

- All decoders are built by simply implementing minterms for each combination of the inputs
- This means a decoder is really just AND gates with inverters!


Implementing Logic Functions

 - $F = \Sigma_{MNO}(2,3,4,6)$
 $= m_2 + m_3 + m_4 + m_6$
- Since decoders are just minterm generators, just OR together the appropriate minterms




Implementing Logic Functions

 - $F = \sum_{MNO}(2,3,4,6)$
 $= m_2 + m_3 + m_4 + m_6$
- Connect the input variables M,N,O to the inputs of the decoder to produce the minterms




Implementing Logic Functions

 - $F = \sum_{MNO}(2,3,4,6)$
 $= m_2 + m_3 + m_4 + m_6$
- Connect the input variables M,N,O to the inputs of the decoder to produce the minterms
- OR together where $F = 1$




Implementing Logic Functions

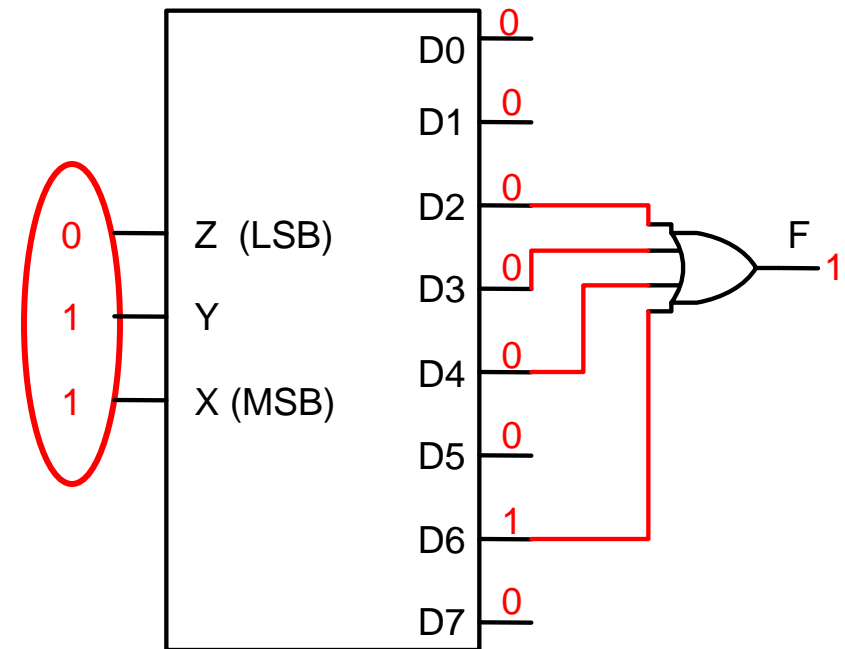- $F = \sum_{MNO}(2,3,4,6)$
 $= m_2 + m_3 + m_4 + m_6$
- Connect the input variables M,N,O to the inputs of the decoder to produce the minterms
- OR together where $F = 1$
- Test it $MNO = 110$




Implementing Logic Functions

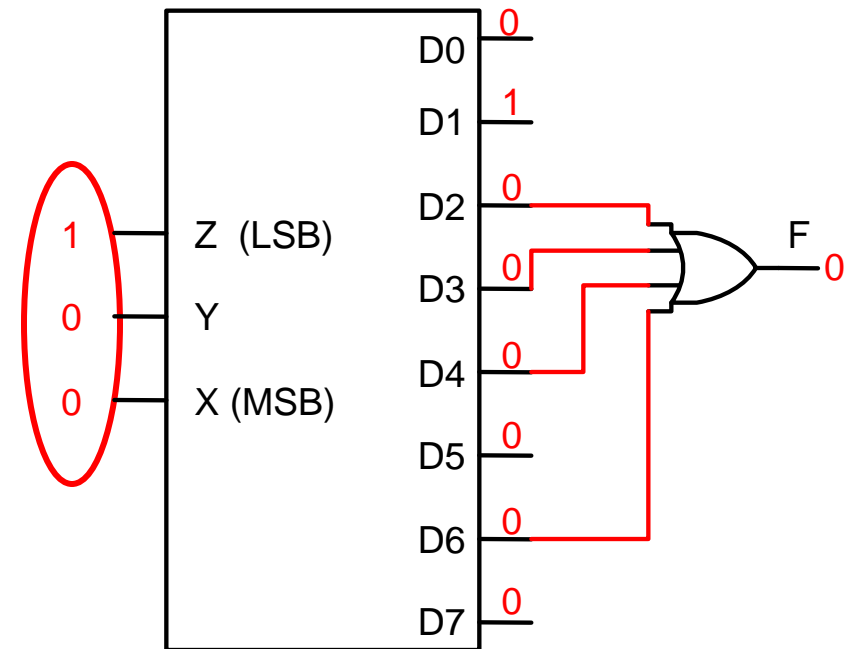- $F = \sum_{MNO}(2,3,4,6)$
 $= m_2 + m_3 + m_4 + m_6$
- Connect the input variables M,N,O to the inputs of the decoder to produce the minterms
- OR together where $F = 1$
- Test it $MNO = 110$
- Test it $MNO = 001$




Designing Circuits w/ K-Maps

 - Given a description...
 - Block Diagram
 - Truth Table
 - K-Map for each output bit (each output bit is a separate function of the inputs)
- 3-bit unsigned decrementer ($Z = X-1$)
 - If $X[2:0] = 000$ then $Z[2:0] = 111$, etc.




3-bit Number Decrementer


| X_2 | X_1 | X_0 | Z_2 | Z_1 | Z_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 |

 

$$Z_2 = X_2X_0 + X_2X_1 + X_2'X_1'X_0'$$

 


$$Z_1 = X_1'X_0' + X_1X_0$$

 

$$Z_0 = X_0'$$

3-bit Decrementer


| X_2 | X_1 | X_0 | Z_2 | Z_1 | Z_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 |

 

- When we have many outputs that are a function of the same inputs, it may be smaller to use a decoder rather than separate logic for each output

Implementing Logic Functions

 - $F = \sum_{MNO}(1,2,3,4,6)$
- Requires 5-input OR gate





Implementing Logic Functions

- $F = \sum_{MNO}(1,2,3,4,6)$
- Requires 5-input OR gate... **too big!**

Implement F another way...

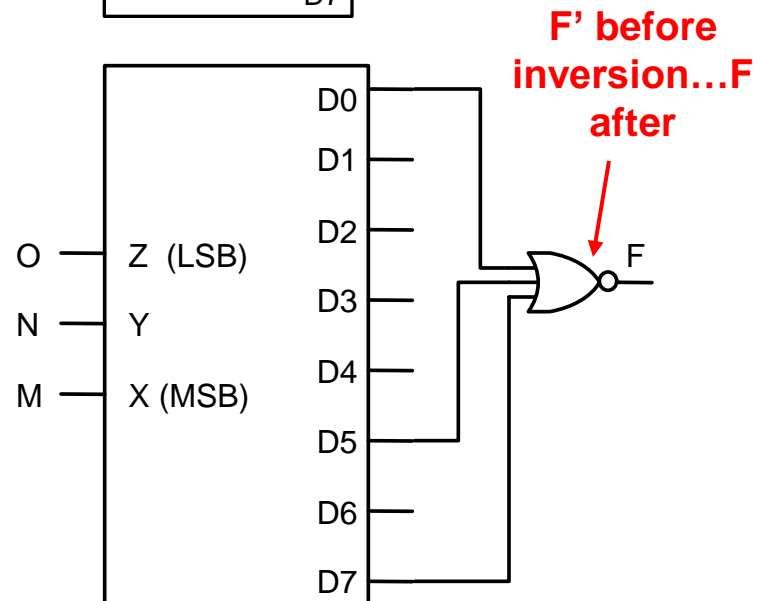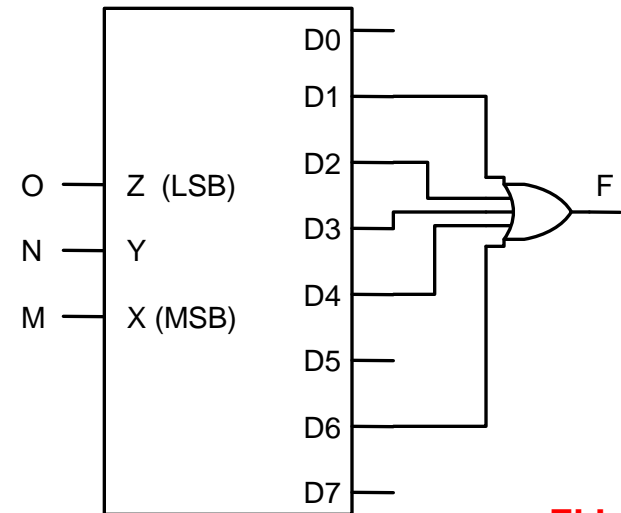- $F' = \sum_{MNO}(0,5,7)$
- Requires a 3-input OR gate
- To get F, just add an inversion at the end
- OR becomes NOR



MULTIPLEXERS

Single Variable Theorem (T1)

$$X + 0 = X \text{ (T1)}$$

| X | Y | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

OR

$$X \cdot 1 = X \text{ (T1')}$$

| X | Y | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

AND

Hold Y
constant

Whenever a variable is OR'ed with 0, the output will be the same as the variable...

“0 OR Anything equals that anything”

Whenever a variable is AND'ed with 1, the output will be the same as the variable...

“1 AND Anything equals that anything”

Single Variable Theorem (T2)

$$X+1 = 1 \text{ (T2)}$$

| X | Y | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

OR

$$X \cdot 0 = 0 \text{ (T2')}$$

| X | Y | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

AND

Hold Y
constant

Whenever a variable is OR'ed with 1,
the output will be 1...


“1 OR anything equals 1”

Whenever a variable is AND'ed with
0, the output will be 0...

“0 AND anything equals 0”


Application: Channel Selector

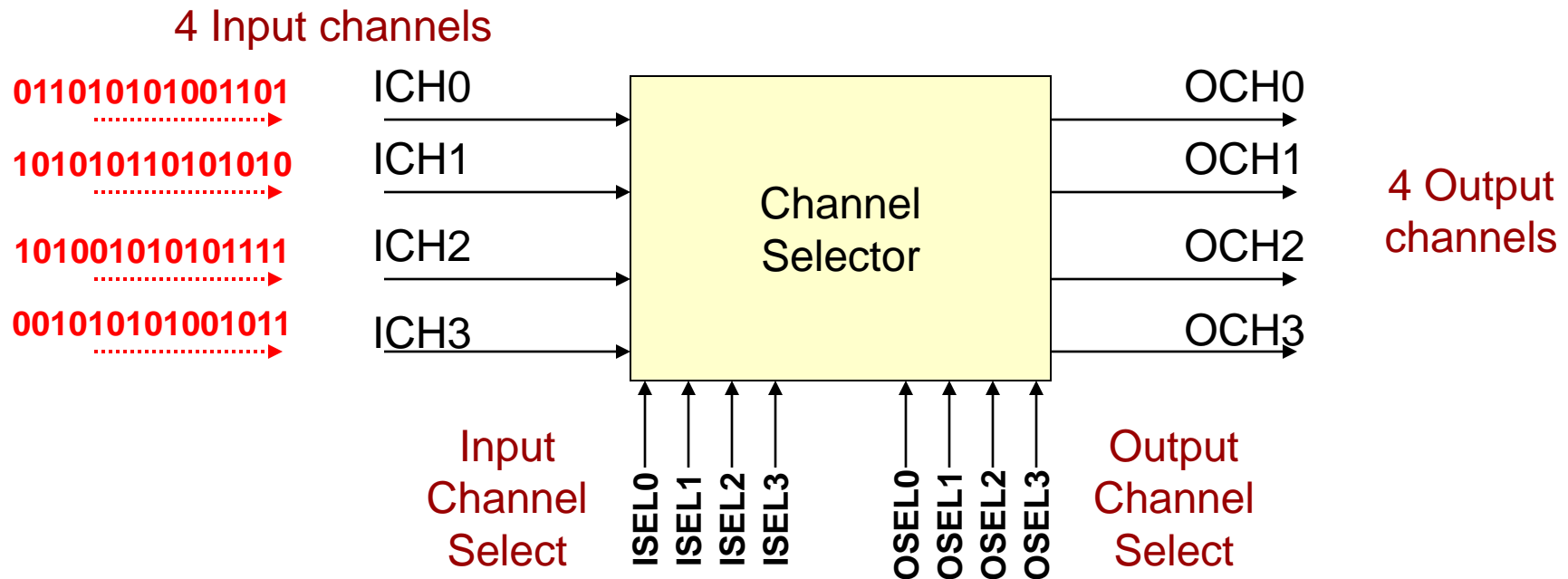- Given 4 input, digital music/sound channels and 4 output channels
- Given individual “select” inputs that select 1 input channel to be routed to 1 output channel




Application: Steering Logic

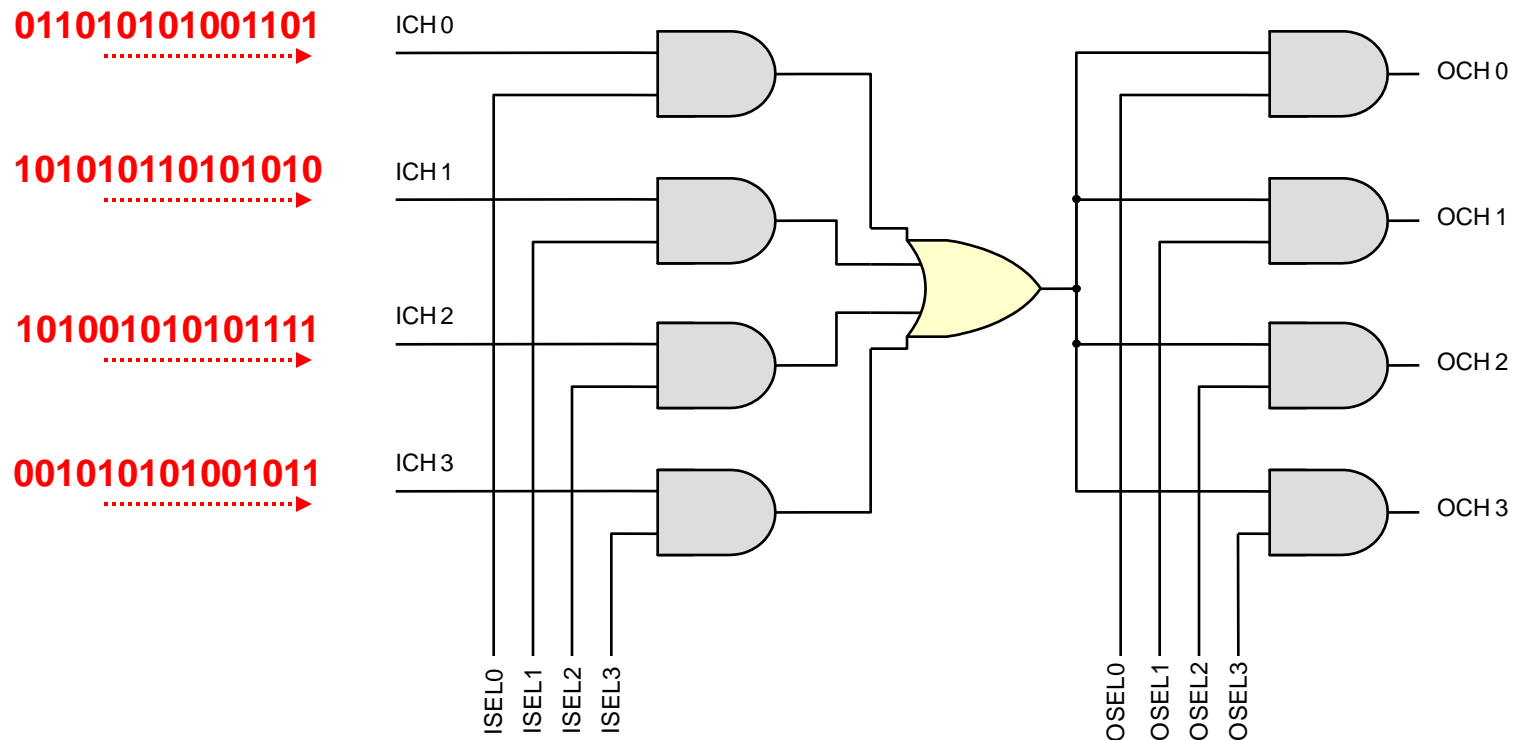- 4-input music channels (ICHx)
 - Select one input channel (use ISELx inputs)
 - Route to one output channel (use OSELx inputs)




Application: Steering Logic

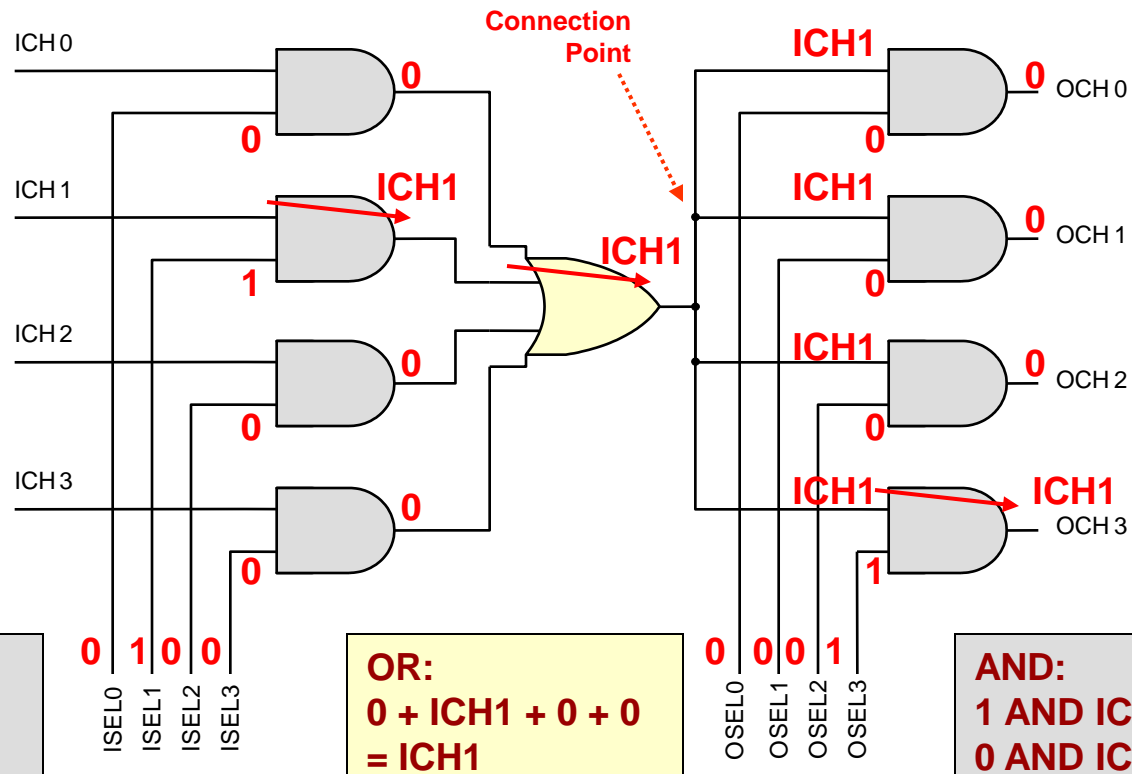- 1st Level of AND gates act as barriers only passing 1 channel
- OR gates combines 3 streams of 0's with the 1 channel that got passed (i.e. ICH1)
- 2nd Level of AND gates passes the channel to only the selected output



Your Turn

 - Build a circuit that takes 3 inputs: S, IN0, IN1 and outputs a single bit Y.
- It's functions should be:
 - If $S = 0$, $Y = IN0$ (IN0 passes to Y)
 - If $S = 1$, $Y = IN1$ (IN1 passes to Y)




```

if(s==0)
  Y = IN0
else
  Y = IN1
    
```


Multiplexers

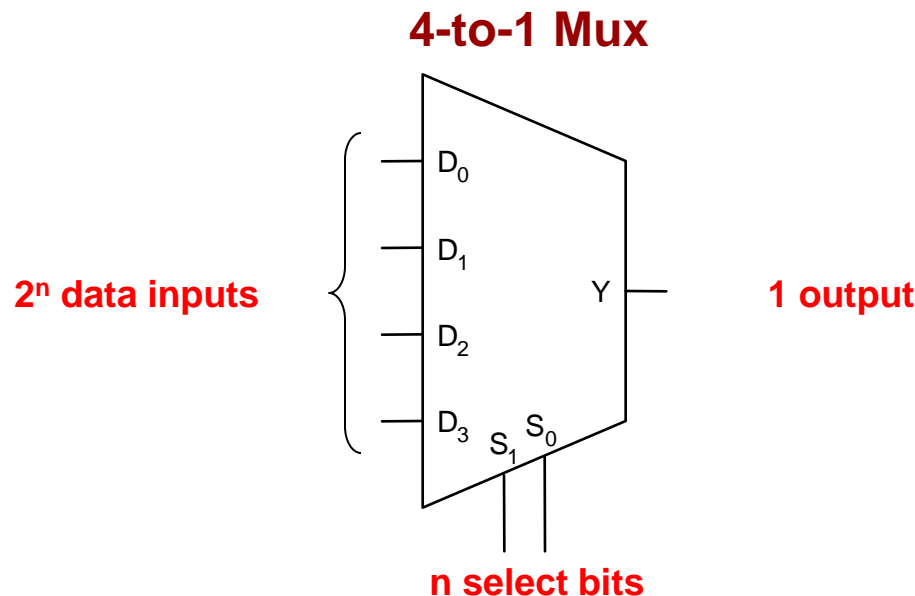- Along with adders, multiplexers are most used building block
- 2^n data inputs, n select bits, 1 output
- A multiplexer (“mux” for short) selects one data input and passes it to the output




Multiplexers

 ② Thus, D2 is selected and passed to the output



① Select bits = $10_2 = 2_{10}$.


Multiplexers

 

**D2 is being selected and passed.
So if it changes the output
changes as well.**

Multiplexers

 ② Thus, D₀ is selected and passed to the output




```

if( S1S0 == 00)
    Y = D0
else if(S1S0 == 01)
    Y = D1
else if(S1S0 == 10)
    Y = D2
else if(S1S0 == 11)
    Y = D3
    
```

① Select bits = $00_2 = 0_{10}$.

Application: Steering Logic

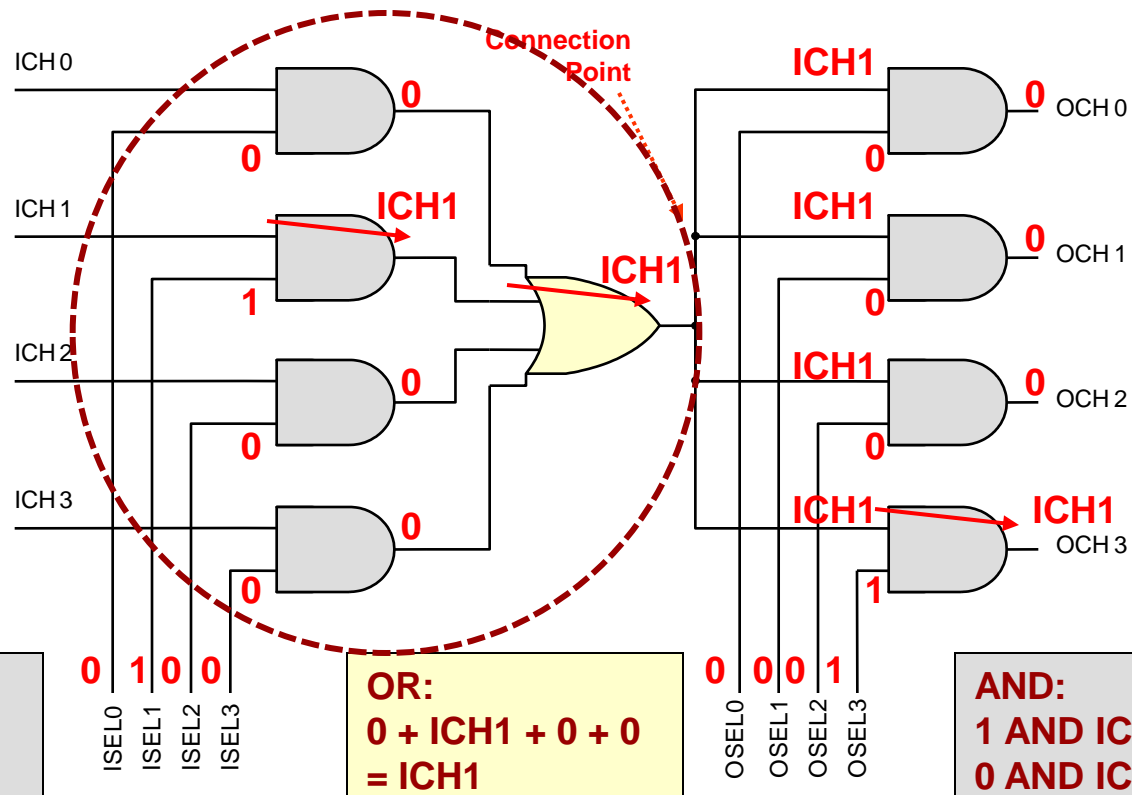
- 1st Level of AND gates act as barriers only passing 1 channel
- OR gates combines 3 streams of 0's with the 1 channel that got passed (i.e. ICH1)
- 2nd Level of AND gates passes the channel to only the selected output



Building a Mux

- To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.


$S_1 S_0 = 01$

 

Building a Mux

- To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.

$S_1 S_0 = 11$

 


Simplify This

- Given $F(x,y,z) = x'yz + y'z'$,
 $F(0,y,z) =$

$$F(1,y,z) =$$

- Given $G(a,b,c,d) = bd' + ab'cd + ac'd'$
 $G(1,1,c,d) =$



2-to-1 Mux

 

```

if(s==0)
  Y = IN0
else
  Y = IN1
    
```

  ② Thus, I₀ is selected and passed to the output



① Select bits = 0




3-bit Prime Number Function

| X | Y | Z | P |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |


Primes between
0-7

| X | Y | Z | P |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Truth Table

   

if(z==0)
output 0
else
output 1

 

Example

Function Implementation w/ Muxes

- Implementing a function using muxes relies is based on Shannon's expansion theorem which states:
 - $F(X_1, X_2, \dots, X_n) = X_1' \cdot F(0, X_2, \dots, X_n) + X_1 \cdot F(1, X_2, \dots, X_n)$
 - X_1 can be pulled out of F if we substitute an appropriate constant and qualify it with X_1' or X_1
- Now recall a 2-to-1 mux can be built as:
 - $F = S' \cdot I_0 + S \cdot I_1$
 - Comparing the two equations, Shannon's theorem says we can use X_1 as our select bit to a 2-to-1 mux with $F(0, X_2, \dots, X_n)$ as input 0 of our mux and $F(1, X_2, \dots, X_n)$ as input 1

Binary Decision Trees & Muxes

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| | 0 | 1 | 0 |
| | 1 | 0 | 1 |
| | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| | 0 | 1 | 1 |
| | 1 | 1 | 1 |

$F(x,y,z)$

| Y | Z | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

$F(0,y,z)$

| Y | Z | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

$F(1,y,z)$

| Z | F |
|---|---|
| 0 | 0 |
| 1 | 0 |

$F(0,0,z)$

| Z | F |
|---|---|
| 0 | 1 |
| 1 | 1 |



$F(0,1,z)$

| Z | F |
|---|---|
| 0 | 0 |
| 1 | 1 |

$F(1,0,z)$

| Z | F |
|---|---|
| 0 | 0 |
| 1 | 1 |

$F(1,1,z)$

  


Splitting on X

- We can use smaller muxes by breaking the truth table into fewer disjoint sets
 - This increases the amount of logic at the inputs though**
- Break the truth table into groups based on some number (k) of MSB's
- For each group, describe F as a function of the $n-k$ LSB's

| X | Y | Z | F |
|----------|---|---|----------|
| 0 | 0 | 0 | 0 |
| | 0 | 1 | 1 |
| | 1 | 0 | 1 |
| | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| | 0 | 1 | 1 |
| | 1 | 0 | 0 |
| | 1 | 1 | 1 |

**$y \text{ xor } z$
 $(y'z + yz')$**


$(y' + z)$

 

Put the k MSB's on the selects

Implement G

| X | Y | Z | G |
|----------|---|---|----------|
| 0 | 0 | 0 | 0 |
| | 0 | 1 | 0 |
| | 1 | 0 | 1 |
| | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| | 0 | 1 | 1 |
| | 1 | 0 | 1 |
| | 1 | 1 | 0 |

 

Shannon's Theorem

- $F(X_1, X_2, \dots, X_n) = X_1' \cdot F(0, X_2, \dots, X_n) + X_1 \cdot F(1, X_2, \dots, X_n)$
- Now recall a 2-to-1 mux can be built as:
 - $F = S' \cdot I_0 + S \cdot I_1$
 - Comparing the two equations, Shannon's theorem says we can use X_1 as our select bit to a 2-to-1 mux with $F(0, X_2, \dots, X_n)$ as input 0 of our mux and $F(1, X_2, \dots, X_n)$ as input 1
- We can recursively apply Shannon's theorem to pull out more variables:
 - $F(X_1, X_2, \dots, X_n) =$
 $X_1' X_2' \cdot F(0, 0, \dots, X_n) + X_1' X_2 \cdot F(0, 1, \dots, X_n) +$
 $X_1 X_2' \cdot F(1, 0, \dots, X_n) + X_1 X_2 \cdot F(1, 1, \dots, X_n) +$

Additional Logic

- Muxes allow us to break a function into some number of smaller, disjoint functions
- Use MSB's to choose which small function we want
- By including the use of inverters we can use a mux with $n-1$ select bits (given a function of n -var's)
- Break the truth table into groups of 2 rows
- For each group, put F in terms of: z , z' , 0 , or 1

| X | Y | Z | F | |
|---|---|---|---|----|
| 0 | 0 | 0 | 0 | z |
| | | 1 | 1 | |
| 0 | 1 | 0 | 1 | z' |
| | | 1 | 0 | |
| 1 | 0 | 0 | 1 | 1 |
| | | 1 | 1 | |
| 1 | 1 | 0 | 0 | z |
| | | 1 | 1 | |


$F(x,y,z)$ can be broken into several disjoint functions

$F_0(z)$

$F_1(z)$

$F_2(z)$


$F_3(z)$

 

Put the $n-1$ MSB's on the selects


More Practice

| X | Y | Z | G |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| | | 1 | 0 |
| 0 | 1 | 0 | 1 |
| | | 1 | 1 |
| 1 | 0 | 0 | 0 |
| | | 1 | 1 |
| 1 | 1 | 0 | 1 |
| | | 1 | 0 |

 

Fundamental Method

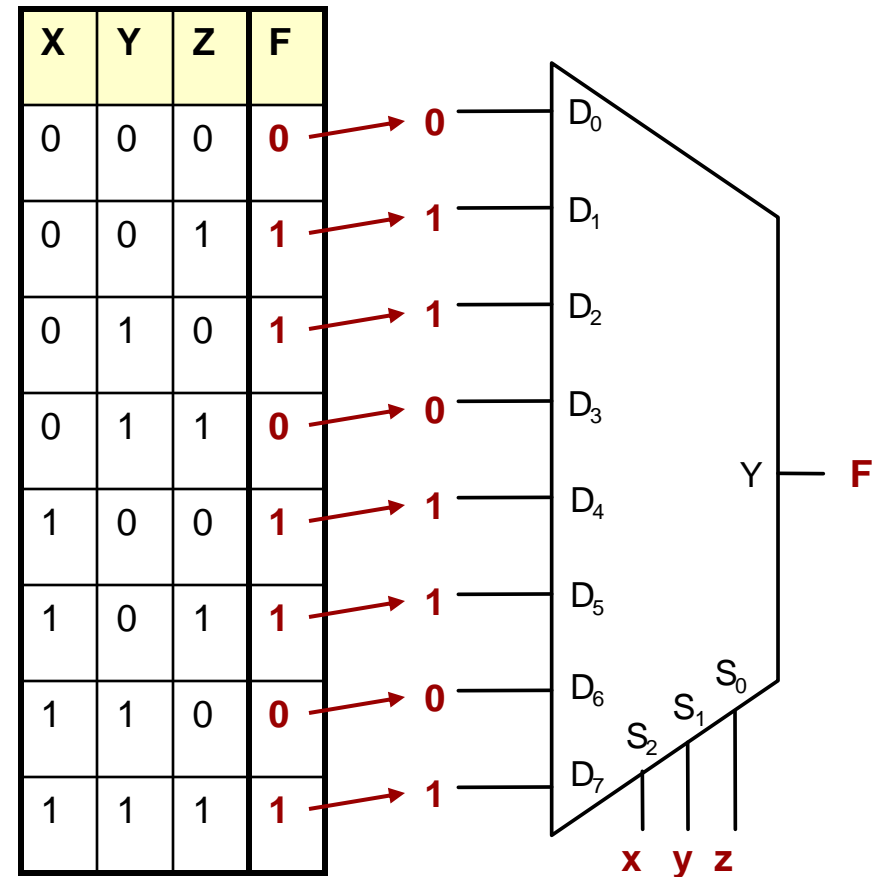- Connect the input variables to the select bits of the mux
- The output of the mux is the output of the function
- Whatever the output should be for each input value, attach that to the input of the mux






Splitting on X

- We can always rearrange our variables if it helps make the function simpler to implement

| | X | Y | Z | F |
|----------|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| | 0 | 1 | 1 | 1 |
| | 1 | 0 | 0 | 0 |
| | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| | 0 | 1 | 1 | 1 |
| | 1 | 0 | 0 | 0 |
| | 1 | 1 | 1 | 1 |

| | Z | X | Y | F |
|----------|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| | 0 | 1 | 1 | 0 |
| | 1 | 0 | 0 | 0 |
| | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| | 0 | 1 | 1 | 1 |
| | 1 | 0 | 0 | 1 |
| | 1 | 1 | 1 | 1 |

   

Implementing Logic Functions



- We can use muxes to implement any arbitrary logic function
- Fundamental method
 - if function has n -input variables, need a mux w/ n -selects
 - requires no additional logic; only the mux
- By adding extra logic in front of the mux inputs we can use a smaller mux...

Binary Decision Diagram

- Graph (binary tree) representation of logic function
- Vertex = Variable/Decision
- Edge = Variable value (T / F)


| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

| X | Y | Z | F |
|----------|---|---|---|
| 0 | 0 | 0 | 0 |
| | | 1 | 0 |
| | 1 | 0 | 1 |
| | | 1 | 0 |
| 1 | 0 | 0 | 1 |
| | | 1 | 1 |
| | 1 | 0 | 0 |
| | | 1 | 1 |

  


BDD's, Muxes, Shannon's Thm.

 - Every node in the BDD is just a 2-to-1 mux
 - View it in the opposite direction (bottom to top)
- Really using Shannon's theorem






If $X=0$,
choose the 0 (False) path
If $X=1$,
choose the 1 (True) path

| X | Y | Z | F |
|----------|----------|---|----------|
| 0 | 0 | 0 | 0 |
| | | 1 | 0 |
| | 1 | 0 | 1 |
| | | 1 | 0 |
| 1 | 0 | 0 | 1 |
| | | 1 | 1 |
| | 1 | 0 | 0 |
| | | 1 | 1 |

 

BDD for F

→ True
- - - False

   

Using a LookUp-Table to implement a function


ROMS AND MEMORIES

Memories

- Memories store (write) and retrieve (read) data
 - Read-Only Memories (ROM's): Can only retrieve data (contents are initialized and then cannot be changed)
 - Read-Write Memories (RWM's): Can retrieve data and change the contents to store new data


ROM's

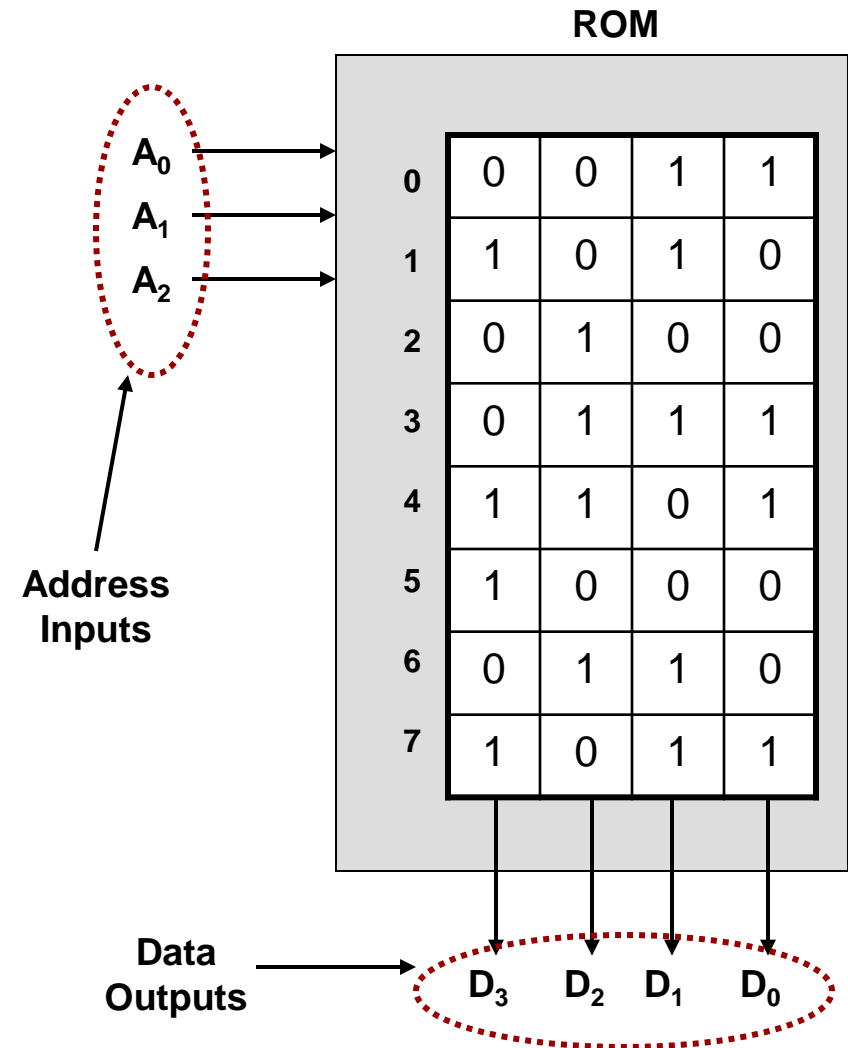- Memories are just tables of data with rows and columns
- When data is read, one entire row of data is read out
- The row to be read is selected by putting a binary number on the address inputs




ROM's

 - Memories are just tables of data with rows and columns
- When data is read, one entire row of data is read out
- The row to be read is selected by putting a binary number on the address inputs



ROM's

 - ROM's are named by their dimensions:
 - Rows x Columns
- n rows and m columns \Rightarrow $n \times m$ ROM
- 2^n rows \Rightarrow n address bits (or k rows $\Rightarrow \log_2 k$ address bits)
- m cols. \Rightarrow m data outputs





ROM's

- One major application of ROM's is to use them as LUT's (Look-Up Tables) to implement logic functions
- Given a logic function use a ROM to hold all the possible answers and feed the inputs of the function to the address inputs to look-up the answer

Implementing Functions w/ ROM's

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |



Arbitrary
Logic
Function

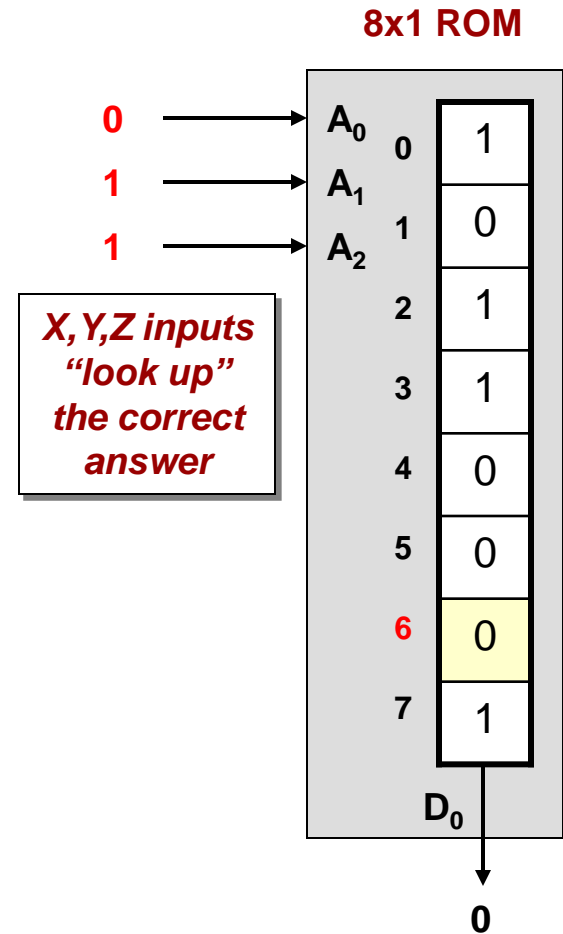 

Implementing Functions w/ ROM's

| X | Y | C _i | C _o | S |
|---|---|----------------|----------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adder

  

4x4 Multiplier Example

Determine the dimensions of the ROM that would be necessary to implement a 4x4-bit unsigned multiplier with inputs $X[3:0]$ and $Y[3:0]$ and outputs $P[?:0]$ (Question: How many bits are needed for P).


Example:

$$X_3X_2X_1X_0=0010$$

$$Y_3Y_2Y_1Y_0=0001$$

$$P = X * Y = 2 * 1 = 2$$

$$= 0010$$

 

Implementing Functions w/ ROM's

- To implement a function w/ n -variables and m outputs
- Use a ROM w/ 2^n rows and m columns
- Just place the output truth table values in the ROM