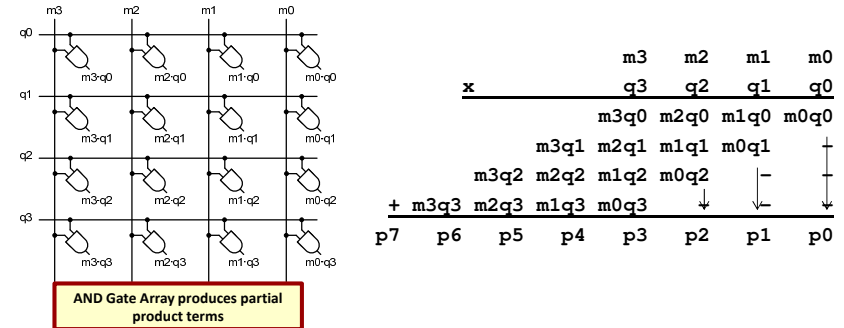


EE 457 Unit 2c


Fast Multipliers

Multiplication Overview

- Multiplication approaches:
 - Sequential: Shift-and-Add produces one product bit per clock cycle time (usually slow)
 - Combinational: Array multiplier uses an array of adders
 - Can be as simple as N-1 ripple-carry adders for an NxN multiplication




Array Multiplier

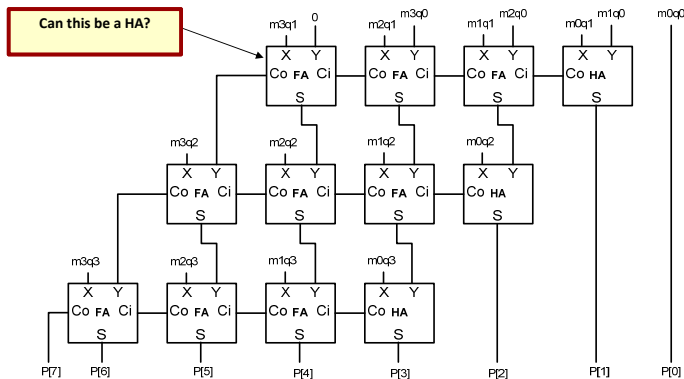

- Maximum delay = _____
 - Do you look for the longest path or the shortest path between any input and output?
 - Compare with the delay of a shift-and-add method

Pipelined Multiplier

 
- Now try to pipeline the previous design



Determine the maximum stage delay to decide the pipeline clock rate. Assume zero-delay for stage latches. How does the latency of the pipeline compare with the simple combinational array of the previous stage?

Carry-Save Multiplier

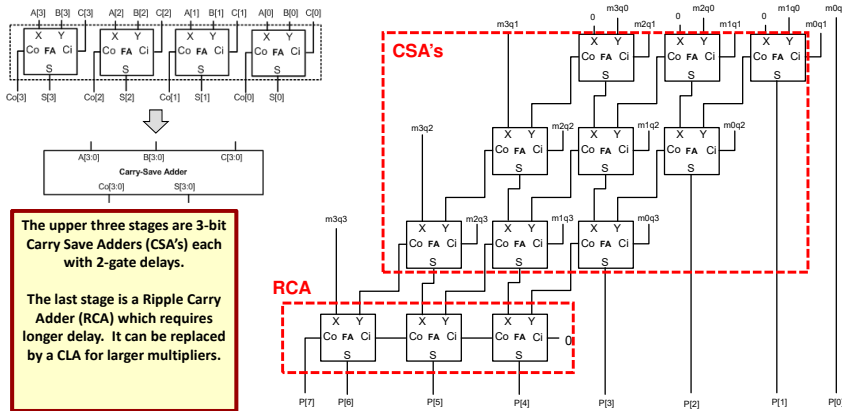
- Instead of propagating the carries to the left in the same row, carries are now sent down to the next stage to reduce stage delay and facilitate pipelining



Carry Save Adders



- Consider the decimal addition of $47 + 96 + 58 = 201$
- One way is to add _____ to get _____ and _____
- Here the _____ column cannot be added _____ is produced
- In the carry-save style, we add the _____ column and _____ column simultaneous
 
$$\begin{array}{r} 1 \quad 1 \\ 47 \\ + 96 \\ \hline 143 \\ + 58 \\ \hline 201 \end{array}$$




Carry-Save (3,2) Adders

- A carry save adder is also called a (3,2) adder or a (3,2) counter (refer to Computer Arithmetic Algorithms by Israel Koren) as it takes three vectors, adds them up, and reduces them to two vectors, namely a **sum vector** and a **carry vector**
- CSA's are based on the principle that carries do not have to be added _____, but can be combined _____
- An n-bit CSA consist of n disjoint full adders

  

1-bit FA vs. 1-bit CSA

 
- Any difference between an ordinary full adder and 1-bit CSA?



- 16-bit wide CSA takes (**more / equal / less**) time to produce its outputs compared to an 8-bit wide CSA
- Carry-save adder (**is / is not**) useful in adding only 2 numbers


CSA Organization

 - We can arrange our CSA's in a _____ manner where _____ partial product is added per CSA (after the first level)



Wallace Tree Multiplier


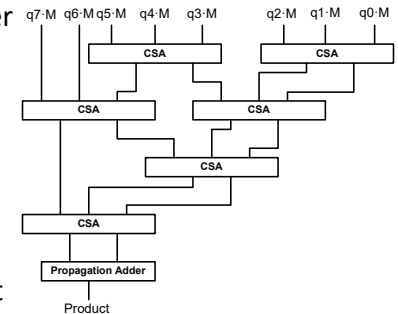
- Using the previous example as a template, to build an NxN multiplier you need (n-1) of (n-1) bit CSAs followed by a final (n-1)-bit RCA
- Delay = Delay of (n-1) CSA's + Delay of (n-1) bit RCA = _____
- We can reduce the CSA component of the delay by organizing the CSA's in a _____ (i.e. _____ delay)



Note: The vectors (partial products) need to be aligned before summing. These details are not shown in the block diagram.

Logic Delay

  - Consider the gate arrangement for OR'ing 8 bits
- Linear:
 - Delay = _____ gates
- Tree
 - Depth of tree = _____ = _____ levels
- Consider OR'ing 16-bits using 4-bit OR gates, how many levels would you need?




Wallace Tree Discussion

- A 4-input OR gate reduces 4 literals to 1 (i.e. a factor of 4 reduction)
- A CSA reduces 3 vectors to 2 vectors (i.e. a factor of 1.5)
 - This reduction factor may not be convenient to develop an efficient tree to sum 16 or 32 partial products
 - Wallace tree may not achieve a great reduction in delay due to wastage of an extra level
- Also not the Wallace tree shown earlier does not show...
 - Size of buses
 - What bits are "retired" progressively
 - Relative significance (alignment) of partial products
 - Size of the carry-propagate adder (e.g. RCA or CLA) needs to be figured out and overall delay estimated

2. (8+2+4+2 = 16 points) 25 min


Multiplication and CSAs:

 - 2.1 8 pts Consider the following adder arrangements for 8 x 8 multiplication reproduced from your classnotes. Find the length of the "Propagate Adder" at the bottom of each. Consider the number of bits you will be "retiring" before reaching the propagate adder and also state its number.



 - 2.2 2 pts The lab #7 on Wallace Tree, based on the figure on the right above, produces the product of two (signed/unsigned) 8-bit numbers.
- 2.3.1 4 pts You are aware that the CSA (Carry Save Adder) accepts three vectors and produces two vectors. Hence it is sometimes called a 3-to-2 reducer. Find how many levels of CSAs you need to reduce 32 partial sums (in a 32x32 Wallace Tree multiplier) into two vectors.

Level 1: 32 vectors $\{ [30] + 2 \} \Rightarrow \{ [30 / (3/2)] + 2 \} = \{ [20] + 2 \} = 22$



Credits

- These slides were derived from Gandhi Puvvada's EE 457 Class Notes